Wireless World

MARCH 1951 · TWO SHILLINGS

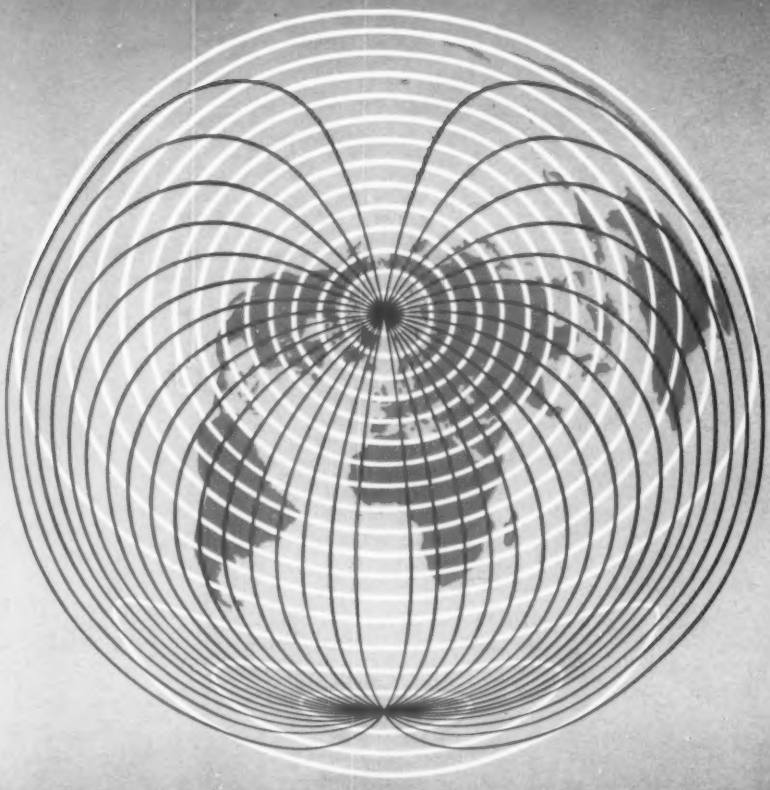

RADIO, TELEVISION AND ELECTRONICS

tailor-made

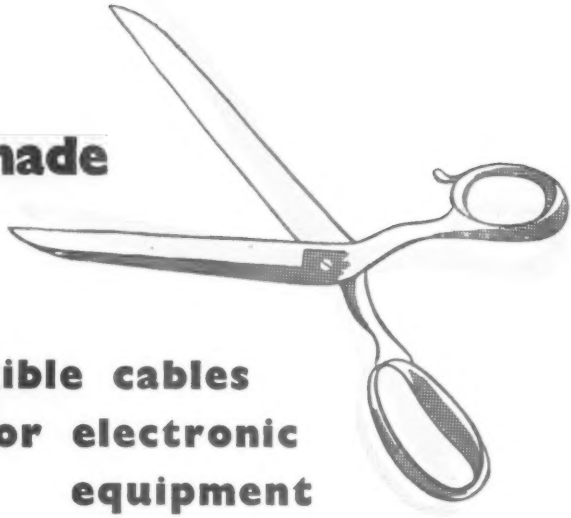

flexible cables for electronic equipment

If you need special multi-unit low-loss cables for electronic equipment—let us design and manufacture them to your requirements. They may include coaxial, twin, quad and small power or control cores in any combination.

BICC can offer you specialised production facilities for this work, as well as the services of skilled engineers who have tailor-made low-loss cables for all current requirements.

Why not take advantage of this opportunity? Write to-day and let us assist you with your problems.

Cables on right are examples which have been designed and manufactured by BICC to meet specialised needs.

Polythene-insulated P.V.C. sheathed multicore cable with microphone and control cores for film studio use.

Multicore polythene-insulated and sheathed television camera cable. Overall diameter 0.5 inches.

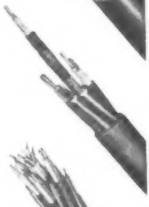

P.V.C. sheathed multicore polythene-insulated flexible television camera cable. Overall diameter 0.8 inches.

BI Callender's

multi-unit
LOW-LOSS CABLES

BRITISH INSULATED CALLENDER'S CABLES LIMITED
NORFOLK HOUSE, NORFOLK STREET, LONDON, W.C.2

AVO

REG. TRADE MARK

WIDE RANGE *Signal* GENERATOR

An inexpensive yet precision instrument designed especially to meet the exacting needs of the modern service engineer and laboratory technician. With six frequency ranges covering 50 Kc/s. to 80 Mc/s., its accuracy is better than ±1% of the scale reading.

50 Kc/s.–150 Kc/s.	1.5 Mc/s.–5.5 Mc/s.
150 Kc/s.–500 Kc/s.	5.5 Mc/s.–20 Mc/s.
500 Kc/s.–1.5 Mc/s.	20 Mc/s.–80 Mc/s.

Scale sub-divisions provide more than adequate discrimination for use in television circuits. Note the starred features below, which combine to maintain a minimum signal of less than 1μV up to 20 Mc/s and less than 3μV between 20 Mc/s and 80 Mc/s.

★OUTPUT 1
Co-axial socket for attenuated output. Force socket located totally within H.F. compartment.

MAINS TRANSFORMER 2
Marked tagboard for inputs of 100–130V. and 200–260V., A.C. 50/60 c/s.

★CAST ALUMINIUM H.F. COMPARTMENT and CHASSIS 3
Large number of fixing holes for H.F. compartment cover ensures excellent electrical bonding and good screening.

FUSE 4
Easily accessible when replacement is necessary.

VALVES 5
Standard types run at a rating to ensure long life.

TURRET COIL SWITCHING 6
Standard "AVO" practice.

★ATTENUATOR SYSTEM 7
Employs close tolerance, high stability midget carbon resistors, low reactance rotary potentiometer modified for H.F. operation with carefully designed screening.

Other features include:

ILLUMINATED SPOT RANGE SELECTOR
Gives rapid identification of operational band with intensified lighting round precise frequency. Fine hair line gives close discrimination, particularly on high frequencies.

STOPS
Separate stops prevent turning of dia. with respect to condenser.

★ **MAINS FILTER SYSTEM**
This is screened from main electrical assembly

BUSHING PLATES
provide additional rigidity for rotary controls

SLOW MOTION DRIVE
substantially free from backlash.

MAINS MODEL 100—130V. and 200—260V. A.C., 50—60 c/s..... £25

BATTERY MODEL..... £24

Sole Proprietors and Manufacturers —

The AUTOMATIC COIL WINDER & ELECTRICAL EQUIPMENT CO. LTD.
WINDER HOUSE • DOUGLAS STREET • LONDON • S.W.1 *Telephone: VICTORIA 3404/9*

S.G.2

A

INTRICATE PARTS

but not too intricate for

Bullers

Made in Three Principal Materials

FREQUELEX
An insulating material of Low Di-electric Loss, for Coil Formers, Aerial Insulators, Valve Holders, etc.

PERMALEX
A High Permittivity Material. For the construction of Condensers of the smallest possible dimensions.

TEMPLEX
A Condenser material of medium permittivity. For the construction of Condensers having a constant capacity at all temperatures.

BULLERS LOW LOSS CERAMICS

BULLERS LTD., 6, Laurence Pountney Hill, London, E.C.4
Telegrams: "Bullers, Cannon, London"
Phone: Mansion House 9971 (3 lines)
Manchester Office: 196, Deansgate, Manchester

SOUND REPRODUCING EQUIPMENT

A 100 Watt Amplifier

The outstanding features of this Philips Amplifier include: a high degree of voltage amplification; an output of 100 watts; and very little waste heat, giving cool running and long life. The output is well maintained even at extremes of the audio spectrum, and generous negative feedback taken over the output transformer provides excellent loudspeaker damping.

A Diffuser Loudspeaker

This Philips all-metal central Diffusion Loudspeaker is for ceiling mounting or suspension. It is attractively finished in a pleasing shade of cream that will harmonise well with any type of surrounding. Dimensions are 15in. diameter, 8in. deep. The loudspeaker is fitted to Philips type 9803 unit, and has a 100-volt transformer tapped for 1, 3 and 6 watt operation.

Send for literature covering the full Philips range of S.R.E.

PHILIPS ELECTRICAL LIMITED

ALSO MAKERS OF: RADIO AND TELEVISION RECEIVERS, LAMPS AND LIGHTING EQUIPMENT, ETC.

AMPLIFIER DEPARTMENT, CENTURY HOUSE, SHAFTESBURY AVENUE, LONDON, W.C.2.
A 687 A

G.E.C.

Germanium diodes

have many advantages—electrical and physical, which makes a substantial appeal to the professional radio engineer and the serious experimenter. Being so small they can be soldered directly into the part of the circuit where they are wanted and without any consideration of mounting methods or special holders.

They require no heater power and therefore the danger of introducing hum does not exist, neither has screening to be considered.

A minimum life of 10,000 hours means that they need not be easily accessible for replacement and the special sealed and robust construction ensures immunity from damage by vibration or atmospheric conditions.

As replacements for thermionic diodes, G.E.C. germanium diodes are always worth considering and the main points which have to be taken into account are reverse resistance and permissible reverse voltage. Their low shunt capacitance will always be advantageous compared with thermionic diodes.

From the point of view of the experimental worker they are invaluable because of their versatility, and they can equally well be used for say, an improvised source of bias from a heater supply, a probe voltmeter at television frequencies or in one of the many circuits of which the following are typical examples.

For further information write to:
Osram Valve and Electronics Dept.,
Magnet House, Kingsway, W.C.2.

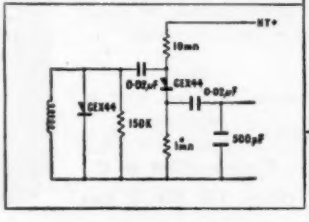

T.V. Sound Detector and Noise Limiter

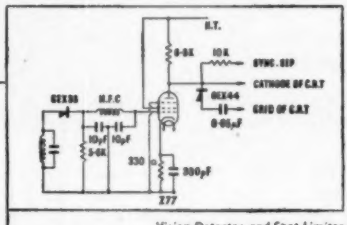

Vision Detector and Spot Limiter

THE GENERAL ELECTRIC CO. LTD., MAGNET HOUSE, KINGSWAY, W.C.2

SO SMALL— IT DOES A BIG JOB

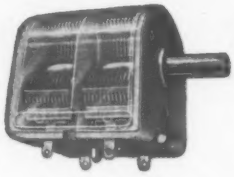

Miniature in Size, but big in performance. *The M.M. 2 Gang Condenser* has frame dimensions of only $1\frac{7}{16}$" x $1\frac{13}{32}$" x $1\frac{11}{16}$". Complete with dust cover. Cat. No. 4702.
PRICE 10/6

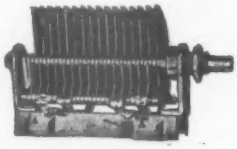

TYPE 604 (illustrated) is a low-loss short-wave condenser suitable for Chassis or one-hole fixing. Brass vanes are soldered to supports and electroplated.

TYPE 603 is a split stator condenser of similar construction.

The S.1 series in both types are particularly suitable for low power transmitters.

PRICES: Type 604 .. 15/3—17/0
Type 603 .. 16/0—17/6

Replacement Scales calibrated to Copenhagen Plan now available for :—

Airplane Drive .. .. .. **2/3** *retail*
Squareplane Drive .. .. **2/6** *retail*
Full Vision Drive .. .. **2/9** *retail*
S.L.8 or S.L.5 Drive .. .. **4/6** *retail*

PRECISION COMPONENTS BY

JACKSON

BROS (LONDON) LIMITED

KINGSWAY · WADDON · SURREY

Tel.: Croydon 2754-5 Grams: Wolfilco, Souphone, London

ACE MODEL 600

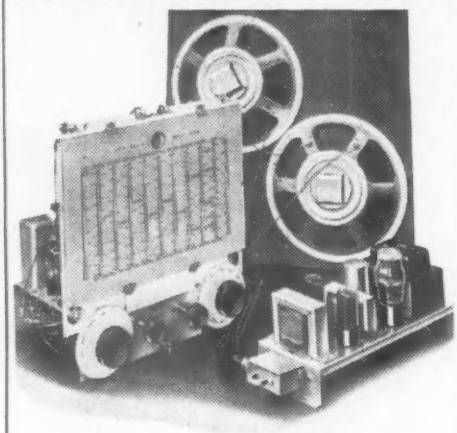

AVAILABLE IN CHASSIS FORM

An outstanding achievement in radio engineering

- ★ **9 Valves**
- ★ **9 Wavebands**
- ★ **Tuned RF Stage**
- ★ **Permeability Tuning on Short Waves**
- ★ **Full Bandspreading on 11, 16, 19, 25, 31, 41 and 49 m Bands**
- ★ **Plus Trawler and Medium or Medium and Long Bands**
- ★ **10 Watts Push-Pull Output**
- ★ **Twin 10" Speakers**

Price £25 0 0 plus £5 11 2 tax

ACE MODEL 600 CONSOLE

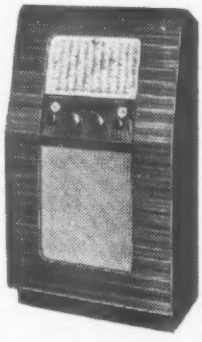

Mode. 600 chassis and speakers in magnificent walnut cabinet of special acoustic design

Size:
40 in. × 20 in. × 12 in. (approx.)

Price £30 0 0
plus £6 13 4 tax

MAJOR DISTRIBUTORS

7 CAVENDISH PLACE

LONDON W.1

Tel.: WILlesden 6713

CINTEL

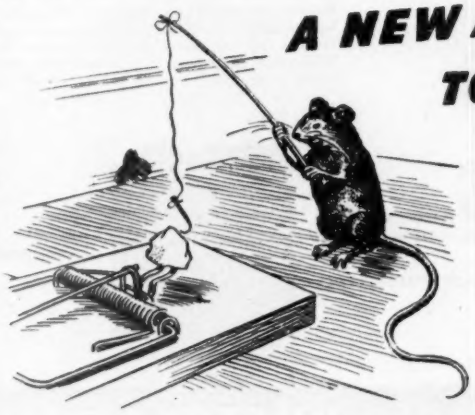

A NEW APPROACH TO AN OLD PROBLEM...

THERE are many problems which confront the electronic engineer from day to day which may be regarded as "necessary evils" and one of these is the correction of phase-distortion in an amplifier.

The 'CINTEL' ADJUSTABLE PHASE CORRECTOR

is a new approach to the solution of this old problem and enables the phase distortion in any wide band amplifier of 75 ohms impedance to be corrected simply by "turning a knob."

For full technical details please write for leaflet No. PUCI/1.

CINEMA-TELEVISION LIMITED

A Company within the J. Arthur Rank Organisation

FOREMOST IN THE MANUFACTURE OF

• Counters & Chronometers • Metal Detectors • Oscilloscopes • Photo-Electric Cells • Cathode Ray Tubes • Geiger-Muller Tubes • Electronic Instruments

WORSLEY BRIDGE ROAD · LONDON · S·E·26

Telephone: HITher Green 4600

Northern Agents:
F. C. ROBINSON & PARTNERS LTD
287 Deansgate, Manchester 3

Scottish Agents:
ATKINS, ROBERTSON & WHITEFORD LTD
100 Torrisdale Street, Glasgow S.2

CINTEL

REGISTERED TRADE MARK

YOUR EQUIPMENT CAN HAVE THE PROFESSIONAL LOOK

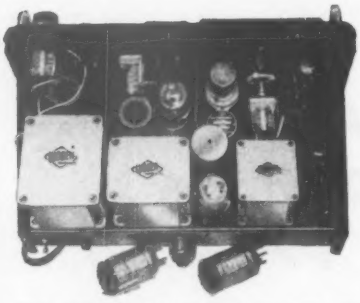

BY USING WODEN POTTED COMPONENTS

Woden Potted Transformers and Chokes ensure a clean layout with uniform smart appearance. They are used by many leading Radio and Television Manufacturers and this is sufficient testimony to the high standard of efficiency which characterize these components. Available for "Wireless World" Williamson Amplifier, "Electronic Engineering" Home Built Televisor and other popular circuits.

THE EQUIPMENT SHOWN IS THE TOP BAND CABINET TRANSMITTER AS DESCRIBED IN THE "SHORT WAVE MAGAZINE."

SEND FOR ILLUSTRATED LITERATURE AND PRICE LISTS OF OUR COMPLETE RANGE.

WODEN TRANSFORMER CO. LTD

MOXLEY ROAD BILSTON STAFFS

PHONE BILSTON 41959

I.T.L.

CLEARLY BETTER

When a factory needs a sound system—and it's a thing few modern factories can do without—it needs something that will reproduce words and music as clearly as they were delivered to the microphone, in spite of possible distracting noise. This is the end to which G.E.C. sound systems were designed and built; and is one of the reasons why they are so well suited to modern factories. The other reasons? You can count in unobtrusive loudspeakers, simple installation, easy controls and economy too. If you need a sound system in your factory we'll be glad—without obligation to you—to give you details and estimates. You will find our address below.

SOUND SYSTEMS BY G.E.C.

ELECTRIC CO LTD · MAGNET HOUSE · KINGSWAY · LONDON · WC2

THIS G.E.C. ADVERTISING MEANS NEW BUSINESS FOR YOU

The advertisement on the left for G.E.C. Sound Systems is appearing in FACTORY MANAGER, MAKER UP, MASS PRODUCTION, TAILOR AND CUTTER. Follow up this advertising by 'tying up' with your own local publicity . . . and take full advantage of G.E.C. technical co-operation

THE GENERAL ELECTRIC COMPANY LIMITED
MAGNET HOUSE, KINGSWAY, LONDON, WC2

'Frequentite' is the most suitable insulating material for all high frequency applications. Seventeen years ago we introduced the first British-made low-loss ceramic, and consultation with us before finalising the design of new components is a wise precaution.

STEATITE & PORCELAIN PRODUCTS LTD.

Head Office : Stourport-on-Severn, Worcestershire. Telephone : Stourport III. Telegrams : Steatain, Stourport

S.P.72

PLUGS & SOCKETS

for CO-AXIAL CABLES

These plugs and sockets are designed for use with either solid or airspaced dielectric cables. The patented method of connecting the plug to the metal braiding of the cable ensures positive contact and grip without soldering. The centre conductor of the cable passes through the hollow centre pin for easy soldering. The thermosetting plastic insulating material between the plug body and pin remains unaffected by heat from soldering. The socket with two-hole mounting flange incorporates a 'click' action retaining spring which prevents the plug from loosening through vibration. Both plug and socket bodies are of Nickel-plated brass, and the contact pins are Silver-plated brass.

●

BRIEF SPECIFICATION

These Plugs and Sockets are manufactured to an R.E.C.M.F. Specification, and the minimum performance figures after testing to RIC/11 Yellow Specification INCLUDING TROPICAL EXPOSURE TEST, are :—

Capacity (Plug and Socket together)	5 pF max.
Contact Resistance (Outer Contacts)	10 milliohms max.
Contact Resistance (Pin Contacts)	10 milliohms max.
Leakage Resistance	10 Megohms min.
Steady withdrawal force ...	6-16 lb.

PAT. NO. 637613

ANTIFERENCE LIMITED 47 BRYANSTON STREET - LONDON W.1

Pre-Amplifier for Birmingham. High gain, low noise, with built-in power pack, tunable for peak sound and vision. Completely screened. £6/19/6.

MAINS TRANSFORMERS, FULLY INTERLEAVED, SCREENED AND IMPREGNATED. ALL GUARANTEED. ALL PRIMARIES ARE 200/250 v. Half Shrouded.

HSM63. (Midget). Output 250-0-250 v. 60 m/a., 6.3 v. at 3 amps. 5 v. at 2 amps. ... 18/-
HS63. Output 250-0-250 v. 60 m/a., 6.3 v. at 3 amps., 5 v. at 2 amps. ... 18/6
HS80. Windings as above. 4 v. at 4 amps., 4 v. at 2 amps. ... 18/6
Output
HS2. 250-0-250 v. 80 m/a. ... 21/-
HS30. 300-0-300 v. 80 m/a. ... 21/-
HS3 350-0-350 v. 80 m/a. ... 21/-
HS2X. 250-0-250 v. 100 m/a. ... 23/-
HS7S. 275-0-275 v. 100 m/a. ... 23/-
HS30X 300-0-300 v. 100 m/a. ... 23/-
HS3X. 350-0-350 v. 100 m/a. ... 23/-

Fully Shrouded

FSM63. (Midget). Output 250-0-250 v. 60 m/a., 6.3 v. at 3 amps., 5 v. at 2 amps. ... 18/6
Output
FS2. 250-0-250 v. 80 m/a. ... 23/-
FS30. 300-0-300 v. 80 m/a. ... 23/-
FS3. 350-0-350 v. 80 m/a. ... 23/-
FS2X. 250-0-250 v. 100 m/a. ... 25/9
FS7S. 275-0-275 v. 100 m/a. ... 25/9
FS30X. 300-0-300 v. 100 m/a. ... 25/9
FS3X. 350-0-350 v. 100 m/a. ... 25/9
All the above have 6.3-4-0 v. at 4 amps., 5-4-0 v. at 2 amps.
FS43. Output 425-0-425 v. 200 m/a., 6.3 v. 4 amps., C.T. 6.3 v. 4 amps., C.T. 5 v. 3 amps. Fully shrouded. ... 51/-
FS80. Output, 450-0-450 v. 250 m/a., 6.3 v. 2 amps., C.T. 6.3 v. 4 amps. C.T. 5 v. 3 amps. Fully shrouded. ... 75/-
F30X. Output, 300-0-300 v. 80 m/a., 6.3 v. 7 amps., 5 v. 2 amps. Framed, Flying leads. ... 31/9
F3SX. Output, 350-0-350 v. 250 m/a., 6.3 v. 6 amps., 4 v. 8 amps., 4 v. 3 amps., 0-2-6.3 v. 2 amps. Fully shrouded. ... 71/6
FS160X. Output 350-0-350 v. 160 m/a., 6.3 v. 6 amps., 6.3 v. 3 amps., 5 v. 3 amps. Fully shrouded. ... 45/-
FS43X. Output, 425-0-425 v. 250 m/a., 6.3 v. 6 amps., 6.3 v. 6 amps 5 v. 3 amps. Fully shrouded. ... 69/-
HS6. Output, 250-0-250 v. 100 m/a., 6.3 v. 6 amps., C.T. 5 v. 3 amps. For receiver R1355. Half shrouded. ... 29/3
HS150. Output, 350-0-350 v. 150 m/a., 6.3 v. 3 amps., C.T. 5 v. 3 amps. Half shrouded. ... 30/9
F36. Output, 250-0-250 v. 100 m/a., 6.3 v. 6 amps., C.T. 5 v. 3 amps. Half shrouded. ... 30/9
FS120. Output, 350-0-350 v. 120 m/a., 6.3 v. 2 amps., C.T. 6.3 v. 2 amps., C.T. 5 v. 3 amps. Fully shrouded. ... 33/-
PRI/1. Output 230 v. at 30 m/a., 6.3 v. at 1.5/2 amps. ... 23/-
The above have inputs of 200/250 v.
FS150. 350-0-350 v. 150 m/a., 6.3 v. 4 amps., 5 v. 3 amps. ... 34/9

FILAMENT TRANSFORMERS

F4 Output, 4 v. 2 amps. ... 9/-
F6. Output, 6.3 v. 2 amps. ... 9/-
F6X. Output, 6.3 v. 0.3 amps. ... 6/-
F12X. Output, 12 v. at 1 amp. ... 9/-
F12. Output, 12.6 v. tapped 6.3 v. at 3 amps. ... 18/6
F24. Output, 24 v. tapped 12 v. at 3 amps. ... 26/-
F12 and F24 framed with Flying Leads.
FU6 Output, 0-2-4-5-6.3 v. at 2 amps. ... 11/-
F29. Output, 0-2-4-5-6 3 v. at 4 amps. ... 20/9
FU6 and F29 clamped with Flying Leads.
F5. Output, 6.3 v. at 10 amps. or 5 v. at 10 amps. or 12.6 v. at 5 amps. or 10 v. at 5 amps. ... 37/9
F6/4. Output, four at 6.3 v. tapped at 5 v. at 5 amps. per winding, giving by suitable series and parallel connections 24 v. at 5 amps. 20 v. at 5 amps., 18 v. at 5 amps., 15 v. at 5 amps., 12.6 v. at 10 amps., 10 v. at 10 amps., 6.3 v. at 20 amps., 5 v. at 20 amps. ... 57/-
F5 and F6/4 framed with Flying Leads.
F66X. Output 0-4-6.3 v. 3 amps. ... 19/6
FU12. Output 0-12-24 v. 1 amp. ... 19/6

OUTPUT TRANSFORMERS

MOP1. Ratios 26, 46, 56, 66, 90 120-1 50 m/a. max. current. C.T. for Q.P.P. Class B, etc. Secondary 2/4 ohms. Top panel and clamped, each. ... 6/-
OP1. Midget Power Pentode, ratios 30, 60, 90-1, 40 m/a., Secondary 2/3 ohms., each. ... 4/-
OP2. Midget Pentode, ratios 45-1, Secondary 2/3 ohms, 40 m/a. per doz. ... 39/6
OP10. 10/15 watts output. 20 ratios on Full and Half primary ... 19/9
OP30. 30 watts output, 20 ratios on Full and Half primary. ... 28/6
Williamson's O.P. Transformer to Author's specification ... £4/3/6
Chokes for Williamson's Amplifier. 30H at 20 m/a. ... 15/6
10H at 150 m/a. ... 35/-
Choke C4. 60 m/a., approx. 8 H., 350 ohms. ... 5/-
Choke C5. 40 m/a., approx. 5 H., 360 ohms. ... 4/-
Choke C6. 50 m/a., 50 H., 1,500 ohms. ... 22/-
Belling Lee Co-Axial Plugs. Type 642/P., each. ... 1/3
Belling Lee Co-Axial Sockets. Type 604/S, each. ... 1/3
B.I. Condensers, all new. 8 mfd. carton type, 3/2 ea. 8×8 mfd. carton type, 4/9 ea. ; 8×8 mfd., can type, 5/- ea. ; clips for same each 5d.

C.W.O. (add 1/- in £ for carriage), all orders over £2 carriage paid. Trade enquiries invited.

H. ASHWORTH (Dept. W.W.)

676 GT. HORTON ROAD, BRADFORD, YORKS.

Introducing the lesser known pages of our catalogue

MARCONI INSTRUMENTS LIMITED

FIELD STRENGTH MEASURING EQUIPMENT

Type TME 18

It may not be generally known that, in our range of Communications Test Gear, we number certain unique instruments which, designed for highly individual functions, demonstrate the extraordinary virtuosity of Marconi engineers. The user of these specialised types turns naturally to Marconi Instruments for all his test gear—knowing that a mastery of the more intricate measuring problems makes light of those more commonly encountered.

FIELD STRENGTH MEASURING EQUIPMENT TME 18 operates in conjunction with a series of five interchangeable loop aerials to cover the frequency band 150 kc/s to 25 Mc/s. The measurement is carried out by the substitution of a locally generated e.m.f. of frequency and magnitude equal to that of the signal received. The method of calibration reduces to simple terms the computation of field strength in decibels relative to one microvolt per metre. Field strength range: minimum of 1μV to maximum of 5V per metre, depending on frequency. The output can be monitored by panel meter or writing recorder. The equipment can be arranged for operation from a car type accumulator or a.c. mains.

MARCONI INSTRUMENTS LTD., St. Albans, Herts. Telephone: St. Albans 6161/5

Wayne Kerr

INDUCTANCE METER

Designed to provide simple and direct reading measurement of inductance values between 0.05 microhenry and 100 millihenrys. A stable variable-frequency oscillator is used to resonate the unknown inductance with a fixed standard capacitor. Provision is made for the measurement of Q at resonance frequency. Calibration and scale reading accuracy are sufficient to provide direct readings of inductance values within 2 per cent. above one microhenry. Relative measurement can be made with greater accuracy. The instrument is very compact, measuring only 7¼" high, 7¾" wide and 7⅝" deep at base.

THE WAYNE KERR LABORATORIES LTD. NEW MALDEN SURREY : MALDEN 2202

CHARLES AMPLIFIERS 1951 MODELS

● *K51 HIGH FIDELITY AMPLIFIER*

K51 High Fidelity Amplifier incorporates several features of advanced design, including a detachable remote control unit, the output stage is Triode-connected KT66 valves in P.P., with negative feedback. The controls include input selector, Mic, Radio, Gram. 33/78 ; bass control, and treble control with both boost and cut. Output 6 watts, 3, 7 and 15 ohms at below .5% distortion, 30-20,000 cps., **£17/17/-.**

30 PAGE ILLUSTRATED CATALOGUE

OF AMPLIFIERS, TUNING UNITS, LOUDSPEAKER CHAMBERS, ETC.

★ *Write today for YOUR copy*

● *THE RC TUNING UNIT*

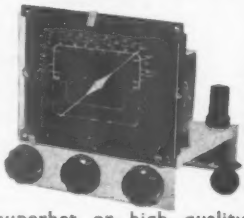

The RC Tuning Unit is a highly sensitive 3 wave-band, 4 valve unit employing an RF stage on all bands. A switch permits superhet or high quality TRF reception from local stations, the RF stage ensures that continental stations and short-wave signals are of real entertainment value, delayed AVC and I.I. Detection are used. Guaranteed for 2 years, **£14/18/6** (inc. P.T.).

Charles
AMPLIFIERS (SALES) LTD

181 KENSINGTON HIGH STREET, LONDON, W.8 Phone : WEStern 3350

YOU COULD MAKE AN AIRCRAFT "talk"

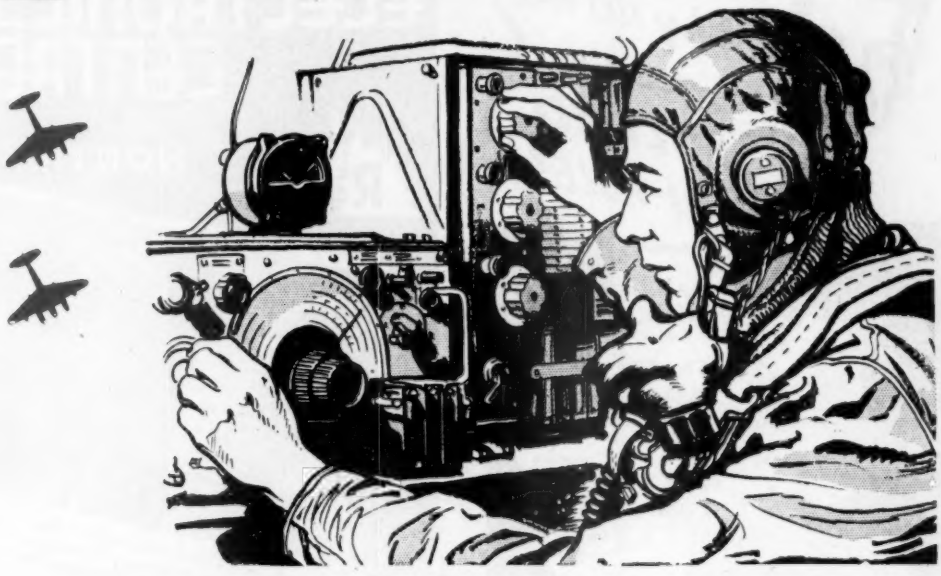

A Lincoln, a Hastings, a Sunderland could no more fly without its Signaller than the "Queen Elizabeth" could sail without her Radio Officer. Often flying long distances, the Signaller maintains communications by keeping in touch with other aircraft and Ground Stations. He is not only a skilled wireless operator but also an expert operator of radar navigational aids and secret radio devices. To qualify for this fascinating and important career, you must first satisfy the R.A.F.'s high standards of intelligence and physique. If you can, you will be certain of N.C.O. rank: and, later on, have a good chance of gaining a commission.

There are also special opportunities for certain Qualified Pilots, Navigators and Signallers who are above the normal age limits for direct entrants.

★ *If you are between 14 and 17—and keen—join the* AIR TRAINING CORPS. ★

Fly in the

ROYAL AIR FORCE

and be trained to lead!

TO: ROYAL AIR FORCE, (DEPT. W.D.9D.) VICTORY HOUSE, LONDON, W.C.2.

★ *Send details of* (1) *direct entry for flying duties* (2) *special schemes for ex-pilots and navigators (give previous rank)* (3) *special schemes for ex-signallers.*

* *delete two of these.*

NAME.....

ADDRESS .....

AGE..... .....

Applicants from the U.K. only.

—because we have recently completed demonstrations in the areas shown above, and proved to dealers and others that the Model 63A Folded Dipole gives an extraordinarily good picture in districts previously regarded as "black" areas.

The Model 63A has both gain **AND** broad bandwidth and is the foremost correctly matched high gain Television aerial today. Model 63A with 10ft Dural Mast, **£10/10/-** retail (extra for 16ft. mast **£1/8/-**).

Aerialite Limited are the actual manufacturers of all Aerial Equipment for Radio and Television, and we make a full range of Co-axial and Air-spaced Feeder Cables in our Laboratory controlled factories. Lists supplied on request.

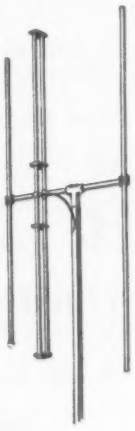

Aerialite LTD.

CASTLE WORKS, STALYBRIDGE, CHESHIRE.

ELECTRONICS CENTRE of the NORTH

R & P

Typical example of Cintel Electronic Metal Detector installed on Biscuit Conveyor and fitted with automatic ejector mechanism for removing contaminated biscuits.

- **DISTRIBUTION** Suppliers and Stockists of all types of Electronic Instruments and equipment.
- **COMPLETE INSTALLATIONS ENGINEERED.** Metal Detection. Batch Counting. Electro-chemical Controls. Radiation Thickness Measurement.
- **DESIGN of ANCILLARY EQUIPMENT**
- **MAINTENANCE & SERVICE**

AGENTS FOR

CINEMA-TELEVISION LTD.
MULLARD ELECTRONIC PRODUCTS LTD.
BALDWIN INSTRUMENTS.
KELVIN & HUGHES STRAIN AND PEN RECORDERS.
COSSOR OSCILLOSCOPES.
FURZEHILL LABORATORIES.
WAYNE KERR LABORATORIES, and all leading manufacturers of electronic instruments

Write us to add your name to our mailing list for regular information on new instruments and development.

F. C. ROBINSON & PARTNERS LTD
287 DEANSGATE MANCHESTER
DEAnsgate 6601

We've no YES-MEN at Keighley

...they're all KNOW-MEN

IT isn't always easy to resist the suggestion that price is the final consideration when selling in a competitive market. That is why we employ a team of knowledgeable, strong-willed "know-men" specially briefed to reject any compromise with quality.

We at Keighley are not satisfied by the knowledge that each switch we turn out will function correctly when it leaves our hands — we must also know that it will continue to do so throughout the life of the appliance it is designed to control.

Only then can our "know-men" feel satisfied that their job is well done. And—secure in the knowledge that fundamental simplicity of design, meticulous inspection at each production stage and rugged construction have provided a more than adequate margin of electrical and mechanical safety—they can then turn their attention to the unravelling of the next knotty problem.

And how much extra does the discriminating appliance manufacturer pay for this higher standard of quality? In a word — nothing. For the price he pays for his Cutler-Hammer Switches is immediately reflected in longer trouble-free service, reduced maintenance costs and enhanced goodwill for his product.

"THE SWITCH PEOPLE"

NSF

CUTLER-HAMMER
APPLIANCE SWITCHES
C-H

BRITISH N.S.F. CO. LTD
KEIGHLEY · YORKS
Phone: Keighley 4221/5 Grams: ENESEF, Keighley
LONDON OFFICE: 9 Stratford Place, W.1. Phone: Mayfair 4234
Licensees of Igranic Electric Co. Ltd. for the above products of Cutler-Hammer Inc. Milwaukee, U.S.A.

● Other British N.S.F. Products include: 'OAK' Rotary, Push-button and Slider switches; Carbon and wire-wound potentiometers for Television and Radio applications.

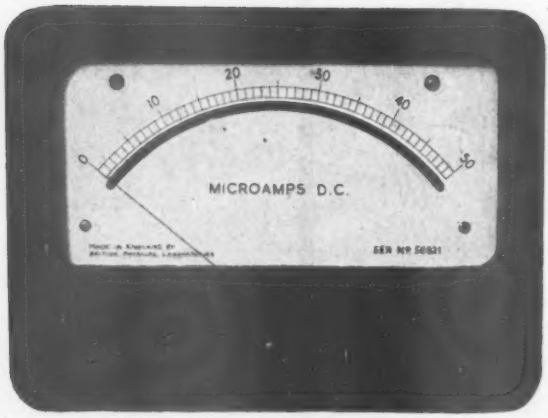

SIZE	2½"	3½"	5"
RANGE	25μA to 50A	10μA to 50A	10μA to 50A

PRICE

50μA	62/-	76/-	105/-
200μA	50/-	61/-	95/-
1mA	42/-	54/-	87/-

(Export prices on application)

All sizes available with MIRROR SCALE

1st Grade Accuracy

SENSITIVE PANEL MOUNTING METERS

For particulars of these and our full range of measuring instruments write to :—

BRITISH PHYSICAL LABORATORIES

HOUSEBOAT WORKS · RADLETT · HERTS · Telephone: RADlett 5674-5-6

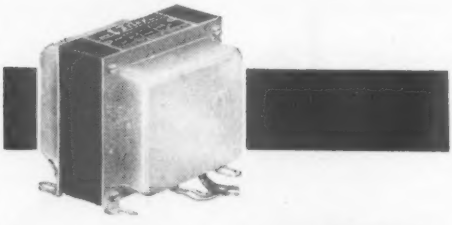

MAINS TRANSFORMERS & CHOKES

Varley REGD. TRADE MARK

All "Varley" products are manufactured from the highest quality materials.

Transformers, etc., are individually wound and have interleaved windings with ample insulation, ensuring freedom from breakdown.

The comprehensive range of Shielded and Open type Transformers available meets the requirements of every circuit. Write for list, etc.

MADE BY

OLIVER PELL CONTROL LTD

CAMBRIDGE ROW · WOOLWICH · S·E·18

Telephone WOOLWICH 1422

THE NEW BRADMASTER MODEL 5 TAPE DESK *for* 1951

● Built to professional standards ● Two speeds—3¾ and 7½ inches per second ● Fast wind and rewind—full reel rewound in 1½ minutes ● Heavy alloy flywheel. Freedom from "wow" and "flutter" ● Double servo brakes on each hub ● Push Button control ● Three heavy duty motors ● Three shielded Bradmatic heads ● Size : 13¾in. x 15½in. x 6½in. deep.

PRICE : £37.10.0

A PLUG BOX can also be fitted to the above equipment containing three compartments which provide shielding for the head leads and eliminating hum and cross talk. Also fitted with three coaxial plugs and sockets, facilitating connection of the desk to amplifiers, etc. **PRICE** (fitted underneath desk) **£1.5.0**

Hi-fidelity magnetic sound heads :	
type 5 R.P. (record/play head)	£3. 5.0 each
type 5 E (erase head)	£3. 5.0 ,,
Super fidelity magnetic sound head, type 6 R.P. (record/play head)	£3.15.0 ,,
Screening Cans, best quality (all mumetal)	8.0 ,,
composite (constructed of steel and mumetal)	4.6 ,,
Oscillator coils	8.0 ,,
Tape on 7in. reels, 1,200ft.	
Emitape, type 65	£1. 5.0
G.E.C. Grade "A"	£1.10.0
Durex type, MC I—III	£1.15.0

Trade supplied. Send for lists to sole Manufacturers :—

BRADMATIC LIMITED

STATION ROAD, ASTON, BIRMINGHAM, 6

Telephone: East 0574. *Telegrams:* Bradmatic, Birmingham

VALVES For SPECIAL PURPOSES

27M1 High Vacuum photo-multiplier

WITH HIGH RESPONSE IN THE VISIBLE REGION

Because of its high sensitivity, low noise level, low dark current and freedom from distortion, the Ediswan Mazda 27M1 may be used for light operated relays, for film scanning, facsimile transmission and in scientific research involving low light levels: and in many applications its small size is an advantage. The 27M1 is capable of multiplying very small currents produced under weak illumination by an average value of one million times when operated at 100 volts per stage.

The resultant output current is a linear function of the exciting illumination under normal operating conditions. Since secondary emission occurs instantaneously, the frequency response is flat up to the frequencies at which transit time becomes a limiting factor.

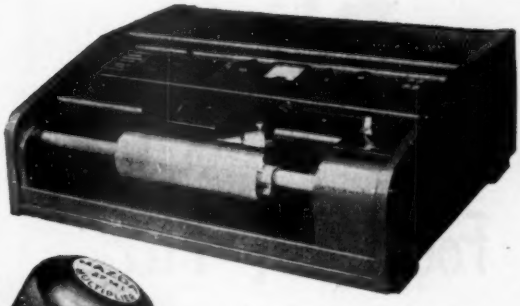

Muirhead Phototelegraphic Transmitter, Type D-106-A

A particular application of the 27M1 photo-multiplier is in the Muirhead Phototelegraphic Transmitter, type D-106-A where its above mentioned properties enable a compact and highly efficient instrument to be obtained.

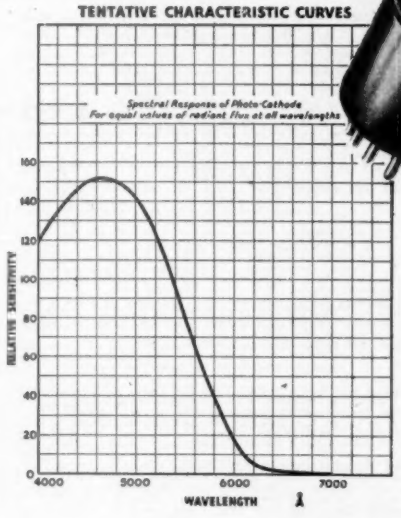

RATING

Maximum Anode Supply Voltage (volts)	*1,100
Maximum Potential Anode/Secondary cathode K10 (volts	120
Maximum Anode Current (mA)	1.0
Cathode k1 sensitivity (μA/lumen)	†10

(Vk1=0, all secondary cathodes joined at 100 volts)

* With respect to cathode.

† The sensitivity is on the basis of a lamp colour temperature of 2700°k and a light area of 4 mm x 20 mm

Further details of the 27M1 and other photo-multipliers are available on request.

EDISWAN

MAZDA

THE EDISON SWAN ELECTRIC CO. LTD., 155 Charing Cross Road, London, W.C.2

Member of the A.E.I. Group of Companies

RV32

Focus on 'Flu...

Electron microscopes magnifying 150,000 times are now able to throw much more light on the infinitesimal 'flu germ, making new medical attacks on the disease possible.

By similar concentration - of skill, effort and experience, on one object only - Parmeko produce transformers that are used throughout the Electronic and Electrical Industries, one application being the electron microscope itself.

PARMEKO *of* **LEICESTER**

Makers of Transformers for the Electronic and Electrical Industries

THE THREE 'R's

3", 3½", 6"
RECTANGULAR INSTRUMENTS
by
PULLIN

Series 30

Series 35

These three rectangular instruments are designed on symmetrical lines, thus giving a distinctive clear, open scale and pleasing appearance. Each size available in all standard ranges The Series 65 and 35 can be fitted with dial illumination.

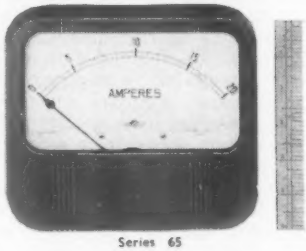

Series 65

MEASURING INSTRUMENTS (PULLIN) LTD.
Electrin Works, Winchester Street, Acton, London, W.3.
Telephone ACOrn 4651/3 & 4995

M.R. SUPPLIES Ltd

The following selected material, being in new or otherwise excellent condition, is guaranteed to be in perfect electrical and mechanical order. All prices nett. No faulty goods ever despatched.

THERMOSTATS. (Ex-A.M.) Switch 1.5 amp. at 240 v. On at 32 deg. F, off at 49 deg. F, therefore right for frost protection. **4/6** each. **45/-** doz.

CAPILLARY THERMOSTATS. Range 55/90 deg. F. Switch with 5 amps. at 240 v. Tube 3ft. long. For air or immersion. **17/6** (despatch 1/-). Also High Temperature model, in at 115 deg. C. (239 deg. F.), and out at 100 deg. C. (238 deg. F.) with 5ft. tube, switch 10 amps. at 240 v. **18/6** (despatch 1/6).

VACUO THERMO-COUPLES (S.T.C.) 5 m/a. (10 m/a. max.). Unmounted, with four leads. In 2in. by 1in. vacuum tube, brand new, boxed **8/6**.

SHADED POLE INDUCTION MOTORS (Hoover). Brand new 200/250 v. A.C. R.P.M. constant at 1,200, very silent running. For wire recorders, cine projectors, gram. motors, cooling and extractor fans, stirrers, etc. Body 3¼in. × 3¼in., with shaft each end. **29/6** (despatch 1/-).

AIR COMPRESSORS, superior model with steel cooling fins. Up to 300 lb. sq. in. Overall length 8½in. With sunk 6-key splined drive, **29/6** (despatch 1/-). **PRESSURE GAUGES** (Bourdon) 0/350 lbs. sq. in. In sturdy brass housing, 3in. dial, 4in. mounting flange, in makers' boxes, **14/6** (despatch 9d.).

REDUCTION GEAR BOXES (Admiralty—Mercedes Benz). Ratio 25 : 1 down. Steel worm to bronze gear, worm 1in. dia., gear 4in. dia. (approx.), suitable for high duty. With shafts and couplers. Housing 6in. by 7in. high. New, slightly soiled, **37/6** (despatch 2/-).

AIR BLOWERS, fitted Brooks 1/8th H.P. (1/4th H.P. frame). Induction motor, 220/250 v. A.C. 2,800 r.p.m. Outlet 3in. × 2in., reconditioned as new. **£5/7/6** (despatch England 5/6). Also Keith, Blackman model rated for 220 v. D.C. 3,000 r.p.m. Round outlet 3¼in. internal (4in. hose connection). Overall length 16in., height 13in., brand new, paint slightly soiled, **£7/10/-** (despatch England 8/6). Also **MINIATURE BLOWER**, operation 24/36 v. A.C./D.C. 7,000 r.p.m. Overall length 4¼in., **15/-** (despatch 1/-).

OVERLOAD AND SHORT CIRCUIT TRIPS, Ironclad housing 7in. × 4in. × 2¼in. 200/250 volts A.C. only. 5.8 amp., **16/6**, 15 amp., **19/6**. Switch opens circuit on accidental short or overload and can be closed again when cause is remedied—saving fuse replacements. Excellent bargain—sturdily made. (Despatch of either 1/6).

DISTRIBUTION BOXES, brand new. Fitted 7 Slydlok Fuses (5, 15 and 30 amp.), 2 × 30-amp. two-pole Rotary switches, 1 × 10-amp. Rotary switch, 1 Tumbler switch, 1 × 10-amp. 3-pin socket. Smartly housed in metal case 15¼ × 11¼ × 3in. deep with hinged top section giving access to fuses, enamelled ivory. Useful in laboratory, darkroom, kitchen, etc., **29/6** (despatch 3/-).

DELCO EXTRACTOR FANS, high duty 12in. model. 220/250 v. A.C. Mounting ring 14in. dia. Induction motor **£5/17/6**. Or with protective grille, **£6/5/6**, both carriage paid England and Wales.

SMALL EXTENSION SPEAKERS, made by Goodmans for Admiralty. Fitted 3½in. P.M. m/coil unit (15 ohms) in neat cast housing 6¾ × 3 × 3¼in., with vol. control and mounting lugs. Useful also for intercom., **15/-** (despatch 1/6).

EVERSHED OHM-METERS, second-hand ex-Govt., tested, less battery. Range 0.1-200,000 ohms, in two scales. With leads, prods, carrying case, etc. True ohm-meters and very useful instruments, **65/-** (despatch 1/6).

EVERSHED BRIDGE MEGGERS (250 v.) S.H. ex-Govt. Each one expertly tested before despatch. Range, Megger 0/50 ohms. Bridge, .001-100,000 ohms, shown in four digit windows, with 10/1 and 100/1 multiplier and divider. With carrying case, **£15** (despatch 4/6).

In Stock :—Range of Centrifugal and Vane Pumps, Vitavox P.A. Units and Horns, Speaker Tripods—details on request.

M.R. SUPPLIES Ltd., 68, New Oxford Street, London, W.C.1
Telephone : MUSeum 2958

1

The problem of supplying the Corner Ribbon Loudspeaker to the public is not easy. The testing of loudspeakers for instance becomes increasingly difficult the more the loudspeaker approaches perfection. This, together with the desirability of some control over its installation, severely limits the number which can be produced and thereby prohibits general release for random trade distribution. Enquiries in the first place should be sent direct to us at Huntingdon.

2 Tracing distortion can be divided into three separate components. One component can (theoretically) be overcome in good pick-up design. The remaining two are fundamentally present in the recording system used and each is a definite though different function of the response characteristic. The optimum correction varies with the recording and, it appears, can best be met by controlling the balance of very high harmonics, using just sufficient slope necessary to offset the slope or rate at which distortion increases with frequency.

IT is now nearly eighteen months since we first published details of the Corner Ribbon Loudspeaker (1). There is evidence that the use of these loudspeakers in a number of leading laboratories is undoubtedly resulting in a higher accuracy in subjective work on the ideal requirements for a monaural system (i.e. practical radio and record material).

In our own programme, we have used the speaker in an attempt to investigate the relationship of tracing distortion to the response characteristic (2). This analysis has resulted in the design of the Q.U.A.D. amplifier, the controls of which correct for the programme or recording IN FULL because the compensation for distortion is separated from the control of balance.

We suggest you write for the Q.U.A.D. booklet. Those skilled in the art of acoustics will readily appreciate the advantages of the more important developments in the specification detailed therein.

Since at least one major limitation is present in reproduced sound, it follows that final judgment of the whole can only be subjective. When listening to the Q.U.A.D. amplifier, notice particularly how the best possible quality is extracted from each and every programme and recording without upsetting correct orchestral balance.

The Q.U.A.D. amplifier complete in two units as illustrated £33.

ACOUSTICAL MANUFACTURING CO LTD
HUNTINGDON · HUNTS · TEL: 361

Simphonic

• PORTABLE • SELF CONTAINED • EASY TO OPERATE • HIGHLY EFFICIENT

Brief Specification :

WORKING VOLTAGE	—200/250 volts A.C. 50 c/s.
TAPE SPEEDS	—7½in. sec. and 12in. sec.
RUNNING TIMES	—30 minutes and 20 minutes.
REWIND	—Provision for fast rewind or forward running of complete spool in one minute.
ERASING	—Any recording may be erased. Erasure is automatic, preventing double exposure
OUTPUT	—2 watts.
TERMINATIONS	—Inputs for microphone and radio and outlets for external speaker.
DIMENSIONS	—18½ x 13½ x 10in.
WEIGHT	—38 lb. complete.
ACCESSORIES	—Supplied complete with microphone, tape and spools.

Simon SOUND SERVICE

Recorder House, 48-50 George Street, Portman Square, London, W.1, England

Telephone : **Welbeck 2371 (4 lines)** *Telegrams :* **Simsale, Wesdo, London.** *Cables :* **Simsale, London**

L. P. RECORDS
sound better still . . .
if you fit

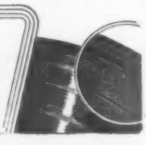

GRAMPIAN

MODEL 492 4-watt AMPLIFIER UNIT

For A.C. mains, 110/260 v. Gives necessary bass compensation for L.P. records with separate bass and treble tone controls. Fitted with switch to correct frequency response for 33⅓ or 78 r.p.m. records and also radio input position.

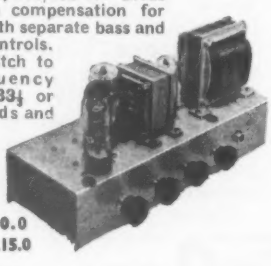

Retail price **£17.0.0**
Cover extra **£1.15.0**

Write for details to

GRAMPIAN REPRODUCERS LTD
9 HANWORTH TRADING ESTATE, FELTHAM, MIDX.
Telephone : **FELtham 2657/8.** *Telegrams :* **"Reamp. Feltham."**

18210C

Instruments for Research and Industry

Model 26 LABORATORY VALVE VOLTMETER

This instrument sets an entirely new standard of performance in mains operated valve voltmeters. It measures d.c. and a.c. voltages from 0.2 to 250v. and has an upper frequency limit of 200 Mc/s. Four resistance ranges extending up to 500 megohms and a decibel range are included.

The meter is a six inch movement with a mirror scale.

★ *Accuracy on all voltage ranges conforms to B.S. 89 : 1937 for First Grade moving coil meters—a performance which has not hitherto been claimed for any valve voltmeter.*

ELECTRONIC INSTRUMENTS LTD
17 PARADISE ROAD RICHMOND SURREY ENGLAND

$E=mv^2$

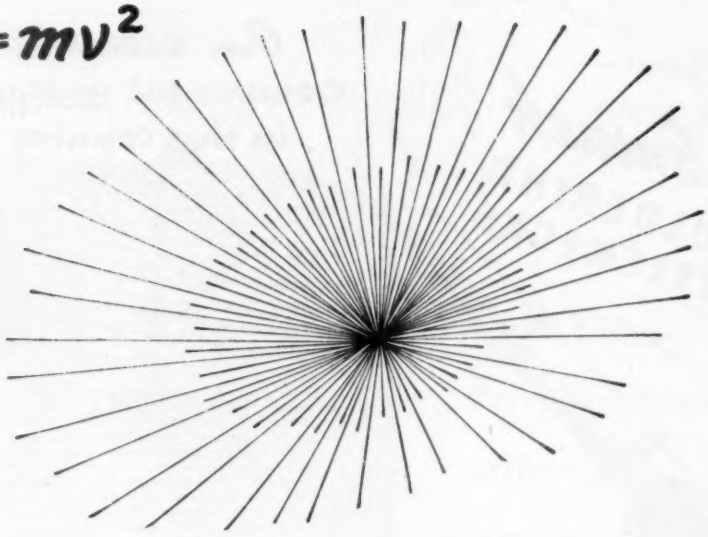

... and the future

It is inevitable that nuclear energy will one day become a normal part of the routine of our lives, its use an every day occurrence, its control as consistently conformable to rule, and as much taken for granted, as electricity is today.

It is obvious that this control will require new forms of insulation, and undoubtedly somewhere in their construction porcelain will play a vital part... and it is equally obvious that only the finest porcelain will be good enough.

This being so it is certain that the stamp of Taylor Tunnicliff will be as much impressed on the future as it is upon the insulators of modern times.

TAYLOR, TUNNICLIFF PORCELAIN

TAYLOR, TUNNICLIFF & CO. LTD. *Head Office*: EASTWOOD · HANLEY · STAFFS · Stoke-on-Trent 5272-4
London: 125 HIGH HOLBORN, W.C.1. Holborn 1951. *Factories at*: Hanley, Stone and Longton, Staffs.

Smash SOLDERING BOTTLENECKS

with

Wolf ELECTRIC SOLDERGUNS

TYPE 51

Whatever the operation it can be done better, faster and cheaper with Wolf Solderguns. For example, there is nothing to touch the automatic gun (illustrated above) for efficiency and economy in modern assembly shops. It has automatic feed, a trigger solder-feed action and perfect tool balance. There are Wolf models for every type of soldering from fine instrument to heavy industrial work. Only Wolf offer all these soldering advantages—

OFF-STRAIGHT EASY-GRIP HANDLE · PERFECT CONTROL · QUICKER HEAT-UP · LOCALISED HEAT · LOW CURRENT CONSUMPTION · MAINTAINS CORRECT HEAT · A MODEL FOR EVERY PURPOSE

5 OTHER MODELS TO CHOOSE FROM

★ Obtainable from all leading tool merchants and factors.

Wolf ELECTRIC SOLDERGUNS

WOLF ELECTRIC TOOLS LTD., PIONEER WORKS, HANGER LANE, LONDON, W.5

B9

An essential component unique in this country

Seamless, one-piece, metal bellows combining the properties of a compression spring capable of repeated flexing, a packless gland, and a container which can be hermetically sealed. Hydraulically formed by a process unique in this country, they are tough, resilient, with a uniformity of life, performance and reliability unobtainable by any other method.

FOR: Automatic coolant regulation. Movement for pressure change. Packless gland to seal spindle in high vacua. Reservoir to accept liquid expansion. Dashpot or delay device. Barometric measurement or control. Pressurised couplings where vibration or movement is present. Dust seal to prevent ingress of dirt. Pressure reducing valves. Hydraulic transmission. Distance thermostatic control. Low torque flexible coupling. Pressure sealed rocking movement. Pressurised rotating shaft seals. Aircraft pressurised cabin control. Refrigeration expansion valves. Thermostatic Steam Traps. Pressure amplifiers. Differential pressure measurements. Thermostatic operation of louvre or damper.

Write for List No. N800-1.

Drayton 'Hydroflex' METAL BELLOWS

Drayton Regulator & Instrument Co. Ltd., West Drayton, Mdx. · W. Drayton 2611

Widney-DORLEC

REGISTERED TRADE MARK

CABINET SYSTEM

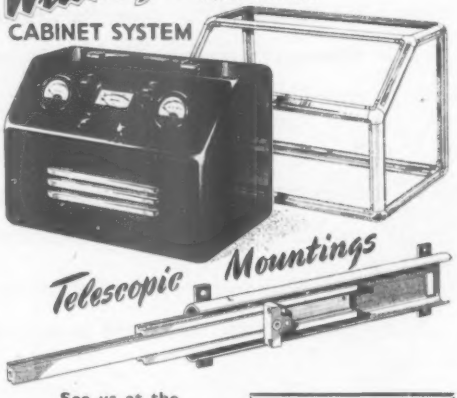

Telescopic Mountings

See us at the R.E.C.M.F. Exhibition STAND 104 APRIL 10th, 11th and 12th.

Technical Advisor : C. H. DAVIS 59, BROMPTON RD. LONDON, S.W.3.

A Widney PRODUCT

SOLD ALL OVER THE WORLD

MANUFACTURERS

ESTABLISHED 1890

HALLAM, SLEIGH & CHESTON LTD WIDNEY WORKS · BIRMINGHAM · 4

Phones: Aston Cross 0914 (4 lines) · Grams: Superfine, Birmingham 6

THE COSSOR DOUBLE BEAM OSCILLOGRAPHS

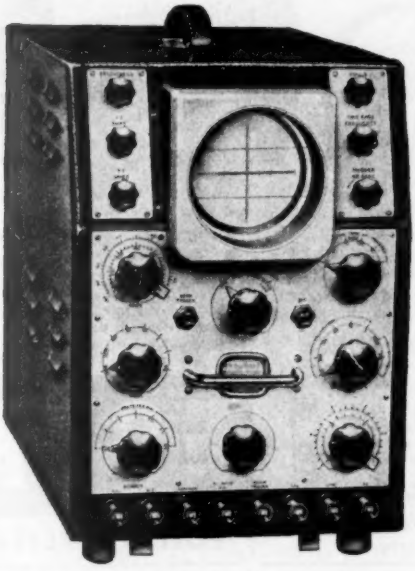

Can this Instrument solve a problem for you?

Here are some details of Model 1049 as illustrated: The Double Beam Tube presents two simultaneous independent traces over the full diameter of a 90 mm. screen, and provision is made for the measurement of both input voltage and time upon the calibrated dials of the instrument. The Oscillograph is particularly suitable for obtaining permanent photographic records using the Cossor Model 1428 Camera for which a Motor Drive Attachment Model 1429 is available.

Widely different industries are daily finding new uses for the COSSOR Double Beam Oscillograph. Sometimes it provides the answer to an industrial problem of long standing. The tracing and measurement of noise, strain and vibration are typical everyday applications of this versatile instrument which is already helping engineers in industries as far apart as brewing and the manufacture of jet engines. Call on our technical advisory staff if you have a problem. They will quickly let you know whether the Oscillograph can help you.

COSSOR

Double Beam OSCILLOGRAPHS

Please address enquiries to:
A. C. COSSOR LTD., INSTRUMENT DIVISION (Dept. G), HIGHBURY GROVE, LONDON, N.5.
Telephone: CANonbury 1234 (30 lines) C1.21

VARIABLE- BUT DEPENDABLE

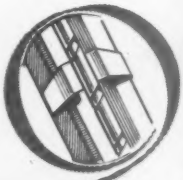

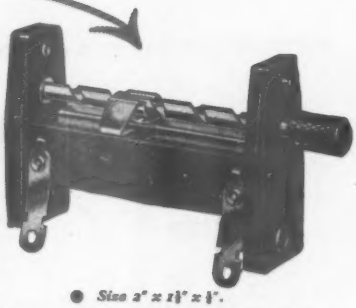

The value of the new EGEN midget pre-set variable resistor to the television and electronics designer and radio engineer has been enhanced by a new double slider, giving greater stability and making accurate adjustment easier. It has a rating of 2½ watts and is designed for panel or chassis mounting; available in any value from 10 ohms to 25,000 ohms.

- *Size 2" x 1½" x ¾".*
- *Worm drive for smooth action.*
- *Rachet action prevents over-winding.*
- *Silver-plated solder tags.*

This new resistor can be supplied in groups mounted to a common panel, suitably engraved, if required.

R.E.C.M.F. Exhibition — STAND No. 26

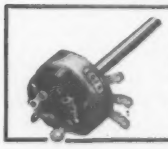

—and a better carbon potentiometer
The complete electrical stability of the EGEN POTENTIOMETER is achieved by a specialised method of carbon deposition. Perfect mechanical action further contributes to its outstanding reputation for reliability.

EGEN ELECTRIC LTD.
Charfleet Industrial Estate, Canvey Island, Essex. 'Phone: Canvey 691

EGEN
POTENTIOMETERS

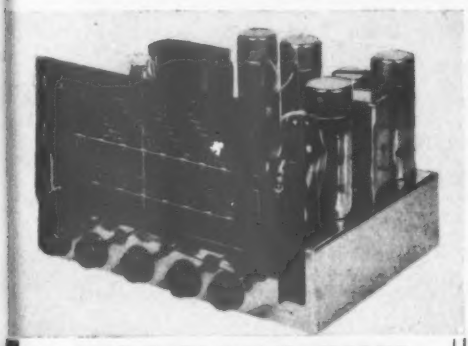

BUILD WITH OUR HANDSOME HOME CONSTRUCTION UNITS !

ANYONE can build this magnificent SUPERHET !*

Using the new and improved unique point-to-point Construction Sheets for our famous 6 v. A.C. Super (with the latest 40 Tuning Unit) you can, for an evening's entertaining construction, complete a receiver (without ANY test gear) whose range and performance will at least equal that of commercially built units at double the cost !

As our delighted friends already know the secret is our pre-aligned **40 TUNING UNIT** comprising the famous 3 band 40 Coil pack, " **MM** " **I.F.T.'s**, new 8in. x 6in. 3 colour Dial and J.B. 3-gang- READY ALIGNED, MATCHED and SEALED ! Price **99/6** (inc.) or **£6 0 3** with J.B. S.L.S. spin-wheel Tuner.

NOTE for Connoisseurs :—Our 40 Feeder using above Tuning Unit with HI-FI switching for local stations (and Gram.) with 10w. push-pull Quality Amplifier and variable negative feedback is the TOPS ! (Ideal with Williamson.)

* Letters of praise received daily from beginners and experts !

F.J.M., of S.E.14, states : " . . . it does all you claim. . . . . I had the surprise of my life when it went perfectly first time—it is the best set I've ever heard. "

For constructional details, illustrations, eleven circuits, data, etc., send **1/6** NOW for LATEST EDITION of " Home Constructor's Hand-book. "

All items supplied by Mail DIRECT ONLY from :

RODING LABORATORIES
70, LORD AVENUE, ILFORD, ESSEX

SILVERED MICA CAPACITORS

SMALL SIZES
HIGH STABILITY
CLOSE ELECTRICAL LIMITS

STABILITY RADIO COMPONENTS

COMMERCE ESTATE, WOODFORD AVENUE, LONDON, E.18. Telephone : BUCkhurst 6501/2

. . . and talking of 'mikes'* and 'speakers' . . .

. . . which, of course, we do nothing else but, it is as well to remember for your own peace of hearing that we at VITAVOX have specialised in the design and manufacture of sound reproduction equipment for nearly a quarter of a century and are still endeavouring to satisfy other people's ears but not our own. Below are depicted the principal products in the VITAVOX range of which we'll be happy to send you full details of any or all on request. If you have a really good dealer near you, you can hear them for yourself.

it sounds right with VITAVOX

* we hate people who abbreviate "microphone" to "mike", but the advertisement looks even more stupid if we say "mics".

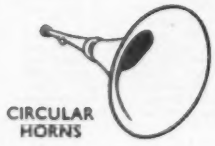
CIRCULAR HORNS

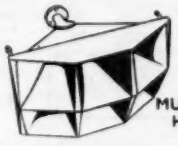
MULTICELL HORNS

TYPE "A" MICROPHONES

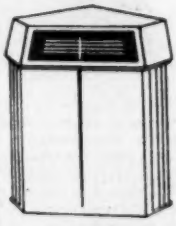
KLIPSCHORN REPRODUCERS

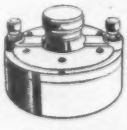
PRESSURE UNITS

CONE SPEAKERS

TYPE "B" MICROPHONES

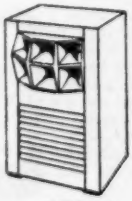
BITONE REPRODUCERS

VITAVOX LIMITED · WESTMORELAND ROAD · LONDON · N.W.9 · ENGLAND

Telephone: COLINDALE 8671. Grams: VITAVOX, HYDE, LONDON. Cables: VITAVOX, LONDON, ENGLAND

5442

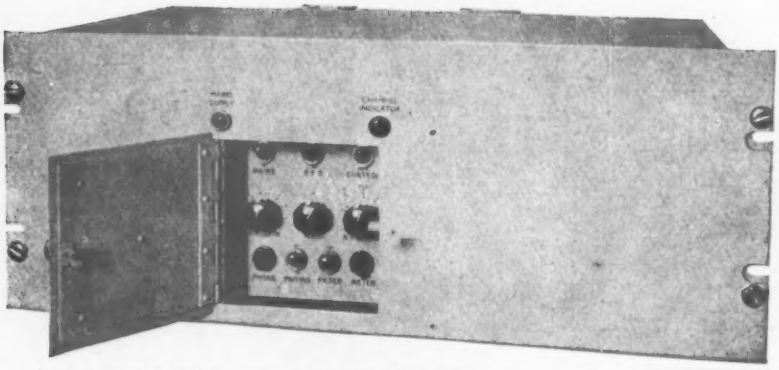

An Important Receiver...

. . . in the extensive Redifon range of communications radio is the R.93—a fixed frequency, single channel receiver covering 2 to 20 Mc/s. Its crystal controlled oscillator and other special features make this the ideal unattended receiver for point-to-point and ground-to-air channels and it has full remote control facilities. Specialised applications of the R.93 include monitoring, diversity reception or frequency shift working.

The Redifon range includes MF, HF and VHF transmitters, receivers, radio telephones, navigational aids, AF amplifying systems and other electronic equipment. Enquiries for single units or complete networks including aerials, masts, power supply, land line amplifiers, remote controls and other apparatus are welcome.

AIRPORT **Redifon** Radio

Radio Communications Division

The R.93 is designed to the specification of International Aeradio Limited

REDIFON LIMITED, BROOMHILL ROAD, WANDSWORTH, S.W.18

DESIGNERS & MANUFACTURERS OF RADIO COMMUNICATION & INDUSTRIAL ELECTRONIC EQUIPMENT

Phone: VANdyke 7281

Precision ELECTRICAL MEASURING INSTRUMENTS *by* **SIFAM**

ENGLAND

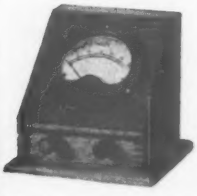

This Bench type portable instrument is used in many laboratories where consistent accuracy is demanded. Single or multi ranges for D.C. or A.C., calibrated to customers requirements. Sizes 3½", 4" or 6" instruments. Accuracy B.S. First Grade.

The 4½" square type instrument is the latest design embodying all the latest improvements. It has a large open scale so much desired for modern switchboard practice. The case is of black bakelite, and the instrument can be supplied in all ranges for D.C. It can be also fitted with a metal rectifier for A.C. working. Accuracy B.S. First Grade.

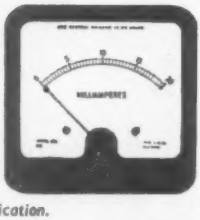

Prices on application.

PROMPT DELIVERY AND TWELVE MONTHS GUARANTEE

SIFAM ELECTRICAL INSTRUMENT CO., LTD.,
LEIGH COURT - TORQUAY - *Telephone: TORQUAY 4547/8*

DENCO *TWO SHOTS FROM OUR LOCKER*

WE AIM AT PERFECTION WITH REAL VALUE FOR MONEY

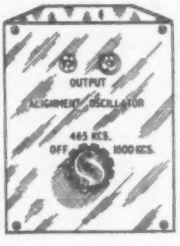

D.A.O.I. ALIGNMENT OSCILLATOR.

This unit provides a modulated signal for the alignment of I.F. amplifiers and associated circuits. The two standard frequencies of 465Kc/s. and 1,600 Kc/s. are selected at the turn of a switch. The modulation frequency is approximately 800 cps. An output of approximately 50 MV. is available at the terminals. All supplies are derived from one U.10 cell and one 1289 battery inside the unit. Consumption is 50 MA. Single valve type DL.92 is used. Dimensions of case: Width 3¾in., Depth 2¾in., Height 4¾in. complete but less battery.

47/6

T.P.A.I. TELEVISION PRE-AMPLIFIER.

A really first class amplifier, suitable for any transmission and any make of receiver—The price? Just 29/6 complete with EF91 valve

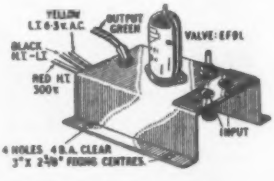

The above from all good class Stockists, or in the case of difficulty write us direct. Full details are available.

DENCO (CLACTON) LIMITED
OLD ROAD, CLACTON-ON-SEA, ESSEX.

NITROGOL ...itors

QUALITY has always been the basis of Dubilier technical supremacy and in the television field too, this factor has confirmed Dubilier's lead in the international field.

Thus it is natural that only components of tested quality and worth will satisfy television engineers. Experience has proved that Dubilier Nitrogol Capacitors, acknowledged by technicians throughout the world for their reliability, are best suited to the manufacturer of television apparatus.

In such applications as radar, amplifiers, undersea cable repeaters and industrial electronic applications, Nitrogol Capacitors are again a prime necessity.

Comprehensive catalogues giving detailed information of capacitors and technical service are available upon request.

DUBILIER
CONDENSER CO. (1925) LTD.

DUBILIER CONDENSER CO. (1925) LTD., DUCON WORKS, VICTORIA ROAD, N. ACTON, LONDON, W.3
'Phone: Acorn 2241 (5 lines). 'Grams: Hivoltcon, Wesphone, London. Cables: Hivoltcon, London. Marconi International Code

D38A

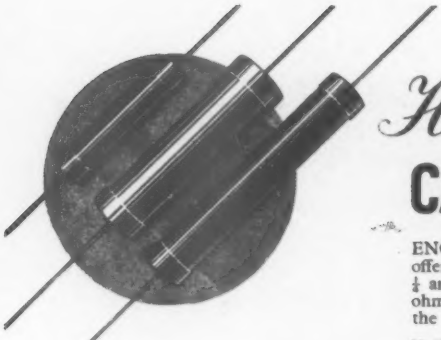

High Stability
CARBON RESISTORS

ENGINEERS will be interested in the improved stability offered by Painton Resistors. e.g., Type Approval of the ¼ and ½ watt Painton Types has recently been extended to ohmic values greatly exceeding those otherwise shown in the "Blue Book."

Full details on request.

BUYERS will be interested in competitive prices and rapid and reliable delivery. Bulk supplies of most types are available at short notice. Quotations will be gladly supplied on request.

Control by
PAINTON

PAINTON & CO LTD · KINGSTHORPE · NORTHAMPTON · *TELEPHONE 2820*

As specified for conversion of the Type 25 unit of the TR.1196. Type 18 and war-time utility receivers and others

WITH THE
OSMOR
'Q' COILPACKS
SUPERHET and T.R.F.

The OSMOR "Q" Coilpack does not "whistle while it works" but gives you perfect performance in every way. And it saves time, money and hours of wasted effort puzzling over complicated wiring circuits. Just 5 connections, 5 minutes' work and the job is done—and well done!

Send stamp for FREE new circuits, lists of Coils, Coilpacks, Dials and all Radio Components, etc.

★ **New wavelength scales** for Type A dials **8**/- each

OSMOR RADIO PRODUCTS LTD. (Dept. W.16)
BRIDGE VIEW WORKS, BOROUGH HILL, CROYDON, SURREY
Telephone: Croydon 1220

Any Voltage regulation problems?

Do power cuts upset your production?

A Variac infinitely variable voltage regulating transformer will probably solve your problem. Write for 32 page Catalogue V549 which gives full details of the Variac transformers and their manifold applications.

CLAUDE LYONS LTD

180 Tottenham Court Road, London, W.1. *Tel: MUSeum 3025/6*
and 76 Oldhall Street, Liverpool 3, Lancs.

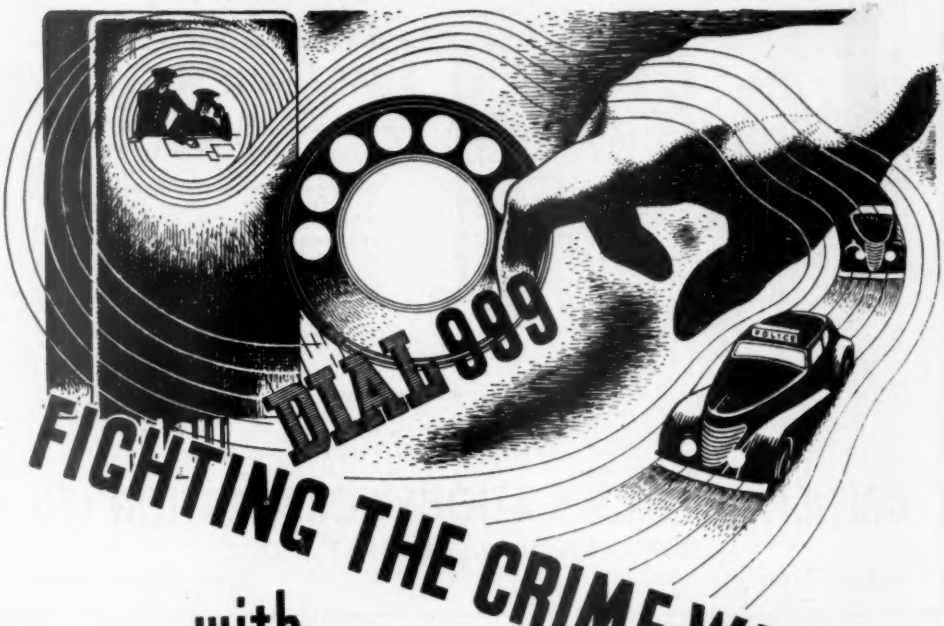

FIGHTING THE CRIME WAVE...

with G.E.C.

QUARTZ CRYSTAL UNITS

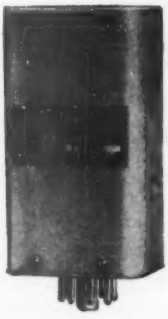

The Police "999" emergency call system depends for its successful operation on instantaneous radio communication between Police headquarters and the fleet of patrol cars. Radio equipment in the patrol cars is used under the most arduous conditions but it must be available for instant use 24 hours in the day.

No wonder then that more and more Police authorities throughout the country are using G.E.C. quartz crystals in their radio equipment.

Pioneering research and experience in making over a million units, ensure a product of the highest quality. For all your quartz crystal requirements be sure to specify G.E.C.

Quick delivery service for urgent requirements for experimental or replacement purposes.

Write for our leaflet QC.4904.

SALFORD ELECTRICAL INSTRUMENTS LIMITED

PEEL WORKS · SILK STREET · SALFORD · 3 · LANCS.

A SUBSIDIARY OF THE GENERAL ELECTRIC CO. LTD. OF ENGLAND

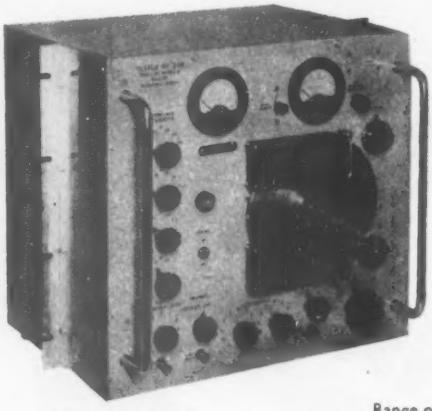

SELECTIVE

TRANSMISSION MEASURING SET

MODEL RP 3110

Designed and Manufactured for G.P.O.

This is a precision instrument for measurements on multi-circuit coaxial cable carrier systems by means of a comparison with locally generated signals of known frequency and level.

Frequency coverage : 60 Kc/s — 3 Mc/s in 7 ranges.

Calibration accuracy : below 0·2% or 2 Kc/s whichever is the greater.

Power supplies :
200 — 250 Volt, 50 c/s

Range of measurements :
through levels + 10 db to - 61·5 db
or terminated levels + 10 db to - 81·5 db
referred to 1mW in 75 ohms

BRITISH COMMUNICATIONS CORPORATION LTD.

GORDON AVENUE, STANMORE, MIDDX.

Telephone : GRIMSDYKE 2266. Cables : DISC, STANMORE.

Only with CO-AX R.F. CABLES

AIR-SPACED ARTICULATED

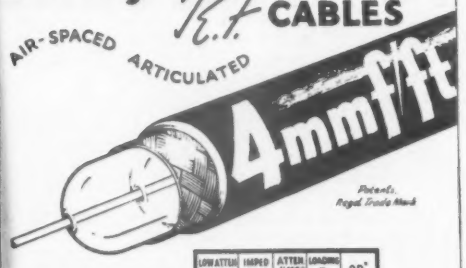

THE LOWEST EVER CAPACITANCE OR ATTENUATION

IMMEDIATE DELIVERIES

SPECIALISTS IN AIR-SPACED ARTICULATED CABLES SINCE 1929

TRANSRADIO LTD

138A CROMWELL ROAD LONDON SW7 ENGLAND

LOW ATTEN. TYPES.	IMPED. OHMS	ATTEN. db/100ft at 100 Mc/s	LOADING fm. Mc/s	Q.D."	
A1	74	1.7	0.41	0.36	
A2	74	1.3	0.34	0.44	HIGH POWER FLEXIBLE
A34	73	0.6	1.5	0.88	
LOW CAPAC. TYPES.	CAPAC. mmf/ft	IMPED. OHMS	ATTEN. db/100ft at 100 Mc/s	Q.D."	
C1	7.3	180	2.5	0.36	
P.C.1	10.2	132	3.1	0.36	PHOTOCELL CABLE
C11	6.3	173	3.2	0.36	
C2	6.3	171	2.15	0.44	
C22	5.5	184	2.8	0.44	
C3	5.4	197	1.9	0.64	
C33	4.8	220	2.4	0.64	VERY LOW CAPACITANCE
C44	4.1	252	2.1	1.03	

SPHERE INSTRUMENTS

TELEVISION ADAPTOR UNIT TYPE S.C. "88"

Adaptor Unit S.C. "88" eliminates costly troublesome conversions

IT ADAPTS THE "LONDON" - DESIGNED TELEVISION RECEIVER FOR SUTTON COLDFIELD RECEPTION — PERFECT SOUND AND VISION

Small and compact, the unit, embodying power-pack, and all the necessary "works," is simply fitted between aerial and set. Set itself is entirely untouched, and in its original state—thus retaining its full "design-efficiency." Of particular interest to "Fringe" viewers. Real saving of time, trouble and cost.
Full details supplied.

Price 7 Gns. nett

Two models : "L" for 30/35 miles radius of transmitter "F" for "Fringe" areas.

Manufacturers:

SPHERE RADIO LIMITED

HEATH LANE, WEST BROMWICH, ENGLAND

"FLEXILANT"

MOUNTINGS

"Rubber to Metal in a fine working partnership"

This group from our range of "FLEXILANT" general-purpose light, and instrument, mountings is backed by the good service manufacturers expect from us.

We investigate all mounting problems. May we investigate yours?

TYPE No. 10. Bonded Rubber Bobbins for Mountings and Couplings for use in compression and shear.

TYPE No. 38. Light instrument mounting.

TYPE No. 67. Tumbler Switch Seals.

RUBBER BONDERS LIMITED

IN ASSOCIATION WITH EMPIRE RUBBER COMPANY

(PROPRIETORS H. G. MILES LTD.)

DUNSTABLE, BEDS.

8.8.72

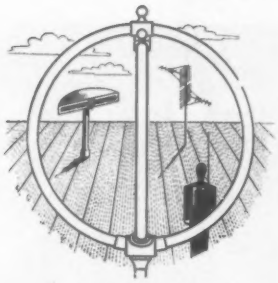

A GREAT NAME

is a stake in the future

Marconi research made radio possible. From the experiments of Guglielmo Marconi in 1895 the whole of the world's network of wireless communication and electronic vision has sprung. Many have followed Marconi, and after 50 years Marconi leads still.

Enthusiasm, patience and unshakeable faith activate the research workers of Marconi. The present and the past are their books of reference ; in their work they write the volume of the future in wireless, and all that wireless means.

Marconi

THE FIRST AND GREATEST NAME IN WIRELESS

MARCONI'S WIRELESS TELEGRAPH COMPANY LIMITED · MARCONI HOUSE · CHELMSFORD · ESSEX

HENLEY TELEVISION

AERIAL LEAD-IN CABLES *for trouble-free reception*

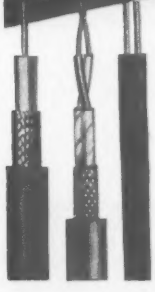

We manufacture a complete range of Television Lead-in Cables for Local and Fringe Area service ; full details sent on request.

In addition we make all types of Polythene and P.V.C. Cables for radio, radar and for all branches of H.F. work. Our long experience enables us to produce cables with specified characteristics and we shall be pleased to put forward suggestions.

(L to R): Coaxial ; Balanced Twin Screened (U.K. Pat. No. 559518); Twin Unscreened.

W. T. HENLEY'S TELEGRAPH WORKS CO. LTD.
51-53 HATTON GARDEN, LONDON, E.C.1

— towards perfection —

Most Trusted Name in Loudspeakers

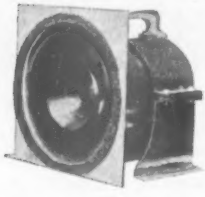

Only by the exacting skill of the craftsman in every stage of making, has the Lowther drive unit maintained its "second to none" reputation throughout the world.

LOWTHER P.M.2 drive unit for horn loading.

The supreme performance in conjunction with either Lowther P.W.I corner cabinet or Voigt Reflector corner cabinet has yet to be surpassed !

Further details gladly sent upon request :—

THE LOWTHER MANUFACTURING CO.
(The Laboratory Production unit)
LOWTHER HOUSE, ST. MARK'S ROAD., BROMLEY, KENT. Phone RAV. 5225

DATA ON THE MT57 TRIODE MERCURY VAPOUR RECTIFIER, ONE OF THE RANGE OF MULLARD THYRATRONS

LIMITING VALUES (ABSOLUTE RATINGS)

Maximum Peak Anode Voltage*	
Inverse	1000V
Forward	1000V
Maximum Cathode Current. 25c/s and above.	
Peak (for general control service)	15A
Peak (for ignitor firing service)	40A
Average (for general control service)	2.5A
Average (for ignitor firing service)	1.0A
Maximum averaging time	15 secs.
Surge (maximum duration 0.1 secs.)	200A
Maximum Grid Voltage.	
Before conduction	-500V
During conduction	-10V
Maximum Grid Current.	
Average (Averaging time 15 secs.)	0.25A
Maximum Grid Resistor	0.1MΩ
Min. Cathode preheating time.	300 secs.
Condensed Mercury Temperature Limits.	40 to 80°C

CHARACTERISTICS.

Heater Voltage			5.0V
Heater Current			4.5A
Capacitance Anode-grid			4μμF
Deionisation Time (approx.)			1000 μ secs.
Ionisation Time (approx.)			10 μ secs.
Anode Voltage Drop			16V
Control.			
Anode Voltage	60	100	1000V
Critical grid Voltage (approx.)	0	-1.75	-6.5V

Base 4-pin UX.

* 1500V for condensed Mercury temperature up to 75 °C

THYRATRONS

for fixed and mobile applications

The Mullard range of Thyratrons has now been extended to include types suitable for use in both fixed and mobile equipments.

For fixed power and motor speed control applications, a selection of Mercury Vapour tubes is available providing maximum average anode current ratings from 0.5 to 6.4 amperes.

For relay, switching and motor control applications in aircraft, ships and industry where movement is encountered, a selection of rare gas-filled tubes is also available. Important among these is a series of xenon-filled tubes with anode current ratings from 0.1 to 6.4 amperes. On account of the small variations-with-temperature of xenon gas, these tubes are ideal for use in equipments operating over a large ambient temperature range.

The Thyratron illustrated and described here is the 2.5 amp. MT57. Full details on the complete range of Mullard Thyratrons will be supplied on request.

Mullard

INDUSTRIAL POWER VALVES · THYRATRONS · INDUSTRIAL RECTIFIERS · PHOTOCELLS FLASH TUBES · ACCELEROMETERS · CATHODE RAY TUBES · STABILISERS AND REFERENCE LEVEL TUBES · COLD CATHODE TUBES · ELECTROMETERS, ETC.

MULLARD ELECTRONIC PRODUCTS LTD., CENTURY HOUSE, SHAFTESBURY AVENUE, LONDON, W.C.2

MVT 96

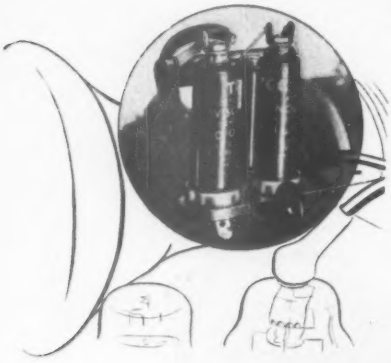

BOOST YOUR EXISTING E.H.T. SUPPLY

You have a television receiver that is now not so new. No doubt you would like to substitute a modern tube and obtain a brighter and improved picture. Of course, you want to retain the existing E.H.T. supply, but it is insufficient for the higher anode voltage required. A problem with an easy solution. A Flyback E.H.T. Booster, which can be incorporated in your receiver, either commercial or home constructed, without disturbing or over-stressing the existing E.H.T. components. Easily and cheaply constructed, the only components required are one 2MΩ 1 watt resistor, two 0.001 mFd 6kV capacitors and a 36EHT miniature high voltage rectifier.

For further details of the Flyback E.H.T. Booster and also methods of obtaining E.H.T. supply using

WESTINGHOUSE WESTALITE

36 E.H.T. MINIATURE HIGH VOLTAGE RECTIFIERS

send 6d. in stamps for a copy of "The All Metal Way" (which also includes details of H.T., L.T. and H.F. rectifiers) to Dept. W.W.3.

WESTINGHOUSE BRAKE & SIGNAL CO. LTD., 82 York Way, King's Cross, London, N.1

BSR Induction Motors..

FOUR POLE MOTOR FP 10

A precision engineered well balanced motor, designed to give constant, trouble free performance indefinitely. This motor is used extensively in many wire and tape recorders, and gramophone units now manufactured.

Note these features :—Fully protected • Dual voltage range • Negligible external magnetic field • Oil impregnated self aligning bearings • Speed constancy and silent running.

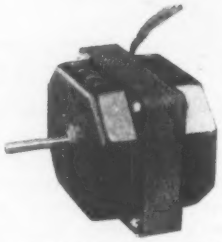

Speed (light) 1400 r.p.m. Torque 3 inch ozs. Weight 1¼ lbs.

TWO POLE MOTORS SR1 & SR2.

A rugged and highly efficient motor that will stand heavy overloads, and for intermittent ratings is capable of giving up to twice the rated power. Used extensively in many motion displays, fans and gramophones now manufactured. SR1 MODEL; Speed (light) 2750 r.p.m. Torque 3.0 inch ozs.—Weight 2.31 lbs. SR2 MODEL; Speed (light) 2750 r.p.m. Torque 2.0 inch ozs.—Weight 1.7 lbs.

..Leaders in their field

Birmingham Sound Reproducers Ltd., Old Hill, Staffs. Tel. Cradley Heath 6212/3

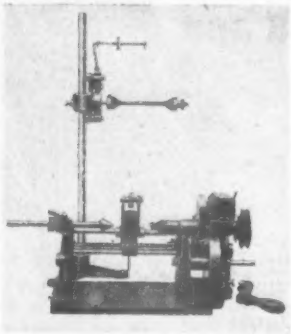

Sole Agents Abroad.

K. G. Khosla & Co., 22, School Lane, New Delhi, India.

Stahlts Octave Houart, 14, Quai de L'Industrie, Seleusin-les-Liege.

R. H. Cunningham P.T.Y. Ltd., 62 Stanhope Street, Malvern, Victoria, Australia.

Heftye & Frogr, Oslo, Norway. Storgaten, 15.

MODEL "Q"

AUTOMATIC COIL WINDING MACHINES

AND HAND WINDING MACHINES

Machines supplied complete with stand motor and Two-Speed Friction Clutch

ETA TOOL CO

(LEICESTER) LTD

29a, WELFORD ROAD, LEICESTER

'Phone—5386

LONDON CENTRAL RADIO STORES

Government Surplus – Immediate Delivery from Stock

PHILCO Reconditioned 5-VALVE SUPERHET RECEIVERS

Long and medium wavebands. A.C./D.C. 200-250v. Built-in 8" mains energised speaker. In walnut cabinet (slightly soiled), size 19 × 13 × 10 ins. Every set has been overhauled at our works.

PRICE **90'-** Carr. and pkg. 7/6.

N.B.—There is a shortage of Utility sets but we have been fortunate in replacing these with the above excellent 2-waveband receivers.

WESTINGHOUSE BATTERY CHARGER.

Size 16 × 16 × 22in. A.C. 200-250 v. 50 cycles. Output 6-8 v. D.C., 32 amp. Weight approx. 140lb. Price Carr. & pkg. 20/-. **£20 . 0 . 0**

BALL MICROPHONE. Manufactured by Standard Electric. All in perfect condition Suitable for broadcasting and recording Moving Coil (Dynamic). Omni-directional. No energising necessary. High Fidelity. Coil Impedance 15 ohms and will work very well in conjunction with an ordinary speaker transformer. Is of the type used by many leading bodies, such as the B.B.C. and G.P.O. for high fidelity reproduction.

£4 . 17 . 6

BUBBLE SEXTANTS MK. 9A. Equal to new. Complete with 6 extra bulbs **45/-** Ditto, Mk. 9... **35/-**

WALKIE TALKIE (Transmitter and Receiver) **Type 38 Mk. II.** Range 7.4—9 Mc/s. Requires 3 v. L.T. 120/150 v. H.T. In perfect working order. Complete with four ARP12, one ATP4 valves, one pair throat mikes, pair headphones and aerial. In metal case. Free circuit diagram—batteries not supplied. (Carr. & Pkg. 2/6) **£3 . 8 . 6**

ASTRA COMPASSES. Complete with transit box. Useful for surveying, etc., **15/6.**

UNISELECTOR SWITCHES.
4-bank, full-wipers **37/6**
6-bank, half-wipers **27/6**
3-bank, full-wipers **19/6**
Have various applications, including automatic tuning, circuit selection, etc. Operates on 25-50 v.

EX-ADMIRALTY DOUBLE TWIN SLIDING AND TAPPED RESISTANCES, 0.2 amp. 2,000 ohms. In metal cabinet **17/6.**

VOLTMETERS. Centre zero reading 0-3 and 0-30 D.C. **17/6.**

NEW NIFE ACCUMULATORS. 2.5 v. 2½ amp./hours for 8 hours. Size 3 × 4½ × 1¼in. (Flat) **6/6.**

EX-R.A.F. NO. 62 VISION UNITS. VCR97 Tube, 12 valves, condensers, resistances, etc., **55/-**, plus 5/- carr. and packing.

CAMERA MOTORS. 24 v.A.C./D.C., size 3×2×1¼in. **8/9.**

MAP / READING TORCH. Powerful magnifying lens, 3in. diam. In bakelite case. Fitted with dimmer switch Takes 2 U2 cells. With bulb, less batteries, **22/6.**

VIBRATORS, 2-VOLT, Type R70C. 7-pin self-rectifying. Output 200 v. at 60 mA. Made by Electronic Laboratories Inc., **7/6.**

6-VOLT, Type 560. 6-pin self-rectifying, **7/6.**

MALLORY, Type 650, 6-volt 4-pin American base, **7/6.**

MALLORY, Type G620C. 12-volt, 4-pin, American base, **7/6.**

10,000 OHM WIREWOUND POTENTIOMETERS 2/6.

SELF-ENERGISING TABLE MICROPHONE AND HEADSETS (Sound Power) Mounted on a fully adjustable stand with on/off switch. this Microphone operates without batteries or current. Useful for house to garage or workshed and for telephone conversations up to approx. one mile. Unused in Cartons, **12/6**

WESTINGHOUSE BATTERY CHARGER

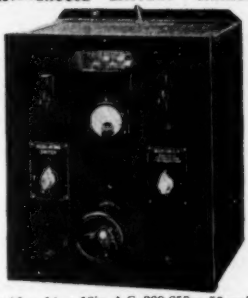

Size 16 × 14 × 12in. A.C. 200-250 v. 50 cycles Output D.C. 185 v. 0.75 amp. Weight approx. 50lb. Price Carr. & Pkg. 15/-. **£8.15.0**

PHOTO-ELECTRIC CELLS Type G516

These cells are the gas-filled type with caesium Cathode. Made by Cintel. Minimum sensitivity 100μA/lumen, working volts 100 D.C. or peak A.C. Projected cathode area 16 sq. cm. Suitable for 16 mm. Home Cinema Talkie equipment, Safety Devices, Colour and Photo Matching, Burglar Alarms, Automatic Counting, Door Opening, etc. Brand new in original cartons **42/6**

PHOTO ELECTRIC CELLS, TYPE CV143 Small infra-red image glass converter, tube, 50-100 v. Suitable for all purposes **14/6** N.B. — We cannot enter into correspondence regarding these.

PHILIPS 6-VALVE COMMUNICATIONS RECEIVER

AS NEW

16-50 200-550 and 880-2,500 metres. R/F., F/C., 2 I.F.'s D.D.T. Pentode Output. Spin-wheel tuning. In black metal case with built-in speaker. Complete with power pack, AC 200-250 v. Can also be supplied with 12 v. D.C. power pack if required **£16.10.0**

MEGGER CIRCUIT TESTING OHMMETER

3-terminal type made by Evershed & Vignoles, Ltd. Two ranges: Inner scale 0-1,000; outer scale 100-200,000 ohms and infinity Green bakelite case, size 5½ × 4 × 2¼in deep. Complete with test prods. In solid leather carrying case. Price less battery. **77/6**

LONDON CENTRAL RADIO STORES, 23 LISLE ST. (GERrard 2969) LONDON, W.C.2

Closed Thursday 1 p.m. Open all day Saturday and weekdays 9 a.m.—6 p.m.

R&A

Still More Arithmetic

(But we promise it's the last)

$$UO + CR = SR^n$$
$$MO + D + CR = SR\infty$$
$$UO - CR + LS\,(R \,\&\, A) = -SR$$

What DO these rather odd-looking equations mean? A glance below will make them as clear as daylight.

UO = undistorted output
CR = cabinet resonance
MO = maximum output
D = total distortion
SR = sales resistance

You may still feel that you cannot take the third one on trust . . .

Right, then: ask for the proof — check the value of LS (R & A) for yourself. We are confident enough of the result.

REPRODUCERS AND AMPLIFIERS LIMITED
WOLVERHAMPTON · ENGLAND
Telephone : Wolverhampton 22241. Telegrams : Audio, Wolverhampton

ALL the A.C. power you require from your D.C. supply

with a

Valradio

D·C·/A·C· CONVERTER

Models for Electric Gramophones from £8, plus 10%

Models for
- Radio-grams
- Autochange Radio-grams
- Radios
- Televisions, etc., *from £10.15.0, plus 10%*

These Converters are also suitable for 3-speed motors

Input 6, 12, 24, 32, 50, 110 or 200/250V. D.C.
Output 230V. 50 or 60 c/s

Valradio *Descriptive literature WW1, from the manufacturers :*
57 FORTESS ROAD, LONDON, N.W.5
Telephone : GULliver 5165
Overseas Enquiries to nearest E.M.I. Organisation Depot.

"WEYRAD"

B-A-N-D-S-P-R-E-A-D UNITS

DESIGNED FOR HIGH PERFORMANCE UNDER ADVERSE CONDITIONS

FULLY TROPICALISED COILS ON MOULDED FORMERS. AIR DIELECTRIC TRIMMERS

6 EXPANDED RANGES 3 GENERAL COVERAGE

USING 2-SECTION TUNING CONDENSER

STANDARD VERSIONS

B.S.3	B.S.5	B.S.11
13 Metres	13 Metres	11 Metres
16 "	16 "	13 "
19 "	19 "	16 "
25 "	25 "	19 "
31 "	31 "	25 "
41 "	41 "	31 "
13-43 "	43-140 "	13-43 "
43-140 "	175-570 "	43-140 "
175-570 "	800-2000 "	175-570 "

TENTH SWITCH POSITION FOR PICK-UP OPERATION

WEYMOUTH RADIO MFG. CO., LTD.,
CRESCENT STREET, WEYMOUTH,
DORSET

Recognised as the Most Reliable Valveholders

McMURDO Moulded Valveholders

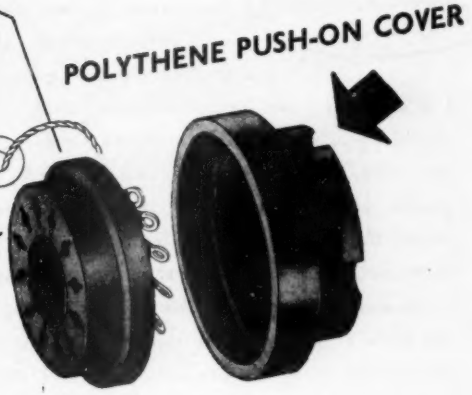

B12A—Duodecal

FOR CATHODE RAY TUBES

Ref. No. **B.12/U.1**—moulded in **Phenol-Formaldehyde**
" " **B.12/U—** " " " " " **with Polythene Cover**

THE McMURDO INSTRUMENT COMPANY LTD. VICTORIA WORKS, ASHTEAD, SURREY · ASHTEAD 3401

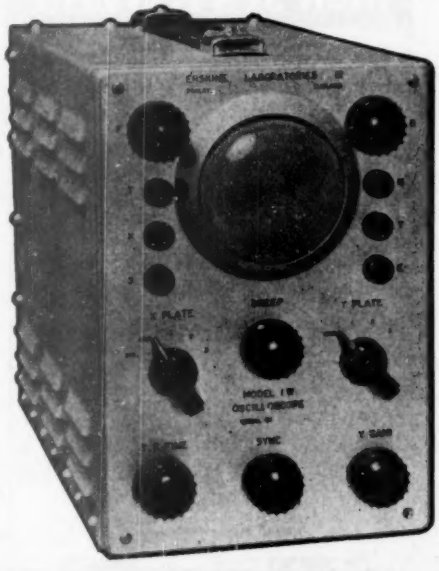

TELEVISION & RADAR

SQUARE WAVES

THIS OSCILLOSCOPE HAS A STEPPED Y-AMPLIFIER GAIN CONTROL COMPENSATED, ON EACH STEP OF APPROXIMATELY 6 DB., TO ENSURE ACCURATE REPRODUCTION OF SQUARE WAVES

OTHER FEATURES

BUILT-IN WOBBULATOR
TIME-BASE 10-250,000 c/s
BRILLIANCE MODULATION
SHIFT CONTROLS, etc., etc.

PRICE **£25** MODEL 11W
WRITE FOR DETAILS ALSO OF MODEL 1B, £15
HIRE PURCHASE TERMS AVAILABLE

ERSKINE LABORATORIES LTD., SCALBY, SCARBOROUGH, YORKS.
(THE DEVELOPERS and MANUFACTURERS OF THE NOW FAMOUS TYPE 13 FOR THE SERVICES)

ULTRA
eccentricities

No TV set that has ever been made yet has been immune from the need for some after-sales service. But 90% of the difficulty in coping with adjustments and breakdowns is diagnosing what has gone wrong. That is why we always give Ultra Television Dealers the fullest possible technical information about the product they are handling, in the form of service sheets dealing with circuitry and component values, valve trouble diagnosis (showing, for example, the effect of every possible valve electrode internal short circuit in the performance of the set) and, in fact, a classification of almost every symptom of trouble and its treatment, all of which help to make Ultra TV just about the best value for money on the market today.

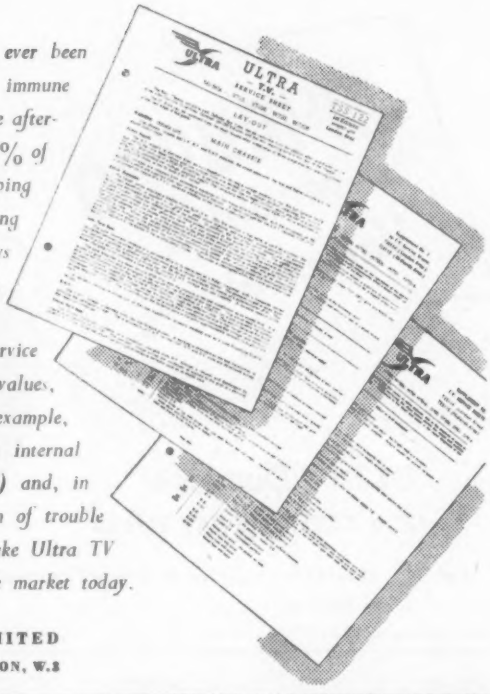

ULTRA ELECTRIC LIMITED
WESTERN AVENUE, ACTON, LONDON, W.3

E.M.I. TRAINING for the best posts

E.M.I. INSTITUTES, THE COLLEGE BACKED BY THE GREATEST ELECTRONIC INDUSTRY IN THE EMPIRE.

Daytime Attendance Courses

Radio, Television, and other Industrial Electronic subjects. Principles and Practice of Radio—1 year. Telecommunications Engineering—2 years, leading to City & Guilds Final Certificate. Electronic Engineering—3 years (*including one year's practical training in E.M.I. Factories*)—leading to C & G full Technological Certificate.

★ **Next courses commence April, 1951.** ★
Early enrolment is advised.

Moderate terms. Facilities for easy payment.

Write for free Brochure to the Registrar, Dept. 16

E.M.I. INSTITUTES
10, PEMBRIDGE SQUARE, BOTTING HILL GATE, LONDON, W.2. TELEPHONE: BAYSWATER 5131/2

Associated with "H.M.V." MARCONIPHONE COLUMBIA ETC

HIGH SENSITIVITY

"F" "K"

Because of their High Sensitivity the S. G. BROWN Type "F" (Featherweight) Headphones are a popular choice by all requiring efficient, long, and dependable service.

D.C. Resistance 4,000 ohms. Impedance 14,000 ohms at 1,000 c/s. Sensitivity 8 db. below 1 microwatt per bar at 1,000 c/s. Weight 9 oz.

The S. G. BROWN Type "K" Moving Coil Headphones supply that High Quality Reproduction so essential for DX work, monitoring, laboratory purposes, etc.

D.C. Resistance 47 ohms. Impedance 52 ohms at 1,000 c/s. Sensitivity 1.2 x 10^{-12} watts at 1 kc/s. = .0002 Dyne/CM².

Send for Brochure "W." It gives details of all types of S. G. Brown headphones.

S.G.Brown, Ltd.
SHAKESPEARE STREET, WATFORD, HERTS.

YOUR ULTIMATE CHOICE

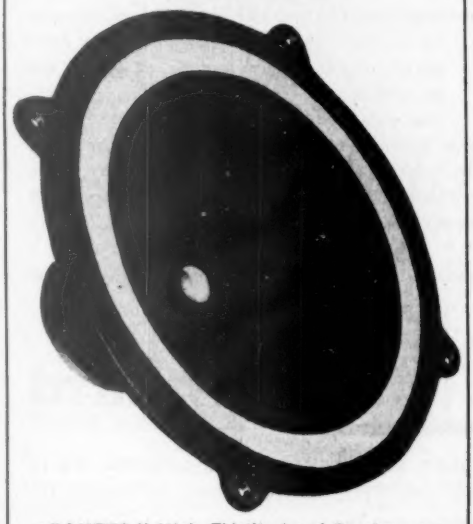

"BAKERS" High Fidelity Loud Speakers are now in constant demand by Acoustical Laboratories, Gramophone Societies, and the true Music Lovers throughout the World. No finer speaker exists today, for over twenty-five years' experience of speaker design renders each model the finest value that money can buy.

12" "TRIPLE CONE" and 18" "DUPLEX"
12" SINGLE CONE MODELS AVAILABLE

Write for Descriptive Leaflet giving full technical details (or better still call for an audition) of :—"BAKERS" SPEAKERS, RECEIVERS AND AMPLIFIERS.

★ EXPORT ENQUIRIES INVITED
(*We still have a few overseas Agencies available*)

TRADE DISCOUNTS ON REQUEST

BAKERS
'Selhurst'
RADIO

Pioneers of Moving Coil Speakers Since 1925

Dingwall Road, Croydon Telephone : CROydon 2271

15 mA (Subminiature Double-ended Electrometer)

XE2

The XE2 is an electrometer valve of the highest class.

It combines very high leakage resistance and very low grid current with small size, low filament current and a robust construction.

The double-ended construction and the siliconed bulb ensure the maintenance of the high performance of the XE2 even under humid conditions.

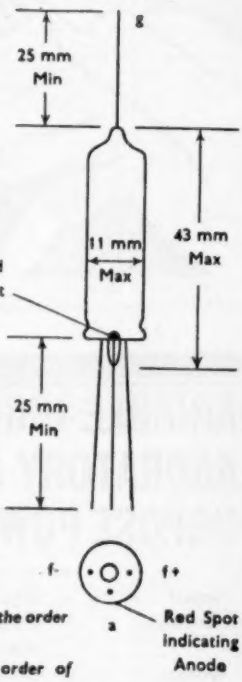

***Leakage Resistance :** in the order of 10^{-16} ohms.*

***Grid Current :** in the order of 10^{-15} amps.*

HIVAC
THE SCIENTIFIC VALVE
BRITISH MADE

GREENHILL CRESCENT,
HARROW-ON-THE-HILL, MIDDLESEX

Telephone : HARrow 2655

Trump card for designers

The sheer convenience of its size alone, is enough to recommend the W 99 to any designer cramped for room by the conventions of modern design. But that's not all! Add mechanical strength and long life and he holds an unbeatable hand.

This metallised paper capacitor uses an entirely new type of moulded housing providing a clean finish and hermetic sealing. Rugged construction with very strong end connections. Insulation resistance not less than 20,000 megohms. Temp. range – 40°C. to + 71°C.

Higher temperature types available.

Wkg. Voltage	Cap. Range. µF			Size
150 D.C.	0.004	to	0.01	A
	0.02	to	0.04	B
350 D.C.	0.001	to	0.003	A
	0.004	to	0.01	B
600 D.C.	2.5pF	to	0.0005	A
	0.001	to	0.002	B
300 A.C.	0.00005	to	0.001	A
	0.002			B

Why not send for full details?

REGISTERED TRADE MARK

HUNTS CAPACITORS

THE TRADE MARK OF RELIABILITY

SIZES A. ⅜" x ⅝" B. ½" x ⅞"

A. H. HUNT LTD. WANDSWORTH, LONDON, S.W.18

Telephone: BATtersea 3131. *Established 1901*

VARIABLE HIGH VOLTAGE LABORATORY & GENERAL PURPOSE POWER SUPPLY

TYPE 103 PMA

Input - - -	230 V.A.C. 50 c/s
Output - -	500-12,000 V 1 mA maximum
Meter - - -	Calibrated 0-12 KV.
Case - - -	Blue stove enamelled steel case, 20½" x 10½" x 10½"

Full details of our standard equipment from 2,000 to 50,000 volts are available.

HAZLEHURST DESIGNS LTD
34a, POTTERY LANE
LONDON, W.11

TELEPHONE: PARK 6955

FRITH RADIOCRAFT LTD.

for

RADIOGRAM EQUIPMENT

These items available from stock :—

B.S.R. MU-10 2-speed motors with 10in. turntable and rubber mat. A.C. only 200-250 v. 50 c/s. Speed change from 33 to 78 effected by removing turntable and reversing drive pulley. Price £3.15/-.

B.S.R. MU-12 2-speed motors as above, but with instantaneous lever action speed change. Price £5.19.10.

RICHARD ALLAN portable case record player incorporating COLLARO 3/514 3-speed unit for 33, 45 and 78 r.p.m. Two high fidelity PU heads. Microgroove head fitted with sapphire. Auto stop, Walnut finish cabinet. Price £18/4/-.

CHANCERY G33 epicyclic unit for playing LP records on standard 78 r.p.m. turntable. Price £3.12.6. Decca microgroove PU to match £2.9.9.

DECCA twin-head pickups incorporating turnover crystal cartridge and twin sapphires. Inside of PU head turns completely over for playing standard or LP records. Safety position at centre. Price £3/19/4.

" ACOS " GP20 pickups, limited supply. Price £3/11/3. GP19-LP head for microgroove records. Price £2/3/4.

MARCONI type 14 pickups, complete with matching transformer, now halved in price, £2/8/4.

" GOLDRING " lightweight magnetic pickups £1/10/-.

GARRARD RC-70 auto-changers for D.C. ONLY 100-250 v. Price £16/1/2.

COLLARO AC504 radiogram units with magnetic PU Price £5/18/-.

" STENTORIAN " die-cast speakers, 8in. PM type S810 24/-, 10in. PM type S1012 37/6. Latest 2½in. do. 15/6, 3½in. 16/6. 10in. Twin Concentric with de luxe transformer £7/7/-. Less transformer £6/6/-.

WHARFEDALE de luxe speakers. Super 8/CS £4. Golden 10 £4/3/-. Golden 10/CS £4/15/-. W12 £7.10/-.

" SKYWAY " constructional designs. " Junior " PP amplifier, 2 x 6F5s, 2xEL32s, 5Z4. Kit less valves £4/14/-. Design 6d. " Baby Grand " de luxe PP amplifier, 6SL7, 6SN7, 2x6V6s, 5R4. Kit less valves £7/15/-. Design 1/-.

" SKYWAY SEVEN " design for luxury radiogram chassis. 7 valves 6K8, 6K7, 6Q7, 6C5, 2x6V6s, 5R4, separate power pack for ease of fitting. Basic parts cost only £4/19/3 (chassis, dial assembly and drive, tuning condensers, coil pack and IFTs), 8 page design 1/-.

FRITH RADIOCRAFT LTD.

69-71 CHURCHGATE, LEICESTER. Phone 58927

A TRADITION OF EXCELLENCE
FIDELITY
EFFICIENCY

GOODMANS

Leading British Name in the Field of

LOUDSPEAKER MANUFACTURE

AXIOM
REGD TRADE MARK
TWIN CONE P.M. LOUD-SPEAKERS

AXIOM 150 A 12in. 15-watt High Fidelity unit with twin curvilinear diaphragm (Pat. 451754). Flux density, 14,000 gauss; Total flux 158,000 maxwells on a 1¼in. pole; frequency coverage 40-15,000 c.p.s., free from bass modulation effects. An ideal reproducer for the record enthusiast and connoisseur.

AXIOM 22 A 12in., 20-watt unit, also incorporating Goodmans patent exponential twin cone. Flux density, 17,500 gauss. With a frequency range of 40-15,000 c.p.s., free from sub-harmonics and bass modulation effects, the Axiom 22 brings High Fidelity into the field of High Power sound reproduction.

Please write for details

A Bass Reflex Cabinet and a corner cabinet have been specially designed for these loudspeakers and working drawings are available.

For use with these models we recommend Goodmans High Fidelity Heavy Duty Output Transformers. Types H.4 and H.6. Nett weights, 5lbs. and 5lbs. 3oz.

GOODMANS INDUSTRIES LIMITED, Lancelot Road, Wembley, Middlesex. *Phone WEMbley 1200*

Because we believe . . .

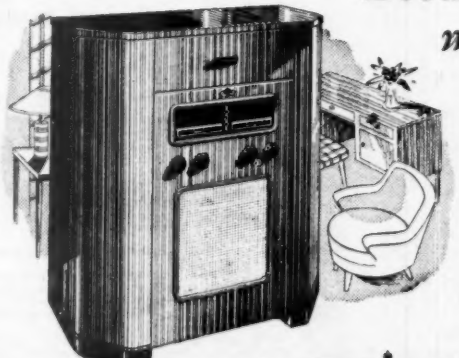

modern Radio demands instruments capable of better reproduction, we have pioneered high quality push-pull circuits to sell at modest prices.
The AMBASSADOR Six-Fifty Radiogramophone is an example of such an instrument. Six valve A.C. superhet circuit with two output valves in push-pull. Twelve-inch loudspeaker. Garrard auto-record changer for all types of records.
Walnut cabinet with record storage space.

Cash Price .. **£78**
For Single Speed **£72**

Obtainable from Ambassador Agents only. Illustrated leaflet on this and other models on request to:—

AMBASSADOR OF GREAT BRITAIN REG'D

Hire-purchase terms are available

AMBASSADOR RADIO, PRINCESS WORKS, BRIGHOUSE, YORKS

Model 1200 B Oscilloscope with model 1400 B Alignment Signal Generator

Weight 18lbs. Size 7" x 8" x 9"
PRICE £33 12 0

D. C. OSCILLOSCOPES

Model 1200 B	Model 2000
Tube dia....2.3/4"	Tube dia.....6"
Frequency Response .....D.C.-100 Kc/s	Frequency Response .....D.C.-100 Kc/s
Deflection Sensitivity .....7 mV/mm.	.....1 mV/mm.
Time Base 5c/s-20 Kc/s in 5 ranges	...30 secs. 100 Kc/s

Write for specifications to

INDUSTRIAL ELECTRONICS

Makers of
Industrial Controls and Precision Instruments

99, GRAYS INN RD., LONDON, W.C.1

Telephone: Holborn 9873/4

can you really wait 25 to 50 weeks?

We think NOT—and so our entire stock is at your disposal

OAK SWITCHES (to your requirements).

WELWYN, E.M.I. HI-STAB RESISTORS 1% 2% 5%

TCC CONDENSERS. CLOSE TOLERANCE MICA and SILVER MICA CONDENSERS.

AVO TEST EQUIPMENT.

VITREOUS RESISTORS.

PARTRIDGE & WODEN TRANSFORMERS.

WHARFEDALE SPEAKERS.

TELE-RADIO (1943) LTD.

177, EDGWARE ROAD, LONDON, W.2

Tel. PAD. 6116
PAD. 5606

Shop Hours
Mon.-Sat. 9 a.m.—6 p.m.
Thursday 9 a.m.—1 p.m.

ICS

HOME STUDY backs radio experience with sound technical knowledge

MANY men who wished to link their radio experience with a sound technological background have received successful instruction by means of an ICS Course. Its value has been proved not only to amateurs but to men who already have a professional interest in radio and television engineering, including those taking qualifying examinations. It is invaluable, also, to students who wish to prepare themselves for a job in this field. Courses of instruction covering radio and if necessary, television, include the following :

Complete Radio Engineering . Radio Service Engineers Radio Service and Sales . Advanced Short-Wave Radio Elementary Electronics, Radar and Radio Television Technology

And the following Radio Examinations :

**British Institution of Radio Engineers
P.M.G. Certificates for Wireless Operators
City and Guilds Telecommunications
Wireless Operators and Wireless Mechanics, R.A.F.**

Write today for our FREE "RADIO" booklet which fully describes the above ICS Courses and the facilities for the complete study of Radio and/or Television technology. The ICS Advisory Department will also give free and impartial advice on the need for and the means of instructing

International CORRESPONDENCE SCHOOLS

Dept. W.L.30, International Buildings, Kingsway, London W.C.2

The New

MAGNAVISTA

Filtachromatic Television Lens

FOR LARGER PICTURES IN LIGHTER ROOMS

The filter is *inside* the lens! Light-loss is minimised! Thus, you don't have to increase the "brilliance" and shorten the life of your tube.

Magnavista, the precision lens, incorporates this new development at no extra cost. Now, more than ever, no television set is fully equipped without its Magnavista.

Remember, there is a Magnavista model to suit every set.

PRICES:

There are over 18 different Magnavista models at prices ranging from £4.14.6 to £7.17.6.

a product of

METROPEX LTD

38 GT. PORTLAND ST., LONDON, W.1

Estd. L·R·S 1925

For PROMPT and EFFICIENT SERVICE

CASH or EASY TERMS

Equipment purchased from us on Easy Terms is supplied through our own scheme, no Finance Company being involved.

ARMSTRONG ALL-WAVE CHASSIS

(*including speaker and output transformer*)

MODEL EXP 83/3. Cash £18/17/1 or £8.0.0 with order and 6 monthly instalments of 40/-.

MODEL RF.103/3. Cash £25/12/6 or £9.0.0 with order and 6 monthly instalments of 60/-.

WHARFEDALE LOUDSPEAKERS

MODEL W 12/CS. Cash £8 or 40/- with order and six monthly instalments of 22/-.

MODEL W 15/CS. Cash £12/10/- or 60/- with order and 7 monthly instalments of 30/-.

MODEL SUPER EIGHT CS/AL. Cash £4/5/- or 35/- with order and 3 monthly instalments of 20/-.

All other Wharfedale Equipment available.

GOODSELL AMPLIFIERS & TUNERS

The new range of High-grade Units is now available on our Easy Terms.

SHAVE THE MODERN WAY

BY USING A

REMINGTON-RAND ELECTRIC SHAVER

It really does give a better, more pleasant and quicker shave than the blade and soap method.
We are so convinced you will agree, that we shall be pleased to send either model on **TEN DAYS' FREE TRIAL** on receipt of deposit.

THE 'FOURSOME' (for average beards). Cash £7/16/5 or 30/- with order and 7 monthly instalments of 20/-.

THE 'FIVE' (for stubborn beards). Cash £8/17/7 or 50/- with order and 7 monthly instalments of 20/-.

Both models supplied in beautiful silk-lined case. Prompt despatch per registered post. Write for the free Remington Brochure.

PROMPT DELIVERY GUARANTEED

All goods despatched carriage paid. Cash orders by return. Descriptive literature available on request. Kindly enclose Stamp.

The LTD

L.R. SUPPLY COMPANY

(LONDON RADIO SUPPLY CO.),

BALCOMBE, SUSSEX

YOU CAN MAGNETICALLY RECORD
using your Gramophone Motor as a Drive

Necessary parts, also usable later for a more ambitious job, plans available, 1 Spool Diamond Magnetic Recording Tape and 1 take-up spool, 2 Corner Brackets, 1 Roller, 1 Record-playback Head Kit, 1 Friction Clutch, 1 Dual-purpose Supersonic Oscillator and Two-stage Preamplifier and your Radio Chassis. Set of parts £7.15.0 or items supplied separately.

Also Constructional Data for Wire and Tape Recorders 5s.

PARK RADIO OF MANOR PARK, 676/8, 783 Romford Road, London, E.12

UNRIVALLED PERFORMANCE
THE "RD BABY DE-LUXE" AMPLIFIER

Now accepted as the most outstanding low priced amplifier, no other similarly priced amplifier has ALL these features :

* High sensitivity * 3 inputs, mic., P.U., radio. * Push-pull output. * 24 DB N.F.B. * Range 30-20,000 cps. * 5 watts output with less than ·5 per cent. total harmonic distortion. * Complete stability. * Detachable pre-amplifier with engraved control panel. * Accurate compensation for H.M.V. and Decca standard, American NAB, and Decca LP records. * Suitable for use with the Decca 3378 playing-desk direct.

Built by craftsmen to the highest standards, this amplifier represents the finest value available in High Fidelity to-day.

PRICE :—Main amplifier ...	...	£11 10 0
Pre-amplifier ...	...	£4 10 0
Engraved panel ...	...	10 6

Full details forwarded on request.

DEMONSTRATED DAILY

At our Greenwich premises—10 a.m.-6 p.m., also in London at Webb's Radio Ltd., Gramophone Exchange Ltd., and Tele-Radio (1943) Ltd.

ROGERS DEVELOPMENTS CO.

116, Blackheath Road, GREENWICH, London, S.E.10

Telephone: TIDeway 1723

B.P.L. TEST SETS

NOW AVAILABLE

AT NET PRICES

B.P.L. UNIVERSAL TEST SET
£5 - 18 - 6

B.P.L. SUPER RANGER 1,000Ω/v.
£13 - 10 - 0

B.P.L. SUPER RANGER 20,000Ω/v.
£15 - 10 - 0

Prices include postage and packing, and are applicable to Home Market only.

Send your order direct to:

BRITISH PHYSICAL LABORATORIES
HOUSEBOAT WORKS, RADLETT, HERTS.
Tel.: Radlett 3674-5-6

ANOTHER 'FIRST' BY Wharfedale

THE SUPER 12/CS/AL

sets new standards in sound reproduction

Wharfedale specialised knowledge and experience is evident in the new, compactly designed Super 12/CS/AL. Providing the instant response needed for true-to-life reproduction, it incorporates a specially designed cone with bakelised apex, cloth suspension and aluminium speech coil of 8-10 ohms or 12-15 ohms, the response being effective from 30 cycles to 20k. The high flux density of 17,000 lines gives exceedingly sharp transient response and ample tonal range.

WEIGHT 18½ lbs.
TOTAL FLUX 190,000 LINES
CONE RESONANCE 35-45 CYCLES

RESPONSE CURVE OF SUPER 12/CS/AL

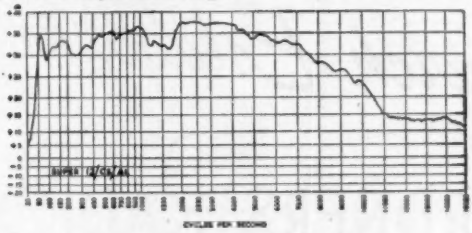

PRICE NOW

£14-10-0

Made and guaranteed by

WHARFEDALE WIRELESS WORKS · BRADFORD ROAD · IDLE · BRADFORD · YORKS.

Telephone: Idle 461

Ceramic Hermetic Seals & Bushes

by

U.I.C

UNITED INSULATOR CO. LTD. OAKCROFT RD. · TOLWORTH · SURBITON · SURREY

TELEPHONE ELMBRIDGE 5281 CABLES CALANEL SURBITON

QUALITY GR RELIABILITY

Transformers for the Electronic Industry, Radio & Research Establishments

GARDNERS RADIO Ltd

SOMERFORD • CHRISTCHURCH • HANTS

TELEPHONE: CHRISTCHURCH 1025

And a Richard Allan extension speaker to go with it Sir?

— if you connect it with flex to your main set you will then have radio in two rooms at the same time. Yes, it is lovely isn't it? This one is called the Major—a lovely cabinet—in fact a lovely speaker for the sitting-room, Sir. Yes, it stops all that messing about when you have company—no need to move your main set about if you have a Richard Allan speaker. Yes Sir, £3 8 6. Thank you, Sir.

Are you missing extra sales?

Extra Sales make extra profits!

BABY 42/- MINOR ... 55/- MAJOR 68/6

STANDARD Walnut ... £4 7 6 STANDARD Mahogany, light or dark oak ... £4 10 0 DE-LUXE ... £4 17 6

CONSOLE Walnut ... £6 15 0

CONSOLE Mahogany £7 10 0 **Richard Allan** PRESTIGE Console £13 10 0

RADIO LTD., BAFFLETTE HOUSE, BATLEY, YORKSHIRE.

Please note that "BONNIE" and "JUNIOR" models are now out of production.

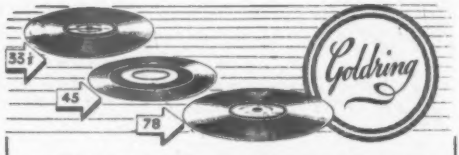

3 WAY PICK-UP FOR STANDARD AND LONG PLAYING RECORDS

Goldring introduces Pickup 150, incorporating the first British **Magnetic** Cartridge. Cartridge 150X available separately. The movement of this Cartridge is of balanced armature construction, and combines high output with wide frequency range and exceptionally low tracing distortion. Needle armature is easily replaceable by user.

Data	78 r.p.m.	45 and 33⅓ r.p.m.
Armature resonance	16 kc/s	9 kc/s
Output	70 mV	Equivalent to 150 mV on 78 r.p.m
Tracking weight ...	15-20 grms.	7 grms
Load	30 kΩ	30 kΩ
Stylus	.003 code blue	.001 code yellow

Comprehensive information service on circuitry available to users

Write for full technical information to :—

ERWIN SCHARF

49-51a, DE BEAUVOIR ROAD, N.1

Telephone : CLIssold 3434

'Let's have "THE GONDOLIERS" AGAIN!'

Whatever your favourite piece of music, the Soundmirror will record it and play it back for you again and again. There is no end to the thrills which this new magic entertainer can bring. It will record the humorous patter of your favourite comedian, the art of the orator, the fun of a party or important family occasions like weddings.
It will play them back with perfect fidelity immediately it is recorded and as often as you wish. Unwanted recordings are automatically erased as new ones are made and the magnetic tape used time and time again.

MODELS FROM £69 . 10 . 0 exclusive of microphone.

Manufactured under agreement with the Brush Development Co., of the U.S.A. Licensed under the Brush Development Co., the Brush Crystal Co., Magnetone Inc., and Thermionic Products Ltd. Patent No. 454595 and others : and patents pending in all the principal countries of the world.

THE **Soundmirror**
MAGNETIC TAPE RECORDER

CALL ON YOUR LOCAL RADIO DEALER AND HEAR YOUR OWN VOICE RECORDED OR WRITE FOR BROCHURE, WHICH GIVES FULL DETAILS, TO THE MANUFACTURERS.

THERMIONIC PRODUCTS LTD.
(Division SM/WW), Hythe, Southampton. 'Phone : Hythe 3265
London Showrooms : **Morris House, Jermyn Street, S.W.1**
Telephone : Whitehall 6422 (5 lines). *Sales and Service Centres : Manchester, Birmingham, Bristol, Leeds, Newcastle, Glasgow, etc.*

The Famous
FA 22

THE PROVEN LONG-DISTANCE AERIAL

Many thousands of these Aerials are giving splendid results throughout the country. Its sturdy design will appeal to Dealers in exposed and coastal areas. The demand for this Aerial is greater than ever before, because the FA22 is the most consistently successful Aerial made today.

£5.12.6 Complete. LONDON or MIDLAND.
GUARANTEED FOR TWO YEARS

and **NOW** **TELEGRAFT** have designed an aerial for those nearer the transmitter :—

A WORTHY COMPANION FOR THE FA22

The **TS 50**

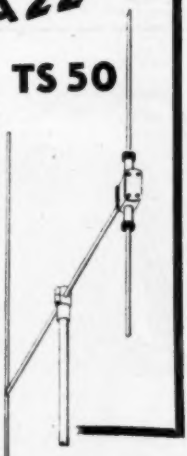

an "**H**" with all the features you've asked for at an amazingly low price.

STUDY THIS SPECIFICATION
THE **TS 50** retains the well known **TELEGRAFT DIPOLE FEEDER BOX**
½" diameter Aluminium Alloy Tube **COLLECTORS AND REFLECTORS**
New Type **REFLECTOR ASSEMBLY**
Die-cast **MAST-HEAD** casting
.15 Wave-length **SEAMLESS STEEL SPREADER**
7ft. **SEAMLESS STEEL MAST**
STEEL LASHING with welded joints
12ft. 7-strand **GALVANIZED LASHING-WIRE**
3 **CORNER-PLATES**, "J" Bolts, "U" Bolts, **ROPE GRIPS, THIMBLES, Etc.**
STOVE ENAMELLED THROUGHOUT

£3.17.6 Complete.
LONDON or MIDLAND.

Depots :— BIRMINGHAM, BRISTOL, MANCHESTER, WORTHING.

SCOTTISH ENQUIRIES :
LOUIS GRACE,
38, Langside Place Glasgow S.1.

Contact your Wholesaler and insist on **TELECRAFT** *Send for Descriptive Literature*

LIMITED
QUADRANT ROAD : THORNTON HEATH SURREY
Tel. : THOrnton Heath 2905

TELCON at ALEXANDRA PALACE

Recent T/V programmes from Alexandra Palace have been broadcast from a stand-by aerial, to enable the main aerial and built-up feeder system to be overhauled.

The power of these transmissions, 17 kW peak white, was fed to the aerial by a standard Telcon Type A.S.84.A1 co-axial cable. This low-loss semi-air-spaced thimble-insulated cable, with an outer sheath of seamless high conductivity aluminium, has carried this power load without trouble during the overhaul period, whilst its high electrical uniformity has been well proved by the absence of reflections.

TELCON METALS — TELCON CABLES — TELCON PLASTICS

Engineering data sheet free on request.

THE TELEGRAPH CONSTRUCTION & MAINTENANCE CO. LTD.

Head Office : 22 Old Broad Street, London, E.C.2.
Telephone : LONdon Wall 7104

Enquiries to : Telcon Works, Greenwich, S.E.10.
Telephone : GREenwich 3291

Founded 1864

TRAINING IN ELECTRONICS

RADIO-TELEVISION and other INDUSTRIAL ELECTRONIC subjects

HOME STUDY COURSES

City and Guilds Telecommunications and A.M.Brit. I.R.E. examinations • Radio and Television Servicing Certificates • Advanced Radio • Television • Industrial Electronics • Mathematics

FREE BROCHURE gives full details of these and Daytime Attendance Courses.
Moderate terms. Facilities for easy payment.

Write to Dept. 16,

E.M.I. INSTITUTES

10, PEMBRIDGE SQUARE, NOTTING HILL GATE, LONDON, W.2. TELEPHONE: BAYSWATER 6131/2

Associated with "H.M.V." MARCONIPHONE COLUMBIA ETC.

I. 20

It's a ticklish business...

Quantity production of I. F. transformers and tuning coils is a bit tricky, as in any field where unvarying standards and fine limits are required. Add really reliable delivery to these desirable technical features, and you have the reason why so many 'leave it to E. T. A.'

We shall be pleased to have your enquiry for coils and I. F. transformers. Please mention type and quantities when writing.

E T A

West Hill, St. Leonards-on-Sea

PHONE : HASTINGS 471

Connoisseur Products

TWO SPEED-MOTOR. At the turn of a switch you have two speeds. 33.1/3 or 78 r.p.m. The Turntable is a full 12" diameter; its main spindle precision ground and lapped, runs in phosphor bronze bearings. The synchronous motor is virtually vibrationless and is suitable for playing standard, transcription and microgroove recordings.

Retail price without pickup - - - - - - £14 12 6
Purchase Tax - - - - - - - - £6 6 9

SUPER LIGHTWEIGHT PICKUP for standard and microgroove recordings. The interchangeable heads are fitted with an easily replaceable armature system complete with a semi-permanent sapphire. Armature mass 20 milligrams. Extremely low mass at needle point (4/5 m.g. only) allowing for reduction in downward pressure to 10/12 grams for standard recordings, and 5/7 grams for microgroove recordings.

Prices: With one Head - £4 0 0, plus £1 14 8 Purchase Tax
Extra Heads, each - - £2 10 0, plus £1 1 8 Purchase Tax
Spare armature System with Sapphire, 14/8 including Tax.

THE CONNOISSEUR Varigroove Recording Unit. 33.1/3 and 78 r.p.m. 100 to 300 GROOVES PER INCH continuously variable. MOVING COIL CUTTER HEAD of entirely new design. Patented method of suspension allowing use of large magnet system, producing sensitivity and response hitherto unobtainable. All patterning effects eliminated, allowing micro-groove recordings to be made with ease.
15 ohms Impedance. Frequency response 30 - 15,000 c.p.s
LESS THAN 5 WATTS required to fully modulate.
Price £150 0 0

ALSO HIGH FIDELITY AMPLIFYING EQUIPMENT

A.R.SUGDEN AND CO. (ENGINEERS) LTD., BRIGHOUSE, YORKSHIRE.

SIGNAL GENERATOR

TYPE 5

100 KC/S-130 MC/S

PRICE £14.0.0

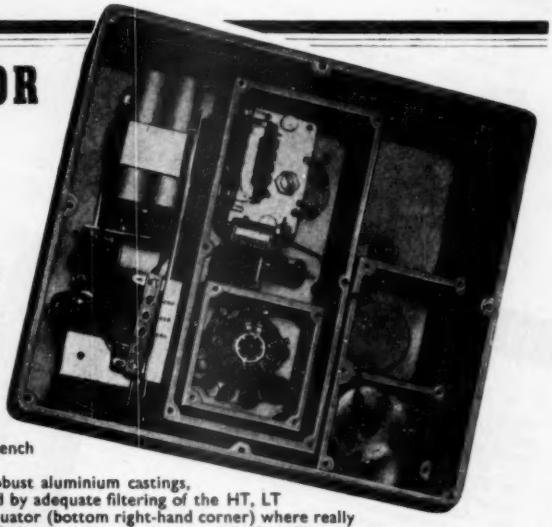

The illustration shows our new *SIGNAL GENERATOR TYPE 5* with the back and three internal screen covers removed. Experienced engineers will recognise at once that it possesses all the desirable features for good design and efficient performance, hitherto obtainable only in very expensive instruments.

It is intended for serious work on television, radio and electronic equipment where efficient attenuation and extremely low stray field are essential. Compact, rugged in construction and completely reliable, it is the ideal instrument for use on the test bench and in the service department, etc.

The RF oscillator is triple-screened by means of robust aluminium castings, and the efficiency of this method is further enhanced by adequate filtering of the HT, LT and mains supplies. Attention is drawn to the RF attenuator (bottom right-hand corner) where really efficient screening ensures the effective operation of these vital controls over the whole frequency range.

Send for illustrations and pamphlet S5 which fully describe this remarkable instrument, enclosing P.O. for 2/6 if circuit diagram required.

HOMELAB INSTRUMENTS, 68A COBDEN ROAD, LONDON, E.11

'Phone: LEY. 5651

Hear these amplifiers first . . .

PORTABLE BATTERY MAINS BM40

An attractive appearance and unique construction combined with first-rate performance give this instrument a hallmark of distinction. Peak power 40 watts, 30 watts undistorted. Designed for both A.C. Mains and 12-volt battery operation. Provision for independent electronic mixing of two microphones and one gramophone channel. Built-in vibrator. Special tone control circuit, with independent bass boost and cut, and treble boost and cut. These and many other features make the BM40 the most up-to-date amplifier available. List price £50.

MOBILE CAMPAIGN OUTFIT MA15

An ideal equipment for mobile applications, giving crisp, clear messages. The outfit comprises: 15 watt amplifier for either 6 volts or 12 volts operation; hand microphone type M.C.B., and co-axial weatherproof loudspeaker. A gramophone input and battery-saver switch are incorporated.
List price £48 10s.

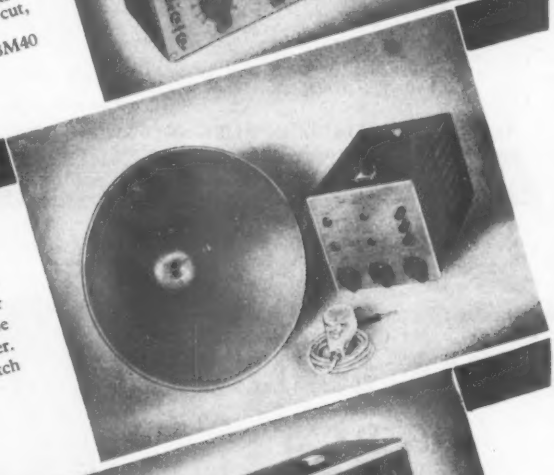

30 WATT PORTABLE PA30/B

A 30 watt amplifier for public address men. Inputs for moving coil or ribbon microphones and gramophone. Tone control. Illuminated panel and output signal level indicator. Outputs: 7.5, 15 ohms and 100 volt line. Operates from 200/250 volts A.C. mains, or 12-volt battery when used with battery adaptor unit type LT30. An ideal equipment for P.A. vans, general installations and outdoor requirements. Supplied in a handsome portable case.
List price: PA30/B Amplifier, £40.
LT30 Battery Adaptor, £12 10s.

BIRMINGHAM SOUND REPRODUCERS LIMITED
CLAREMONT WORKS, OLD HILL, STAFFS. TEL. CRADLEY HEATH 6212/3

BSR BRITISH SOUND REPRODUCERS

Wireless World

RADIO, TELEVISION AND ELECTRONICS

40th YEAR OF PUBLICATION

Managing Editor: HUGH S. POCOCK, M.I.E.E.
Editor: H. F. SMITH

MARCH 1951

In This Issue

EDITORIAL COMMENT 83
STEREOPHONIC SOUND. By *J. Moir* 84
MAGNETIC RECORDING TAPE. By *H. G. M. Spratt* .. 88
HOW RELIABLE IS A RADIO VALVE? 91
MULTI-CARRIER AIR COMMUNICATIONS 92
VECTOR DIAGRAMS—3. By "*Cathode Ray*" 95
SHORT WAVE CONDITIONS 99
TRANSATLANTIC TESTS 100
WORLD OF WIRELESS 101
HARBOUR-CONTROL RADAR 105
U.S. COLOUR TELEVISION 107
TESTING STEEP-SLOPE VALVES By *J. C. Finlay* 108
IONOSPHERE REVIEW: 1950. By *T. W. Bennington* .. 109
STABILIZING FEEDBACK AMPLIFIERS. By *Thomas Roddam* 112
GROUPED COMPONENT REFERENCES. By *L. Bainbridge-Bell* 115
SOUND REINFORCING. By *D. W. Pipe* 117
MANUFACTURERS' PRODUCTS 119
UNBIASED. By "*Free Grid*" 120
LETTERS TO THE EDITOR 121
RANDOM RADIATIONS. By "*Diallist*" 124

PUBLISHED MONTHLY: Price 2/- (last Thursday of preceding month) by ILIFFE & SONS LTD., Dorset House, Stamford Street, London, S.E.1. *Telephone:* Waterloo 3333 (60 lines). *Telegrams:* "Ethaworld, Sedist, London." *Annual Subscription:* Home and Overseas, £1 7s. 0d.; U.S.A. $4.50, Canada $4.00. BRANCH OFFICES: *Birmingham:* King Edward House, New Street, 2. *Coventry:* 8-10, Corporation Street. *Glasgow:* 26a, Renfield Street, C.2. *Manchester:* 260, Deansgate, 3.

Important trends in VALVE DESIGN

MULLARD OUTPUT PENTODE PL82

The PL82 is an output pentode on the all-glass B9A (Noval) base. It has been introduced in the Mullard World Series of television valves for use as either the audio output valve or as the frame output valve. For these two functions it is, therefore, an alternative to the pentode section of the triode-pentode ECL80.

As an audio output valve it is rated for an output of 4 watts at 10% total distortion when operated at anode and screen voltages of 170 V. The drive voltage for this output is 6.0 V r.m.s. The valve may therefore be used in receivers where the audio output of the ECL80 (1.0 W for 10% total distortion at anode and screen voltages of 170 V) is insufficient.

When the PL82 is employed as a frame output valve, the frame circuit should be designed to operate on a peak anode current of 90 mA, the valve being operated at an anode voltage of 50 V and screen voltage of 170 V. These figures allow for valve spread and for deterioration during life. For an average new valve the peak anode current will be 140 mA at the same anode and screen voltages, and grid bias of −1 V.

RATINGS AND CHARACTERISTICS

Heater

Suitable for series operation, A.C. or D.C.

I_h	0.3 A
V_h	16.5 V

Capacitances

C_{in}	11 μμF
C_{out}	8.3 μμF
C_{a-g1}	< 1.0 μμF
C_{g1-h}	< 0.15 μμF

Characteristics

V_a	170	200	V
V_{g2}	170	200	V
I_a	53	45	mA
I_{g2}	10	8.5	mA
V_{g1}	−10.4	−14.2	V
g_m	9.5	8.2	mA/V
r_a	20	24	KΩ
μ_{g1-g2}	10	10	

Limiting Values

$V_{a(b)}$ max.	550 V
V_a max.	250 V
*$+V_{a(pk)}$ max.	2,500 V
$-V_{a(pk)}$ max.	500 V
p_a max.	9 W
$V_{g2(b)}$ max.	550 V
V_{g2} max.	250 V
p_{g2} max.	2.5 W
I_k max.	75 mA
V_{g1} max. (I_{g1} = +0.3 μA)	−1.3 V
R_{g1-k} max. (audio output valve)	1.0 MΩ
R_{g1-k} max. (frame output valve)	2.2 MΩ
V_{h-k} max.	150 V
R_{h-k} max.	20 KΩ

* Max. pulse duration 10% of one cycle with maximum of 2 m sec.

Reprints of this article may be obtained free of charge from the address below.

Mullard

MULLARD ELECTRONIC PRODUCTS LTD.,
TECHNICAL PUBLICATIONS DEPARTMENT,
CENTURY HSE., SHAFTESBURY AVE., W.C.2.

MVM157

Wireless World

MARCH 1951 VOL. LVII. No. 3.

Television in the Cinema

COMMENTING on the Beveridge Report, which was issued just before our last issue appeared, *Wireless World* expressed general approval of the basic findings of the Committee. We have since seen no reason to change that opinion, but there are one or two secondary matters that have been accorded unsatisfactory treatment. These should be discussed before the Report is debated in Parliament.

The worst case is that of television in the cinema. Here the issue has been confused to such an extent that, unless we believed that everyone concerned had been actuated by the best motives, we would be tempted to say that the majority of them have been party to a conspiracy to fog the real issues. The real point, made by a correspondent whose letter appears on another page, is that basically cinema television has nothing to do with broadcasting, the B.B.C. or, for that matter, the Beveridge Committee. It is mainly a matter of point-to-point communication, either by wire or wireless, and so comes under the monopoly of the Postmaster General.

One might expect at least that the Post Office evidence would have helped to dispel the fog. On the contrary, it goes a long way to make it more dense, though the extremely cautious memorandum submitted by the G.P.O. to the Committee sets out to explain the issues under discussion. As an example, we may cite the Post Office description of a hypothetical radio system comprising a station feeding a group of cinemas in a fair-sized town. It is stated that such a system "would, in effect, amount to something very like broadcasting." We can find in the Final Acts of the Atlantic City Conference no justification for that view, and contend it is no more like broadcasting than, say, the service conducted for passenger liners, which transmits news bulletins by radio telegraphy to a designated group of ships which subscribe to the service. In fact, it is less like broadcasting, in any sense of the term, as the hypothetical television station mentioned would confine itself to a 10-degree beam.

The Post Office then raises in its memorandum the bogy of unauthorized interception by the public of cinema television transmissions. This has been swallowed hook, line and sinker by the Beveridge Committee. In the Report it is said "there is nothing wrong in allowing a member of the public to catch (*sic*) at home if he can a transmission directed to a cinema." As to whether it is right or wrong raises ethical issues that we cannot discuss here, but it is certain that it would be illegal and contrary to the terms of the broadcast licence, which allows only the reception of authorized broadcasting stations. Undue fear of the bogy of interception would spell the end of all radio development.

In our view, the cinemas do not make out a good case for their natural desire to stake a claim in television, nor does the B.B.C. in its equally natural desire to avoid what it clearly (but we think wrongly) considers to be an encroachment on its monopoly. Of all the contributions to the evidence, that of Sir Robert Watson Watt (given on behalf of Paramount) stands out above the rest. After pointing out how the real problems have become confused, he goes on to say that "the B.B.C. has no *locus* as judge or negotiator in the claim that the Postmaster General should issue licences [to the cinemas]."

In spite of the large amount of space given to the subject of cinema television in the Report, the final recommendation does not, we feel, amount to very much; it certainly lacks the air of realism. The recommendation is that the P.M.G. should, if channels can be made available, grant licences to responsible bodies to transmit pictures for public showing. The pictures thus transmitted would have to be made available to the B.B.C. and others on terms approved by the P.M.G. This seems to be a very unattractive arrangement from the point of view of the cinemas, and unlikely to introduce any real competitiveness in the field of television.

We do not hold any special brief for the cinemas in the matter of television; our sole concern is that unnecessary barriers should not be placed in the way of development of what may well become an extremely important extension of the radio art.

Stereophonic Sound

By J. MOIR,* M.I.E.E.

A Review of the Basic Principles Involved

IT is difficult to decide whether Mother Nature has provided us with two ears as an insurance against total disablement through damage to a single organ, or whether she finds justifiable advantages in the additional information obtained as a result of the duplication. Whatever the reason for their presence the possession of two ears enables a sound field to be sampled at two points spaced apart by the width of the head (about 21 cm) and this facility does undoubtedly have some advantage both practically and æsthetically. Without philosophizing as to whether the two ears are the result of the advantages they bestow or *vice versa*, attention will be concentrated on the limitations of our present "one-eared" reproducer systems and the possibility of overcoming them.

The advantage of two ears that is immediately apparent is that they are of immense help in locating the position of a sound source, giving the same three-dimensional significance to our acoustic environment as our two eyes give to the visible environment. Unless one has had the opportunity to listen monaurally and binaurally it is difficult to indicate the sacrifice that is made in accepting a monaural system, so recourse will be made to quoting some typical opinions by workers in the field. Thus J. P. Maxfield, of Bell Telephone Laboratories, has said, "I would rather hear 2-channel reproduction good to 6 kc/s than single-channel reproduction good to 15 kc/s. It is more pleasing, more realistic, more dramatic." Other engineers have suggested cut-off frequencies between 4 kc/s and 8 kc/s as the binaural channel bandwidth equivalent to a 15-kc/s monaural channel. However, it should be stressed that the difference is not really one that can be adequately expressed in terms of bandwidth, my own impression being that a monaural channel compresses a hemispherical world of action into a tunnel, cramping and confining the room dimensions.

Before proceeding it should be noted that for reasons that will become clear in later discussion, the limitations of a monaural channel cannot be assessed by stopping one ear with the finger.

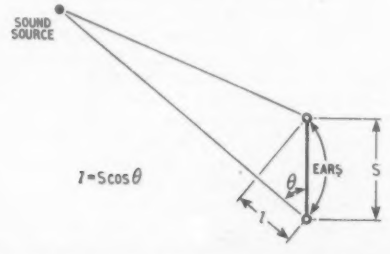

Fig. 1. Calculation of path length difference between source of sound and the two ears.

The differences, worth while or otherwise, between a monaural and a binaural (or stereophonic) system arise because the two ears sample the sound field at two points spaced apart by that obstruction known as the head. Sound from any source not situated in the vertical plane passing through the centre of the head will therefore reach the two ears with a time difference given by

$$t = l/34{,}300 \text{ secs.} \qquad (1)$$

where l is the difference (cm) in path length between the two ears and the source. This path length difference l, obtained as shown in Fig. 1, is given by $l = s\cos\theta$ where s = ear spacing and θ = angle to line through ears. The path difference is obviously a function of the displacement of the sound source from the median plane. This difference *and the presence of the head as an obstruction in the sound field* increase the information supplied to the brain in the following respects.

(1) For impulsive or transient sounds the initial wave front will strike the two ears with a time difference given by equation (1). The maximum time difference will occur when the sound source is in line with one ear and will be approximately equal to 0.00063 sec.

(2) For a repetitive signal such as a single musical note the instant at which the peaks of the waves strike the two ears will differ by the same time interval as for an impulsive noise, but if we assume (somewhat diffidently) that the ear cannot distinguish one peak from another only time differences corresponding to less than one cycle of the incident wave frequency will be significant. In this case it is conventional to refer to this as a phase difference between the sound reaching the two ears, one complete cycle being 360 degrees or 2π radians, though it should be noted that the differences listed as (1) and (2) are really manifestations of the same thing, a time difference.

(3) For any type of sound there will be a loudness difference between the sound reaching the two ears, this difference being due to the increased attenuation of the longer path to the farther ear.

(4) While the loudness difference due to (3) is not large, significant differences in loudness do occur when the sound is pure tone at frequencies over about 1,000 c/s or when the incident sound is complex and contains high frequency components. This loudness difference arises because the two ears are separated by the mass of the head, which introduces diffraction effects which are a function of the incident sound frequency.

Diffraction is a universal phenomena, which may be briefly explained as follows. A wave in water, air or any other medium will on meeting an obstruction "bend round" the obstacle to some extent, but in all cases the obstruction will cast a shadow on the side remote from the incident wave. The

* British Thomson-Houston Company.

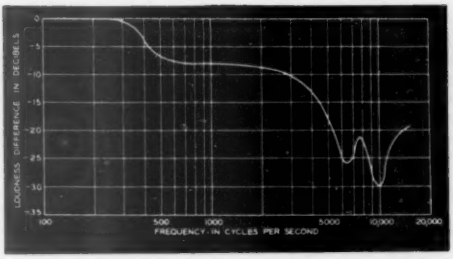

Fig. 2. Loudness difference produced in the right ear when a source of sound of pure tone is moved from the right to the left of an observer.

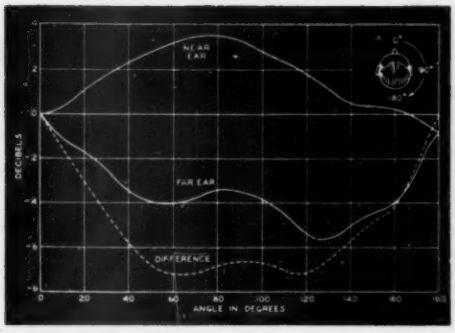

Fig. 3. Variation in loudness as a speech source is rotated in a horizontal plane around the head.

Fig. 4. One method of stereophonic reproduction might be equivalent to picking up the original sound field existing at side A of a soundproof wall by a number of microphones, and reproducing it through a complementary series of loudspeakers on side B.

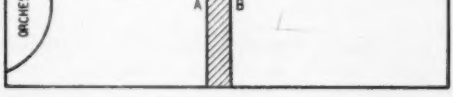

" depth of the shadow," i.e., the decrease in intensity of the wave, is a function of the ratio, obstacle-diameter/incident-wavelength, and is small when the obstacle has dimensions small compared to the wavelength. Where the obstacle is several wavelengths in diameter a strong shadow is cast. An exact calculation of the field distortion is a matter of extreme difficulty, but as in this instance the diffraction effect round an average head is our only interest, an experimentally determined curve Fig. 2* is of interest as showing the order of the loudness difference that results in the two ears as a source of tone is moved round the head.

The everyday sounds are mainly complex and the resultant loudness difference will therefore depend upon their frequency composition, but Fig. 3 indicates the sort of result that is obtained when a source of speech is rotated round an observer's head from front to back.

(5) As the diffraction effects are a function of frequency, the frequency characteristic as well as the loudness of a complex sound differs at the two ears. With experience monaural location is possible with one ear only, presumably due to these changes in character.

It was noted earlier that these differences vanish for sound sources lying in a vertical plane through the centre of the head, as all points in this plane are equidistant from the two ears, though some differences in character occur between sound arriving from straight ahead and straight astern due to diffraction effects from the ear lobes. The precision of location in the vertical plane is therefore rather low, though possible when the head is free to make some exploratory movements.

There are, therefore, at least five ways in which right ear sound may differ from left ear sound, and from these differences and some experience the brain is enabled to reconstruct the acoustic scene with surprising accuracy.

Current radio broadcast and recording techniques are almost exclusively monaural, using a single microphone and transmission channel. Spatial information on the sound source is almost entirely absent and angular localization impossible though localization in depth is still possible. Depth localization is almost entirely dependent upon the ratio of the reverberant to the direct sound reaching the ears and is largely independent of the possession of two ears. This ability is presumably the result of long experience and it is well confirmed by experiment.

It should be noted that the use of two microphones connected in series or parallel at the studio end is of no value as an aid to stereophony, as the individual signals, though they may differ in phase and amplitude, lose their separate identity in the single electrical circuit. If this individuality is to be preserved, there must be two completely separate channels between the microphones and the listener's ears and this leads fairly easily to the simplest method (in some ways) of achieving stereophony. Two microphones, preferably non-directional, are mounted in a dummy head, the leads being carried back through separate amplifiers to separate earpieces worn by each member of the audience. This effectively transports each listener to the point in the sound field at which the dummy head has been placed and there is no doubt that the realism that can be secured by this means is really remarkable. The wearing of headphones is a habit that is unlikely to return and other means of achieving stereophony must be found if it is to be commercially successful.

Instead of transporting the audience to the sound field existing in the microphone position, the alternative approach of transporting the sound field to the audience would appear to have advantages. Referring to Fig. 4, showing a long hall divided by a transverse wall assumed to be soundproof, the problem would appear to be one of reproducing the sound field existing on side A, at side B. At a prohibitive level of expenditure, this end could be achieved if

* This figure, together with Figs. 3 and 5, are reproduced from *Bell System Technical Journal*, Vol. 8, April 1934.

wall A were covered with microphones, spaced perhaps at one-foot centres, each individually connected through its own amplifier to a speaker located on wall B opposite the microphone. While this might be feasible if wire lines were the only connecting link it is obviously impossible where the sound must be recorded or a radio link must be used, and it is therefore necessary to consider means of simplification.

It was noted earlier that localization in the vertical plane is poor and this suggests that transmission of "vertical" information is perhaps unnecessary. On these grounds all but one horizontal row of microphones and speakers might be removed, a very considerable simplification that proves entirely successful. Pursuing a similar line, though possibly without the same soundness of reasoning, it is found that three channels can give very good stereophony, and even two channels can be made to give good results. Two or three channels are approaching commercial feasibility and it is therefore important to make an experimental verification of the limitations of each method. Bell Telephone Laboratories have studied these problems in some detail and Fig. 5, taken from a paper[1] by Steinberg and Snow, summarizes the results on some of the possible 2- and 3-channel systems.

On the left is an outline of the test set up, the microphones being placed in a room 29ft square, the loudspeakers being placed on the stage in a small auditorium and concealed from the audience by a thin curtain. In all the tests a caller occupied fifteen positions on the stage in a random order, but always including the nine positions shown at the top, while the audience, seated in a group in the rear third of the auditorium, marked on a stage plan the apparent position of the caller on the virtual stage. As a final check the caller moved over to the auditorium and repeated his calling positions behind the curtain while the group attempted to locate his position, no electro-acoustic link being involved.

In the first test a straightforward 3-channel system was used, the results indicated opposite the system diagram near the top showing that localization was good, though the apparent width and depth of the stage were slightly reduced by the 3-channel link.

In the next test a straightforward 2-channel system was substituted, but the accuracy of localization decreased appreciably. Reduction in the number of channels has obvious commercial advantage and the three following tests were designed to evaluate the performance that might be obtained if the amount of equipment was reduced. In the simple 2-channel system it will be noted that the centre position suffers most, whereas the centre position is probably the most important of all in practice. The alternative layout tests were therefore mainly designed to pull the centre position forward into prominence. It will be seen that though none of the alternatives approach the performance of the 3-channel system, they do effect an improvement, but they do not represent all the possible alternatives, so it might be unwise to assume from these tests that there is no future in a 2-channel system.

[1] "Auditory Perspective—Physical Factors" by J. C. Steinberg and W. B. Snow. *Electrical Engineering*, Jan. 1934, and *B.S.T.J.*, April 1934.

Fig. 5. Diagram of arrangement (left) for sound localization tests and (right) the results obtained.

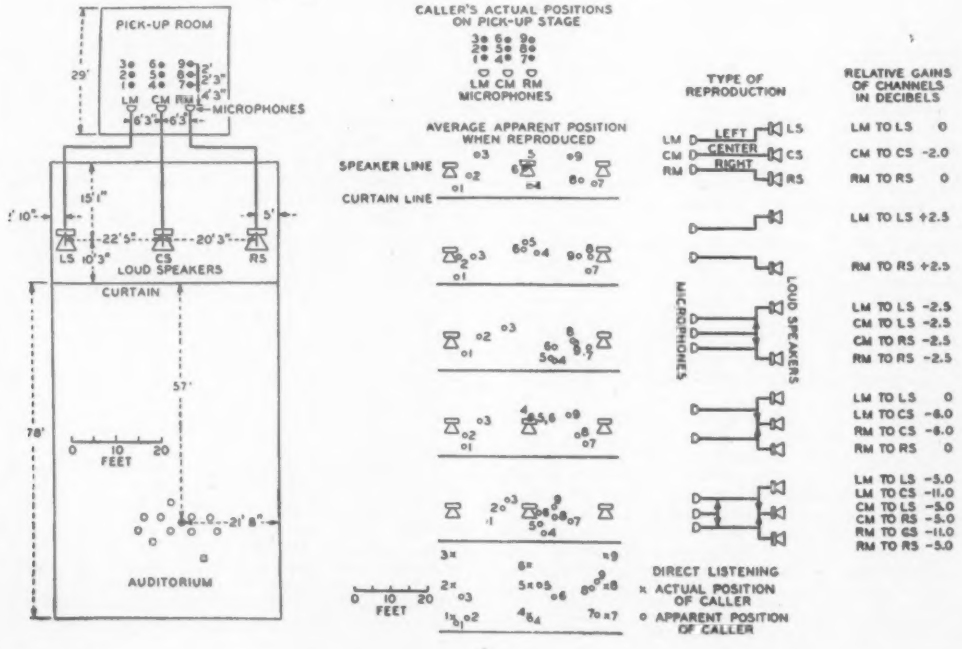

Two or three channels are a feasible proposition using magnetic recording on ¼-in tape to give two or three parallel tracks, and two tracks are possible on discs, using lateral modulation for one channel and vertical modulation for the second channel. The problem of radio transmission is a little more troublesome, largely due to the international difficulties, and it would appear that 2-channel transmission might only be possible in the medium-wave band if two stations were transmitting the same programme simultaneously. This is current practice and it would only require minor modification to radiate left ear programmes from, say, London, and right ear programmes from the Midland Regional station. For e.h.f. broadcasting stations the problems are less difficult; and there is the possibility of simultaneously modulating a single carrier with a number of channels. Without difficulty p.c.m. (pulse code modulation) could be adopted to provide two or three channels and in view of its high overall efficiency this would seem to merit particular attention.

As it is not the purpose of this article to go into details of the equipment but to concentrate on the fundamental of stereophony it will be concluded with a return to the question, "What makes it stereophonic?" Earlier it was shown that the two spaced ears or microphones produced signals which differed in at least five respects, and it is interesting to speculate on the relative importance of the individual contribution to the overall result. It is all the more interesting because there appears to be singularly little agreement on the subject, some authority could be quoted to show that the main factor is any one of the five points discussed, so readers may justifiably feel that the next section lacks precision.

Considering first the response to pure tones, there can be little difference in the amplitude of the left and right ear signals in the low-frequency range. The head represents an obstacle only a small fraction of a wavelength long at, say, 100 cycles, so diffraction differences must be insignificant. If the brain cannot distinguish the peak of one cycle from another, wave-point differences would appear to contain no useful information and the brain is left to estimate position from the phase difference at the two ears. There appears to be no reason why this should not be at least partially satisfactory.

With increase in frequency a point is approached at which the ear spacing is one wavelength and just beyond this the ears may each have the same signal phase but displaced by exactly 2π radians, i.e., the two ears are "on" the same points on successive cycles. Ambiguity will occur between this frequency and a half this value, and, as the mean ear spacing is approximately 21 cm, phase would appear to be of doubtful value as an information carrier above perhaps 700-800 c/s. However, it is just in this region that diffraction effects are commencing to produce significant intensity differences, as reference to Fig. 2 will show, and thus it would appear that on single tones phase is important in the low-frequency range, up to 700-800 c/s, with intensity difference playing the significant role above this frequency.

The more common noises do not have the simplicity of a single-frequency tone and on complex sounds, other factors are probably of importance.

Loudness differences at the two ears will be greatly magnified owing to the large reduction in the intensity of the high-frequency components at the far ear, while the character of the sound at the two ears will also differ appreciably due to the same cause.

On transient sounds, the time of arrival of the wave front at the two ears will also show significant differences, and, as sharpness of wave front indicates the presence of high-frequency components, intensity and character differences will also be produced.

It would appear that all the five effects listed may make significant contributions to the localization of the more usual sound sources, the contribution due to phase difference at the lower frequencies probably being of the least importance.

Further improvement in the quality of reproduced music due to improvement in frequency response seems remote, and it may prove that more acceptable improvements are achieved by diverting our efforts to the problems of stereophony.

Electronic Photography

Image Converter Tubes Used for High-Speed Phenomena

UNTIL now, much of the fame of the image converter tube has rested on its ability to see in the dark objects which are illuminated only by infra-red radiation, and this ability has been exploited in various ways in war-time to enable observations to be made at night without the aid of a tell-tale searchlight. The photocathode of an image converter, unlike the human eye, is sensitive to infra-red radiation, and when the infra-red image is focused on to it electrons are released in a corresponding pattern. These are focused into a beam either electrostatically or electromagnetically and are accelerated, after which they impinge on a fluorescent screen and so create a visible reproduction of the original invisible image.

A further possibility inherent in the tube is that the electron beam can be deflected and chopped, and this is now being utilized in high-speed photography for doing electronically what mechanical devices have so far failed to do. With the normal cameras for photographing high-speed motion, writing speeds of up to 2,000 metres per second have been achieved, but with the use of the image converter, this upper limit can be increased to as much as 100,000 metres per second. J. A. Jenkins, of the Mullard Electronic Research Laboratories, described two methods of application in a lecture he gave at the Engineering Centre, Glasgow, last September. In one, the phenomenon to be photographed is seen from behind a narrow slit, an image of which is focused on to the photocathode of the converter tube. The resultant electron image of the slit is then broadened out into a rectangle by back-and-forward deflection, as given by the time-base of an oscilloscope, so that a time axis is applied to the phenomenon and the tube screen presents a two-dimensional picture which can easily be photographed. In the other method a series of separate pictures are produced on the screen by deflecting the electron image from one position to another and, during movements, shutting off the electron beam by suitably pulsing the tube voltages. The screen of the converter is photographed by an ordinary camera in both methods.

Magnetic Recording Tape

Characteristics Considered in Relation to the Recording Process

By H. G. M. SPRATT,* B.Sc., M.I.E.E.

WHILE it is necessary to go back to the beginning of the century to trace the origins of magnetic recording, modern technique, which exploits the advantages of high-frequency bias, can be said to date from the development of the German "Magnetophon" equipment during the last war. From that time onwards, one outstanding advance alone has taken place, namely the introduction of higher-coercivity materials. This article will try to give as comprehensive a description of magnetic tape as is possible in the space available and will not only cover the subject as a whole, but also explain the advantages arising from recent developments.

Most equipments of present-day design can utilize tape of standardized dimensions. A plastic or paper base, of thickness about 0.0015in and width 0.25in, is provided on one side with a coating containing magnetic iron-oxide powder to give a thickness not greater than 0.0024in. On passing the tape over the air gap of an electromagnetic circuit, known as the recording head, in which a varying magnetic flux is generated by a.f. currents in the windings, corresponding alternate north and south poles are set up in the coating by virtue of the leakage field at the gap. Because of the coercivity of the magnetic material, these form open permanent magnets, each pair of poles with its own associated flux field. Accordingly, if the tape is then passed over the air gap of another magnetic head or circuit provided with a pick-up winding, an e.m.f. will be set up in this winding which, after suitable amplification and equalization, will reproduce with more or less fidelity the original signals applied to the recording head. The words "more or less" are used advisedly, for a bare system on these lines would result in distressingly low fidelity. Fidelity in a communication system implies absence of distortion, low noise level, and a level frquency response. None of these essential features comes naturally. They have to be achieved.

To return to the general description, however, an erase head is generally located before the recording head. This unit is similar to the others, but is fed with a steady a.c., preferably of the same frequency as that used for the h.f. bias described later. Its function is to wipe out existing signals on the tape prior to recording. Thus, if desired, all three heads can be in operation together, the first erasing existing signals, the second recording new signals, and the third reproducing them. The air-gap lengths vary from 0.25×10^{-3}in for a pick-up head to $2\text{–}3 \times 10^{-3}$in for an erase head. Standard tape operating speeds are 30, 15, $7\frac{1}{2}$, and $3\frac{3}{4}$in/sec. The first speed will probably soon be obsolete, but an additional one of $1\frac{7}{8}$in/sec shows signs of coming into use.

Before proceeding to details, it is rather important to present a more realistic picture of the tape and the gap over which it passes. For the sake of simplicity this is invariably depicted in technical literature somewhat similarly to Fig. 1(a) and as such cannot fail to give an incorrect picture of the relative dimensions involved. For a coating thickness of 0.0007in, a gap length of about 0.001in, and a lamination depth at the gap of 0.020in, the enlargement at Fig. 1(b) is a more faithful representation. To complete the picture, the wavelengths for a 250 c/s and for a 5 kc/s signal at a tape speed of $7\frac{1}{2}$in/sec have been included. It is interesting to attempt to envisage the relative strengths of the leakage fields at one or two thousandths of an inch away from the tape surface at such wavelengths.

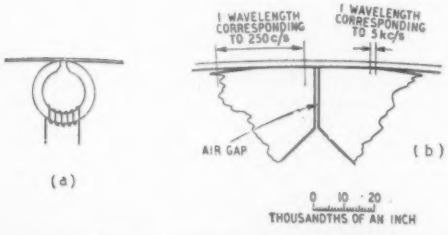

Fig. 1. (a) Conventional illustration of tape and head. (b) Tape and air-gap region of head, drawn to scale.

Basic Frequency Characteristic

As Fig. 1(a) suggests, the function of the reproducing head is to provide a low-reluctance return path for the leakage flux from the tape and to bring about flux linkages with the pick-up coil. The instantaneous recording current i will be given by the exprssion $i = I_m \sin \omega t$, where I_m is the peak value of the current. If demagnetization effects and changes of flux distribution with frequency are ignored, the corresponding leakage flux ϕ from the tape will be proportional to this current. Furthermore, as long as the air gap is small compared with the wavelength on the tape, the instantaneous voltage e set up in the pick-up coil will be proportional to the rate of change of this flux, and is evaluated by differentiating, i.e., $e = k\omega\phi \cos \omega t$ and the r.m.s. value E will equal $k_1\omega\phi$. For constant-current recording, i.e., constants ϕ, E will be proportional to the frequency, rising 6 db per octave. With rising frequency, however, the ratio wavelength/air-gap decreases and an effect analogous to the slit effect in light recording appears. This modifies the expression for the voltage giving $E = k_1\phi \sin (\pi l/\lambda)$,

* Durex Abrasives Ltd.

where l is the air-gap length and λ the wavelength. Fig. 2 shows the resulting curve for pick-up voltage versus frequency, the latter expressed in the normalized form l/λ and also in kc/s for a speed of 7½in/sec and an effective gap of 0.0005in, constant-current recording being assumed. This curve shows that, after rising steadily to a maximum value at a frequency corresponding to a wavelength twice that of the gap, the voltage output falls sharply to zero at $\lambda = l$. With a further increase in frequency the voltage again rises to a maximum and then again falls to zero at $\lambda = \frac{1}{3}l$ and so on. If this gap effect alone had to be considered, the successive voltage peaks would be equal in magnitude. Two other effects, however, cause a gradual fall with frequency, one, the demagnetization effect, which also is dependent on the wavelength and is discussed later, and the other, the iron losses in the pick-up head, a smaller effect dependent on frequency.[1] The quantity l was given as the *effective* gap length, which is not the same as, but is often considerably greater than, the physical gap. The discrepancy arises from the great difficulty in producing a gap to the required mechancial precision.

Magnetization

An explanation of the magnetization process taking place in the coated material demands a return to elementary magnetism. Fig. 3(a) shows a typical BH curve and hysteresis loop for the type of magnetic material employed in magnetic tapes. The first is a static curve of magnetization taken up to saturation, but the loop is of a shape and symmetry such as are reached only after several cycles have been experienced. These curves are, therefore, not really appropriate for studying the induction occurring in the magnetic material, but they can at least be employed to refresh our memory on the general principles of magnetization for high-coercivity materials. Incidentally, it must be admitted that because of their familiarity they are almost universally used for comparison purposes and for relating performances. With the application of a magnetizing field to a material in a completely unmagnetized state, the induction will rise from O following the curve OA and will reach some such peak value as A, depending upon the strength of the field. During subsequent reversals of the field, hysteresis loops will be traced out which take on the final form ABCDEFA when a steady state has been reached. If then at any instant the magnetizing force is removed, the iron will be left magnetized with an amount of remanent induction depending upon the point in the cycle at which the removal or switch-off takes place. Thus, if the switch-off takes place at P, when the magnetizing force is falling, the resulting remanent induction will be OB. If, however, it occurs when the magnetizing force has exactly the same value, but is rising, i.e., at Q, the remanent induction will be OQ_1. Again, for the sake of simplicity, demagnetization effects have for the time being been entirely disregarded.

By contrast with Fig. 3(a), Fig. 3(b) shows the curve followed in the initial cycle of magnetization by a field insufficiently strong to cause saturation. The lines PP_1 and QQ_1 indicate that the remanent induction bears a relation to the loop similar to the one above. It will be observed that both branches AB and BA_1 show appreciable curvature, although admittedly without the points of inflexion associated with saturation. For all that, the whole curve is asymmetrically disposed about the horizontal axis and, as suggested above, will not become symmetrical until several cycles have passed. Bearing in mind the fact that the magnetizing force is a measure of the recording input and the remanent induction a measure of the output, one might reasonably conclude that linear operation was out of the question and fidelity of reproduction impossible. Nevertheless, a closer examination of the loop reveals more or less linear portions in each branch following the "bottom bends," e.g., LA_1. If operation could be restricted to these portions, there would be a chance of an approximation to linear working. The introduction of supersonic bias makes this restriction possible.

The recording head is provided not only with the normal coil carrying the signal current, but also with an additional coil fed with a steady current of frequency some 4 to 7 times that of the highest-frequency signal to be recorded. The optimum current—for maximum amplitude and freedom from distortion—of this supersonic bias, as it is called,

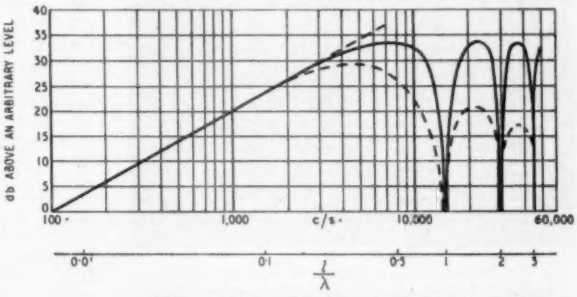

Fig. 2. Voltage output from pick-up head, using tape recorded at constant current. The output falls to zero when the gap length equals any integral number of wavelengths.

Fig. 3. (a) Typical BH curve and hysteresis loop for magnetic tape material. (b) Initial loop for H less than saturation value.

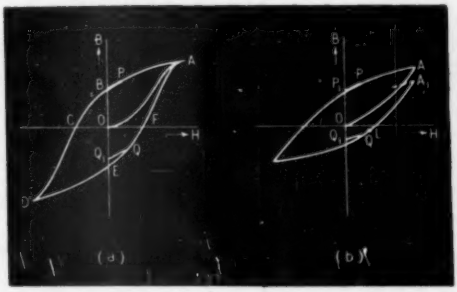

[1] "Overall Frequency Characteristic in Magnetic Recording" by P. E. Axon. *B.B.C. Quarterly* 5 (No. 1) 1–8 (1950).

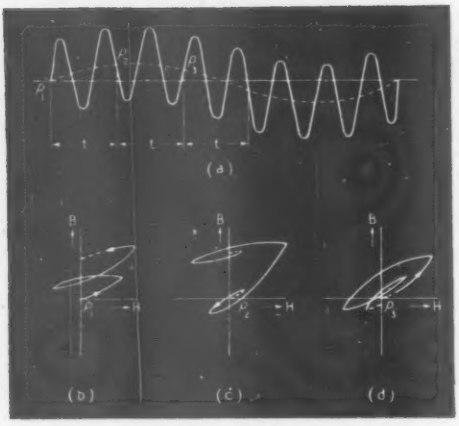

Fig. 4. Graphical presentation of magnetization by an a.f. signal with supersonic bias.

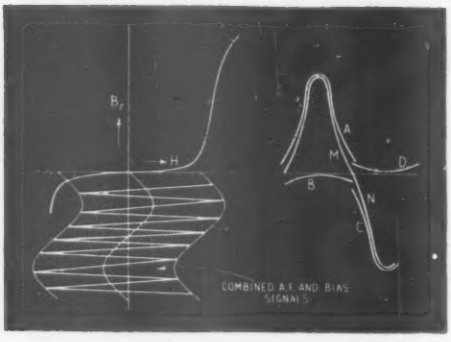

Fig. 5. Construction of output characteristic for a.f. signal with supersonic bias, using the remanent induction curve, B_rH.

Fig. 6. Relationship between bias, output and harmonic distortion.

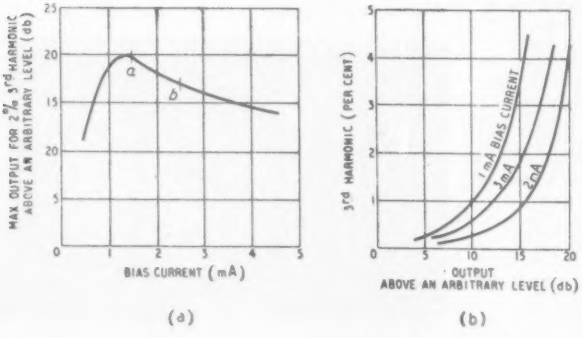

has to be established by adjustment, but is usually about three times that of the maximum signal current. The signal and bias currents, it should be realized, are mixed in the recording head and not intermodulated.

Two graphical constructions introduced by Holmes and Clark[2] show clearly from different viewpoints the action of supersonic bias which are depicted and described below. Fig. 4(a) shows the combined supersonic bias and a.f. signal. Let us assume that a magnetic element approaching the gap is quite unmagnetized, is entirely uninfluenced by a magnetizing field both before and after passing the gap, and—for simplicity—experiences about $1\frac{1}{2}$ h.f. cycles only during the passage. Actually, the number is more likely to be about five, but even so a steady state will not be reached. Then Figs. 4(b), (c) and (d) indicate the magnetization cycles experienced by elements entering the gap at points p_1, p_2, and p_3, t representing the transit time across the gap. It is interesting and gratifying to find that: first, elements at points such as p_1 and p_2, associated with positive signal excursions, are left with a positive remanent induction, while a point such as p_3 tends to receive negative induction; secondly, the remanent induction is, at least qualitatively, proportional to the signal amplitude at the instant of leaving the gap; and thirdly, the smaller a.f. signals obviously influence the remanent induction value far more than the h.f. bias does.

The second construction, Fig. 5, is reminiscent of the construction used to determine the dynamic characteristic of two valves in push-pull when biased just above the bottom bend. The curve corresponding to the static I_a-V_g line is the remanent induction curve, i.e., one obtained by plotting the remanent induction B_r against the magnetizing force H. As is usual, the "input," i.e., the combined a.f. and bias signals are plotted as abscissae while the B_r values corresponding to the points on the input envelopes are projected to give two pairs of "output" curves A, B, C, and D. Substraction of B from A, and D from C give two further curves M and N which combine to produce one complete cycle of approximately sinusoidal form, the output characteristic. Although this last construction will not stand up to a rigid investigation, it does in fact give results similar to those actually obtained. It should be mentioned at this point that small traces only of the bias signal will be left on the tape owing to demagnetization effects, as is explained at some length below. The bias has in fact already served its purpose by shifting the a.f. signals out of the initial magnetization region of the BH curve into the linear portion beyond the bottom bend.

Provided the frequency of the bias is made sufficiently high to avoid serious interaction with the third harmonic of the highest a.f. signal to be transmitted, its value is not critically important, although it has been suggested[3] that the higher the frequency, the less the noise. Ignoring this last factor, we can safely adopt 50 kc/s as a suitable frequency

[2] "Supersonic Bias for Magnetic Recording," by L. C. Holmes and D. L. Clark. *Electronics*, July 1945.

[3] "Some Distinctive Properties of Magnetic-Recording Media," by R. Herr, B. F. Murphy and W. W. Wetzel, *J. Soc. Mot. Pict. Engrs.*, 52, 77-88, Jan. 1949.

for a.f. recording. The choice of bias amplitude is, a different matter, since on its value depends the slope on the BH curve at which the a.f. signals work and the extent of the linear portion available for them. It is, accordingly, not surprising to find two quite different optimum values of bias current, one corresponding to maximum sensitivity, e.g., ratio of output to input, and the other to maximum distortionless output. It is fortunate that in general the sensitivity versus bias current curve, after rising sharply to a maximum value, tends to fall off slowly, since not infrequently the optimum value for distortionless output lies above that for sensitivity. Figs 6(a) and (b) show curves which confirm this. Needless to say, the operating point would be chosen somewhere between *a* and *b* in Fig. 6(a), the region corresponding to maximum distortionless output. Apart from all this, however, where a choice exists, preference should be given to a low rather than to a high value. This is because the higher current will have the combined effect of recording signals which are subsequently harder to erase, and at the same time of partially erasing the higher a.f. signals.

(To be concluded)

How Reliable is a Radio Valve?

IN giving an answer to this question, it is important that the radio valve should be considered against the background of its various applications, for obviously there is a greater need for reliability in some than in others. On this basis an opinion was expressed recently by Dr. G. H. Metson, who considered that the valve was quite reliable enough for present-day entertainment purposes, hardly adequate for serious industrial use, and quite inadequate for aircraft equipment or for those who sank their hopes in subaqueous telephony. He was opening a discussion meeting at the I.E.E. on this same subject, and among the important side-issues he raised were such topics as the possibility of devising some quantitative yard-stick as a measure of reliability and whether it was feasible to manufacture "reliable" valves for special purposes as distinct from "ordinary valves."

Several speakers gave information on specific valve types. It was mentioned, for instance, that C. S. Cockerell had obtained a broad average indication of reliability from some tests he had done on the valve types CV131, CV136, CV138 and CV140. Out of 18,700 samples, 697 had either developed faults during a 50-hour test on stationary racks or had been found to be faulty when drawn from stores. One speaker stated that the average life of 27 valves in a certain civil aircraft equipment during one year's operation was only 1,600 hours, and he added that, of the 17 per cent of aircraft delays ascribable to radio failures, 60 per cent could be put down to faulty valves. A Post Office engineer complained that valves were not so rigorously tested as other components, and stated that the number of telephone faults traced to valves was comparable to that caused by all other associated components.

Miniature valves were mentioned by several speakers as not having yet achieved a satisfactory average life, and the comment of one speaker was that the manufacturers were tending to make the ratings too high, so that a greater performance was demanded than valves of such a size could give. He had found that if the valves were operated at 80 per cent of their specified ratings, a more reasonable life could be expected.

It was pointed out by other speakers, however, that the figures given appeared pessimistic, and the meeting was reminded that most of the valves mentioned were broadcast-receiving types. Current experience with miniature valves appeared to indicate that the number of "catastrophic" failures did not exceed 1 per cent, and that these valves would last for thousands of hours if they were run under proper conditions.

The causes of valve failures were also discussed, and one suggestion was that valve designers worked to an accuracy that did not allow for possible overloading caused by the wide tolerances of related components generally found in practice. There was a difference of opinion on whether the switching on and off of heaters was detrimental to the life of a valve. Further causes of failure mentioned were insufficient control of heater voltage; mechanical defects, such as loose spacers; vibration; clumsy insertion of valves into their sockets; and badly designed sockets which strained the valve pins. It was also pointed out that sometimes a valve was replaced in an equipment in which the running conditions had already been upset by the failure of the original valve, so that the replacement was at once overloaded.

A significant topic that arose was the necessity for a distinction between valve reliability and life. Although most people looked for long life as a part of reliability, one was not necessarily a criterion of the other. Dr. Metson pointed out that reliability was mainly governed by mechanical faults, which were usually revealed very early in the life of the valve, whilst longevity was largely a matter of cathode processing. The first aim of manufacturers should be to give reliability, since this was a basic necessity for all valves; then longevity could be provided for if required.

Statistics were mentioned as a means of calculating the probability of survival during any period and so indicating when replacements were advisable. It was generally agreed that they would give some idea of the probable further life of the large number of valves already in existence, but a more analytical study of individual specimens was necessary to determine the actual reasons for the failures.

It was generally agreed that the cost of faulty valves was not so much that of the replacements themselves but that of having to keep spare equipments in readiness—and, of course, the loss of goodwill.

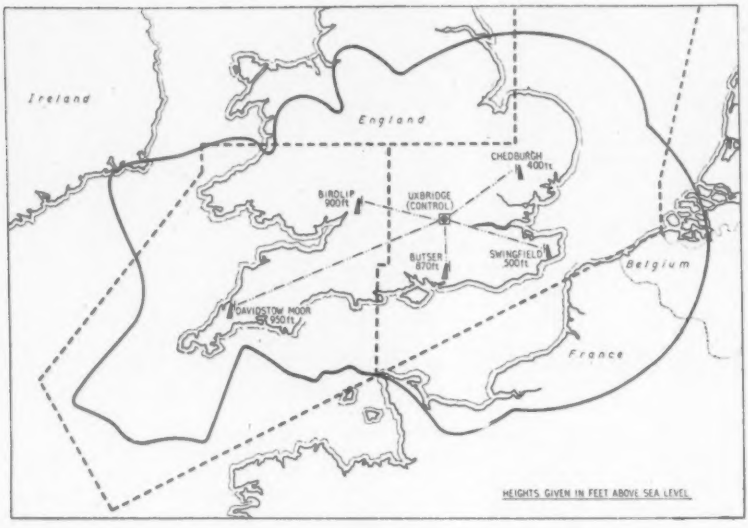

(Left) **Fig. 1.** Map of the country served by the southern chain of v.h.f. stations used for communication with civil aircraft. All five operate as a multi-carrier system on one channel in the band 118 to 132 Mc/s. Theoretical coverage at 10,000 ft.

(Right) **Fig. 2.** The wide-band vertical dipole aerial used at the M.C.A. stations.

(Extreme right) **Fig. 3.** View of the transmitting hall at Butser, showing the eight T1131A transmitters and, facing them, a crystal comparator unit for checking the frequency of crystals.

Map and Photos : Courtesy Ministry of Civil Aviation.

Multi-Carrier Air Communications

V.H.F. Wide Coverage Scheme for Civil Aviation

RADIO telephony in the v.h.f. band 118-132 Mc/s is now almost the sole means of communication with aircraft over relatively short distances and in the vicinity of aerodromes. Transmissions on lower frequencies, though accepted, are being discouraged in favour of the higher frequencies.

With the higher speeds reached by modern aircraft it was realized some time ago that the range covered by a ground station of 50 watts or so, which is the normal power of equipment in general use, was inadequate when large numbers of aircraft tended to converge on to a busy airport.

In looking for a way of extending the coverage obtainable with v.h.f. the Ministry of Civil Aviation has been experimenting with the multi-carrier idea whereby a number of transmitters are installed at strategic sites and all modulated from a common source. These appeared so promising that a full and comprehensive scheme was worked out for the complete coverage of the British Isles and its regular air approaches by v.h.f. radiotelephony.

Actually the communications network is part only of a much larger plan, which involves the use of radio beacons of various kinds to guide aircraft into a number of air lanes, or "airways" as they are called, and to enable them to navigate these airways by means of radio marker beacons located at known points.

Since aircraft fly in both directions along the airways, constant communication between air and ground is essential for safe flying and this is where the v.h.f. radiotelephone finds its principal use.

In order to bring aircraft into airports like Heathrow, Northolt and Prestwick, for example, radio contact has to be made with the aircraft well over a hundred miles from its destination and, if necessary, slow down its progress to avoid dangerous congestion over the aerodrome. In order to effect this the country is divided into four main radio control areas, termed Flight Information Regions.

The F.I.R. radio controllers direct aircraft into the airways, guide them along at specified heights and eventually pass them into an inner control zone, which may be under the airport controller, or to an intermediate control such as exists in the London area.

The two southern flight information regions are for the most part acting as a single region with the control centre at Uxbridge, but there is a control at Gloucester for handling aircraft using the aerodromes situated in that part of the country. Other control centres are at Preston and at Prestwick.

Whilst the various regions differ in the actual number of transmitting and receiving sites employed, the basic system of operation is the same throughout and it will thus suffice if a description is given of one only. The combined south-eastern and south-western was selected as the control centre at Uxbridge and one of its stations, Butser, just north of Portsmouth, were conveniently situated for a visit.

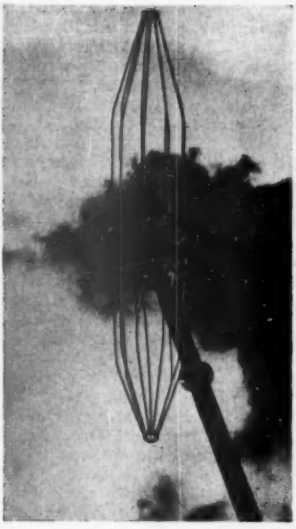

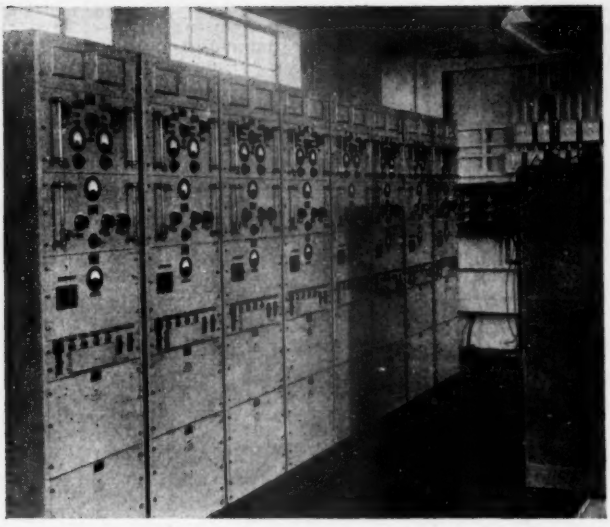

Disposed throughout the two southern regions are five combined transmitting and receiving stations, the sites being chosen at Chedburgh, near Bury St. Edmunds, Birdlip, near Gloucester, Davidstow Moor, near St. Eval, Butser, near Portsmouth and Swingfield, near Folkestone. They are thus very widely spaced geographically and an elaborate system of land lines is needed to link them to Uxbridge and provide for remote control of the transmitters. Lines, which are mainly for carrier current operation, are supplied and maintained by the Post Office.

Each of these stations will be able to send and receive simultaneously on four different channels, although at the time of our visit two only were ready for immediate operation.

One transmitter at each of these stations is allotted to a single channel on about 126 Mc/s. Three have a 10-kc/s frequency separation and the most widely spaced pair (Davidstow Moor and Chedburgh) share a common frequency. Together the five stations give an estimated coverage over an area enclosed by the full-line boundary on the map in Fig. 1. It represents approximately all that country south of a line drawn from the Humber to the Mersey, but excluding North Wales and Anglesey. It takes in the southern approach to the St. George's Channel, the south-east tip of Eire, covers the Scilly Isles and part of the French coast from Cherbourg north-eastwards to the Schelde in Holland. Aircraft flying over French, Belgium or Dutch territory are, of course, subject to control of those countries. The nominal separate jurisdiction of the two southern flight information regions is shown by the broken-line boundaries.

As already mentioned two transmitting channels are in operation at each station, but all five are not operating on the same alternative channel. The one centred on 126 Mc/s gives a general coverage and the alternatives are arranged, at present, to give a more localized service. For example, Chedburgh, Birdlip and Davidstow Moor form a three-station chain on 122 Mc/s covering the north and north-western approaches, while Butser operates on a single frequency covering the south and south-west, and Swingfield provides a third channel for local coverage to the east and south-east. Thus there are four communication channels available in this area although individual stations at present operate on two only.

The locations of the stations are all on high ground as the elevation figures on Fig. 1 testify. At each site there is a 120-foot wooden tower supporting four wide-band vertical dipoles taking the form shown in Fig. 2. Each aerial is sensibly flat over the band 118 to 132 Mc/s and the arrangement is that two are earmarked for transmitting and two for receiving, but one only of each pair is in use at a time.

This policy of duplication of equipment is followed throughout the entire radio chain. For example, there are, or will be, eight transmitters at each station, one for each of four operating channels with a reserve alongside and with automatic change-over switching. Heater current is supplied to all valves in the reserve transmitter, and the crystal oscillator, which is in a temperature-controlled oven, is kept at the operating temperature for immediate use. In Fig. 3 is shown an imposing row of eight modified T1131A transmitters installed at Butser. The nominal output of this set is between 40 and 50 watts in the band 118-132 Mc/s.

An interesting feature of the transmitter layout is the provision of a frequency comparator which enables each crystal oscillator to be compared in frequency with its stand-by and also with a third acting as a spare. All these are checked regularly and the differences noted. The aim is to keep all three crystal units within a few cycles of each other so that whenever the reserve transmitter comes into operation it is substantially on the same frequency as the other.

At present one receiving and one transmitting aerial only is in use at each station. This means that each aerial is operating simultaneously on two frequencies, either sending or receiving. The system employed was originally developed by the Admiralty and is known as "Common Aerial Working." A form of

automatic trap is included in the lead from the aerial feeder to each transmitter, which effectively bars the passage of the r.f. output from one transmitter to the other and directs it into the aerial. The same process, but in reverse, takes place for receiving.

The simultaneous use of one aerial for two transmitters close in frequency makes use of two well-known characteristics of resonant lines. One is that a quarter-wave section of line, or feeder cable, short-circuited at one end exhibits an extremely high impedance at the opposite end, and the other is that a high "Q" resonator has a high non-reactive impedance at the frequency to which it is tuned, but for all practical purposes is a short circuit off tune.

By connecting a quarter-wave section of line in series with a resonator (cavity resonators are employed) in the branch feeder to each transmitter, or receiver, as shown in Fig. 4 entire independence of operation is achieved. To a signal at frequency F_1 arriving at the junction A the system takes on the appearance of Fig. 5. Since the resonator Res_2 is tuned to a different frequency it is virtually a short circuit to frequency F_1, and as Q_1 is resonant also at F_1 its end at point A offers a very high impedance to the signal and diverts it into Q_2, which being non-resonant at F_1, does not affect the behavour of Res_1, which appears as a very high impedance across the line to R_{x1} at frequency F_1. At frequency F_2 Res_1 becomes the short circuit and Res_2 the high impedance so that signals are thus diverted into receiver R_{x2}.

The same system is employed for transmission, and to follow the operation it is only necessary to reverse the order and regard the transmitters as the source of signals, whereas the aerial was so taken for the explanation of the principles.

When more than two transmitters, or receivers, are employed a compromise adjustment of the quarter-wave line sections (Q_1 and Q_2 in Figs. 4 and 5) is necessary, and they are then made on electrical quarter wavelength at the mid-band frequency.

The advantages claimed for the common aerial system are that in the first case fewer aerials are needed—two instead of eight excluding reserves—and one mast suffices as the aerials can be arranged so that the receiving one is in the minimum field of the transmitting aerial. For this reason the aerials as seen at Butser are mounted in a line vertically (vertical polarization is employed), and while this leads to a small reduction in height of some, it avoids undesirable complications elsewhere. It is said that the system leads to a saving in site space and also to some economy in telephone lines and terminal equipment.

For receiving, a modified version of the R1392A ground receiver is used. It is a 15-valve superhet designed for fixed-frequency operation in the band 100-150 Mc/s, and it has a crystal-controlled oscillator and a chain of frequency multipliers. There are two r.f. stages and three i.f. Eight of these receivers, each with a separate power unit, will be installed in a fully screened room to prevent interference from harmonies of the adjacent transmitters. Four will be active and four on immediate reserves. The receivers at Butser are shown in Fig. 6, the four seen in this view serving for the two channels at present in operation and there is space alongside for four more. Their power units can be seen below the writing shelves.

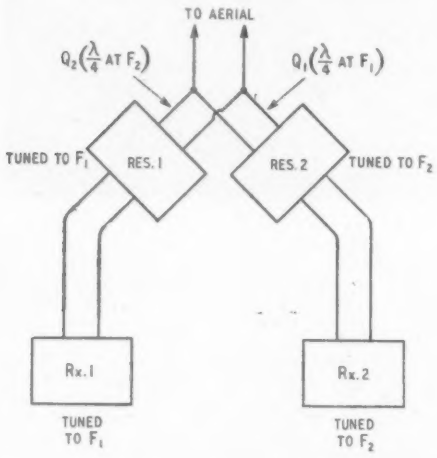

Fig. 4. Schematic arrangement of the common aerial system of operation showing position of quarter-wave lines and resonators for operation on two channels which should have a minimum spacing of 2 Mc/s.

Fig. 5. Equivalent circuit for Fig. 4 as seen by a signal arriving at the point A at a frequency of F_1.

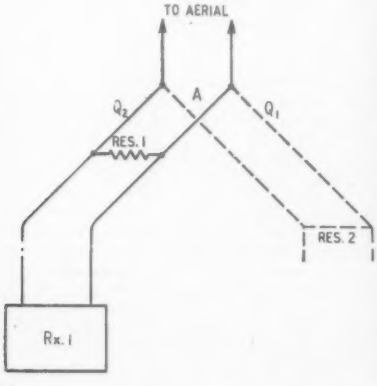

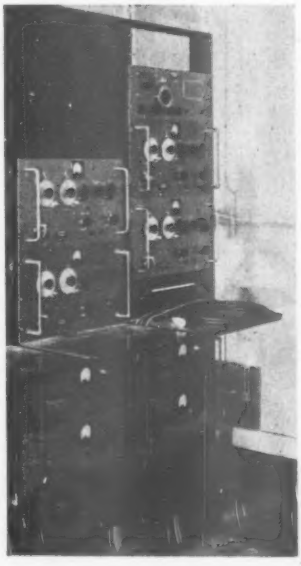

Fig. 6. Corner of a receiving room showing four R1392A receivers in position—two active, two reserve—with power units below the writing shelves. (*Photo: Courtesy of Ministry of Civil Aviation.*)

These Valves make News!

VOLTAGE REGULATORS—TYPES VR75/30 VR105/30 VR150/30

British made Stabilisers of the above types are **now available from stock**

Their electrical characteristics, dimensions and base connections are identical to the American Counterparts bearing the same type number.

NOTE: Some American Manufacturers code these valves

OA3/VR75
OC3/VR105
OD3/VR150

Type VR75/30

Minimum starting voltage ..... 105 volts
Nominal operating voltage ..... 75 volts
Minimum operating current ... 5 mA
Maximum operating current ... 40 mA

List Price **17/6**

Type VR105/30

Minimum starting voltage ..... 135 volts
Nominal operating voltage ..... 105 volts
Minimum operating current ... 5 mA
Maximum operating current ... 40 mA

List Price **17/6**

Type VR150/30

Minimum starting voltage ..... 185 volts
Nominal operating voltage ..... 150 volts
Minimum operating current ... 5 mA
Maximum operating current ... 40 mA

List Price **15/-**

BRIMAR

WRITE NOW TO DEPT. 4530
for data sheets on the above valves.

TECHNICAL ADVICE SERVICE

STANDARD TELEPHONES AND CABLES LIMITED, FOOTSCRAY, SIDCUP, KENT.

high fidelity

MICROPHONES

FOR PUBLIC ADDRESS, RECORDING, AMATEUR RADIO

TYPE MIC 22

This model incorporates the famous Acos "Filtercel" insert giving extreme sensitivity and high fidelity. Response is substantially flat from 40-6,000 c.p.s. The microphone is vibration and shock proof and is not affected by low frequency wind noises. Two alternative mountings are available for the MIC 22 head :—

MIC 22-2 is supplied as a complete unit incorporating an attractive desk stand with cable side entry

MIC 22-1 is for fitting to any British or American type standard floor stand and can also be used as a hand microphone.

PRICE £6. 6s. *(Either Model)*

TYPE MIC 16

Incorporates the Acos Floating Crystal Sound Cell giving a response substantially flat from 30-10,000 c.p.s. Performance is unaffected by vibration or shock and low frequency wind noise. As in the case of the MIC 22, two alternative mountings are available for the MIC16 Head :—

MIC 16-2 is a complete desk stand unit with side cable entry.

MIC 16-1 is ready for fixing to either British or American type floor stands by means of a knurled ring.

PRICE £12. 12s. *(Either Model)*

COSMOCORD LIMITED, ENFIELD, MIDDX.

Vector Diagrams

By "CATHODE RAY"

3.—*Enter the Valve*

THIS final chapter in the series was actually the original starting point. If you remember, a demand had arisen for some light on a subject which appears to have been illuminated seldom and not always helpfully—vector diagrams of valve circuits—but when I came to look into the matter I found that a large part of the trouble was due to varying and confused practices in connection with vector diagrams in general, and—even more basically—in the specifying of circuit currents and voltages.

The main conclusions so far have been that the usual methods of referring to voltages as "V_1," etc., aided perhaps by one or two arrows, leave room for doubt as to what exactly is meant; in particular, it is quite easy to arrive at opposite conclusions about the direction or polarity of a voltage. And that the double-subscript notation ("V_{ab}") obviates all this, provided that there is agreement to work throughout in either rises or falls of potential. And that those who adopt this notation often seem to work in falls, which is a pity because the reverse has certain advantages, not the least being that it enables the same notation to be applied in a particularly neat and foolproof manner to the vector diagram also.

Just as a reminder, Fig. 1 shows an example of this technique. (a) is the circuit diagram, with the component junctions lettered and an arbitrary direction of current marked by a broad arrow head. (b) is the corresponding "generalized" vector diagram, with a broad arrow to indicate the arbitrary phase of the current. The whole diagram is supposed to be rotating anticlockwise. In the position shown, with the I vector pointing to 3 o'clock—the conventional zero—the current is just about to begin its positive half-cycle. The position of *a*, vertically above *c*, means that point *a* in the circuit is then at its maximum positive voltage relative to *c*. And so on. The whole situation can be visualized quite easily and unmistakably. The effect of tying any point in the circuit to earth or zero potential is represented by pinning the corresponding point in Fig. 1(b) to the table, so making it the centre of rotation. If one particular circuit point is known to be earthed, that fact can be indicated in the vector diagram by converting it into the "particular" form, which for earthed *a* would be Fig. 1(c). Note how clear and free from unnecessary labels both circuit and vector diagrams are. No voltage labels are needed, but any voltage can be precisely referred to in either direction; the voltage driving current through R, for example, (reckoned in the same direction round the circuit as the current) is V_{ca}.

The first thing to decide when bringing in the valve is whether to treat it as a real valve, with electrons flying across a vacuum under the influence of anode and grid bias voltages as well as of any alternating ("signal") voltages that may be superimposed on them, or whether we are going to substitute an imitation valve made of ordinary circuit components like those in Fig. 1(a). When studying the thing for the first time it is quite essential to adopt the first method, if only to be sure that the second method, when we come to use it, gives nearly enough the same answer. But the first method calls for a good deal of concentrated thought, on lines outside ordinary LCR electrical theory, and once we have learnt the reality of the matter we can save ourselves a vast amount of effort on many subsequent routine calculations by neglecting the features of the valve that have only a slight effect on the result, so enabling an artificial valve to be substituted, reducing the work to ordinary circuit calculation. It is rather like the necessity for an engineer to have learnt the principles of multiplication and division and logarithms at some time or other, even though in practice he does nearly all his calculations mechanically on a slide rule.

If you object on principle to "mathematical abstractions," then by all means do it the hard way every time and good luck to you. But don't complain that it *is* hard and that lengthy arguments arise if you try to fit the real valve into simple Ohm's Law. It won't go. The only sure way of dealing with an actual valve is according to its own behaviour as found by experiment. If you attribute to it an anode resistance, then it has to be a variable resistance controlled by the various electrode voltages.

On the other hand if you have no conscientious objection to making use of the short-cut "valve equivalent generator," remember (a) that it is only a fake, capable of giving answers near enough if used intelligently within its limitations, but very misleading outside them; and (b) that it relates to a.c. only, so h.t. batteries and other accessories necessary to the proper functioning of the real valve are as superfluous to it as a cup of tea would be to a robot.

Fig. 1. A simple sample of the recommended technique: (a) the circuit diagram; (b) the general form of the vector diagram; and (c) the particular form of vector diagram corresponding to point *a* in the circuit being kept at zero potential. In all three diagrams a thick arrow head denotes current.

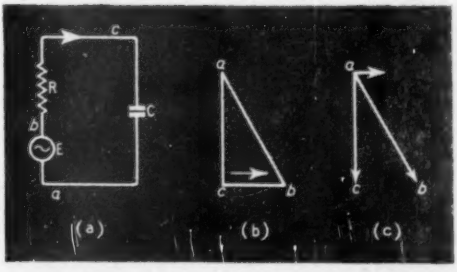

Since vectors also refer to the a.c. component only, there is obviously a good argument in favour of using them in conjunction with the imitation valve. As is well known, in its simplest and most usual form this substitute consists of a generator developing an e.m.f. equal to $-\mu V_g$ volts, and having a resistance in series, the so-called incremental or a.c. anode resistance, denoted by r_a.

There have been lengthy disputes in high places over the minus sign. I am one of those who favour using it, on the ground that it is necessary if the imitation valve is to imitate the actual performance of the real valve, assuming (as most people do most of the time) that the anode and grid voltages are both reckoned relative to the cathode. Those who reckon the grid voltage relative to the cathode and then prefer to stand on their heads and reckon the cathode voltage with respect to the anode are rewarded for their effort by being able to dispense with the minus. Their main objection to the minus, apparently, is that if the e.m.f. of the generator in the imitation valve is regarded as acting from cathode to anode the positive direction of the signal current caused by it in the anode circuit is opposite to the steady feed current caused by the h.t. supply. Why that should worry anybody, seeing that the h.t. supply has nothing to do with the imitation valve, and should have been sent away along with the real valve, I don't know, but apparently it does.

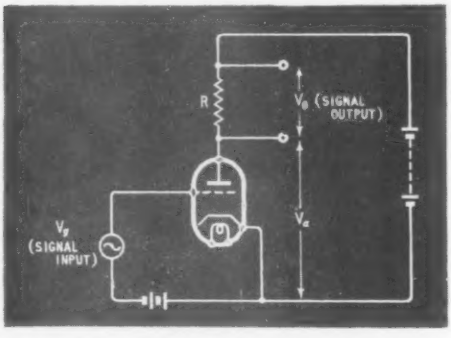

Fig. 2. Circuit diagram of a simple resistance-coupled amplifier.

Fig. 3. "Equivalent" imitation valve substituted for the real valve in Fig. 2. The only difference between (a) and (b) is in the layout of the drawing.

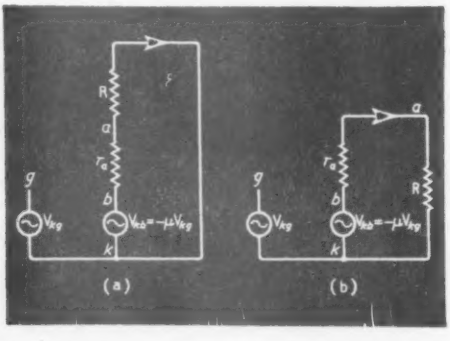

Readers who did not see, or have forgotten, the last instalment may be wondering what use a minus sign has in a purely a.c. system anyway. If μV_g were the only driving voltage in the system there would be no sense in putting a minus in front of it; but actually one of the most important things to be taken into account is the phase relationship between the anode voltage and the signal voltage at the grid, V_g. The experimental fact is that in a resistance-coupled amplifier the output voltage, at the anode, is opposite in phase to the input voltage, at the grid. Unless ordinary circuit calculations performed on the circuit containing the imitation valve give the same result, then our imitation valve is no good and we had better throw it away. The minus sign is the simplest way of ensuring the right phase relationship.

Resistance-coupled Amplifier

But all this should be easier to follow if we try an actual example, Fig. 2. This is a conventional circuit diagram of a real valve arranged as a resistance-coupled amplifier. V_g and V_0 refer only to the alternating parts of the voltages at grid and anode. V_0 is being caused by the current from the h.t. battery varying due to the resistance of the valve being varied by V_g, so varying the voltage dropped across R. Beginners sometimes get into difficulty about the relationship between V_0 and V_g. I have even known a self-styled teacher "explain" the phase-reversal in the valve amplifier by using a diagram like this to show that V_g is opposite in phase to V_0. What he did not appear to perceive is that V_0 is identically the same alternating voltage as V_g, and it is merely the way the diagram is drawn that encourages one to reckon it in the opposite direction round the circuit. Without altering the *alternating* voltages in any way, the upper terminal of V_0 can be slid along the connecting wire and past the h.t. battery to the cathode side. V_0 and V_a then coincide and it is no longer possible not to see that they are the same. Reckoning the same voltage in opposite directions round a circuit and discovering that the results are 180° out of phase doesn't prove anything about valves; it leads to nothing more interesting than the not unfamiliar fact that $-(x) = -x$. The phase reversal is actually a result of the nature of the valve, explained in any book on it. And seeing that its nature is somewhat complex and not within the scope of elementary circuit arithmetic we now regretfully turn it out, along with the h.t. battery, the grid bias battery, the filament heater, the valve holder, and any other details of the equipment, and substitute our ersatz valve (Fig. 3) which requires none of these things.

Both (a) and (b) are the same diagram; the only difference is that (a) is laid out as like Fig. 2 as possible, for the benefit of the less experienced readers, whereas (b) is a little neater. The comparison provides another opportunity of getting used to the fact that the alternating voltage across the coupling resistor R is the same voltage as the one from anode to cathode. Note that although there is now no real valve in the circuit—so no grid or anode—the lettering has been chosen to remind us of the corresponding terminals of the real valve—*g* for grid, *a* for anode, and *k* which is the standard symbol for what classical

scholars like " Free Grid " call the kathode. Terminal *b* in the imitation valve doesn't exist in the real valve, so one can't use it. If you want a mnemonic, *b* can be thought of as locked away inside the " bottle". The input signal voltage is now called V_{kg} to make quite clear that it is acting in such a way as to raise the potential in the direction *k*-to-*g*. If, as is customary, we reckon the anode voltage also with reference to cathode, then the signal anode current must be shown flowing in that direction, and to get the phase reversal the valve " generator " voltage must be minus relative to V_{kg}.

Now at last we get to the valve vector diagram. So much care having been taken over the preliminaries, there is nothing to it. We have a perfectly ordinary circuit, labelled in our foolproof manner, and the problem is actually simpler than Fig. 1. Draw the arbitrary current vector (Fig. 4). Then a line *ka* parallel to it, proportional in length to R, to represent the voltage (from the imitation valve) driving current through R. Then an extension *ab*, proportional in length to r_a, to represent the voltage driving current through r_a. So now we have *kb* representing V_{kb}, the imaginary generator e.m.f., and need only draw a line $1/\mu$ times as long and in the opposite (minus) direction to represent V_{kg}. The voltage amplification is, of course, V_{ka}/V_{kg}, and the phase shift is seen from Fig. 4 to be 180° (as if we didn't know it ! But it is nice to find that our substitute gives us the right answer). If we work out V_{ka}/V_{kg} by arithmetic from Fig. 4 we find it agrees with the familiar formula $\mu R/(R + r_a)$.

This circuit, with its entire absence of reactance, is so easy to do by arithmetic that the only purpose in drawing the vector diagram is to get used to the technique. Incidentally, in this type of amplifier it is usual to earth the cathode (directly, or through a large by-pass capacitor) so if you like you can mark " *k* " in Fig. 4 with a little circle and draw arrow heads pointing away from it at *g*, *a*, and *b*. But one of the merits of the generalized diagram is that you can use it to see what happens when you earth any point you like. Suppose we try turning it into a cathode follower. In a cathode follower the anode is kept at earth potential, so far as signal voltages are concerned, so all we do is make Fig. 4 rotate about *a* instead of *k*. The output voltage is now drawn from the cathode, and is V_{ak}, while the input voltage is V_{ag}. So the output voltage is in phase with the input and is inevitably less than the input. Which again agrees with what actually happens with a real valve.

And by sticking the pin through *g* we can study the earthed-grid (or, as the Americans among us say, " grounded-grid ") amplifier.

For the sake of practice you might care to try the " concertina " phase-splitting circuit, made from Fig. 3 by inserting a resistance equal to R between *k* and the common earth line (which you might label *e*). Although V_{kb} is still $-\mu V_{kg}$, the input voltage is of course V_{gg}, which, if you have drawn the diagram correctly, is larger than V_{ak} and in phase with it, while the other output voltage, V_{ea}, is equal to V_{ak} but in opposite phase.

Next, let us see what happens if the original amplifier is used at such high frequencies that the capacitance from anode to cathode (C_{ak}) provides a relatively low-impedance path (Fig. 5). This confronts us for the first time with a parallel circuit and therefore with the necessity for making a current

Fig. 4. Generalized vector diagram relating to Fig. 3.

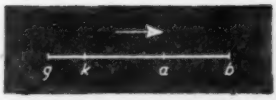

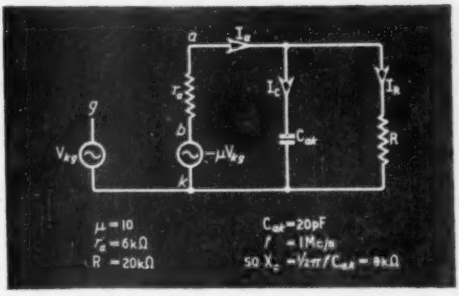

Fig. 5. Equivalent circuit diagram corresponding to Fig. 2 at radio frequency, taking account of the stray capacitance between anode and cathode.

Fig. 6. (a) Current vector diagram in anode circuit of Fig. 5. The voltage diagram is completed in (b).

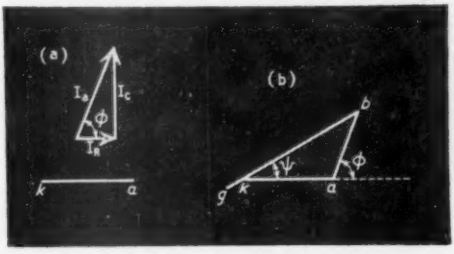

diagram. Hitherto the golden rule has been to start with the current, because in a purely series circuit that is the one thing common to all its components, and the voltages are easily calculated from it. Now there are different currents flowing through R and C_{ak}. But there is a common voltage across them (V_{ka}) so we start with that. We know I_R is in phase with it, and that I_C leads it by 90°. And that I_R is equal to V_{ka}/R and I_C is equal to V_{ka}/X_C. To make the thing more definite let us suppose that the component values are as listed below Fig. 5.

We begin by drawing a vector to represent V_{ka}, the required output voltage (say 50), at any convenient phase and to any convenient scale, Fig. 6(a). The I_R vector must be parallel to it and pointing in the *k*-to-*a* direction. As I_R is $V_{ka}/R = 50/20 = 2.5$ mA, its length should represent that to any convenient current scale. The I_C vector must lead *ka* by 90°, and its length must represent $V_{ka}/X_C = 50/8 = 6.25$ mA. The length of the I_a vector—the vectorial sum of I_R and I_C—will then tell us that I_a is 6.73 mA.

Since the I_R vector is parallel to *ka*, we now know the angle, ϕ, by which the anode signal current leads the output voltage. It is just over 68°. So we can proceed to complete the voltage diagram, Fig. 6(b)

We already have ka; and ab, representing the voltage V_{ab} applied to r_a, being in phase with I_a, must be drawn parallel to the I_a vector. It is equal to $I_a r_a$, which is 40.4 volts. That fixes the line kb, the length of which tells us that V_{kb} is 75 volts. V_{kg} is $1/\mu$ times as large (7.5 volts) and in the opposite direction. One effect of C is now seen to be to make the output voltage lag more than 180° behind the input, but this increase, ψ, is less than ϕ—actually 30°. The amplification—given by the ratio of ka to kg—is $50/7.5 = 6.7$. Without C_{ak}, or at low frequencies, it would be $10 \times 20/(20 + 6) = 7.7$. Considering how heavily C_{ak} shunts R, the drop in voltage amplification that it causes is not as much as one might have expected before drawing the diagram.

Let us now take the plunge and tackle the notoriously difficult tuned-anode tuned-grid oscillator circuit. It can be represented reasonably accurately by the "equivalent" circuit shown as Fig. 7. Here L_1 and R_1 are the inductance and loss resistance of the grid tuning coil, and C_1 the grid tuning capacitance (including the grid-to-cathode capacitance of the valve); L_0, R_0, and C_0 are the anode tuning ditto; and C_{ag} is the anode-to-grid capacitance of the valve.

The difficulty about analysing this circuit is that it seems to consist of a set of interlinked vicious circles! Of course the working-out depends a good deal on how much one is given or assumes and what one is setting out to find or prove. If all the component values and the frequency are given, then one can tackle it bit by bit in the same way as Fig. 5, gradually building up the complete voltage and current diagrams. If the result makes $V_{kb} = -\mu V_{kg}$, then oscillation will take place at that frequency. But it would be an incredible fluke if values at random turned out that way; so perhaps it will be better if we assume likely values for all except the anode tuning coil, and then see if the impedance required there to sustain oscillation is physically possible.

Having explained the previous examples in such detail, I hope it will be enough to give a summary of one possible sequence. Remember that with the rise-of-potential convention I have been using, the voltage required to drive current through any impedance has to be reckoned in the direction of the current through the source of the rise; not through the impedance itself, which of course is a fall. So if we begin by assuming I_{L1}, the voltage across it is V_{kp}, not V_{pk}. Provided that care is taken over this there should be no mistakes. So here goes.

Fig. 7. Equivalent circuit diagram of tuned-grid tuned-anode oscillator, with arbitrary current directions marked. (Any of these directions could be reversed, provided that the corresponding current vector was also reversed.)

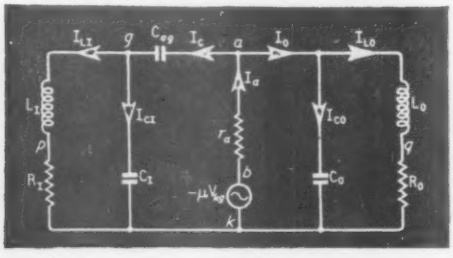

Assume I_{L1}. That gives V_{kp} (in phase) and V_{pg} (90° leading) and hence (by addition) V_{kg}. Remember that normally the reactance of L_1 will be many times greater than R_1, so I_{L1} will be found nearly 90° behind V_{kg}, as in Fig. 8(a). Then draw I_{C1} leading V_{kg} by 90°, and if you take my tip you will choose a frequency that makes the reactance of C_1 rather higher than that of L_1, so that I_{C1} will be less than I_{L1}. Adding the two currents gives I_C, and V_{ga} must lag it by 90°. Normally C_{ag} will be small, so make V_{ga} quite large. You now have V_{ka}, and also $V_{kb}(= -\mu V_{kg})$. And so V_{ab}, and, in phase with

Fig. 8. How the vector diagram for Fig. 7 is built up bit by bit: (a) the assumed I_{L1} and the grid tuning coil voltage diagram derived from it; (b) adding the grid tuning capacitance current gives the phase of I_C and enables the voltage diagram to be completed; (c) I_0 is the difference between I_a and I_C; (d) I_{C0} can be calculated, leading to I_{L0}, which corresponds to a typical tuning coil worked slightly below the resonant frequency; and in (e) the foregoing portions of the current diagram are put together.

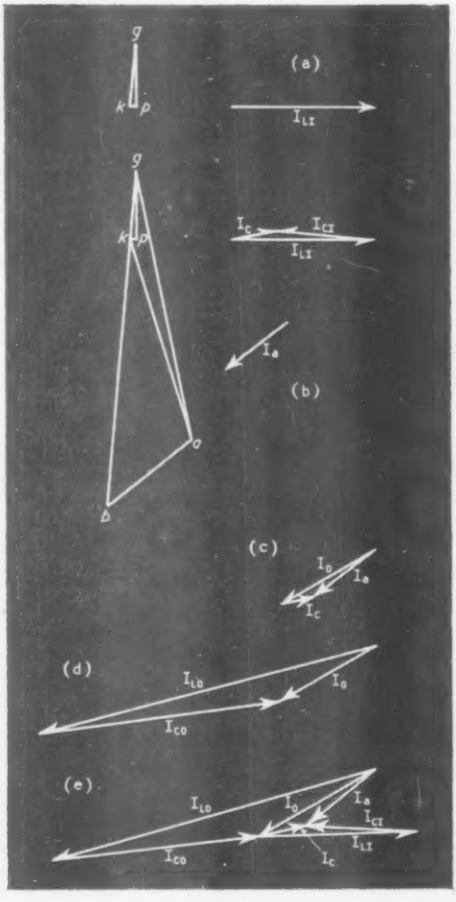

it, I_a (Fig. 8(b)). Not knowing I_0, you will have to assume a length for I_a. One would expect it to be such as to make I_0 (the difference between I_a and I_c) a good deal larger than I_c (Fig. 8(c)). I_{C0} follows from the known V_{gs} and C_0, leading V_{as} by 90°; and deducting it (vectorially, of course) from I_0 gives the I_{L0} necessary for this whole system to operate (Fig. 8(d)). If the values chosen elsewhere have been at all suitable, it should be found that I_{L0}, driven by V_{gs}, can be fulfilled by an inductive reactance somewhat smaller than the capacitive reactance of C_0, without calling for a negative value of R_0. You may remember that an essential condition for oscillation in this type of circuit is that the anode load must be inductive, that is to say, I_{L0} must be larger than I_{C0}, so that the resultant I_0 lags the anode voltage V_{gs} by nearly 90°.

If any readers are grieved because I have spent most of the time introducing a new-fangled type of vector diagram instead of explaining at length the more orthodox kind I used in "Miller Effect"* I am sorry, but I really think it is an improvement. However, if you don't like it, you can fix your earthed point every time, and draw the arrows pointing away from it, as in Fig. 1(c), and attach the current vector there, and label the vectors with any notation you like, so long as it avoids the ambiguities I pointed out.

It may be as well to mention, as a postscript, that the imitation valve used here is only one of two kinds—the more commonly used one, known as the equivalent voltage generator. The other, which gives the same answer rather more easily in parallel anode circuits fed from high resistance valves like pentodes, is a constant current generator $-g_m V_g$, with r_a in parallel.

*August, 1949, p. 307.

SHORT-WAVE CONDITIONS

January in Retrospect : Forecast for March

By T. W. BENNINGTON (*Engineering Division, B.B.C.*)

DURING January the average daytime maximum usable frequency for these latitudes was somewhat higher, and the night-time m.u.f. about the same, as during the previous month. Not much seasonal change in m.u.fs would have been expected as between December and January, and the higher daytime m.u.f. during the latter month may have been due to a decreased amount of ionospheric storminess.

Day and night working frequencies conformed more nearly to expectations than they have of late, in fact, they seemed to fit the curves given in the December *Wireless World* very well. Early and late in the month there was some transatlantic communication on 28 Mc/s, but during most of it the highest daytime m.u.f. was below this—in the vicinity of 22-25 Mc/s. Night-time m.u.fs were generally low, being usually below 8 Mc/s after about 2200 g.m.t., though towards the end of the month higher frequencies did remain usable later than this.

Very little Sporadic E was observed during the month On the 30th, however, this phenomenon was noticeably present. Sunspot activity was, on the average, slightly lower than during the previous month.

Conditions were relatively undisturbed during January, the 13th-14th and the 22nd-25th being the only really disturbed periods. A very minor storm occurred during the period 17th-19th. One Dellinger fade-out, severe in its intensity, took place at 1627 g.m.t. on January 22nd.

Forecast.—During March, it is expected, there will be a decrease in the daytime m.u.fs for these latitudes, whilst the night-time m.u.fs will continue to increase.

The net effect of the ionospheric variations on long-distance working frequencies should be that those for east-west circuits should decrease slightly during the daytime, whilst those for north-south circuits should show an increase. Frequencies as high as 28 Mc/s should become frequently usable over the latter path but not over the former. Moderately high frequencies should be usable for a considerably greater part of the day than during February over all circuits, and night-time working frequencies should be generally higher, those up to 9 Mc/s remaining of use for the greater part of the night over many circuits.

There is unlikely to be much Sporadic E capable of sustaining propagation on very high frequencies. Over medium distances the normal E layer may control transmission for a short daily period only. There is often an increase in the amount of ionospheric storminess around the equinoxes, so some periods of severe disturbance are likely during March.

The curves indicate the highest frequencies likely to be usable over four long-distance circuits from this country during the month.

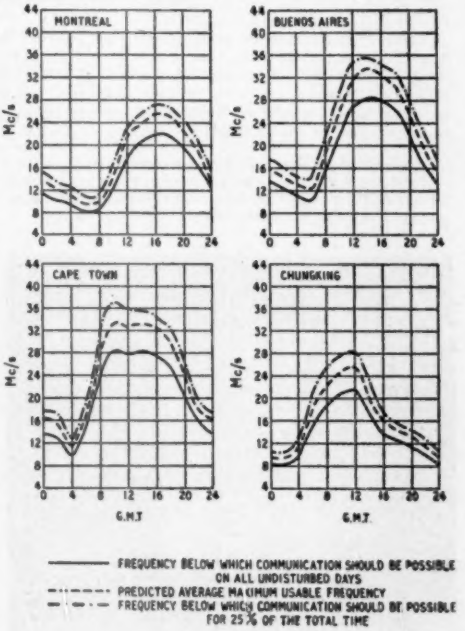
MONTREAL
BUENOS AIRES
CAPE TOWN
CHUNGKING
Mc/s
G.M.T.
FREQUENCY BELOW WHICH COMMUNICATION SHOULD BE POSSIBLE ON ALL UNDISTURBED DAYS
PREDICTED AVERAGE MAXIMUM USABLE FREQUENCY
FREQUENCY BELOW WHICH COMMUNICATION SHOULD BE POSSIBLE FOR 25 % OF THE TOTAL TIME

Transatlantic Tests

Memorial to the First Amateur Station to Span the Atlantic on "Short Waves"

WHEN the term "short-wave" was used thirty years ago to describe the transatlantic tests organized between amateurs in the U.S. and the U.K. it conjured up in readers' minds wavelengths no shorter than 200 metres.

Whereas at the end of the first world war long-range overseas radio communication was conducted on wavelengths of thousands of metres, to-day, of course, the same, and greater, distances are covered on wavelengths of less than 40 metres. What was probably the first step in the change from long to short waves for long-distance communication was the series of transatlantic tests between British and American amateurs conducted in 1921 under the auspices of this journal and the American Radio Relay League. It was in February of that year—just thirty years ago—that arrangements were made for a number of amateur stations to radiate morse transmissions in an endeavour to establish transatlantic communication using no greater power than that permitted by the licensing authority in each country. In the U.K. it was 10 watts, whereas in the U.S. 1 kW was permitted. It was for this reason that it was decided the American amateurs should transmit and the British endeavour to receive the signals.

Twenty-five amateur stations in the States and some 250 amateurs in this country participated. Although thirty or more logs were received by *Wireless World*, not one entrant received a single word or signal which could unquestionably be attributed to an American amateur station.

Three of the original operators of station 1BCG, including Major Armstrong (left), and Paul Godley (second from right) who operated the receiving gear in Scotland, were present at the dedication of the memorial.

Commenting on the results in *Wireless World* of 5th March, 1921, we wrote "The two main difficulties with which the entrants had to contend, apart from the weakness of the signals, were (1) harmonics from high-power stations on long wavelengths . . . and (2) jamming from other entrants, who in spite of urgent requests, and contrary to the conditions of their licences, persisted in using self-heterodyne receivers, which radiated and completely spoilt the reception for any other amateurs in the vicinity."

This disappointing result did not act as a deterrent from further effort and arrangements were made for another attempt in December of the same year. So great was the enthusiasm shown by American amateurs that the A.R.R.L. invited one of its members—Paul F. Godley—to set up a receiving station in this country "to supplement the efforts of the British amateurs."

Early in December 1921 the tests opened with transmissions from 27 American amateurs on wavelengths between 200 and 375 metres, some using spark and some c.w.

Of the large number of British amateurs who entered for the test, eight were successful in logging signals from the U.S.—all c.w. The American representative, who established his receiving station at Ardrossan, Scotland, was the most successful, however, logging all the stations. When commenting on this we wrote that it was "perhaps by reason of the fact that the authorities did not restrict him in the matter of aerials and location" that Paul Godley achieved such success. Godley's "Beverage" antenna exceeded the length then allowed to British amateurs.

To commemorate the station 1BCG which sent "the first message ever to span the Atlantic on short waves" a granite memorial has been erected at Greenwich, Conn., near the site of the original station which was built and operated by members of the Radio Club of America. At the dedicatory ceremony the operators of the station on that historic occasion were presented with medallions. Among the recipients were Major Edwin Armstrong—who, incidentally, contributed a letter on the a.m./f.m. controversy in the February issue—and Paul Godley, who operated the receiving station in Scotland.

To mark the thirtieth anniversary of these tests the Radio Club of America has issued a commemorative copy of its *Proceedings* with the title "The Story of the First Trans-Atlantic Short Wave Message" which is obtainable from the headquarters of the Club, 11, West 42nd Street, New York, 18, N.Y., price one dollar. It includes a description of the transmitting and receiving stations and reprints of the articles in *QST* of February 1922, giving Paul Godley's report.

THE "BELLING-LEE" PAGE

Providing technical information, service and advice in relation to our products and the suppression of electrical interference

Conversion Kits Holme Moss (Channel 2)

We have decided that conversion kits to convert Sutton Coldfield to Holme Moss Installations need only be limited to quite a small range, i.e., five individual kits. Fig. 1 illustrates the range which we will have available. These will be kept at as low prices as are economically possible, and prices will be announced later, but we wish to emphasise that conversions will be available for a period of 3 months only, i.e., from a date one month prior to the opening of the new station, to a date 2 months following the opening.

This period, in our view, offers sufficient opportunity for decisions to be taken, orders placed and delivery effected. It will help us also, in avoiding undesirable interruption of our normal production.

The need for conversion kits should be confined to the area north of a line through the following towns (west to east), Caernarvon, Wrexham, Stoke-on-Trent, Newark and Skegness. Experience may show that the nature of the ground favours reception from one station more than the other from either side of this line, or that the signal strength from Sutton Coldfield, at any given point, is sufficient to make a changeover of set or aerial of no practical value.

Again, in framing our policy, we have borne in mind that :

(a) In many cases, it will be less expensive to install a new inexpensive aerial in a different position.

(b) The end cost of the changeover should be kept as low as possible by the **avoidance of changed cable runs.**

(c) The converted installation should have a new lease of life and be virtually as good as new.

To avoid confusion with our accepted list numbers, the above and subsequent conversion kits for new stations will be identified by the channel number (Holme Moss—Channel 2) and a letter suffix, i.e., A, B, C, D, E.—thus 2/A, 2/B, etc.

NOTE :— For "Multirod" conversions to simple dipole or "H" a piece of L.688 semi-air-spaced coaxial cable with "Belling - Lee" plug L.734/P should be used to replace the ¼-wave transformer.

EXISTING AERIAL	CONVERSION REQUIREMENT			
Sutton Coldfield Channel 4	For simple Dipole	For 1/7 wave "H"	For ¼-wave "H"	For "Multirod"
½λ L802/4/C-/L or -/W	KIT 2/A Description below	KIT 2/C Description below	NIL	NIL
½λ L801/4/C - L-/9 or -/12	KIT 2/A ½" Dipole Elements Insulator, Screws & Plug for crossarm	KIT 2/C ½" Elements 1/7 wave crossarm Insulator and Screws	KIT 2/D ½" Elements and ¼ - wave crossarm, Insulator and Screws	NIL
Multirod L.800/4/14 L.800/4/C-	KIT 2/B As above, but with stand-off arm	KIT 2/C Description above	KIT 2/D Description above	KIT 2/E Complete Multirod top

FIG. 1

New Coaxial Plug

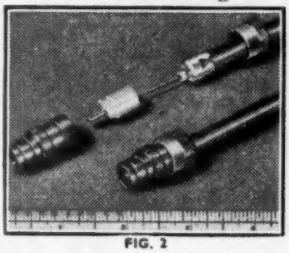

FIG. 2

Our new coaxial plug L734/P, as illustrated Fig. 2, will supersede L642/P, other than for government requirements. The list price of both plugs will be 1/6 each, due to price increases in raw materials.

The new plug will be completely interchangeable with L642/P and more adaptable, in that it accepts coaxial cables of outside diameter from semi-air-spaced 5/16in. to 5/32in. solid, thus also replacing plugs L632 and L727.

Suppression on board ship

The following is an extract from a letter we recently received from a ship's chief officer :

"I have just given your L300/3 suppressor a 3 months' trial whilst on a West African voyage, and have had excellent results with it."

He then goes on to say, "The best results were obtained with long and medium wave stations, which before fitting your suppressor were lost in interference at 2,000 miles. I have now heard these stations without any interference at 3,500 miles, and it is now possible to receive the Light programme on long wave on the West African coast, providing there are no electrical storms about."

In our reply we stated that the L300/3 suppressor was primarily designed for use on receivers operated on a 200-250 volts supply. In this particular case, as the supply would be 110 volts, the current consumption would be higher than that normally used at home.

We mentioned that we have designed a special suppressor for ship board use, L305, which is rated at 2 amperes, this being effective over the medium and short wavebands only. However, the L300/3 is provided with fuses and if these remain intact, there should be no difficulty in this direction.

BELLING & LEE LTD
CAMBRIDGE ARTERIAL RD. ENFIELD. MIDDX. ENGLAND

AMAZING

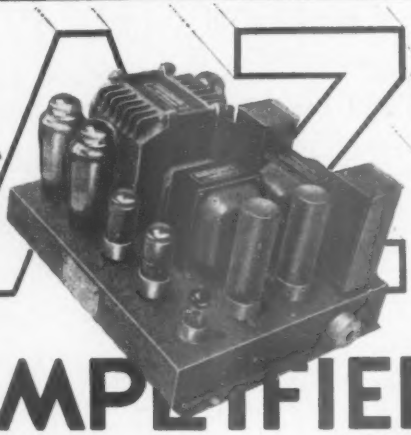

AMPLIFIER

TYPE A-Z

0.18% DISTORTION INCLUDING REMOTE TONE CONTROL STAGE AT 12 WATTS.
AN EXCLUSIVE PERFORMANCE CERTIFIED BY THE NATIONAL PHYSICAL LABORATORY.

Price: £30-0-0 complete

Works : WEST ST., FARNHAM, SURREY
FARNHAM 6461-2-3

Sound Sales Ltd.
Manufacturers of Electronic Products
LLOYDS BANK CHAMBERS
125 OXFORD ST., LONDON, W.1
GERrard 8782

ROLA

One in Ten million!

For efficiency and fidelity each Rola speaker is indeed "one in a million" but in a more literal sense, every Rola you receive is one in ten million speakers which are proving the superiority of Rola performance throughout the world. So let figures speak for themselves and specify Rola.

Manufacturers Enquiries to:—
BRITISH ROLA
FERRY WORKS, SUMMER ROAD, THAMES DITTON, SURREY (*Emberbrook 3402-6*)

Wholesale Enquiries to—**SOLE DISTRIBUTORS**

LONDON & NORTH:—
CYRIL FRENCH LTD.,
HIGH ST., HAMPTON WICK, MIDDX. (*Kin. 2240*)

SOUTH:—
ROBSHAW BROS.,
10, EXETER RD., THE SQUARE, BOURNEMOUTH. (*Tel.: 5896-7*)

ROLA *The Speaker You Know by Ear*

WORLD OF WIRELESS

Festival Radio Convention ◆ T. L. Eckersley Honoured ◆ G3FB, Festival Station ◆ R.E.C.M.F. Show ◆ Television Servicing

Brit. I.R.E. Convention

DURING the Festival of Britain the British Institution of Radio Engineers plans to hold a Convention, the various sessions of which will be held in different centres.

The first session, covering electronic instrumentation in nucleonics, will be held on July 3rd and 4th at University College, London. Eight papers, including that of the chairman, Dr. Denis Taylor (Atomic Energy Research Establishment, Harwell), dealing with the applications of radioactivity in industry and the techniques employed in the associated electronic apparatus will be given.

"Valve Technology and Manufacture" is the title of the second session to be held on July 5th and 6th and of which J. W. Ridgeway (Ediswan) will be chairman. This session will also be held at University College, London.

University College, Southampton, is the venue for the third and fourth sessions, "Radiocommunication and Broadcasting" and "Radio Aids to Navigation," respectively. Paul Adorian (Brit. I.R.E. President) is chairman of the third which will be held on July 24th and 25th and F. S. Barton (Telecommunications Research and Development Establishment, M.o.S.) chairman of the fourth, to be held on July 26th and 27th.

The fifth session, on "Television Engineering," of which L. H. Bedford (Marconi's) is chairman, is to be held at King's College, Cambridge, from August 21st to 24th.

H. J. Leak will be in the chair at the last session which will deal with "Audio-frequency Engineering" and will be held from September 11th to 13th. The venue has not been decided, but it is hoped to be near Earls Court, London, where the National Radio Exhibition will be in progress.

The first day of each session is planned to open at 3.0, and subsequent days at 11.30. Each day's proceedings are scheduled to terminate at 7.0.

Dutch Television

DETAILS of the standards to be employed for the Dutch television service, which supplement those published recently in "Random Radiations," have been sent by a correspondent and are given below.

The first transmitter is to be erected at Lopik-Ijsselstein, near Utrecht, and the frequencies to be employed are 62.25 Mc/s vision, and 67.75 Mc/s sound. At present experimental transmissions are radiated from the Philips (Eindhoven) station on 48.25 Mc/s vision, and 53.75 Mc/s sound.

The Dutch standards are: 625 lines, picture frequency 25 per second (interlaced), picture ratio 3:4, negative picture modulation, single sideband, 5-Mc/s picture channel, f.m. sound (frequency deviation 50 kc/s), horizontal aerial polarization and total bandwidth 7 Mc/s.

Our correspondent adds that the sound transmitter at Lopik will probably be used outside programme hours for f.m. test transmissions.

Faraday Medallist

THE twenty-ninth award of the Faraday Medal has been made by the Institution of Electrical Engineers to T. L. Eckersley, B.A., B.Sc., Ph.D., F.R.S., for "his achievements in the field of radio research and, in particular, for his outstanding contributions to the theory and practice of radio-wave propagation."

Dr. Eckersley, who is senior research engineer of Marconi's W.T. Co., joined the National Physical Laboratory in 1910 at the age of 24, and after war service in the Royal Engineers joined Marconi's in 1919 where his work has been chiefly concerned with the study of radio-wave propagation. When in 1946 he was awarded a Fellowship of the American Institute of Radio Engineers it was stated that both his approach to the problem of propagation from the standpoint of practical communications and his invention of mathematical tools for the computation of radiated fields are "achievements of lasting value . . . and form a monument of which he may be justly proud."

T. L. ECKERSLEY, F.R.S.

The Faraday medal is awarded by the I.E.E., not more than once a year, for notable scientific service or industrial achievement in electrical engineering or for conspicuous service rendered to the advancement of electrical science.

R.I.C. Change

UNDER the new constitution of the Radio Industry Council an executive committee, consisting of two members from each of the four constituent associations (B. R. E. M. A., R. C. E. E. A., R.E.C.M.F. and B.R.V.M.A.), is appointed. This year's committee, which will meet monthly to conduct all the ordinary business of the R.I.C., consists of:—P. D. Canning (Plessey), G. Darnley Smith (Bush), M. M. MacQueen (G.E.C.), G. A. Marriott (G.E.C.), F. S. Mockford (Marconi's), L. H. J. Phillips (Metrovick), W. F. Randall (Telcon), and J. W. Ridgeway (Ediswan).

The new Council of the R.I.C. consists of sixteen members—four from each constituent association—and nominations are for one year only. At the first meeting of the Council J. W. Ridgeway, O.B.E., was elected chairman, and G. Darnley Smith, vice-chairman.

Festival Amateur Station

AS already announced (December 1950, issue) an amateur transmitting station is to form part of the Land Travel Exhibition which is being organized in conjunction with the Festival of Britain. This station, which will be set up for about three weeks in each of the following cities, Manchester, Leeds, Birmingham and Nottingham, and operated by local amateurs, has been allocated the call sign G3FB.

An amateur in each of the centres to be visited will be responsible for maintaining a rota of operators, and Class B licence holders who are interested to help are invited to get in touch with the responsible amateur. The dates of operation and the responsible amateurs are: Manchester, May 4th-26th, I. D. Auchterlonie (G6OM), 4, Stand Close, Ringley Road, Whitefield, Manchester; Leeds, June 23rd-July 14th, C. A. Sharp (G6KU), 56, Moore

Avenue, Wibsey, Bradford; Birmingham, August 4th-25th, organizer not yet announced; Nottingham, September 15th-October 6th, J. J. Curnow (G6CW), "The Yews," Mapperley Plains, Nottingham.

Components Show

THE eighth annual exhibition of components, valves, materials and test gear to be organized by the Radio and Electronic Component Manufacturers' Federation will be held at Grosvenor House, Park Lane, W.1, from April 10th-12th. It will open each day at 10.0 and close at 6.0 on the first two days and 5.0 on the last.

The space available for the exhibition is more than in previous years, so that there will be greater ease of access to the 101 stands.

This is not a public exhibition and admission is limited to ticket holders. Readers who have a professional, industrial or trade interest in components should apply for tickets to the R.E.C.M.F., 22, Surrey Street, London, W.C.2.

Television Servicing

CANDIDATES living outside the service area of a television station may now sit for the theoretical section of the R.T.E.B. examination for the Television Servicing Certificate providing they undertake to sit for the practical examination within twelve months of the opening of a station in their area.

The next examination will be held in May. Particulars are obtainable from the Radio Trades Examination Board, 9, Bedford Square, London, W.C.1.

Candidates will not receive the certificate until the practical examination has been passed.

Airmet

A CORRESPONDENT in *The Aeroplane* (January 19th) suggests that even if the present wavelength *impasse* was solved, say by the use of a frequency of the order of 7 Mc/s, for the re-introduction of the Airmet weather service, the authority responsible—whoever that may be—may consider that the cost of the service for 21,400 (the number of petitioners) is not justified.

He estimates that as the information is already available at the Central Forecasting Office, Dunstable, the cost of transmission could be kept down to £7,000-£8,000 a year. He suggests that every wireless licence holder should be made to contribute consciously to the return of a first-class weather broadcasting service by charging an additional penny for each future wireless licence (a penny stamp to be fixed and cancelled by the P.O. date stamp at issue). "Twelve million pence is £50,000, which would give us the world's finest possible weather service continuously, all round the clock on short wavelengths suited to the incidence of light and darkness," he adds.

Wenvoe Television Station

THE negotiations for the site on St. Lythan's Downs, near Wenvoe, Glamorgan, about five miles from Cardiff, for the fifth B.B.C. high-power television station have now been completed. The station, to be known as the Wenvoe transmitter, will be on a site 400ft above sea level and will have a 750-ft mast—to be supplied by B.I. Callender's Construction Co.—similar to that at Sutton Coldfield. A feature of the 50-kW E.M.I. vision transmitter is that the carrier wave will be modulated by the vision signal in a low-power stage instead of in the output stage as has been customary in previous installations.

The 12-kW sound transmitter is to be supplied by Standard Telephones and Cables.

The anticipated service area—calculated from tests using a 1-kW transmitter with the aerial suspended from a balloon flown at 600ft above ground—was given on the map published in our last issue.

PERSONALITIES

J. W. Ridgeway, O.B.E., who, as already mentioned, has been elected chairman of the reconstituted Radio Industry Council, is director and manager of the Radio Division of the

J. W. RIDGEWAY, O.B.E.

Edison Swan Electric Co. He was also recently elected for the seventh term of office as chairman of the British Radio Valve Manufacturers' Association.

D. W. Heightman, who recently resigned from the Board of Denco (Clacton), Ltd., of which he was the founder in 1938, has joined the English Electric Co. as chief television engineer at the Liverpool Works.

L. H. J. Phillips, who, as stated elsewhere, is the new chairman of R.C.E.E.A., is manager of the radio sales department of Metropolitan-Vickers. During the 1939-45 war he left the Metrovick research section to become head of the radio department of the Royal Aircraft Establishment, Farnborough. He became Deputy Director of Communications Development in the Ministry of Aircraft Production and returned to Metrovick in 1945.

L. H. J. PHILLIPS

A. H. Ginman has relinquished the presidency of the Canadian Marconi Company and is succeeded by S. M. Finlayson. After serving with Marconi's in this country, Mr. Ginman went to America as an operator and in 1911 became manager of Marconi's W.T. Co. of America. He held various administrative posts in overseas telecommunication organizations and for some time prior to going to Canada in 1935 was general manager of the parent company.

IN BRIEF

Licences.—The number of television licences more than doubled during 1950. The increase during the year was 346,400 bringing the total to 586,100. The total number of sound and vision licences current at the end of December was 12,295,000, an increase of 113,700 during the year but a decrease of 36,900 on the November figure.

Rugby Jubilee.—To celebrate the twenty-fifth anniversary of the opening of the G.P.O. Rugby station, which was brought into service on January 1st, 1926, a dinner was held in the town on January 11th. Among the 100 or more present was H. Faulkner, the first Rugby engineer-in-charge, who is now deputy engineer-in-chief G.P.O.

Amateur Television.—It is learned from the European Broadcasting Union that the Netherlands Government has allocated the 146-148-Mc/s and 420-460-Mc/s bands to amateurs for the transmission of television.

Ultrasonics.—A course of four lectures on ultrasonics is to be given by L. I. Farren, M.B.E., Whit. Schol., M.I.E.E., of the G.E.C. Research Laboratories, at the Polytechnic, Regent Street, London, W.1, at 6.30 p.m. on Fridays, March 2nd, 9th, 16th and 30th. The lectures, each of which will last about one and a half hours and will be followed by a discussion, will cover, respectively, fundamentals, generation of ultrasonic waves, reception of ultrasonic waves and the applications of ultrasonics. Enrolment forms for the course, for which the fee is ten shillings, are obtainable from the Head of the Electrical Engineering Department at the Polytechnic.

Reunion Dinner of the Royal Engineers, Wireless Signals (1914-1919) Association, which is being resumed after a lapse of some years, will be held at the White Horse Hotel, Congreve Street, Birmingham, on April 7th. Further particulars are obtainable from C. R. Johnson, 88, Fox Hollies Road, Acocks Green, Birmingham, 27.

Valve Manufacture.—The Minister of Supply, in reply to a question in the House, stated that he was unable to give an assurance that adequate supplies of non-ferrous metals will be available to meet all the commitments of the radio valve manufacturers.

Radar Reunion.—The fifth annual reunion of the Radar Association will take place at the Royal Empire Society Hall, Northumberland Avenue, London, W.C.2, on March 10th. Tickets, price 8s 6d, and further particulars are obtainable from the Radar Association, 83, Portland Place, London, W.1.

Television Cameras with a full-range test pattern engraved on the face of the pick-up tube are now being produced by Marconi's and eight are to be supplied to the B.B.C. These monoscope cameras will facilitate the checking of transmissions from mobile stations without taking an ordinary camera out of service. It will also ensure constancy of test transmissions. The output of the cameras is of standard form with blanking but without sync signals.

"Explaining Television."—To assist prospective purchasers of television receivers by answering such questions as "Do I need an aerial? ", "What size tube? ", "What is television going to cost? " etc., the Radio & Television Retailers' Association has prepared a booklet for distribution by R.T.R.A. dealers. "Explaining Television," as it is called, includes field-strength maps of both the Alexandra Palace and Sutton Coldfield transmitters.

B.S.R.A. Diary.—Data on disc, film and tape recording and reproducing, standard and microgroove records and on the majority of pick-ups are given in the sixteen pages of information included in the 1951 edition of the B.S.R.A. Diary which is obtainable from H. M. Blaber, 0, Stanton Road, West Wimbledon, S.W.20, price 4s 3d, including postage.

Appointments Bureau. — J. Muil, A.M.I.E.E., who has been for the last five years with the Technical and Scientific Register of the Ministry of Labour, has been appointed Registrar and Secretary of the Professional Engineers' Appointments Bureau, 9, Victoria Street, Westminster, S.W.1.

Gratis.—A.A. Electrical Co., Ltd., inform us that they are supplying and fitting interference suppressors free of charge to customers' cars and vans at their Chiswick Works, 67, Rothschild Road, London, W.4.

"Radio World Digest" is the title of a new quarterly magazine published by the Eurap Publishing Co. which also issues the weekly *European Radio* giving details of foreign programmes. *Radio World Digest* gives general information on world broadcasting and schedules of regular transmissions in English from overseas stations. It costs one shilling.

S.R.E.—It is claimed that the installation of sound reinforcing equipment in the Banqueting Hall of the Glasgow Municipal Buildings by Philips Electrical has made it possible for the first time in 62 years for a full audience of 800 to hear clearly all that is said from the platform. The installation includes twenty-one 8-in reproducers, each of which is fitted with a deflector panel to prevent the sound rising to the roof of the building.

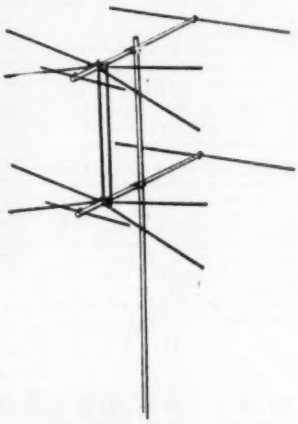

AMERICAN television aerial. This broad-band array with director and reflector covers all frequencies at present used by U.S. television stations (54-216 Mc/s). It is produced by the Walter L. Schott Co., Beverley Hills, Calif.

Malaya.—The Director of the Department of Broadcasting in the Federation of Malaya has urged importers to maintain a good supply of sets in 1951 so that the Government's efforts to keep the Malayan public properly informed may be effective.

"Square-Wave Generators."—In this article (p. 35, our January issue) the last part of the inscription to Fig. 2 should read "at (b) is the waveform at 8 kc/s"—not 80 kc/s.

INDUSTRIAL NEWS

R.C.E.E.A. Council.—At the annual general meeting of the Radio Communication & Electronic Engineering Association—one of the constituent bodies of the Radio Industry Council—the following member firms (with, in parentheses, the representative) were re-elected:—B.T.H. (V. M. Roberts), E.M.I. (J. S. Carr), G.E.C. (M. M. MacQueen), Kelvin & Hughes (C. G. White), Marconi's (F. S. Mockford), Metrovick (L. H. J. Phillips), Mullard (T. E. Goldup), Murphy (K. S. Davies), Plessey (P. D. Canning), Pye (C. O. Stanley), Rediffon (B. St. J. Sadler) and S.T.C. (L. T. Hinton). The new chairman is L. H. J. Phillips and K. S. Davies is vice-chairman.

Denco advise us that the manufacturing and sales rights of the DCR19 communications receiver and the associated equipment (all-wave coil turret (CT4), i.f. transformer (IFT9) and 1.6-Mc/s crystal filter unit) have been transferred to the recently formed Heightman Company of 25, Coppins Road, Clacton-on-Sea. Denco will continue the production of their other radio and television components.

A Decimal Point was omitted from the percentage of regulation given for the Furzehill stabilized power supply units on p. 24 of the advertisements in our January issue. The figure should have been 0.5%.

Murphy announce that they have received an unsolicited order for a substantial quantity of broadcast receivers from a New Orleans importer.

Radio Buoys & Beacons, Ltd., is the name given to the recently formed electronics division of Venner Time Switches, Ltd., New Malden, Surrey.

T.C.C. reports that although 1949 was a good year for export sales, the 1950 figure exceeded it by 61%.

MEETINGS

Institution of Electrical Engineers

Radio Section.—"London-Birmingham Television Radio-Relay Link," by R. J. Clayton, M.A., D. C. Epsley, O.B.E., D.Eng., G. W. S. Griffiths and J. M. C. Pinkham, M.A., on March 1st.

"Design Considerations for a Radiotelegraph Receiving System," by J. D. Holland, on March 7th.

"The Testing of Fine Wires for Telecommunication Apparatus," by R. C. Woods and J. K. Martin, and "The Use of an Electrostatic Wattmeter for Magnetic-Loss Measurements," by J. Choudbury, M.Sc.Tech., and Arvon Glynne, M.A., on March 13th.

Informal Lecture on "Radio Astronomy," by A. C. B. Lovell, Ph.D., on March 19th.

Education Circle.—Discussion on "The Best Means of Explaining the Internal Operation of Electronic Valves," opener A. F. H. Thompson, M.A., at 6.0 on March 5th.

The above meetings will be held at 5.30 (unless otherwise stated) at the I.E.E., Savoy Place, W.C.2.

Cambridge Radio Group.—Discussion on "Is there an Optimum Speed for a Gramophone Record ?" opener G. F. Dutton, Ph.D., B.Sc.(Eng.), at 8.15, on March 6th, at the Cavendish Laboratory, Cambridge.

North-Eastern Radio Group.—Informal Lecture on "The Nervous System as a Communication Network," by J. A. V. Bates, M.A., M.B., B.Chir., on March 5th.

Informal Lecture on "The Acoustics of Studios and Auditoria," by W. Allen, on March 19th.

Both meetings of the North Eastern Radio Group will be held at 6.15, at King's College, Newcastle-on-Tyne.

South Midland Radio Group.—Informal lecture on "The Magnetic Tape Recorder," by G. F. Dutton, Ph.D., B.Sc.(Eng.), at 6.0, on March 19th, at the Imperial Hotel, Birmingham.

Southern Centre.—"The Radar-Sonde System for the Measurement of Upper Wind and Air Data," by F. E. Jones, M.B.E., B.Sc., Ph.D., J. E. N. Hooper, B.Sc., and N. L. Alder, B.Sc., at 7.30, on March 21st, at the R.A.E. Technical College, Farnborough.

Oxford District.—"The Use of the Synchrotron and other Particle

Accelerators in Atomic Research," by C. H. Collie, M.A., B.Sc., at 7.0, on March 14th, at the Electricity Showrooms, Southern Electricity Board, 37, George Street, Oxford.

London Students' Section.—Visit to E.M.I. Studios, Abbey Road, London, N.W.8, at 10.30 a.m., on March 10th.

British Institution of Radio Engineers

London Section.—"Nuclear Scintillation Counters" by J. B. Birks, B.A., Ph.D., at 6.30 on March 29th at the London School of Hygiene and Tropical Medicine, Keppel Street, London, W.C.1.

North Western Section.—"A Survey of Television Development and its Problems" by H. J. Barton-Chapple, B.Sc., at 7.15 on March 1st at the College of Technology, Manchester.

Merseyside Section.—"The Use of Foster's Theorem in Circuit Design" by E. Williams, Ph.D., at 7.0 on March 1st at the Electricity Service Centre, Whitechapel, Liverpool.

Scottish Section.—"High-Fidelity Sound Reproduction" by D. T. N. Williamson at 7.0 on March 6th at the Natural Philosophy Department, The University, Glasgow, and at 7.0 on March 7th at the Natural Philosophy Department, The University, Drummond Street, Edinburgh. Both are joint meetings with the Institute of Physics, Scottish Branch.

"Magnetic Amplifiers" by H. M. Gale, B.Sc., at 7.0 on March 22nd at the Institution of Engineers and Shipbuilders, Glasgow.

South Midlands Section.—"A Transmitter for an Experimental Eight-Channel Carrier Wire-Broadcasting System" by R. G. Kitchenn, B.Sc., at 7.15 on March 14th at the Exhibition Gallery, Public Library, Rugby.

North-Eastern Section.—"Acoustics" by E. G. Richardson, B.A., Ph.D., B.Sc., at 6.0 on March 14th at Neville Hall, Westgate Road, Newcastle.

West Midlands Section.—"Engineering Aspects of Industrial Electronic Equipment" by R. J. F. Howard at 7.0 on March 28th at the Wolverhampton and Staffordshire Technical College, Wolverhampton.

British Sound Recording Association

Discussion on the measurement and use of standard frequency discs for the calibration of gramophone pickups; opener H. Davies, M.Eng., M.I.E.E., at 7.0 on March 16th at the Royal Society of Arts, John Adam Street, London, W.C.2. The paper by R. W. Lowden on "The Design of a Long-Duration Recording and Reproducing Equipment" has been postponed.

Television Society

Leicester Centre.—"Design of a Combined Radio and Television Receiver," by Alan Bamford, B.Sc. (Ultra, Ltd.), at 7.0, on March 14th, at the Leicester College of Technology, The Newarkes, Leicester.

Junior Institution of Engineers

North-Western Section.—"Marine Radar," by T. R. Goode, B.Eng., at 7.0, on March 5th, at the Manchester Geographical Society, 16, St. Mary's Parsonage, Manchester.

Midland Section.—Lecture on the latest developments in television by J. C. Gilbert at 7.0 on March 14th at the Central Technical College, Suffolk Street, Birmingham.

Institution of Electronics

Midlands Branch.—"Radioactive Tracers: Their Uses in Research and Industry, with particular reference to their potentialities for Industrial Control," by I. S. Hallow, B.A. (Tracer Processes, Ltd.), at 7.0, on March 6th, at the Warwick Room, Imperial Hotel, Temple Street, Birmingham, 2.

Southern Branch.—"A Physicist Looks at Biology" by Dr. W. Summer, A.Inst.P., at 6.30 on March 16th at Southampton University College.

B.B.C. STATIONS

Location, Programmes and Present Power

IN view of the difficulties experienced at present in many areas in receiving satisfactorily the B.B.C. medium- and long-wave transmissions, it has been considered desirable to publish an up-to-date list of British stations to assist readers in making the most advantageous choice of station for the reception of a given programme. The appended list, which gives the actual power used and the maximum power permitted under the Copenhagen Plan, was supplied by the B.B.C.

It is pointed out that there are various reasons why stations are not using the maximum permitted power; for instance where several stations are synchronized on the same frequency the best coverage for the whole group may be obtained with some of them working at a lower power than that permitted.

The power given for Daventry (Third Programme) is that to be used by the new transmitter now under construction.

Frequency (kc/s)	Station	Programme	Power (kW)	Permitted Power
200	Droitwich	Light	400	400
647	Daventry	Third	150	150*
	Edinburgh	"	2	—
	Glasgow	"	2	—
	Newcastle	"	2	—
	Redmoss	"	2	—
692	Moorside Edge	Home (North)	150	150
809	Burghead	Home (Scot.)	100	100
	Redmoss	"	5	20
	Westerglen	"	100	100
881	Penmon	Home (Welsh)	8	20
	Washford	"	100	150
	Wrexham	"	0.25	5
908	Brookmans Park	Home (London	140	150
1052	Start Point	Home (West)	120	150
1088	Droitwich	Home (Midland)	150	150
	Norwich	"	7.5	20
1151	Lisnagarvey	Home (N.Ireland)	100	100
	Londonderry	"	0.25	5
	Stagshaw	"	100	100
1214	Brookmans Park	Light	60	60
	Burghead	"	20	20

* Daventry is allowed 150 kW if the three 15-kW stations provided for in the Plan, also on 647 kc/s, are not used. Total power permitted on this frequency is 165 kW.

Frequency (kc/s)	Station	Programme	Power (kW)	Permitted Power
1214	Lisnagarvey	Light	10	10
	Londonderry	"	0.25	1
	Moorside Edge	"	58	58
	Newcastle	"	2	10†
	Plymouth	"	0.3	2
	Redmoss	"	2	2
	Redruth	"	2	2
	Westerglen	"	50	50
1295	Ottringham	European	150	150
1340	Crowborough	European	150	150
1457	Bartley	Home (West)	10	60
	Clevedon	"	20	60
1546	Belfast	Third	0.25	5
	Bournemouth	"	0.25	2
	Brighton	"	1	5
	Cardiff	"	1	2
	Dundee	"	0.25	2
	Exeter	"	0.1	2
	Fareham	"	1	5
	Hull	"	0.25	2
	Leeds	"	1	5
	Liverpool	"	1	5
	Manchester	"	1	2
	Plymouth	"	1	5
	Preston	"	1	2
	Redruth	"	1	2
	Sheffield	"	1	2
	Stockton	"	0.25	2

† Allocated to Stagshaw

Harbour-Control Radar

New Equipment Designed Specifically for the Purpose

Decca harbour radar display console.

IN many respects the requirements of harbour radar are more stringent than those of shipborne radar. Provided that the clarity and accuracy of the display are good at short ranges near the centre of the picture, the mariner will not be unduly critical of lack of definition or some obscurity of distant features by false returns from side lobes in the aerial characteristic. A harbour authority, on the other hand, must have a clear picture over a very wide area in order that a watch may be kept simultaneously on a large number of vessels, and the range discrimination must be of an exceptionally high order if accurate navigational instructions are to be given in narrow and congested waterways.

The new Decca radar, Type I, has been developed specifically for this purpose, and was demonstrated recently on a site overlooking Southampton Water. The results obtained indicate that a notable advance has been achieved. Range discrimination is of the order of 10 yards, as was clearly demonstrated when a motor yacht circled a navigation buoy at this distance. The critical factor determining range discrimination is pulse length and in the new Decca

(Left) "Half-cheese" aerial and dual r.f. units.

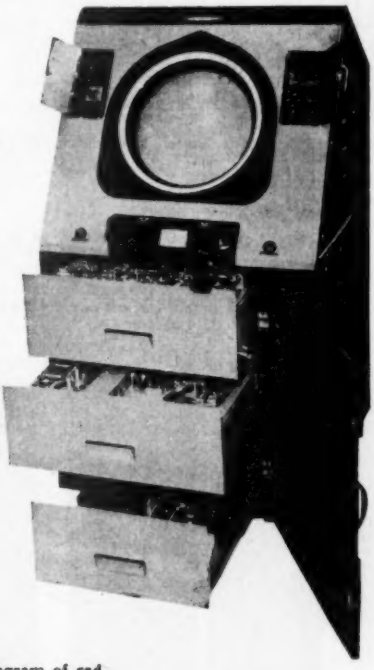

(Right) Display unit opened up for servicing. The top drawer contains the display circuits, the middle drawer the final receiving stages, and the bottom drawer, the power supplies with the exception of the e.h.t. unit.

(Below) Polar diagram of radiation from "half-cheese" aerial.

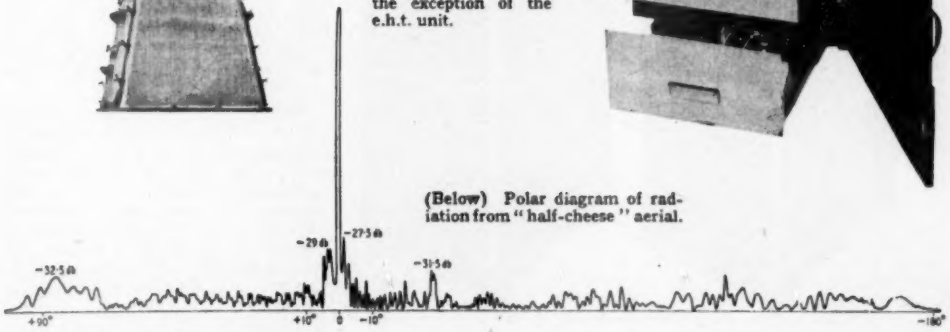

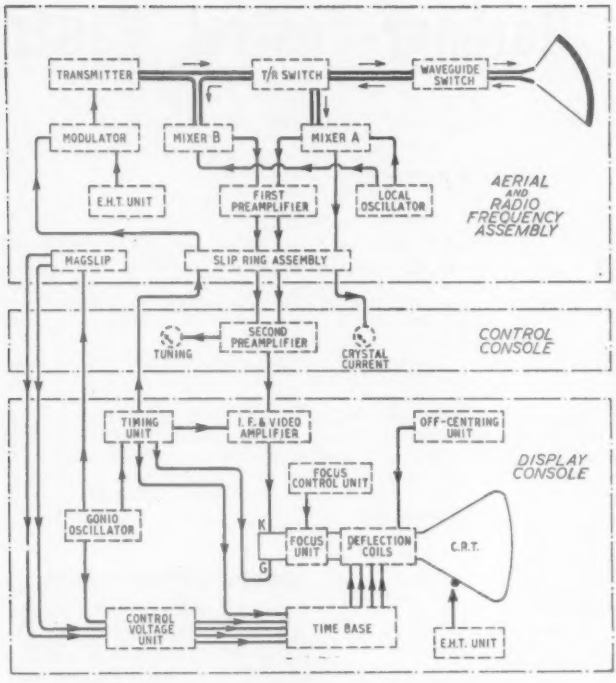

Block schematic diagram of the Decca Type I harbour radar equipment.

(Below) Control cabinet showing, in the top compartments, the twin power packs, and below, from left to right, the second pre-amplifiers on one vertical chassis, the monitor oscilloscope and the master control panel. The front cover panels hinge down to form tables for intruments and tools when chassis are drawn forward for servicing.

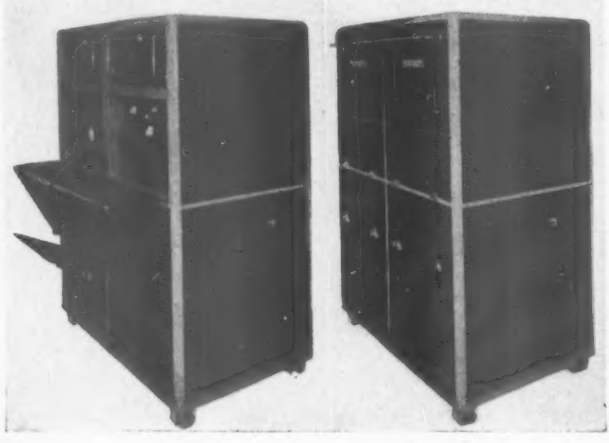

design this has been reduced to the exceptionally low duration time of 0.06 microsecond. This is half the pulse length used in the Decca shipborne radar, in which separate aerials are used for transmission and reception and the range discrimination and minimum range are both 20 yards. In a harbour radar, minimum range is of less importance than on board ship, and the designers have reverted to the normal practice of using a single aerial with a transmit-receive switch. The extinction time of the gas discharge in the switch governs the minimum range, which is about 26 yards in the Type I equipment.

Definition in the p.p.i. picture is a function of beam width, as well as pulse length, and a width of 0.7 degrees (at points 3db down in power) is achieved in the 9ft "half-cheese" reflector which has been adopted for the new design. As the name implies, this scanner is a half-segment of the conventional parabolic cheese reflector, fed from one corner instead of the centre of the aperture. Shadow effects caused by the feeder are reduced, and there is less interference with the main beam from the aerial. As a result, side lobes are reduced in amplitude by as much as 6db, and the picture brightness can be considerably increased without revealing spurious side-lobe returns.

A cathode-ray tube of 15in diameter is used in the display console, and on the lowest range (maximum of the order of 2½ miles) it is possible to distinguish between the point returns from navigation buoys and longer images from vessels; indeed, it is possible with this equipment to obtain a very good idea of the size of the vessel. A screen coating of moderate persistence is employed and the trail left by moving ships gives useful information on the course being steered. Bearings may be taken with the usual graticule and circumferential scale, while range is obtained with a continuously variable marker in association with an external calibrated dial. Three of these display consoles can be used up to a distance of 1,000 yards from the scanner.

Reliability of service is vital in a radar carrying the responsibility of shipping control in a large harbour, and to this end units are duplicated, including the main r.f. unit on the scanner, so that an immediate change-over to the standby units is possible in the event of failure. In most cases the switch-over is instantaneous, and the maximum delay is under half a minute.

In cases where the area under the harbour authority cannot be covered adequately by one scanner, several may be installed at strategic points and the radar information relayed to a central office by means of a centimetre-wave radio link. The bandwidth used will be the same as that of the video amplifiers in the main equipment and definition in the relayed displays will be in no way inferior to the original. It is claimed that coverage of a large area by a number of distributed scanners is capable of giving better local definition at points remote from the central control than the use of a single high-powered scanner. With standardization of the basic unit and a consequent lowering of production costs, it should be possible to meet widely divergent harbour requirements at an economical figure.

Hearing Aid Problems

IN a symposium on hearing aids on 10th January, arranged by the British Institution of Radio Engineers, E. R. Garnett Passe, F.R.C.S., gave an introductory paper on the clinical aspects of deafness and the possibilities of alleviation surgically, medically and by the use of hearing aids. After outlining the elementary physiology of the ear he explained the essential differences between conduction and nerve deafness, and indicated that although little could be done by medical treatment with drugs, promising results had been achieved by surgery.

Mr. Garnett Passe thought that the provision of tone control in hearing aids was important, but there was a limit to the useful compensation which could be employed for high-frequency loss in Corti nerve deafness. In cases where a transition from deafness to more or less normal hearing took place over a narrow volume range, some form of automatic volume control or peak limitation was essential and, if unavoidable, some sacrifice of quality must be tolerated to this end.

A master hearing aid designed at the Post Office Research Station for investigations into the relative merits of automatic level control and peak limitation, as well as the determination of optimum frequency response curves, was described in the second paper by E. Aspinall, B.Sc. This equipment is designed for articulation tests and normally makes use of standard test records. It is being modified for experiments with bone-conduction, as well as normal air-conduction receivers. The automatic level control can be set to start at different levels and the upper limit is maintained constant within $\pm 1\frac{1}{2}$ db over a range of inputs of 30 db. Operating (attack) and release (decay) time constants are variable over ranges of 10-100 msec and 0.25 to ·3 seconds respectively. The peak limiter has a range of 40 db in 2 db steps.

Finally, the construction of a typical commercial hearing aid was described in detail by J. P. Ashton, B.Sc. (Eng.), who paid tribute to the qualities of British sub-miniature valves and indicated the trend of future developments. Some slides were shown of recent American aids employing printed circuits with silkscreen printed carbon ink resistors and miniature bypass and coupling capacitors of high value making use of deposited electrodes on ceramic plates of dielectric constant 3,000 and thickness 0.005 in.

U.S. Colour Television

A Correspondent's Observations

BOTH the General Electric frequency-interlace system, described by A. Dinsdale in the December issue, and the R.C.A. dot-sequential system are very ingenious, but they, and the line-sequential system (developed by Color Television Inc.), suffer from a serious disability, in that three electron guns are essential in the receivers. A single-envelope tube with three guns presents (as R.C.A. admits) a very difficult production problem, and both this and the three-tube system involve grave optical registration difficulties, if colour fringing is to be avoided. Very small changes in the characteristics of the deflection system (such as during warm-up and because of ageing) might cause inaccurate registration or unequal size of the three primary-colour images, producing even more unpleasant psychological effects than those of bad colour printing. Surmounting this hurdle alone would make for a very costly receiver; in the three-tube system, the optical arrangements introduce further difficulties.

The main objection to the C.B.S. system, approved by the F.C.C., has been on the grounds of "compatibility" — a C.B.S. transmission cannot be received on an unmodified black-and-white receiver. On the other hand, this system is "convertible"—a black-and-white receiver with a converter can reproduce, in black-and-white, a C.B.S. colour transmission. Further, a colour disc may be added to the receiver with the converter, which will then present coloured pictures with the original c.r.t. The G.E., R.C.A. and to some extent the C.T.I. systems are compatible, but convertible only with great difficulty and expense—for example, the c.r.t. and associated circuits must be scrapped in favour of very expensive substitutes if colour pictures are to be received.

It therefore seems that the C.B.S. system is the most practical, and that the F.C.C.'s decision was wise. The colour disc may be clumsy, but it is cheap, simple and foolproof. The limitation on picture size could be resolved with projection technique (a small colour disc permits the conversion of those receivers with tubes larger than $12\frac{1}{2}$in dia.). The lack of high-speed electronic switches and filters, and the greater circuit simplicity generally are advantages that surely cannot be ignored. (Is receiver cost no object whatever?) Added to all this is the fact that of all the systems demonstrated, that of the C.B.S. has by far the best colour fidelity—"better in some ways than Technicolor," to quote *Time*.

It is true that the C.B.S. system (frame-sequential, 405 lines, 144 frames, 48 complete colour pictures per second) entails degradation from the American standard of 525 lines interlaced, 60 frames, to something a little poorer than the British, in order to keep within the bandwidth. It is also true that a system which gives equal values to red, blue and green images is not making the best possible use of the bandwidth (for instance, the eye requires very little red detail and good green detail). On the other hand, it seems pointless to use high colour-switching rate systems, which require the satisfaction of a number of very critical conditions and involve very costly receivers, when a relatively cheap and simple alternative is available.

C. F. K. G.

Testing Steep-slope Valves

Problem of Parasitic Oscillation

By J. C. FINLAY, A.M.I.E.E.

RECENT experiences with some of the new miniature valves suggest that special precautions are necessary when checking high-mutual-conductance triodes in the usual multi-valveholder type of tester.

For instance, a new ECC91 miniature double triode was checked for balance, having been plugged into a B7G base which had been fitted in a spare panel position on the valve tester. The two anode readings differed in a ratio of about three, which was clearly excessive for a new valve. However, two further valves gave a very similar result. Subsequent tests, confirmed by a c.r.o., showed that the "low" section was oscillating.

The effect would seem to be due to the multiple electrode leads in the usual valve-tester panels, which can give rise to considerable external anode-grid capacitance when testing triodes and thus encourage parasitic oscillation, particularly with modern high-mutual-conductance types. The tendency is probably accentuated by the transient effect of the a.c. energizing voltages normally used in valve testers.

The high-mutual-conductance requirement was confirmed by testing for hand-capacitance effect with several valve types. Oscillations were found with some 6SN7 double-triodes and the PX_4 power triode but not with the 6N7. Moreover, a "negative" reading of mutual conductance was obtained with the 6SN7. Among pentodes strapped as triodes the EF_{50}, KT61 and KT66 all oscillated but not the KT63; when tested as pentodes there was, of course, no oscillation. Trouble is likely whenever the measured mutual conductance exceeds 3-4 mA/V.

A certain cure which does not interfere with the operation of the tester is to connect a damping capacitor from grid to cathode on the valveholder. For universal suppression it has been found satisfactory to use 100 pF between every tag likely to be used as a grid and the panel frame, which is connected to the low ("cathode") end of the supply transformer and the transformer core, and earthed through the usual third core on the mains lead. In the original case the balances then became reasonable.

If every valveholder is to be individually by-passed in this way the cost of ceramic capacitors is formidable and they will occupy considerable space, but they *must* be fitted as near as possible to the valve pins in order effectively to short-circuit the parasitic tuned circuits formed by lead inductance and capacitance.

A more fundamental cure might be to screen all leads to frame and thus considerably reduce the stray capacitance between any pair of electrodes and increase that between each electrode and frame. Alternatively, one completely suppressed holder might be used with different short adaptors for each valve-base type, but this would be inconvenient and probably more expensive.

Mr. Finlay's note has been passed to the Automatic Coil Winder and Electrical Equipment Company, makers of Avo instruments, who contribute the following comments, written by S. R. WILKINS, *chief electronic engineer.*

WE have noted difficulties that sometimes arise when testing modern high-slope valves in our original valve tester, which was, of course, designed many years ago when the extremely high slopes which are the present-day tendency were not met with.

As Mr. Finlay surmises, difficulty arises when a number of valveholders are wired in parallel. The inductance of this wiring, together with distributed capacity, results in a capacity loaded line being applied to the valve, with the result that the high slope of the latter, together with distributed feedback capacity causes oscillations to take place at a very high frequency determined by the random line constants.

The incidence of this effect will, of course, vary within limits from valve panel to valve panel, depending upon minor variations in the wiring, and, of course, will vary with the effective slope of the valve.

Whilst a certain measure of cure can be obtained by the application of by-pass capacitances connected directly to the valve pins, this necessitates, as your correspondent suggests, the connecting of a suitable capacitance to every pin of every valveholder, the capacitance having to stand up to the maximum peak applied voltage that can be applied for either screen or anode. Even then, since any pin can represent any electrode, depending on the base set-up of the valve in question, the presence of a by-pass capacitance on one electrode may be offset by a similar feedback capacitance of another electrode. This form of cure, therefore, besides being unwieldy and extremely expensive, is not really satisfactory. Further, the effect of loading capacitances can be to transform a line which would normally present too high a resonant frequency for oscillation into one of lower frequency at which oscillations will take place.

A form of cure which we have previously adopted consists in the inclusion in circuit immediately at the valve pin of a resistance stopper, overwound with an inductance so that, when the pin concerned becomes a heater or cathode, negligible d.c. resistance is presented. Here again, since it is impossible to do this for every pin, such stoppers have only been included at carefully chosen pins of specific valveholders, thus minimizing the possibility of oscillation in specific cases where it is liable to occur. This, of course, represents only a partial cure.

Considerable experimental work on this problem has resulted in our introducing on recent models of our valve characteristic meter an entirely new form of wiring design to overcome this trouble in all normal cases. It will be evident that the problem is many times worse on our valve characteristic meter, where the possibility of testing a valve on any portion of its characteristic can mean that a valve may be tested at many times its normal emission and at a point of extremely high anode slope. The method introduced (patent applied for) consists in so wiring the multiple valveholders in that any valve of sufficiently high slope will tend to oscillate at a predetermined frequency depending upon a controlled loop length in the wiring. The loop in question is then suitably resistively damped so that oscillation cannot take place at the frequency in question. Since the resonant frequency of possible oscillation is held within reasonably close limits by the nature of the wiring, this means in fact that oscillation does not occur at any frequency. The number of stoppers to promote this condition is thus reduced to the total number of wiring loops; i.e., one for each pin of the valveholder, and all other more difficult manufacturing methods including the use of screened wiring are thus eliminated.

Results with this system have shown, both on our valve characteristic meter and our valve tester, that valves such as the $KT_{33}C$ can be tested at twice their normal working emission, and with a slope of some 12 mA/V, with complete stability, and, as far as can be at present determined, this very difficult problem which has exercised our minds for many years has now to all intents and purposes been overcome.

HIGH QUALITY REPRODUCTION

"FIFTY and THIRTY WATT" CINEMA AMPLIFIERS as illustrated for single or double P.E.C. input with separate adjustable bias. Full range of tone controls to suit all needs with built-in Exciter Supply if required. PRICES range from **34½ gns.** to **42½ gns.**

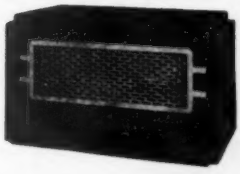

TYPE C.P. 20A AMPLIFIER

For AC Mains and 12 volt working giving 15 watts output, has switch change-over from AC to DC and "Stand-by" positions. Consumes only 5½ amperes from 12 volt battery. Fitted with mu-metal shielded microphone transformer for 15 ohm microphone, provision for crystal or moving iron pick-up with tone control for bass and top. Outputs for 7.5 and 15 ohms. Complete in steel case with valves.

PRICE **£28 . 0 . 0.**

FOUR-WAY ELECTRONIC MIXER

This unit has 4 built-in balanced and screened microphone transformers, normally of 50-30 ohms impedance. It has 5 valves and selenium rectifier supplied by its own built-in screened power pack consumption 20 watts. Suitable for recording and dubbing, or large P.A. Installations since it will drive up to six of our 50 watts amplifiers whose base dimensions it matches. The standard model has an output impedance of 20,000 ohms or less and any impedance can be supplied to order.

PRICE **£24 . 0 . 0.**

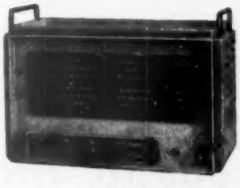

OTHER MODELS IN OUR RANGE OF AMPLIFIERS

"SUPER-FIFTY WATT" - - - - - PRICE **36½ gns.**
"THIRTY WATT" - - - - - - - „ **30½ gns.**
"10-15 WATT RECORD REPRODUCER" „ **25½ gns.**

These are fitted in well ventilated steel cases with recessed controls, as illustrated.

Full details upon request.
EXPORT ENQUIRIES INVITED

VORTEXION LIMITED, 257-261 THE BROADWAY, WIMBLEDON, LONDON, S.W.19

Telephones: LIB 2814 and 6242-3 **Telegrams: "Vortexion, Wimble, London."**

D

MARCONI-SIEMENS

Radio Telephone Terminal

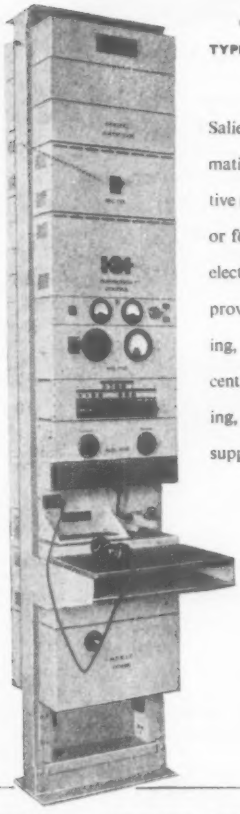

TYPE B

Salient features: Semi-automatic operation with alternative manual control, two-wire or four-wire line connection, electronic voice switching, provision for privacy working, radio calling facilities, centralised test and monitoring, self-contained for A.C. supply.

MARCONI'S WIRELESS TELEGRAPH CO., LTD.
MARCONI HOUSE, CHELMSFORD

SIEMENS BROTHERS & COMPANY LTD.
WOOLWICH, LONDON, S.E.18

WILLIAMSON

Amplifiers

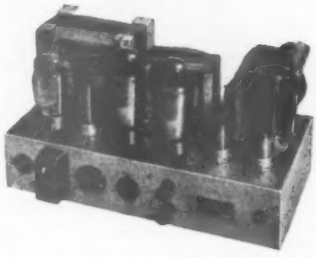

THE WILLIAMSON CIRCUIT AS PUBLISHED IN THE WIRELESS WORLD, AUGUST, 1949, IS THE ACCEPTED STANDARD FOR HI-FIDELITY REPRODUCTION.

Our version of the amplifier uses such constructional refinements as :—

★ **Impregnated grid coupling condensers.**
★ **Paper condensers on the H.T. supply line.**
★ **Matched or close tolerance resistors, where balance is important.**
★ **Cadmium-plated steel chassis.**
★ **Partridge Mains and Output Transformers.**
★ **Model D.P.S. with separate H.T. supply incorporated on the same chassis for use with multi-stage pre-amplifiers.**

Our complete range is :—

Type K.T.66 amplifier to specification **£24.5.0 inc. valves**
K.T.66 D.P.S. **£29.5.0 „ „**
Type P.X.25 D.P.S. as Type K.T.66 D.P.S. but with P.X.25 output valves, **£30.10.0 „ „**
Type E.L.37 D.P.S. 9 watts output, **£18.18.0 „ „**

E.L.37 D.P.S. is a new model, illustrated above, using a special output transformer with sectionalised windings and having an extremely low leakage inductance, together with the latest Mullard 88a valves.

For use with above equipment :—

Wide range four-stage tone-control and equaliser for L.P. and Standard records, with microphone and radio input. Complete with engraved perspex panel **£7.17.6**

Four-Station pre-set superheterodyne receiver with variable selectivity, from ... **£8.15.0**
Tax £1.18.11

GOODSELL LTD.
40, GARDNER STREET, BRIGHTON
Telephone : BRIGHTON 26735

London Representative :
HOLLEYS RADIO, 285, CAMBERWELL ROAD, LONDON, S.E.5. Phone : RODney 4988

Ionosphere Review: 1950

Rapid Fall in Sunspot Activity with M.U.Fs Lower than Anticipated—Forecast for 1951

By T. W. BENNINGTON (Engineering Division B.B.C.)

DURING 1950 the sunspot cycle continued in its "declining" phase, and the rate of decrease in sunspot activity was, in fact, greater than in any year since the maximum in 1947.

The corresponding ionospheric variations—which result from the variation in the amount of solar ultra-violet radiation falling upon the ionosphere, in accordance with the variations in the sun's activity—were also in a generally decreasing direction. The measured ionospheric critical frequencies at the beginning of the year were high, but, so far as daytime values in the northern hemisphere are concerned, after their summer fall they never recovered to anything like their springtime values, but remained low throughout the northern hemisphere autumn and winter. As a result of this the maximum usable frequencies for long-distance short-wave communication—which are directly related to the measured critical frequencies—were, from September onwards, very much lower than had been anticipated earlier in the year. But, of course, since it is not yet possible to forecast in detail the sunspot variations for very long ahead, the detailed behaviour of the ionosphere is also unpredictable far into the future, and occasional sharp disagreement between prediction and actuality are rather to be expected.

Sunspot and Critical Frequency Variations.—In Fig. 1 the top (full line) curve gives the monthly mean value of the sunspot relative number for each month of the present cycle, whilst the two bottom (dashed line) curves give the monthly mean of the F_2 layer critical frequencies for noon and midnight respectively. The latter data were obtained at the Slough station of the D.S.I.R.

Large and erratic variations occur in the monthly values of sunspot number, especially around the maximum, but the general increase towards the maximum (in May, 1947) and the decrease since then, is also apparent. During 1950, it is seen, the decrease became quite rapid and the value of sunspot number for November, 1950, was of the same order as those for late 1945 and early 1946, *i.e.*, about a year after the last minimum.

The curves for the noon and midnight critical frequencies show the large seasonal variations which have occurred, and which, at Slough and other northern hemisphere locations, tend to produce low noon and high midnight values of critical frequency at mid-summer, and *vice versa* towards mid-winter. It is interesting to note that at noon there is usually a small decrease in critical frequency at extreme mid-winter, this giving rise to a double-peaked curve, with its peaks at the early and late winter periods. During 1948 the increase after the mid-winter dip did not

Fig. 1. Monthly mean sunspot numbers and the noon and midnight F_2 layer critical frequencies during the present sunspot cycle.

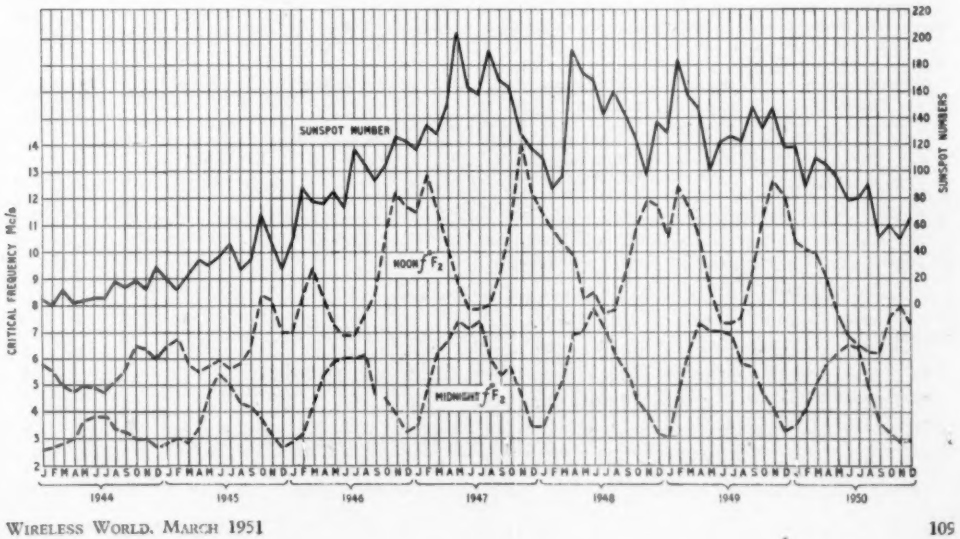
SUNSPOT NUMBER
NOON $f F_2$
MIDNIGHT $f F_2$
CRITICAL FREQUENCY Mc/s
SUNSPOT NUMBERS
J F M A M J J A S O N D J F M A M J J A S O N D J F M A M J J A S O N D J F M A M J J A S O N D J F M A M J J A S O N D J F M A M J J A S O N D J F M A M J J A S O N D
1944
1945
1946
1947
1948
1949
1950

occur, and a similar phenomenon took place during 1950, there being no increase in critical frequency after the January fall. The curves for the winters 1947/48 and 1949/50 were therefore single peaked, and it is interesting to note that, at the time when the secondary increase would have been expected, *i.e.*, about February, there was in both cases a fall in sunspot activity. It seems fairly certain that the failure of the ionosphere to show an increase in its ionization density at these times was thus due to a rather abrupt decrease in the amount of ultra-violet radiation reaching it from the sun.

Turning now to the long period variations in critical frequency it is seen that the fall during 1950 was quite remarkable. In September, 1950, the noon value was as low as that which prevailed in September, 1945, only about a year after the minimum, and it seems that in one year the critical frequencies have changed from "quasi-maximum" to "quasi-minimum" values. The m.u.fs. for short-wave communication have fallen proportionately also, for during the autumn and winter the higher short-wave frequencies, which had been giving good service at this time of the year for some years past, failed to become regularly workable. The night-time m.u.fs., as is indicated in Fig. 1, were also very low.

The question now arises as to how long this depression in the critical frequencies and m.u.fs. will last, or, indeed, whether very low values will not become a permanent feature for several years to come. Well, no one can give a confident answer to such a question because no one can be certain about future sunspot activity. A study of the curves of Fig. 2 may, however, help us a little on this point.

In Fig. 2 are plotted the twelve-month running means of the sunspot number and of the Slough noon and midnight critical frequencies. In this way the erratic month by month variations in sunspot activity and the seasonal variations in noon and midnight critical frequencies are smoothed out, enabling the long-period variations in all these quantities to be more clearly visualized. It is seen that after the sunspot maximum at the epoch May/June, 1947, there were some large up and down variations in the general sunspot activity, but, up to the epoch July/August, 1949, no very pronounced downward trend. Since that time, however, the downward trend has become increasingly pronounced, and this is the result of the decreased activity which took place during 1950. Similarly, in the running mean critical frequency curves there is no very pronounced downward trend until the epoch July/August, 1949, but since then it has become more apparent, due to the fall in critical frequencies during 1950. For the epoch June/July, 1950—the value in whose calculation the last monthly mean for 1950 is included—the running mean value of sunspot number had decreased by somewhat less than one half of the value reached at the maximum. The critical frequency graphs of Fig. 2 show that the running mean critical frequencies, both for day and night, have also fallen by about one half since the sunspot maximum. From this one might conclude that both sunspot activity and critical frequencies are still at a relatively high level.

But these graphs of running means, though they do show very well the general course of the sunspot cycle and the general variation in critical frequencies with it, are apt to be deceptive when used to indicate the situation at any one epoch. In fact, one should note, not only the actual value, but also the way in which it is changing and, so far as the epoch June/July, 1950, is concerned, all quantities are seen to be decreasing rapidly.

Forecast for 1951.—If sunspot activity continues to decrease at its present rate it will not be long before the truly "minimum" conditions are upon us. But considering the present sunspot cycle in relation to its predecessors it seems unlikely that the present rate of decrease will last for very long. Indeed it would be not surprising if the activity were to cease to fall and to remain relatively constant for a year or so, or even to show a general rise for a similar period, at this stage of the sunspot cycle. However, without anticipating such a possibility, we should note that in nearly all the recorded cycles there is a marked tendency for the rate of decrease to diminish when relatively low values of sunspot number are reached.

So far as 1951 is concerned, we might be justified in anticipating that the general level of sunspot activity will continue to decrease, but that the rate of decrease will soon begin to diminish. If this were so we should estimate that the running average of sunspot number for the epoch at the middle of 1951 might be about

Fig. 2. Twelve-month running averages of sunspot numbers and of noon and midnight F_2 layer critical frequencies.

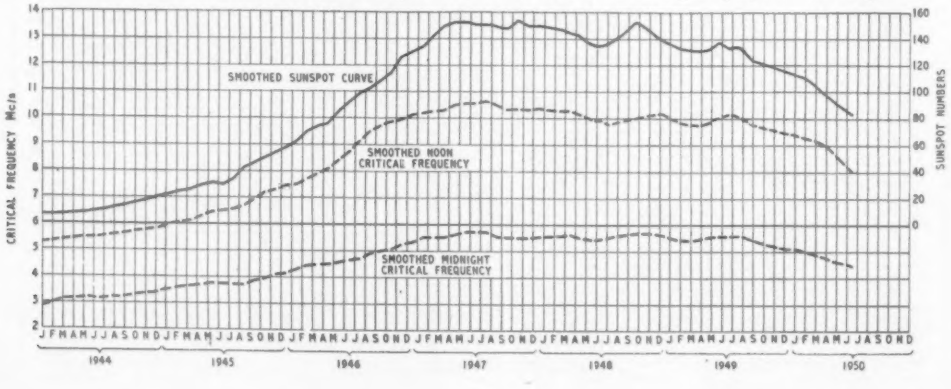
SMOOTHED SUNSPOT CURVE
SMOOTHED NOON CRITICAL FREQUENCY
SMOOTHED MIDNIGHT CRITICAL FREQUENCY
CRITICAL FREQUENCY Mc/s
SUNSPOT NUMBERS
J F M A M J J A S O N D J F M A M J J A S O N D J F M A M J J A S O N D J F M A M J J A S O N D J F M A M J J A S O N D J F M A M J J A S O N D J F M A M J J A S O N D
1944
1945
1946
1947
1948
1949
1950

50, and that the running average noon critical frequency might fall to about 7 Mc/s, and that for midnight to about 4 Mc/s. Critical frequencies during 1951 are, therefore, likely to be low.

The result would be that the m.u.f. for longest distance working in these latitudes should, by November, 1951, have fallen to about 24 Mc/s. This is not a great deal lower than it was in November, 1950, but then it is thought that the abnormally low m.u.fs. during the autumn of 1950 may have been a rather exceptional occurrence and contributed to partly by the large amount of ionospheric storminess which occurred at that time.

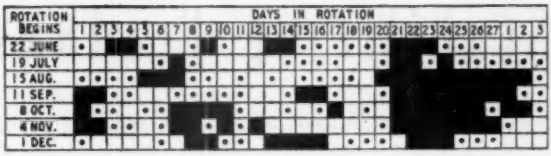

Fig. 3. Day-by-day record of "reception disturbance rating" compiled by the B.B.C. receiving station at Tatsfield for westerly circuits.

However all this may be—and it admittedly is no better than informed guesswork—there are one or two practical points about propagation during 1951 which it may be helpful to mention. It is unlikely that the 28-Mc/s amateur band will become regularly usable again at any time during the year. It may become occasionally usable for long-distance communication over north/south paths in the early spring, and during the summer medium-distance 28-Mc/s communication by Sporadic E may take place, but as a regularly workable band its utility throughout the year is likely to be small. The 26-Mc/s broadcasting band is likely to fail for long-distance communication over north/south paths during the summer, and the 21-Mc/s band to become generally less useful. In short, the highest daytime frequencies will be considerably lower this year than last. At night only the lowest short-wave frequencies are likely to be of use during the winter periods, either at the beginning or end of the year. During the summer, frequencies up to 11 Mc/s may be usable through the night; during the winter period those of the order of 7 or 6 Mc/s only will be usable, the tendency being more towards the lower frequencies at the end of the year than at the beginning. Unfortunately, the congestion which already exists on the short-wave bands is likely to be made worse by this limitation of the workable frequency bands. So altogether it cannot be said that 1951 is likely to be a very good year for short-wave communication, for conditions will render certain higher frequencies unworkable and, favouring the use of the lower short-wave frequencies, will so limit the workable bands that increased interference will result.

Interesting Phenomenon of 1950.—Before dismissing 1950 altogether to the past it may be of interest to call attention to an interesting phenomenon which occurred during the latter half of the year. It is generally assumed that the ionospheric storms which cause havoc to short-wave reception are produced by streams of corpuscles which are shot out from the sun—sometimes from a sunspot and sometimes from a particular active region on the sun which cannot be distinguished by any observable phenomena—called by Bartels an "M" region. These "M" regions seem to be a feature of the declining rather than of the rising phase of the sunspot cycle, and sometimes occur even at sunspot minimum. If the activity of such a region persisted for a relatively long period of time the corpuscular stream would encounter the earth at intervals corresponding to the rotative period of the sun, *i.e.*, each time the sun had rotated so that the active region was pointing towards the earth. Thus the ionospheric storm would recur at intervals corresponding to the rotative period of the sun as observed from the earth—the period of synodic rotation, which is about 27 days.

In Fig. 3 are plotted—along the lines of a Bartels diagram—the "reception disturbance ratings" compiled by the B.B.C. receiving station at Tatsfield from the receiving conditions experienced between June 22nd and December 27th, 1950. The daily period of worst conditions for westerly circuits only has been taken and the disturbance rating plotted for each day according to the following symbols: plain, "much better than normal to normal"; black spot, "slightly disturbed to moderately disturbed"; black, "considerably disturbed to blackout." The black squares may therefore be taken as representing days on which ionospheric storms were definitely in progress. Starting with June 22nd the days are laid off horizontally for the period of the synodic rotation, *i.e.*, for 27 days, and then the days of the next rotation are laid off horizontally underneath those of the first. The first three days of each rotation are repeated at the end of the preceding one for the sake of ease of observation. It will be seen that if an ionospheric storm recurs at intervals of 27 days the black squares will, in a diagram of this sort, fall under each other during successive rotations.

The quite remarkable recurrence propensities of the ionospheric storm which started on July 12th (day 21) are thus made evident, for this storm is seen to have recurred during no fewer than six of the following solar rotations, starting successively on August 8th, September 3rd, October 1st, October 28th, November 24th, and December 22nd respectively, all of which days were either day 20, 21 or 22 in the rotation. It should be mentioned that, because the mean period of the synodic rotation is slightly more than 27 days it might have been expected that the black patch would drift slowly to the right during successive rotations, but the fact remains that, for its first six occurrences, as shown by the Tatsfield data, it always started on the 20th or 21st day. If a similar diagram is drawn for the earth's magnetic field, by allotting similar symbols to the daily magnetic character figures, then the recurrence tendency is again evident for the magnetic storms which accompanied the ionospheric disturbances. Though the starting days for the two phenomena do not always quite coincide, and the black patch indicating the magnetic storms does drift to the right, the two phenomena—magnetic and ionospheric storms—are quite clearly interconnected and are more or less coincident in time. For how long this storm will continue to recur it is, of course, impossible to say, but its future behaviour will be watched with interest. For it is by the study of such phenomena as this that the knowledge of ionospheric disturbances may be advanced and the difficult problem of forecasting them be, in some part, solved.

Stabilizing Feedback Amplifiers

Simple R-C Networks and the Calculations Involved

By THOMAS RODDAM

A PROBLEM which must be fairly common is that of the unhappy man who wants to add feedback to an existing amplifier, or to a slightly modified version of an existing amplifier. What is he to do, if he can't afford a new transformer? This problem does arise in other feedback problems, too, and in this article I want to describe some simple circuits which can be used to help the amplifier characteristics. These circuits are often useful in keeping the size of components down.

First of all, let us assume that our impoverished reader can measure the overall frequency response of his amplifier. He can then determine the phase characteristic by making use of the very approximate results shown as Fig. 1. The phase error is at most 10 degrees and the amplitude error at the corner is exactly 3 db. It is easy to correct this. Our reader having measured his frequency response can now draw the straight-line approximations, using slopes of 20 db/decade, and construct the phase characteristic. This is shown in Figs. 2 and 3. It took about 5 minutes to plot out that phase characteristic. This is not going to be a discussion of the method in detail, but merely a background to what follows, a discussion of how to modify the response in the required way. But I must point out one thing. The reduction in slope above $f/f_0 = 10$ in Fig. 2, keeps the phase below 120 degrees, although the slope at $f/f_0 = 8$ is 40 db/decade, a figure often assumed to imply a phase

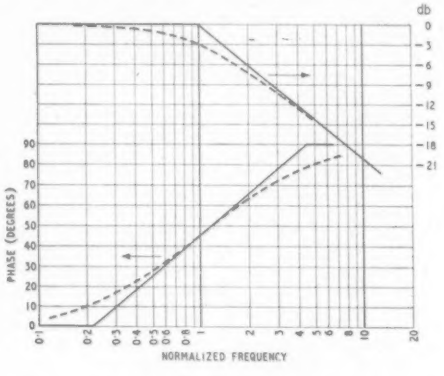

Above : Fig. 1—Simplified amplitude and phase characteristics (dotted lines are exact forms). Frequencies are normalized to f/f_0 or f_0/f where f_0 is the frequency at which the response is 3 db down.

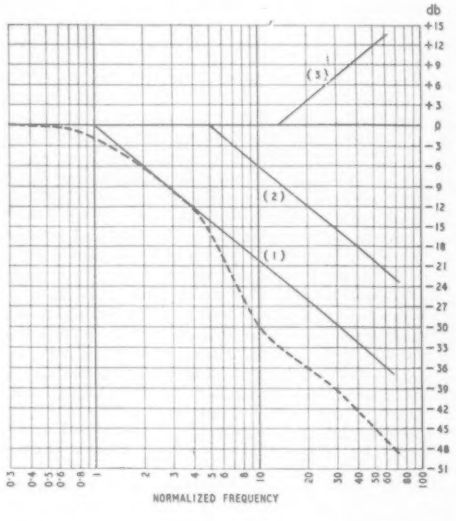

Above right : Fig. 2—Typical amplitude response curve with component "semi-infinite" slopes (1, 2 and 3), from which Fig. 3 is constructed.

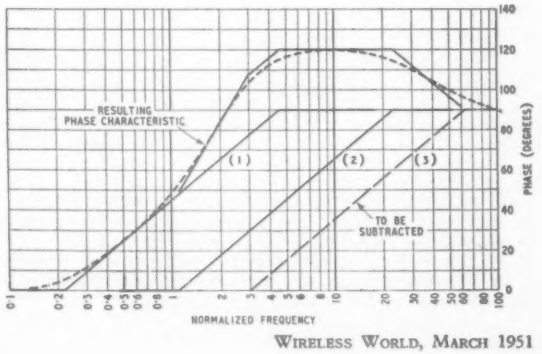

Right : Fig. 3—Phase characteristic constructed from amplitude characteristic of Fig. 2 using curves in Fig. 1.

shift of 180 degrees. One more thing: these are normalized curves, and if you twist them round they also work. The same curves are good for the low-frequency end, remembering that now the scale is proportional to 1/(frequency). And if I go into more detail I shall have no room for the meat: like the Yorkshire farmer, who always told the children: "Them as eats most pudden gets most meat."

The response with which we have normally to deal is fairly flat up to some high frequency (I shall consider the top end first) and then darts sharply down. The result of this sharp descent is that the phase shift runs rapidly up to 180 degrees *before* the amplitude response has dropped appreciably. One amplifier with which I had to deal recently actually had a measured phase shift of 180 degrees at a point at which the amplitude response had *risen* 1 db. As it was necessary to put in 20 db of feedback the whole thing had to be started again. But this was exceptional. Usually it is a matter of raking up another 6 to 10 decibels. How can we do this?

The first, and simplest circuit is that shown in Fig. 4: just an extra capacitance connected across one stage of the amplifier. This has the characteristic shown in Fig. 1, in which the reference frequency is obtained from the equation $\omega_0 CR = 1$, where ω_0 is $2\pi f_0$. In the practical circuit R is the resistance produced by the parallel connection of the anode load resistance, the grid resistance and the valve impedance. Usually the first of these takes control, if pentodes are used, or the valve impedance if triodes are used. The first step, then, is to choose ω_0, 2π times the maximum frequency you hope to take out of the amplifier, and then calculate $C = 1/\omega_0 R$. Suppose that with 10 db of feedback your amplifier just oscillates at a frequency of 100 kc/s. Suppose also that your version of Fig. 3 indicates that you have 90 degrees phase shift at 50 kc/s. Then introducing the circuit of Fig. 4, cutting at 10 kc/s will give a drop of 14 db at 50 kc/s, and will bring the phase shift here up to 180 degrees. Any attenuation elsewhere in the circuit, say 3 db, can be added to this 14 db, so that the circuit will now just be unstable with 17 db feedback. There is a definite gain, even though it is not much.

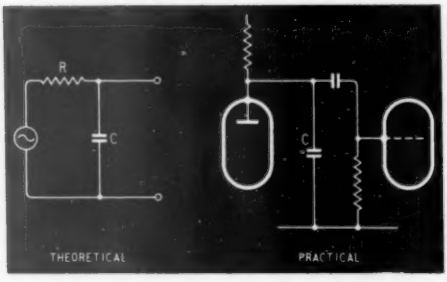

Fig. 4—Simplest form of stabilizing circuit.

The chief use for this simple circuit is across the output transformer. An output transformer works ideally as a low-pass filter, made up of the leakage inductance and the shunt capacitance. This is usually the worst possible form for a feedback amplifier and it is profitable to round off the response by using the circuit of Fig. 4.

What we really need for the inter-stage stabilizing networks is something which provides attenuation without phase shift. Outside a limited frequency range this is provided by the circuit shown in Fig. 5, which can be used across the anode load of a valve. The valve is most conveniently a pentode for calculation purposes. At low frequencies the gain of the stage is gR_1, because C is assumed to be small, but this changes over at high frequencies, where C can be neglected, to $g.[RR_1/(R + R_1)]$. Suppose, for example, $R_1 = 100{,}000\ \Omega$ and $R = 11{,}000\ \Omega$: $g = 2$ mA/V. At low frequencies we have a gain of 200, and at high frequencies a gain of 20. This is a drop of 20 db. The frequency response and phase characteristic are shown, both exactly and using the straight-line approximation, in Fig. 6. The cut-off frequency of this circuit is again determined by the equation $\omega_0 CR_1 = 1$, while the "flattening-out" frequency, which is 10 on this curve, is given by

$$\omega_0 C \left(\frac{R_1 R_2}{R_1 + R_2}\right) = 1$$

The advantage is clear. Instead of a phase shift of 90 degrees at a frequency of 10 on the scale we have only 45 degrees and it is getting less as the frequency increases. The maximum phase shift is obtained half-way down the attenuation char-

Below: Fig. 5—The most useful stabilizing circuit is one connected across the pentode load resistance R_1.

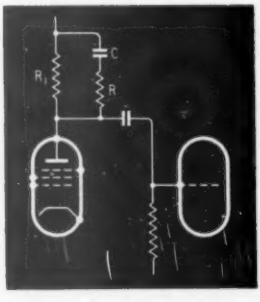

Fig. 6—Typical amplitude and phase characteristics of the circuit of Fig. 5.

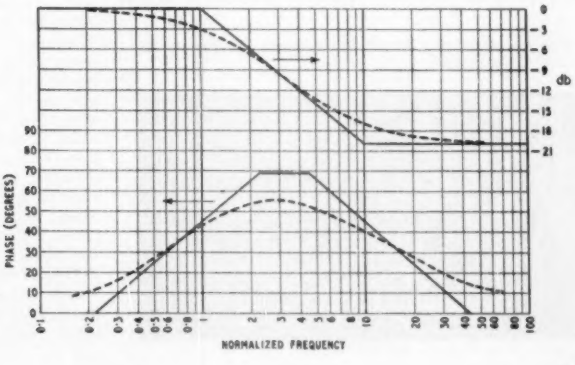

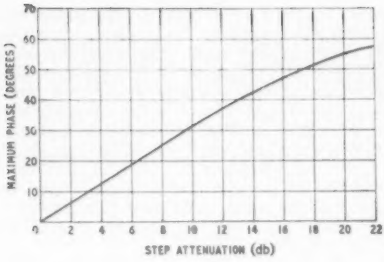

Left: Fig. 7—Maximum phase shift as a function of attenuation in the circuit of Fig. 5.

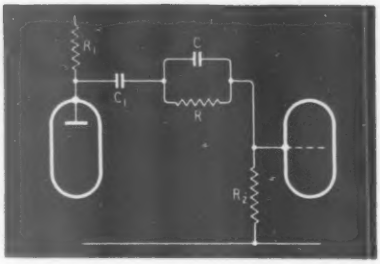

Right: Fig. 8—Low-frequency stabilizing circuit.

acteristic, and I have plotted Fig. 7, which shows the maximum phase shift as a function of the size of the attenuation step.

This circuit really is astonishingly useful, because once the phase shift peak is passed it provides a very wide band response. Let us look at some typical figures. If the valve is a pentode we may have $R_1 = 50{,}000\ \Omega$, and the total capacitance at the anode 40pF. This would normally give a response which fell off by 3 db at $\omega = 1/CR = 500{,}000$, or $f = 80$ kc/s. By taking C in Fig. 5 = 400 pF and $R = 5{,}000\ \Omega$, the response will start to drop at 8,000 c/s, although it is only 6 db down at 16,000 c/s, and this loss of feedback can be tolerated. At 80 kc/s the phase shift will be 45 degrees, and the response will be 17 db down, but the response will then flatten out, at 20 db down, and will extend up to 800 kc/s, the phase remaining below 45 degrees the whole way. Thus in the region which is often most critical, above 100 kc/s, the phase shift is small. A glance at Fig. 6 will show that three circuits of this kind in cascade will have a phase shift of only 165 degrees and 60 db of feedback could be used without instability: without using networks of this type, but using three similar stages, the feedback would be limited to 12 db.

There is a similar circuit available for low-frequency stabilization. This is shown in Fig. 8. If we assume that C_1 is very large indeed, the low-frequency response will, at first, depend on the quantity CR_2. The response will, in fact, be 3 db down when $\omega_0 = 1/CR_2$, and the shape of the amplitude and phase curves is given by Fig. 1, remembering that the "normalized frequency" is now f_0/f, so that if the cut-off (the corner) is at, say 100 c/s, the response is 20 db down at $f_0/f = 10$, or $f = 100/10 = 10$, where the phase is within a few degrees of 90 degrees. But suppose that $R = 9R_2$: the response must flatten out before the 20 db down region is reached, and, in fact, it will be exactly that given in Fig. 6. Again the frequency *decreases* from left to right. Now, at 10 c/s, the phase shift is only 40 degrees. The curve of Fig. 7 applies here too, the step attenuation being simply 20 log $(R + R_2)/R_2$.

What about C_1? This capacitor, at very low frequencies, will also make the response drop, but it is working into an impedance of $(R + R_2)$, so that the new downward trend does not begin until we reach $\omega_0 = 1/C_1\ (R + R_2)$. Let us look at some numbers again. R_2 can be 500,000 Ω, the most that the average valve will stand, and $R = 4.7$ MΩ. Taking $C = 0.01\ \mu$F, the response will start to drop at $\omega_0 = \dfrac{1}{0.01 \times 0.5} = 200$, or $f \simeq 30$ c/s. At 3 c/s the response will be 17 db down ($f_0/f = 10$) and will be flattening out. The phase will not have exceeded 55 degrees and will be approaching zero again. If now we take $C_1 = 0.1\ \mu$F, we shall start to get a new drop at 0.3 c/s, where the phase will be about 50 degrees, and the attenuation 23 db.

These two simple devices can be regarded as patches to a defective design, or they can be used as the keystones of a sound and stable amplifier. The low-frequency circuit, in particular, can often save both money and weight by allowing relatively small capacitances to be used. In this article I am regarding these circuits as patches. How can they best be applied? The obvious first step is to measure the overall response of the amplifier you are trying to add feedback to. Then the phase characteristic can be sketched by the method discussed very briefly at the beginning of the article. A study of the circuit, plus a little arithmetic, should show which part of the circuit does what: all the RC circuits start a 6 db/octave dive at a frequency given by $f = 1/2\pi CR$. The rest is due to the transformer—I assume that we are worrying only about an output transformer. This whole operation should not take more than about 20 minutes. At this point it is necessary to decide where the circuits of Fig. 5 and 8 should be introduced, and how much the step attenuation should be. It is always better to put in more circuits with smaller steps than to try to make one do all the work. I find that the most critical designs, involving very careful adjustment of the critical frequencies, take up to 3 hours, and need about half-a-dozen trial shots to get the required result. But that is only when I want about 40 db of feedback.

It is always the high-frequency end of the response which causes the most trouble. Low-frequency instability can, at the worst, be prevented by brute force methods, a handful of microfarads. One

Fig. 9—Stabilizing circuit in feedback path for use at high frequencies.

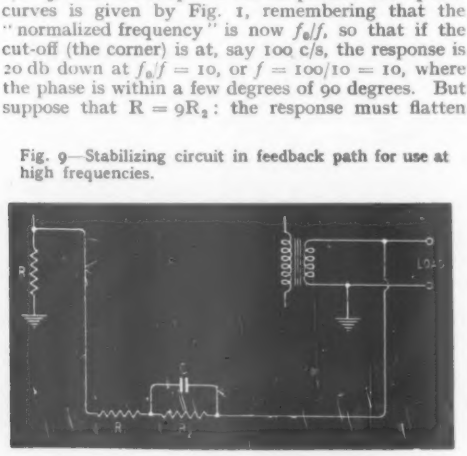

more network, related to those we have discussed, is very useful in controlling the top end. Fig. 9 shows how the normal feedback resistor has been split into R_1 and R_2, with a capacitor C connected in parallel with R_2. Here R is the resistor across which the feedback is applied, and is usually the cathode resistor of the first valve. At low frequencies the feedback depends on the ratio $(R + R_1 + R_2)/R$ in the usual way: at very high frequencies the feedback is increased, and depends on $(R + R_1)/R$. This means that the product $\mu\beta$, so familiar in feedback work, is arranged to remain more nearly constant, since as μ decreases due to the shunt capacitances in the forward path β increases. In the simplest use of this circuit R_1 is made zero, and the capacitor is connected across the whole feedback resistor. We can calculate the sort of size we need quite easily: suppose that R_2 is 10,000 ohms, and that we do not mind the response being about 3 db down at 15,000 c/s. Provided that we have a fair amount of feedback, say 20 db or more, we shall want $CR_2 = \frac{1}{2\pi \times 15{,}000}$, or C = 100 pF.

This shunt capacitor is of very great value indeed. I have used it for stabilizing awkward amplifiers, for providing a smooth roll-off to avoid overshoot on square waves, and for obtaining a particularly high stability margin in an amplifier which had to meet a wide range of load conditions.

In this article I have tried to describe a technique which can be used for patching. Of necessity such a discussion must itself be patchy. I can assure the reader that the method of sketching phase curves from amplitude characteristics is a very useful one, and that I have found it a very powerful way of determining quickly what should be done to bring an amplifier into a stable condition. Certainly there seems to be no alternative if you haven't a very well equipped laboratory to work in, and unlimited time and material.

Grouped Component References

Aids to Reading Circuit Diagrams

By L. BAINBRIDGE-BELL

IN the December, 1950, *Wireless World* M. Bamford drew attention to the difficulty of finding a particular component (though identified by a reference number) in a complicated circuit diagram. He suggested dividing the diagram arbitrarily into numbered vertical strips, a resistor in the 4th strip being numbered, for example, R4.3.

The problem of helping the reader quickly to find a component has exercised many brains. Perhaps the obvious solution would be the strict numbering of components from left to right. This counsel of perfection is nearly always defeated, either because the designer has some last-minute thought and adds a component with the next available reference number (say C33) near the left-hand side of the diagram, or because the diagram is drastically re-arranged after the component references have been allotted.

It has been suggested that a diagram should be divided into functional groups, each group being numbered consecutively from left to right, and that a component (R3) in Group 7 should be called 7R3. This solution breaks down because it is often impossible to decide to which group a component belongs. Mr. Bamford avoids this by the more sensible suggestion of *arbitrary* divisions.

An Inter-Services Committee which has been responsible for the production of the Inter-Services Standard Graphical Symbols for Telecommunication Engineering (known to Service readers as Tels. A301, AP2897 or BR1079 according to the colour of the uniform they wear) has given some thought to this problem. The result of their deliberations appears in paragraphs 85 to 87 and 90 of that publication.

The Location-Strip.—So that any given component can be found quickly in a diagram or line illustration, the coded reference (e.g., R2, C5) should be written beside the components. For each common class of component, a horizontal strip should be drawn across the top of the diagram. At each end of this strip should be shown the reference letter, and in the strip the reference number of each component of that class, vertically above the component, thus:—

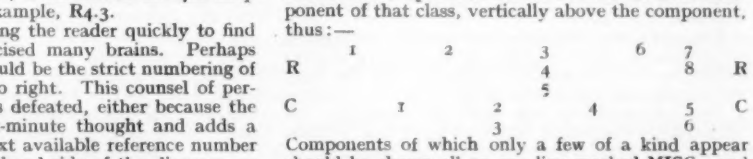

Components of which only a few of a kind appear should be shown all on one line marked MISC., and in this case (only) the full coded reference of each component should be shown, including symbols with no standard reference (referred to as XI, etc.) thus: MISC. LPI XI X2 SWA X3 MISC. In very long diagrams, the reference letters may be inserted at intervals in the horizontal strips, as well as at the ends.

The Map-Grid.—In the case of a diagram which is very complicated, or contains a large number of components, a map-grid system of location using letter-number references may be necessary. The grid lines need not be drawn across the diagram.

The location-strip (which is the only system recommended (on page 15) in BS530:1943) appears to the writer to offer great advantages. When using this aid, the reader scans one row (say R) horizontally until he finds the required component reference (say R15). He then scans vertically up or down until he comes to R15. His eye, instead of roving at random over the diagram, is constrained to follow a unique

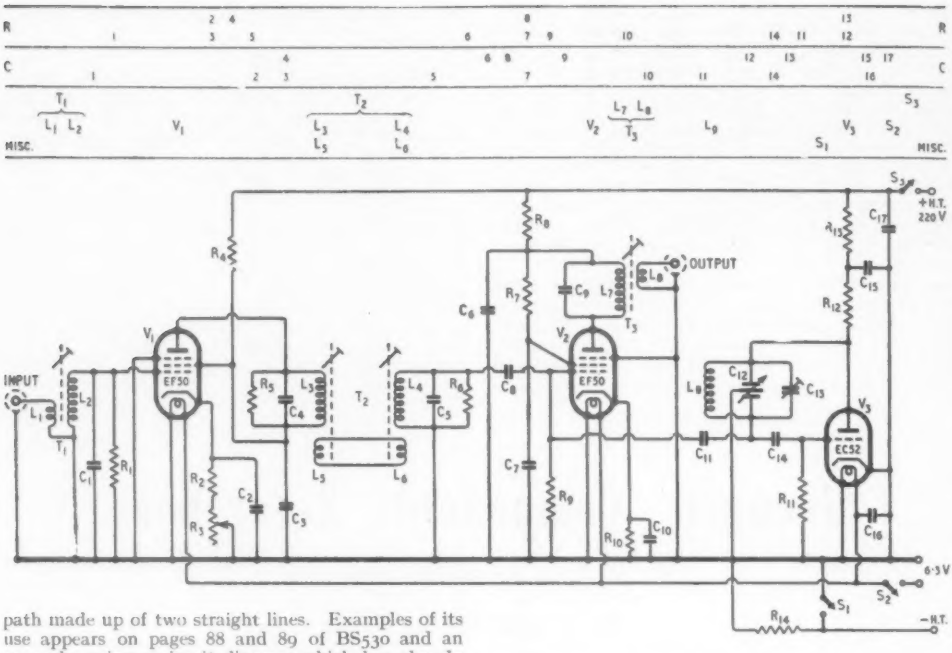

path made up of two straight lines. Examples of its use appears on pages 88 and 89 of BS530 and an example, using a circuit diagram which has already appeared in *Wireless World*, is given in the accompanying figure.

If the diagram is complicated, it is often helpful to put two sets of location strips, above and below. The diagram may naturally divide horizontally in two more or less equal paths; the two sets of strips can then refer to the respective halves nearer to them.

Pros and Cons.—Possible disadvantages are that the strip takes up valuable space, or else it may be difficult to use in a complicated diagram. In this case, the map-grid is the only solution.

The map-grid has one great disadvantage. It necessitates a separate table giving a list of components and their corresponding "map squares." Reference to this table—often on another page—is inconvenient, and often makes the reader "lose his place" in tracing out a circuit. In the writer's opinion, it should be adopted only as a last resort.

The location-strip (which was introduced to the Committee mentioned above by a representative from the Royal Air Force) is a very successful solution to Mr. Bamford's problem and is being increasingly used in electronic circuit diagrams. The writer thinks that it might be adopted with advantage in other fields and in telephone switching and power-control diagrams which often contain many relays and "detached" contacts.

CLUB NEWS

Birmingham.—At the meeting of the Slade Radio Society on March 2nd, C. H. Banks of C.J.R. Electrical and Electronic Development, Ltd., will talk on "High-Quality Tape Recording." At the following meeting (16th) the second of the Mullard filmstrip lectures on television will be given. Meetings are held on alternate Fridays at 7.45 in the Parochial Hall, Broomfield Road, Erdington.

Coventry.—The subject for consideration at the meeting of the Coventry Amateur Radio Society on March 12th is the radio control of models. Meetings are held on alternate Mondays at 7.30 at the B.T.H. Social Centre, Holyhead Road, Coventry.

Edinburgh.—The programme of the forthcoming meetings of the Edinburgh Amateur Radio Club includes lectures and demonstrations on radar navigation aids, audio amplifiers, aerials and radio control of models. Classes are held regularly for the Radio Amateurs' Examination. Meetings are held on Wednesdays at 7.30 at 4, Hillside Crescent, Edinburgh.

Exeter.—Members of the Exeter and District Radio Society will discuss "Servicing Snags" at the meeting at 7.30 on March 1st at the Exeter Hobbies Association Hut, Haldon Road, Exeter. At the meeting on March 22nd the subject to be dealt with is "Oscilloscope Time-base Synchronization."

South Kensington.—The lecture on "Electronic Organs" by L. E. A. Bourn, of the John Compton Organ Company, to members of the City & Guilds College Radio Society at 5.10 on March 5th will be followed by a demonstration of an instrument and a short recital. Members will be inspecting the radio installation at London Airport on March 14th.

Radio Control.—The International Radio-Controlled Models Society, which was formed to further the development of the radio control of models throughout the world, has a number of groups active in this country, including London, Manchester—the British H.Q.—Birmingham and Tyneside. Details of the organization and information on the radio control of models, for which purpose the G.P.O. has allocated 26.96-27.28 and 464-465 Mc/s, are obtainable from the headquarters secretary, T. F. Sutton, The Lodge, Manchester Grammar School, Manchester, 13.

The names and addresses of the club secretaries were given in the directory published in the January issue.

The
WESTON
S.75
Multi-Range
Test Set

53 Ranges with Rotary Switch Selection

This uniquely comprehensive Test Set has 53 ranges for measuring A.C. and D.C. current and voltage, resistance and insulation. It is completely self-contained, with internal batteries to provide power for the ohms ranges and self-contained power pack for insulation measurement at 500v. Selection is carried out by two 20-position switches. A fully-protective safety device is fitted and is operative for forward or reverse overload. The 150-division 6in. scale is uniformly divided and is fitted with an anti-parallax mirror. The set is enclosed in a handsome bakelite case and fully complies with B.S.S. No. 89, covering first-grade instruments. Full details of the ranges covered, and of the complete specification, will gladly be supplied on request.

SANGAMO WESTON LIMITED

ENFIELD, MIDDLESEX

TELEPHONE: ENFIELD 3434 (6 LINES) AND 1242 (4 LINES)
TELEGRAMS: SANWEST, ENFIELD

BRANCHES

Glasgow, Newcastle-on-Tyne, Leeds Manchester, Wolverhampton, Bristol, Southampton, Brighton, Liverpool & Nottingham.

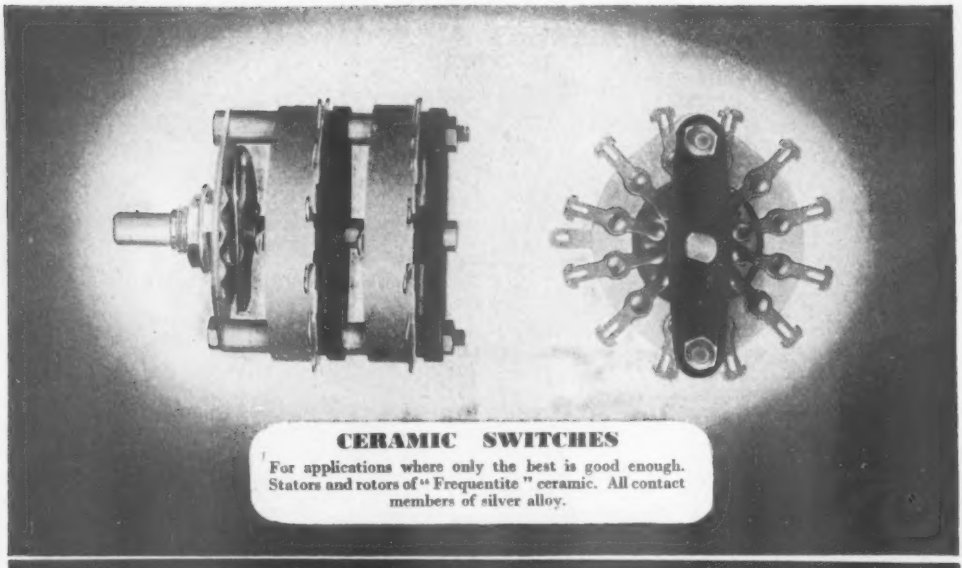

CERAMIC SWITCHES

For applications where only the best is good enough. Stators and rotors of "Frequentite" ceramic. All contact members of silver alloy.

Wright and Weaire Limited

138, SLOANE ST. LONDON S.W.1 TEL. SLOANE 2214 5 FACTORY SOUTH SHIELDS, CO. DURHAM

THERE IS A

W B *Stentorian*

LOUDSPEAKER

for every need

The W.B. range includes speakers from 2½" to 18", among them the famous Concentric Duplex 10" and 12" models.

Illustrated here is the Concentric Duplex Twin Corner Reflex Console with 10" Speaker.

★ *Details on request*

WHITELEY ELECTRICAL RADIO CO. LTD.

MANSFIELD NOTTS

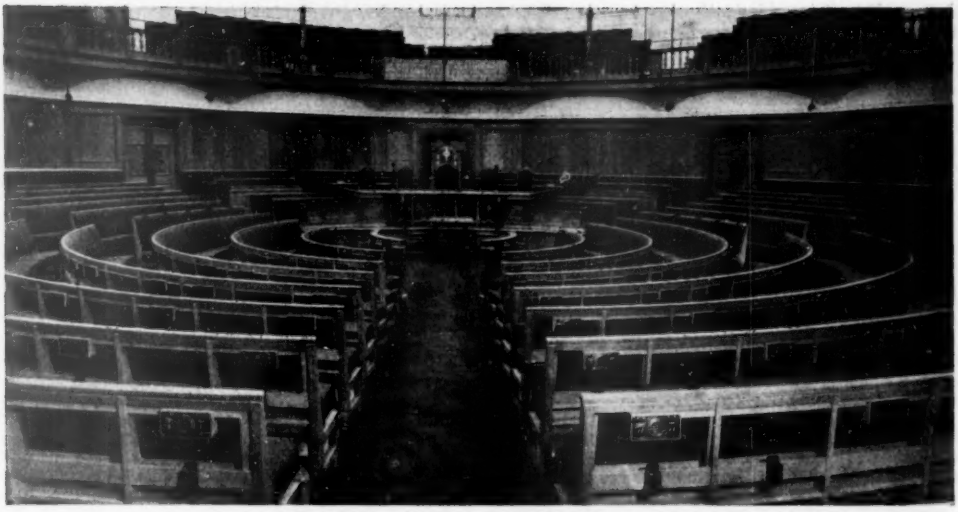

The Assembly Hall, Church House, Westminster, showing the reproducers on the seating and the suspended microphones

Sound Reinforcing

Low-intensity Installation Incorporating Simultaneous Interpretation System

By D. W. PIPE*

IN the past, it has, unfortunately, been common for the electro-acoustic requirements of halls, conference rooms, etc., to be overlooked, and often the technicians have not been consulted until after the building has been completed and in use, with the result that restrictions have been imposed. Designers had to resort to compromise, which has, naturally, affected the overall efficiency of the system as well as offending the beauty of the building.

During the past decade, however, architects and consulting engineers have realized the necessity for incorporating electro-acoustic aids when such halls are designed, or when old buildings are to be reconstructed. It is possible for loudspeakers, microphones and ancillary units to be designed in harmony with the aesthetic requirements, so that, upon completion, the performance of the sound distribution will be both technically efficient and aesthetically harmonious.

The opportunity for the correct approach to the many problems connected with modern speech reinforcement systems was presented when decisions were made to install a comprehensive sound distribution system whilst undertaking the restoration work at Church House, Westminster. In the early stages of that programme, decisions were made to incorporate in the circular Assembly Hall a low-level reinforcement system, combined with a four-channel simultaneous interpretation system, with independent facilities for the three adjacent halls and the provision for the inter-change of speeches between the halls.

The requirements of the functions to be held in the Assembly Hall dictated that for general debates and conferences, any member participating should be able to speak without leaving his seat and yet be clearly heard by all other members, whilst all speeches and debates should be heard clearly by those present in the Press and Public Galleries.

The second main requirement was to provide means of enabling all present to have the choice of selecting any one of four languages to enable multi-lingual conferences to be held with simultaneous interpretation facilities. To incorporate this facility with the main speech reinforcement system it was decided to provide a large number of small loudspeakers accommodated within the seating, and adjacent to those loudspeakers, rotary selector switches connected

* Tannoy Products (Sound Rentals, Ltd.).

to headphone jacks, to enable headphones to be connected to one of four channels, the selection being at the discretion of the user.

Dealing first with the loudspeaker distribution, the units were arranged so that one would feed two seats. The loudspeakers are connected and operated in zones closely associated with the unidirectional microphones suspended above the main seating of the Assembly Hall, with other microphones on the dais.

Positioning of the microphones is such that any member on the main floor of the hall is in the zone of one particular microphone and for this purpose the hall was divided into eleven operational zones. Each microphone is connected to a pre-amplifier, the output of which is connected through a selector switch on the operator's control panel. This is situated in the balcony where the operator has an unobstructed view of the assembly and, thus, is able to select the appropriate microphone circuit whenever a member rises to speak.

The loudspeaker units are connected to operate in zones associated with the microphones, since it is necessary to mute the loudspeakers in the area when the microphone is in circuit, thus enabling the remainder of the loudspeakers to operate at a higher sound level. These muting facilities are achieved by relays which are interlocked with the microphone selector switches. Contacts on these relays select the required attenuation through the use of tapped auto-transformer units. In order to obtain the required level of speech reinforcement with complete freedom from microphone howl, or feedback, adjacent loudspeaker zones are partially muted.

Control panel incorporating loudspeaker, language selectors and phone jacks as used on some seating.

The disposition of the reproducers and interpretation selector units on the seating in the gallery.

As all loudspeaker circuits are connected to the main power amplifier output via relays and multi-tapped auto-transformers, it is possible to adjust the power level to each individual zone, or group, irrespective of the main gain controls of the system, thus the degree of speech reinforcement in the galleries can be adjusted to a higher level.

The originating speech from the Assembly Hall is so arranged that it can be not only connected to the low-level distribution system but also to the interpretation system, to enable it to be heard in any one of four languages via headphones on a pre-determined channel. To enable any conference to be interpreted simultaneously into a maximum of four languages, four dual interpreter's booths are placed on the balcony overlooking the dais. Each interpreter is provided with a pair of headphones, which are energized from the amplifier used for the speech reinforcement system for the Assembly Hall; each interprets simultaneously into one of four pre-determined languages by means of a microphone in each booth, this being connected to one of four high-gain amplifiers associated with the main amplifying system. The main gain controls for the interpretation amplifiers are situated on the operator's control panel to enable a single operator to have means of controlling the interpretation as well as the speech reinforcement system. To compensate for differences in hearing ability of the audience, each headphone outlet socket is provided with a loud/soft switch.

It has already been mentioned that for the seating on the main floor of the Assembly Hall a loudspeaker has been arranged for each pair of seats, and these loudspeakers are mounted on bronze plates on the rear of the seat in front. As there is only one loudspeaker for each pair of seats, the bronze plates are fitted with two separate language selector switches and two loud/soft switches. To maintain freedom of access to each of the seats, the headphone jacks are fitted on the side of each seat.

Owing to the high stepping of the theatre-type seating in the public gallery it was found impracticable to accommodate the sound reinforcement loudspeakers and interpretation control points in a common unit at the rear of the preceeding row of seats. Accordingly, the loudspeakers have been provided in unobtrusive castings fixed on the rear of the seats, one such unit being provided for each two seats, whilst the alternative positions between the seats are provided with similar castings accommodating dual headphone outlet sockets and selector switches for the interpretation system.

For the other but no less important halls, similar facilities to those outlined for the main hall have been provided, but as the seating in them is movable it was not possible to consider fixing, permanently, loudspeaker units or simultaneous interpretation units. Therefore, each of these subsidiary halls has been provided with loudspeakers permanently fixed on the walls, or ceilings, with microphone circuits terminated in sockets at convenient positions. These

microphone and loudspeaker circuits are connected to a recessed control panel in each of the halls to enable a local amplifier and control equipment to be employed. These amplifiers and the main amplifying equipment are inter-connected.

In these halls, transportable interpretation equipment is available and this functions in a similar manner to that described for the main Assembly Hall but, owing to the design of the removable seating each chair is provided with a clip-on metal case accommodating four headphone jack sockets, each being fitted with a coloured disc, and each connected to one of the four language amplifiers.

Each of the microphones in the Assembly Hall has a separate single-valve pre-amplifier from which the signals are selected either at the operator's control panel or from an input selector panel on the main rack apparatus before being connected to the input of a buffer amplifier. This latter amplifier is provided in duplicate—as are the D.C. power units. A third buffer amplifier is provided for connecting tape, wire or disc recorders and can, naturally, be employed for play-back of recordings.

The output of the buffer amplifiers is taken to another control panel on the rack apparatus to enable G.P.O.-type tie lines to be used for receiving programmes from, or transmitting to, places beyond the confines of Church House. After selection of the required buffer amplifier, in which the required tone correction is applied, the signals are amplified by four identical power amplifiers; two of these are associated with the low-level distribution loudspeakers in the body of the Assembly Hall, the third is used for feeding the loudspeakers in the gallery, and the fourth for energizing the subsidiary loudspeaker circuits.

The system of speech reinforcement available in these halls is based on the principles evolved and incorporated by Tannoy Products (Sound Rentals, Ltd.), for the new House of Commons, the House of Lords and the new Legislative Assembly, New Delhi.

Manufacturers' Products

New Equipment and Accessories for Radio and Electronics

Variable Mains Transformers

A NEW range of ten variable transformers, built on the auto-transformer principle and fitted with graduated scales and knobs, has been announced by Philips Electrical, Ltd., of Century House, Shaftesbury Avenue, London, W.C.2. Each model is designed for a particular output in the range 130VA to 2,080VA, and can be supplied either as a bench type or as a type for building into an existing installation. In all models the secondary, or output, voltage can be varied from zero to 20 per cent above the nominal primary voltage.

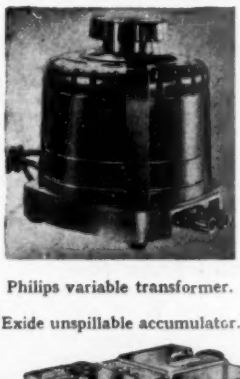

Philips variable transformer.

Unspillable Accumulator

IN the new Exide 2-V cell, type LPM4, designed principally for use in "walkie-talkie" apparatus, special precautions have been taken to prevent spillage of acid. The separators between the plates are constructed of a highly absorbent wood-fibre material that reduces the quantity of freely mobile acid in the cell, whilst the lid has been designed to prevent the free acid from escaping even when the cell is inverted. Another feature is the polystyrene container, which remains unaffected by wide variations of temperature and ensures a long life for the cell even under tropical conditions. The capacity of the LPM4 is 30 ampere-hours, and its charge rate is 2 amperes; it is made by Chloride Batteries, Ltd., Exide Works, Clifton Junction, near Manchester.

Exide unspillable accumulator.

Magnetic Sound Heads

POLE pieces cylindrically ground flush with the end caps are a feature of the tape recording heads produced by Bradmatic, Ltd., Station Road, Aston, Birmingham, 6, and it is claimed that this method of construction produces less wear in the edges of the tape.

Two types are available, 5RP for combined recording and playback, and 5E for erasure; the price is £3 5s each. The heads are reversible so that both gaps can be used to extend the life of the head. Bias and erase frequencies of 30 to 45 kc/s are recommended and the windings are of the high-impedance type. Adjustment is provided in both horizontal and vertical planes and the heads are quickly detachable without unsoldering connections.

In the range of tape recording heads recently introduced by Phidelity Magnetic Products, Ltd., 65-66, Chancery Lane, London, W.C.2, the windings are of low impedance and the mounting is designed for single-screw fixing. The following types are available: Type SA (£3 6s 6d) dual-purpose record and playback, gap 0.001in; Type SE (£3 4s 6d) supersonic erase head, gap 0.005in; Type SR (£3 10s) recording head with separate audio and bias windings, gap 0.001in; Type SP (£3 13s 6d) special recording head, gap 0.00025in.

Half track (¼in wide) heads can be supplied at 10s extra in each case.

Correction

In a note on the Belclere miniature transformer (January issue) the impedance ratio was wrongly given as 250:1. As can be seen from the turns ratio, this should have been 2,500:1.

UNBIASED

By FREE GRID

Television Pirates

I SEE that there is quite a to-do in the columns of some newspapers about the number of television viewers whom the G.P.O. alleges have not taken out licences. All the hoary and futile old remedies which were trotted out years ago to checkmate "sound" pirates are being brought forward once more. Nigh on eighteen years ago, on April 21st, 1933, I pointed out in these columns how futile they were. It is the peremptory demand for forty shillings in a lump sum that makes criminals of otherwise honest citizens, most of whom get their television sets on "easy terms." If the P.M.G. had the courage to declare an amnesty for all offenders and to issue to every viewer a card on which a tenpenny, or even a shilling, stamp could be stuck every week the response would be immediate. Would the football pools enjoy the success they do if their promoters peremptorily demanded that their patrons put down a year's "investments" in a lump sum?

Speed of an Electric Current

MANY people imagine that an electric current moves with almost incredible speed in an ordinary circuit. There is, in fact, much confusion in the average mind about the difference between the speed of an electron when it crawls along an ordinary circuit and when, like the man on the flying trapeze, it flies through the air—or at any rate the inside of one of the "tron" family—with the greatest of ease, urged on by accelerating electrodes and all that. The whole matter is, in its way, as interesting as the difference between an e.m.f. and a p.d. which "Cathode Ray" was discussing recently.

Many years ago (December, 1943) I stated to you on very good authority (Morecroft) that the speed of an ordinary electric current, whether it be propelled by a power station or a humble torch battery, worked out at about walking pace or, in other words, 3 m.p.h. or so. No technical pundit contradicted me; in fact, my statement subsequently received favourable comment from "Diallist" (February, 1944).

This slow speed means that in the case of the ordinary 50-cycle mains supply the electrons in a lamp filament would never leave it, but merely shuffle backwards and forwards a distance of about half an inch, and as for the electrons in a television aerial, why, they hardly have time to move at all, so slow is their speed in comparison with the tremendous sequential rapidity of the directionally alternating shoves which they receive.

My whole interest in this matter was aroused again when I read in *W.W.* (page 6, January issue) that electrical impulses travel along the nerves of our bodies at about 80-100 metres per sec, or 200 m.p.h. When I first read this my eyebrows went up in incredulous astonishment to such an extent that they pushed my bowler hat off, as for the moment I imagined this to be the actual electron speed.

A Red Letter Day

HAGIOLOGY is a subject usually ignored by this august journal, not because it is improper or has anything to do with mothers-in-law, as the less learned of you might think, for it isn't and it doesn't. The reason for its neglect might, to superficial thinkers, seem to be that it has little to do with "Radio, Television and Electronics," to quote the words on the cover of *W.W.*

Hagiology, which literally means the study of holiness, in practice deals with the saints and their works, and so is often referred to by the more particularized word hagiography. Now cynics might say that its connection with wireless seems almost as tenuous as the ether, but I hope to rout them as the Israelites routed the hosts of Midian.

Incredulous astonishment.

September 29th.

The reason for my discussing this subject in *W.W.* is that I am seeking a patron saint of wireless, for it is high time that we had one like other professions and industries such as the medical profession (St. Luke) and the motor industry (St. Christopher). I feel all the more strongly about this now that the craze is growing among garages and car-accessory dealers for selling plaques of St. Christopher, the patron saint of travellers, for bolting on to the radiator of a car.

The question is, of course, who can we choose to be the patron saint of wireless, and that is where you hagiologists and hagiographers may be able to help, for I have several ecclesiastical—and at least one episcopal—readers of this page. First we must decide whether we are going to emphasize the entertainment or the communications side of wireless. I feel it should be the latter. The obvious choice is, therefore, St. Michael, the archangel, for does not the word angel mean a messenger, and are not *all* other angels—including Gabriel, whom the Pope has proclaimed protector of radio communication—invariably coupled with his name?

With regard to an emblem for use on our sets, let us adopt something simple, striking and easily recognized, namely, a michaelmas daisy, and let us set aside September 29th each year for the opening of the National Radio Exihibition at Earls Court which, under the name of Michael-Mecca, might become as well-known as the old Radiolympia. But there is need for haste in the matter if we do not wish to see our profession and industry lapse into paganism, as it well may if the recent suggestion is carried out of adopting "Hermes, the messenger of the gods," as the symbol of the radio industry.

LETTERS TO THE EDITOR

The Editor does not necessarily endorse the opinions expressed by his correspondents.

Beveridge Report

THE B.B.C. monopoly of originating programmes is fundamental. Relay service licences forbid the organization of programmes and the Beveridge report recommends that this condition should continue (38).

Is it not, therefore, somewhat inconsistent to propose (33) that licences might be issued to approved public authorities or voluntary organizations to establish their own local stations? It is true that this proposal is only put forward for extra-high-frequency channels, but that does not alter the fact that it would be driving a tank through the B.B.C. monopoly.

HUGH TILLY.

London, N.W.2.

WHY all this fuss in the "Report of the Broadcasting Committee, 1949," about television in the cinema? Can anyone tell me why a Committee whose terms of reference are confined to broadcasting should concern themselves with matters that relate to point-to-point radio communications? As I see it, the Postmaster-General alone is empowered to say whether a cinema firm shall be granted a licence to transmit pictures by radio for public showing in its theatres. That has nothing to do with broadcasting; no more, in fact, than has the transmission of radio pictures for publication in newspapers.

"RADIOPHARE."

Thorn Needles

ACCEPTING the statement that the six illustrations in Mr. Pollock's article in the December, 1950, issue are to the same magnification and that the sapphire in Fig. 1 has in fact a point radius of 0.0025in, then it is surely futile to consider high-fidelity reproduction with a point that can only trace a standard modulated groove about as well as a pea in a roulette wheel.

I would not contradict the fact that "miniature thorns" cause less wear than harder points, or that they produce quite a nice noise from a record, but I have yet to experience accurate reproduction of the recorded sound using such a point.

C. E. WATTS.

Sunbury-on-Thames.

I HAVE read with interest A. M. Pollock's article, "Thorn Gramophone Needles," in the December, 1950, issue. There are various statements in the article which I cannot reconcile with experiments which I have performed using thorn styli.

It is assumed that the photographs illustrating the article are all reproduced to the same scale of magnification, and that the sapphire stylus is, in fact, 0.0025in tip radius. Use of this reproduction as the standard indicates that the photomicrographs are of the order of x50 diameters magnification.

From this it is deduced that the point of Fig. 2 is 0.0006in radius, with a probable error of 0.0001in. The average included angle of the styli shown is 20 degrees, and this will give a length of approximately 0.2in for the "cone" of the stylus, assuming the rondel is 1/16in diameter (or ⅛in long in the case of miniature thorns of 0.036in to 0.040in diameter).

Referring to Fig. 3, the dimensions (as far as I can measure) of the tip are 0.0012in radius; the bottom appears to be slightly rounded and would probably be a snug fit in the bottom of a modern recording.

Fig. 4 shows an apparent dimension of 0.0016in radius, which is not very much bigger than Fig. 3.

It has been my experience that a thorn stylus wears itself to the full dimensions of the groove in a very short period of time—considerably less than the playing time of a 12in record. The top groove width of a standard 78-r.p.m. record is 0.006in, and I would therefore have expected the photomicrographs to have shown results similar to this.

I must mention, in passing, that I have been unable consistently to obtain a tip of less than 0.002in radius, even using the finest grade of sandpaper, and attempting to use a diamond-loaded lap only resulted in the lap becoming choked. I would be interested to know how Mr. Pollock manages to grind such a fine point, and how many attempts are necessary before the thorn is judged to be satisfactory.

It is a well-known fact that if the stylus point is smaller than the bottom radius of the groove, the point will skate along the bottom of the groove and give rise to quite a lot of distortion and increased surface noise. Mr. Pollock's statement that "the principal difference is a slight change in the pitch or quality of surface noise, but little in the amount" when speaking of response of thorn against sapphire, bears out the statement, because if the pitch

TRIX
Quality
SOUND EQUIPMENT

MODEL T.101

12 Watt
High Fidelity
AMPLIFIER

This latest Trix model is a versatile high fidelity amplifier suitable for numerous applications. It incorporates special twin channel tone compensation circuits with controls for bass and treble boost, and push-pull output stage with inverse feedback, thus providing exceptional quality of reproduction.

Separate input sockets are fitted for gramophone pick-up, microphone and radio inputs with appropriate selector switch on the front panel.

A socket is also incorporated for H.T. and L.T. supply to feed an external mixer or radio feeder unit.

LONG-PLAYING RECORDS
The T.101 gives superb results with "long playing" records as well as standard types.

The output is high impedance, allowing several external speakers to be connected, on long lines without loss of power.

Full details of this amplifier and other models in the large Trix range of Sound Equipment available on request. Send for latest catalogues and price lists.

THE TRIX ELECTRICAL CO. LTD.
1-5 Maple Place, Tottenham Court Road, London, W.1.
'Phone: MUSeum 5817
Grams & Cables: "Trixadio, Wesdo, London."

AMPLIFIERS · MICROPHONES · LOUDSPEAKERS

of surface noise can be detected it means that there is some resonance in the system, and if the pitch of this resonance changes on replacing the stylus it must be connected with the mechanical system of the pickup. I have found that trying to play a 78 r.p.m. record with a 0.001in tip radius stylus often results in a high-pitched whistle, due to (a) the stylus skating along the bottom of the groove, and (b) the increased compliance between the stylus tip and the record groove lowering the resonant frequency.

It is common knowledge that the bottom radius of the groove is much "rougher" than the side walls, and for that reason the dimensions of styli are such that contact is not made with the bottom but only with the sides of the groove. A test was made, using the unmodulated grooves of the H.M.V. test records; an increase in noise level of between 6 to 8 db was observed when a 0.0025in tip radius stylus was replaced by one of 0.001in.

A resonance at 5 to 8 kc/s, with a sharp cut-off above it, gives brilliance often mistaken for extended top response, and whilst I am the first to subscribe to the opinion that the final criteria of performance of any reproducing device must be the aural results, a very good guide as to what results may be expected can be obtained from performance curves of the equipment, particularly frequency response and distortion curves. It would be very interesting to have these performance figures of the pickup using both a sapphire and thorn stylus. If Mr. Pollock is unable to make these measurements himself, I shall be very pleased to put the facilities of my laboratory at his disposal.

STANLEY KELLY.

Enfield, Middx.

Beginnings of Radar

SO long as your contributor "Free Grid" confines himself to the realms of fantasy in his well known and inimitable manner your readers can be trusted to look after themselves: they know when their legs are being pulled. But we have come to trust his accuracy (and memory) when he is dealing with facts. Surely he slipped up badly in your December, 1950, issue where he said, in dealing with the origin of radar, that the N.P.L. used radio waves to find the position of meteorological balloons in 1928. In *Wireless World* for March, 1945, Dr. R. L. Smith-Rose (who should know something about that) said "there was still lacking at the beginning of the 1930 decade a satisfactory practical demonstration that the reflection or scattering of radio waves from an object such as a ship or aircraft was of a sufficiently high order to be detected."

"Free Grid" can hardly plead he was using "radiolocation" in the modern sense to describe both echo and non-echo systems.

Nottingham. J. A. WALKER.

Television Visor

E. G. HARRISON (your December issue) may be interested to know that the pinhole disc (which is of course what he constructed) is often used by practitioners who examine eyes to investigate the possibility of improving the sight.

In principle the pinhole disc in front of the eye may be likened to a pinhole camera, the pinhole reducing the size of the blur circles and thus giving better definition. There is a critical size of hole where the reduction in illumination causes a loss of definition rather than a gain. Possibly it is this lack of illumination in home pictures that limits the use of the pinhole.

In Mr. Harrison's case it sounds as if he has a slight optical error and consequently the pinhole helps to cut down the size of blur circle produced. From his comment that he prefers to view blue to red, I would say that basically he is long-sighted. Blue is refracted more than red by an optical system and consequently blues are seen better by an eye that is long-sighted, and red better by an eye that is short-sighted. This fact is used in a sight-testing instrument known as the Duochrome test.

The size of pupil (or iris mechanism) is controlled by reflex action. The light reflex causes the pupil to become smaller in high illumination and larger in low illumination. It is never, however, a fixed size since as the eye adapts itself to the prevailing condition of illumination, so the pupil size varies, normally becoming slightly larger with time.

One other thing that may govern the definition of the picture is that the eye is not a perfect optical system. Consequently it suffers from aberrations. These are greater when the aperture is large.

If Mr. Harrison is interested in the subject he will find an excellent description of the pinhole in Fincham's "Optics" and of aberrations of the eye in Emsley's "Visual Optics."

F.S.M.C. (Hons.).

E.H.F. Broadcasting

YOUR correspondent R. C. Burnell asks in the January issue for "lots of a.m. broadcasting on e.h.f." This may be satisfactory if one is situated, as he is, some 18 miles from the transmitter. At 57 miles a.m. is very inferior, especially in signal-to-noise ratio.

I note that Mr. Burnell finds the a.m. signal to be the stronger. This is strange, as the relative powers of the transmitters are similar. As a deviation of 75 kc/s is used there should be some five times the audio voltage available from his demodulator.

If an unlimited number of low-power transmitters are used the "land line considerations" which limit the quality of transmission at present will be so multiplied as to be an insuperable barrier to real fidelity. Surely the answer in e.h.f. broadcasting is to have a few f.m. stations, which, by virtue of their superior system of modulation, will give complete coverage of the country.

There are no additional complications to f.m. receivers worth mentioning, and with the development of "know how" in this branch of the art I have no doubt they will become as docile as any a.m. receiver.

F. A. RUDDLE.

Reading, Berks.

E.H.F. Communications

WITH reference to J. R. Brinkley's letter in the October, 1950, *Wireless World*:—

It is obvious that Major Armstrong was writing for home consumption and was considering American practice when he stated that "the use of f.m. for police communication is universal." Universal is perhaps an unfortunate choice of adjective.

The amount of a.m. mobile radio telephone equipment manufactured in this country may be greater than the production of equivalent apparatus for f.m. but, if considered together with American production, it is very small, and therefore Major Armstrong's contention is substantially correct.

In the British market, the a.m. system was the first in the mobile radio telephone field and, as a result, succesful systems were available for demonstration to potential customers before f.m. systems were ready. The performance of the a.m. systems was satisfactory and was, in some cases, enhanced by the technique of using comparatively high-power base station transmitters and low sensitivity mobile receivers. Under these conditions, the advantages of f.m. are not so readily discernible, since the received field strength at the mobile station is so high that the ambient noise level is unimportant and the improved performance of an f.m. system is less noticeable than it is under poor received signal-to-noise ratio conditions. Also, the comparatively low receiver sensitivity tends to set the ultimate limit to the smallness of

the usable signal, whereas receivers of the highest sensitivity used for mobile applications generally have this limit set by the ambient noise level, the effect of which must be more marked with a.m. than with f.m.

In any case, an a.m. system is more expensive and gives less satisfactory performance for the following reasons:—

F.M. Transmitter.—No high power modulator is required but a further stage of high frequency multiplication is used.

Less power is required for a given r.f. output with a consequent reduction in size and weight.

F.M. Receiver.—For a given noise factor, the minimum useable signal is smaller.

The effect of local interference disappears at much smaller distances with f.m. than with a.m.

Screening of the electrical system of the vehicle is unnecessary with f.m.

H. N. GANT.

Southall, Middx.

Power-cut Radio

IN the January issue of *Wireless World* "Free Grid" says he would like to see a mains/battery receiver with automatic change-over to deal with power cuts. I am at the moment listening to a 1939 Pilot "Twin Miracle" receiver which uses a relay circuit in the feed system so that the set starts up on the battery and switches to the mains when the rectifier has warmed up. Should the a.c. (or d.c.) mains supply fail the relay releases and the battery is brought into circuit again. I believe there are other sets arranged to do the same thing but do not know if any one has been put into production since the war.

I. G. BENBOUGH.

Reading, Berks.

Air Traffic Control Records

AT a demonstration of the new sound recording equipment adopted by the Ministry of Civil Aviation, and described by you in the September, 1950, issue, the impression may have been given that the International Civil Aviation Organization were responsible for recommendations concerning the possibilities of erasure and the type of recording medium to be employed.

I think it should be made clear that the I.C.A.O. recommendations on the subject refer only to the provision of recorders, and do not stipulate whether or not the recording medium shall be incapable of being erased or altered without visual evidence of interference.

E. L. BADDELEY,
Senior Press Officer,
Ministry of Civil Aviation.

London, W.C.1.

In Response to Popular request

WE illustrate and list a number of popular **BULGIN** Components which are at the moment available from stock. Owing to the uncertainty of delivery of raw materials they may not be repeated.

A

A UNIT COILS

Use with up to .0005μF. variable capacitor for tuning, *3–30pF. (μμF.) trimming. Padding cap. gives 465 Kc/s I.F.

List No.	λ range in *m*	Essential pF. Range*	Pad	Coil Description‡
C.87	6–12	30–120	Nil	Osc.
C.88	11–22	30–120	—	Signal
C.89	11–12	30–120	Nil	Osc.
C.90	20–50	50–250	—	Signal
C.91	20–50	50–250	0.005μF.†	Osc.
C.92	45–100	50–250	—	Signal
C.93	45–100	50–250	C.P.7	Osc.
C.94	80–220	70–550	—	Signal
C.96	200–550	70–550	—	Signal
C.97	200–550	70–550	C.P.4	Osc.
C.103	1,000–2,500	70–550	—	Signal
C.104	1,000–2,500	70–550	C.P.2	Osc.

* For λ range given; .0005μF. may be used throughout.
† Fixed capacitor used.
‡ Both types double-wound.

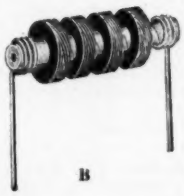

B

B R.F. INDUCTORS IN ORDER OF INDUCTANCE*

List No.	Inductance*	Type, etc. Scrnd.	Iron-Cored	Self-supg. in wiring	Approx. pF.	Max. d.c. mA.	d.c. Ω
S.W.146	0.2 mH.	No	No	Yes	0.5	160	9
S.W.48	2.0 mH.	No	No	Yes	0.5	160	40
S.W.49	15.0 mH.	No	No	Yes	0.8	50	250
S.W.144	30.0 mH.	No	No	Yes	1.0	50	350

* Interpretation of lumped-Z measurement; not for resonance calculations; measured at 1 Kc/s.

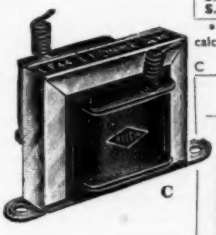

C

C IN ORDER OF INDUCTANCE PER MODEL:—

List No.	Henries at	d.c. mA.	V.*	d.c.Ω	Size O.A.	Fixing
A.F.22	220	0	—	—	2 5/16" × 1" × 1 5/16" high	2×0.120" Ø at 1 1/16" crs.
	50	to				
	68	0.7				
L.F.44	0.25	500	3–4	7	3 3/16" wide,	
L.F.93	37	100	3.75	37.5	1 1/4" deep,	
L.F.43	37	100	3.75	37.5	1 15/16" high	Holes .180" Ø
L.F.39	8.5	60	24	400		Centres 2 1/4"
L.F.67	5	60	12.6	210		
L.F.68	7	50	12.5	250		
L.F.69	10	45	13.5	300	2 11/16" wide,	
L.F.70	15	35	20	580	1 1/4" deep,	Holes .150" Ø
L.F.71	20	30	20	660	1 1/2" high	Centres 2 1/16"
L.F.72	40	20	25	1250		
L.F.74	50	15	22	1500		

* Voltage-drop at current stated, where significant. † Tapped at: 0.5, 1.0, 1.5 2.0, 2.5 H. L.F.93 and 43 are used for tone control, etc.

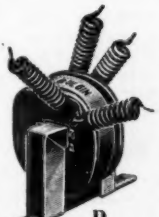

D

D TRANSFORMERS A.F.

List No.	Use	Inductance, H*	Turns Ratio†	Notes on uses, details
L.F.48	Inter-valve	20–30	1 : 2	Double-wound, 1 mA. max.
L.F.49	Microphone	0.25	1 : 35, 70	Double-wound, 50 mA. max.

* Taken at 1 Kc/s and 1 V.a.c., no d.c., by interpretation of lumped impedance (subject to tolerances of ± 50%) of pri. or of effective-pri. Not offered as data for resonance calculations
† Tolerance ± 20%.

Send now for full Catalogue, Lists and Prices, **REF. 185/D.W.W.**, price 1/- post free.

MANUFACTURERS OF RADIO & ELECTRONIC COMPONENTS

BULGIN *Components*

A.F. BULGIN & CO. LTD
BYE-PASS ROAD BARKING
TELEPHONE [illegible] 3474

RANDOM RADIATIONS

By "DIALLIST"

"*M*" *Regions*

IT SEEMS THAT I was not quite right when in a recent note in these columns I attributed the November radio blackout to ordinary sunspots. No less an authority on ionospheric conditions than T. W. Bennington sent me some very interesting information about the real cause. This is news to me; and as I expect it will be news to many readers as well I gladly avail myself of his permission to pass it on. Some of the disturbances which give rise to interference with long-distance radio occur when there are no visible spots, or at any rate none of important size, on the sun's disc. That they are due to solar activity is beyond doubt; nor can it be doubted that particular regions of the sun's surface are responsible, for such disturbances take place when one of these "M" regions, as they are called, is near the central meridian of the sun. There is peace and quiet when the "M" region responsible has been carried by the sun's axial rotation to the side away from the earth; but the trouble often breaks out again when this "invisible spot" arrives once more on the side facing us. The November disturbance was actually due to the fifth return of an "M" region which first made its presence felt in the middle of July, 1950.

Times and Seasons

Blackouts attributable to the familiar visible sunspots are usually most frequent and most severe near the "maximum" of one of the eleven-year cycles. These "M" regions, however, generally cause disturbances after the maximum has been passed and when the decline towards the minimum is under way. They may even continue right on to the minimum period. Exactly what "M" regions are and at what kind of levels in the sun they are developed both seem still to be matters of conjecture. Visible sunspots are believed to be great vortices in the mass of incandescent gases that forms the photosphere. Since they are not visible it seems likely that "M" regions are indications of disturbances taking place far below the surface. I would like to know more about them—and so, I expect, would readers. Do they, for instance, go (as sunspots so often do) in pairs of opposite magnetic polarity? If so, do they show the same queer behaviour as visible sunspots? In these the relative positions of the poles are always the same all through an eleven-year cycle, but a reversal takes place in the following cycle.

Second Thoughts

NOW THAT I HAVE had time to digest the revised edition of "Letter Symbols for Electronic Valves" (B.S.1409: 1950), published by the British Standards Institution, I do not feel anything like so happy about it as I did about the original edition of 1947. The 1947 symbols were simple, logical, straightforward and easily memorized. They were a boon to writers (and readers) of books and articles concerning valves, for they meant that the same thing or property or quality was always denoted by the same unmistakable symbol. They appeared to offer a real hope of a standardization so complete and so satisfactory that it would embrace all technical writing from the "without-tears" popular book to the most learned and most excruciatingly mathematical treatise. Clearly, too, they would be of very great value to valve manufacturers for the presentation in concise form of the nature and performance of their products. To be really useful, symbols must provide a genuine short cut to the point which the writer wishes to make, and his reader wants to grasp in the shortest time and with the least unnecessary mental effort. The whole purpose of symbols is defeated if they become so numerous that considerable effort is needed to commit them to one's memory.

Going Too Far

Most languages are reasonably easy to read or write because their alphabets consist of only some 25-30 letters. The new edition of "Letter Symbols for Electronic Valves" lists over 100 signs and symbols—and that seems to be going too far. It would take quite a bit of practice to use them easily and correctly. It is stated on the cover that they are intended mainly for use in valve catalogues and similar technical literature. The words "similar technical literature" mean, presumably, other technical matter drawn up and issued by radio manufacturers. Even so, I very much doubt if they will make the reader's task easy. The golden rule of making each symbol stand for one thing and one thing only has gone by the board. Thus *m* can signify inner metallic coating or internal mutual inductance; *h*, heater, hexode or heptode; *r*, rectifier or internal resistance; *s* is an internal shield, but S (which should logically represent an external shield) is the sensitivity of a photoelectric cell or c.r. tube.

Marine Radar Again

LETTERS FROM SEAFARING readers of *W.W.*, who comment on the note I wrote some months ago on the use and abuse of ships' radar, continue to come in from ports in distant parts of the world. Some take me to task for having (as they say) stressed the accidents due to the mis-use or non-use of radar equipment, rather than the cases, infinitely larger in number, in which accidents were avoided by the correct use of the radar set. They accuse me of undermining confidence in radar. If I gave any such impression, that must be due to sheer bad writing on my part; for there can be no firmer believer than I in the efficacy of radar as a preventer of disasters at sea and in the air—if full use is made of it. In marine radar that depends very largely on the appreciation by navigational officers of its possibilities and of the accuracy of the information that it supplies. I contended that too few navigators bothered to familiarize themselves with the radar presentation by making it a rule to have the set working *and to study the screen closely* either when entering harbour or when passing near another ship on the open sea in clear weather.

Practice Makes Perfect

My correspondents include both navigating and radio officers. Many of them, I am glad to say, tell me that in their ships clear-weather practice with radar regularly takes place. Some give thrilling accounts of the regular and successful use of radar in narrow waters where foul weather conditions are frequent. Some bear out my contention, telling of senior officers who look on radar as just another of those newfangled gadgets, installed to make the poor sailor's life more difficult.

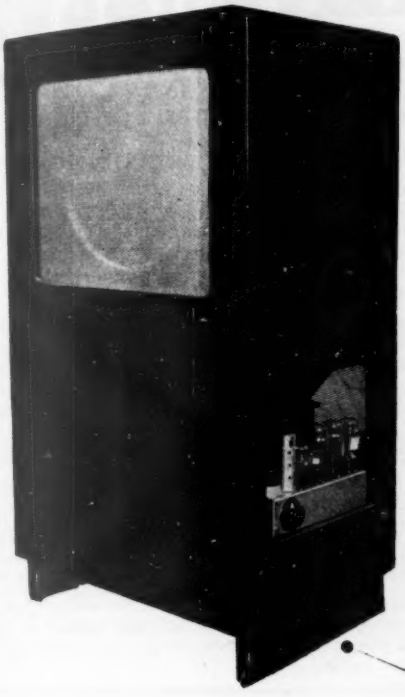

THE NEW

B. B. C. MONITOR LOUDSPEAKER UNIT*

USES A

LEAK TL/12 AMPLIFIER

* *B.B.C. Pat. Application No. 24528/49*

Enquiries for this equipment are invited from overseas broadcasting and recording companies and film studios.

Professional and home applications of the TL/12 amplifier and the new RC/PA/U pre-amplifier are described in a new booklet, W/U, available shortly from your dealer or from us.

H. J. LEAK & CO. LTD. (Est. 1934), Brunel Rd., Westway Factory Estate, Acton, W.3

Phone : SHEpherds Bush 1173/4 Telegrams : Sinusoidal, Ealux, London Foreign : Sinusoidal, London

PREMIER RADIO COMPANY

MORRIS & CO. (RADIO) LTD.

LONG RANGE TELEVISOR KITS FOR—

LONDON & BIRMINGHAM MODELS STILL AVAILABLE

USING VCR97 —— £17 - 17 - 0 —— INCLUDING TUBE

(CARRIAGE & PACKING 15/-)

As is usual in Premier Kits every single item down to the last Bolt and Nut is supplied.
All chassis are punched and layout diagrams and theoretical circuits are included.

FIVE EASY-TO-ASSEMBLE KITS ARE SUPPLIED :—

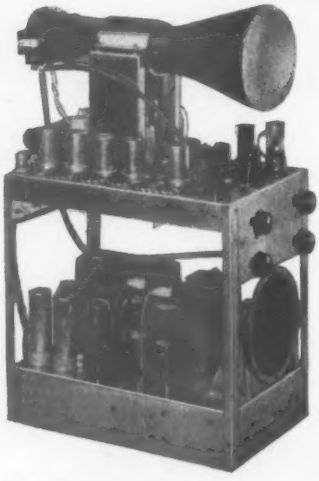

"ELECTROSTATIC" CONSTRUCTION BOOK 2/6

VISION RECEIVER with valves, carriage 2/6.....	£3 13 6
SOUND RECEIVER with valves, carriage 2/6.....	£2 14 6
TIME BASE with valves, carriage 2/6.....	£2 7 6
POWER SUPPLY UNIT with valves, carriage 5/-.....	£6 3 0
TUBE ASSEMBLY, carriage and packing 2/6.....	£2 18 6

This unit includes the VCR97 Tube, Tube Fittings and Socket and a 6in. P.M. Moving Coil Speaker with closed field for Television. The instruction book costs 2/6, but is credited in a Kit for the complete Televisor is purchased.

Any of these Kits may be purchased separately ; in fact, any single part can be supplied. A complete priced list of all parts will be found in the instruction book.

20 Valves are used, the coils are all wound and every part is tested. All you need to build a complete Television Receiver is a screwdriver, a pair of pliers, a soldering iron and the ability to read a theoretical diagram.

The following sensitivity figures prove that the Premier Televisor Kits are capable of reception at greater distances than any other standard commercial kit or receiver whether T.R.F. or Superhet.

VISION RECEIVER.

Sensitivity	25μV. for 15V. peak to peak measured at the Anode of the Video Valve.
Sound Rejection	Better than 40 db.
Adjacent Sound Rejection ...	Midland Model. Better than 50 db.

SOUND RECEIVER.

Sensitivity	20μV. Vision Rejection, better than 50 db.

Conversion to the Scottish Frequency will only be a matter of Coil alteration. Free details will be available when the frequency is announced.

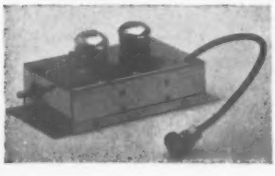

NEW PRE-AMPLIFIER FOR FRINGE RECEPTION AREAS

We can supply the complete kit of parts to make this wide band width Pre-Amplifier using 2-717A Pentodes. For use with Televisors able to supply 130v. 20 mA., H.T. and 6·3v., ·3 amps. L.T.

Completely screened. Includes valves, chassis, diagrams, etc. **27/6**

SEPARATE POWER SUPPLY UNIT KIT IF REQUIRED.
(REQUIRED BY BOTH PREMIER KITS)

21/-

When ordering Televisor or Pre-Amplifier Kits
PLEASE STATE IF THE LONDON, BIRMINGHAM OR HOLME MOSS MODEL IS REQUIRED

CALLERS TO
207, EDGWARE RD., W.2 Phone : AMBassador 4033 (Open till 6 p.m. Saturdays)
AND **152-153, FLEET STREET, E.C.4** Phone : CENtral 2833

Terms of Business : Cash with order or C.O.D. over £1. Send 6d. Stamp for list.

PREMIER RADIO COMPANY

MORRIS & CO. (RADIO) LTD

HOLME MOSS—ARE NOW AVAILABLE

USING 9" OR 12" MAGNETIC C.R. TUBES

£19·19·0 *including all parts, valves and loudspeaker, but excluding C.R. TUBE*

(Carriage and Packing 15/-)

CIRCUIT DETAILS

The Vision Receiver consists of 4 R.F. stages (EF54's) which are followed by a Diode Detector and Noise Limiter (6H6) which is directly coupled to the Video valve (EF54).
Complete Kit with valves, **£3/16/0.**
Carriage and packing 2/6.

The Sound Receiver comprises 3 R.F. stages (6SH7's) followed by a Double Diode Triode (6Q7), which acts as Detector and L.F. Amplifier. A Noise Limiter (EA50) is also incorporated. The output valve (6V6) drives a 10in. P.M. Moving Coil Speaker with closed field magnet, which is included in the time Base Kit.
Complete Kit with valves, **£3/1/0.**
Carriage and packing 2/6.

The Time Bases employ blocking oscillators on both Line (6SH7 and 807), and Frame (VR137 and 6V6). E.H.T. (Non-lethal) is taken from the Line Output Transformer through a voltage doubler employing two valves (VU111). The Sync separators are 6H6 and 6V6.
Permanent Magnet Focusing.
Complete Kit with valves, **£8/5/6.**
Carriage and packing 5/-.

The Power Supply is from a double-wound mains transformer completely isolating the receiver from the mains. The H.T. Rectifier is a 5U4G.
Complete Kit with valves, **£4/16/6.**
Carriage and packing 5/-.

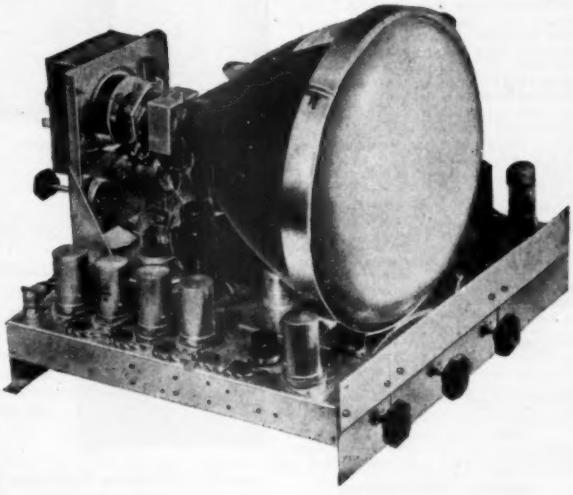

"MAGNETIC" CONSTRUCTION BOOK 3/-

EACH KIT OR INDIVIDUAL PART AVAILABLE SEPARATELY

WELL MADE WALNUT FINISH
PEDESTAL CABINETS
ARE AVAILABLE FROM STOCK

FOR	6in. TUBE KIT	£5. 10. 0	CARRIAGE & PACKING 7/6
,,	9in. ,, ,,	£6. 15. 0	
,,	12in. ,, ,,	£8. 8. 0	

ALL POST ORDERS TO OUR NEW FACTORY AT
740 HIGH RD., TOTTENHAM, N.17. *TOTTENHAM 5371*
TERMS OF BUSINESS, CASH WITH ORDER, OR C.O.D. OVER £1.

PREMIER RADIO COMPANY

MORRIS & CO. (RADIO) LTD.

BUILD A PROFESSIONAL LOOKING RADIO AT LESS THAN HALF TODAY'S PRICE

Two modern receiver kits are available. A three-valve, plus rectifier, T.R.F., and a four-valve plus rectifier superhet. Both are housed in attractive Bakelite Cases, size 12in. x 5in. x 6in.
Each Kit is complete in every detail, nothing has to be made or improvised. Easy to follow, point-to-point diagrams are supplied, making construction very simple. They are for use on 200-250 volt mains and both A.C. and Universal Models can be supplied.
The Dials are illuminated, and the receivers present an attractive appearance.

T R F Valve line up:—
6K7 H.F. Pentode.
6SH7 Detector.
CV1510 Beam Power Output in the A.C. model.
The A.C./D.C. Output Valve is 12A6. Both use Metal Rectifiers.
Waveband coverage is for the Medium and Long bands.
Price £4/19/6. (Carriage and packing 2/6.) With Walnut or Ivory Cabinet.

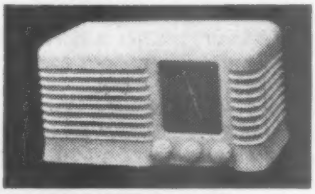

SUPERHET Valve line up:—
6K8, 6K7, 6Q7 and CV1510 Beam Power Output in the A.C. Model.
The A.C./D.C. Output Valve is 12A6. Both use Metal Rectifiers.
Waveband coverage is 16-50, 190-540 and 1,000-2,000 m.
Price £6/19/6. (Carriage and packing 2/6.) With Walnut or Ivory Cabinet.

MOVING COIL METERS.

All 2½in. outside diameter.

50 mA	8/6	40 amp.	7/6
20 amp	7/6	40 v.	5/9
20v.	5/9		
500 microamps	7/6		

All 3½in. outside diameter.

1 mA	15/11	30 mA	10 6
200 mA	8/6	500 microamps	19 6

Thermocouple meters: 2½in. outside diameter.

3 amp.	5/–	3.5 amp.	5 –
3½in. 2 amp. ...	8/6		

Electrostatic ditto, 5K, 4½in. ..... 50 –

METAL RECTIFIERS.

Bridge type:

2 v. .5 amp.	2/–	6 v. 1 amp. ...	4/–
12 v. 1 amp.	8/–	12 v. 4 amp ...	17/6

Half wave:

260 v. 30 mA C.T.	4/–	300 v. 75 mA	5/–

E.H.T. Pencil Type:
Output 650 v. 1 mA, 4/7 each.
1,000 v. 1 mA, 6/- each.
Outputs given are half wave. Two of either Rectifiers can be used in voltage doubling.

CRYSTAL MICROPHONE.

An entirely insulated crystal microphone which can be safely used on A.C./D.C. amplifiers. High impedance. No background noise, really natural tone. The ideal Mike for tape, wire and disc recording and sound projectors. **Price 22/6.** (Price error in previous issue.)

R.107 RECEIVERS in partly dismantled condition. A wonderful spares investment for R.107 owners, 50/- each. Only available to callers.

POWER PACKS, input 200-250 v., 50 cycles. Output 330 v. 60 mA, 6.3 v. 2-3 amp. and 6.3 v. .3 amp. for 6X5 rectifier. Mounted on metal chassis approx. 6 × 6in., fully smoothed, 19/6 each; 6X5 rectifier, 5/- each.

WELDING OR GROUND HEATING TRANSFORMERS. Input 230 v. Output 15 v. 60 amp. Tapped at 14-13.5-13 v. 7½ × 7 × 6in. Weight approx. 50lb. Price 85/-. Carriage and packing, 15/-.

SUPER QUALITY TELEVISION MAGNIFYING LENS. To suit 5in., 6in or 7in. tubes. Increase picture size considerably, 25/- each.

E.H.T. TRANSFORMER. Output 1,000 v. at 1 mA, with two 4 v. 1.5 amp. L.T.s. In power supply this will give an output of 1,500 v. halfwave or 2,500 v. fullwave. Price 17/6.

PORTABLE L.S. CABINETS.

To take 10in. Speaker. Internal measurements 16½in. × 13½in. × 5½in. There is also a small compartment 16½in. × 5½in. × 2½ih. at the top for Cables, etc.
This is an ideal Cabinet in which to construct a portable amplifier, and a chassis specially made to fit the Cabinet can be supplied if required.

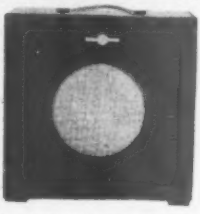

CABINET 10/6
Carriage and Packing 2/6

CHASSIS to fit size 16½in. × 5½in. × 2in. deep. 6/6

NEW A.C. ALL-WAVE SUPERHET KIT.

7 valves (plus rectifiers) for 200-250 v. 40-60 cycles A.C. mains.
4 wavebands, 13.6-52, 51-190, 190-540 and 900-2,100 metres.
Pick-up input. Uses 6K7, 6K8, 6K7, 6B8, 6J5 and two 6V6 in push-pull, giving an output of 10 watts.
Specially designed O.P. transformer to match 6V6s to 3 and 15 ohm speakers.
Negative feedback is applied over 3 stages giving a high fidelity output. Tone control is incorporated, £14/5/-.

Also available for A.C./D.C. mains. Specification as above except that valve line-up is 6K7, 6K8, 6K7, 6Q7, 6J7, two KT33C. In Kit form at £13 8.10.

P.M. MOVING COIL LOUDSPEAKERS.

(3 ohm v/c.)

2½in. Personal Type (15 ohm v/c.)			15/–
3½in. J.P.	9/–	5in. Truvox	10 –
5in. Rola	12/6	6in. Truvox	12 6
8in. Plessey ...	14/6	10in. Rola ...	23 6
12in. Truvox ...	39/6		

5in. Truvox in handsome plastic cabinet (cream or walnut), 6 × 6in. with v./control, 27/6.

WILLIAMSON AMPLIFIER KIT.

We can supply the Kit of Parts for the latest version of this famous amplifier complete in every detail for £10/10/- with valves, output and mains transformers.

WILLIAMSON AMPLIFIER OUTPUT TRANSFORMERS to specification, 63/-. Mains Transformers, 45/-.

NEW BABY ALARM KIT.

A complete Kit of Parts in plastic cabinet to construct a device to enable baby's cries or even breathing to be heard in any selected room in the house. Consists of a 2-valve amplifier (mains operated) with midget telephones which are used as microphone and loudspeaker. May be left permanently connected. Complete with valves, circuit and instructions for 200-250 v. A.C. mains, 55/-.

GRAMOPHONE AMPLIFIER KIT.

Consists of complete Kit of Parts for a 2½ watt mains-operated 2-stage Amplifier for use with any type of pick-up. Volume and tone controls are incorporated. Output impedance is 3 ohms.
Cat. No. AMP147. Price complete, 59/6.
For 200-250 v. mains with valves and diagrams.

BATTERY CHARGER KITS.

All incorporate Metal Rectifiers. Transformers are for use on 200-250 v. 50 cycle mains.
To charge 6 v. Accumulator at 1 amp. with resistance supplied to charge 2 v., 22/6.
To charge 12 v. accumulator at 1 amp., 27/6.
To charge 12 v. accumulator at 4 amp. with resistance and meter, 75/-.

METER KIT
A 500 MICROAMP M/C.

METER, with separate High Stability, High Accuracy, Resistors to measure, 15, 60, 150 and 600 volts D.C. Scale length 1¾in., diameter 2½in. 10/- the complete kit.

ALL POST ORDERS TO OUR NEW FACTORY AT

740, HIGH ROAD, TOTTENHAM, N.17. Tottenham 5371

Terms of Business: Cash with Order, or C.O.D. over £1

PREMIER RADIO COMPANY

MORRIS & CO. (RADIO) LTD.

Great Clearance Offer

OF BRAND NEW & PERFECT

Cathode Ray Tubes & Valves

CATHODE RAY TUBES

C.V. No.	Civil'n No.	Dia. in inches	Focus	Defn.	EHT	O.K. for T.V.	Price	Rail, Pkg. & Insur.
279	—	2.75	E.S.	E.S.	1450	Expmtl.	10/-	2/6
600	5CPI	5	E.S.	E.S.	2 kV.	Yes	25/-	2/6
601	5BPI	5	E.S.	E.S.	2 kV.	Yes	27/6	2/6
817	3EPI	3	E.S.	E.S.	2 kV.	Yes	15/-	2/6
—	VCR528	11.5	E.S.	Mag.	6 kV.	No	60/-	12/6
1140	VCR140	12	Mag	Mag	4 kV.	Yes	90/-	12/6
1384	—	11.5	E.S.	E.S.	4 kV.	Expmtl.	40/-	10/-
1511	VCR511	11.75	E.S.	E.S.	4 kV.	Expmtl.	60/-	10/-
1516	VCR516A	9	Mag	Mag	5 kV	No	40/-	10/-
1522	VCR522	1.75	E.S.	E.S.	800 v.	Yes	15/-	1/6
2880	EM14/1	3	E.S.	E.S.	800 v.	Yes	17/6	1/6
3776	—	5.25	E.S.	E.S. Mag	4 kV.	Expmtl.	20/-	2/6

Acorn Valves: Type **956**, 2/6 each 20/- per dozen. Type **958A**, 3/- each, 24/- per dozen. Types **9004**, **9005**, 3/6 each.

V/M Pentodes **CV 1124** (MSPEN), 4 v. 7-pin base, 5/- each, 36/- per dozen.

Output Pentodes. Type **CV321**. Surplus Equivalent of the KT66 6/6 each, 60/- per doz. No extra charge for matching.

EHT Rectifiers. Type **2X2/879**, 2/6 each, 20/- per dozen.

Mullard **MW 22/3** Television Tubes, 9in. diam, Magnetic. Usual price £11/10/-. To clear, £6/17/6, plus 12/6 carriage, packing and insurance.

VCR 517C C/R Tubes 6½in. Diam.: Green/Blue Screen. Excellent for TV, 20/-. Base 2/6, carriage, packing and insurance 5/-.

In addition we offer the following tubes (for one month only) at the ridiculous price of 5/- each (preferably to callers only as packing, carriage and insurance amounts to 7/6). Types available. **ACR1, ACR2, ACR2X, ACR8, ACR1381.**

VCR 97 C/R Tubes. Have slight cut-off making them unsuitable for T/V use, otherwise perfect, 10/- each. Base 2/6, plus 5/- carriage, packing and insurance.

12in. Electrostatic Television Tubes. Type **63D/S**, Green Screen. 3KV Max. EHT, £3/10/-. Base 2/6, plus 15/- carriage, insurance and packing

UHF Oscillators, Type **RL18**, 5/- ea., 40/- per dozen.

Thyratrons, Type **CV 1141**, 6/6 each, 50/- per dozen. Type **CV 22**, 20/- each.

1-Kilowatt Pentodes. Type **861**, 20/- (callers only).

UHF Triodes. Type **7193**, 1/6 each, 12/- per dozen.

Bayonet Base (Side Contact) Output Valves, Type **EL50**, 6.3 v., 5/- each, 36/- per dozen.

Output Triodes Type **DET 5**. An excellent replacement for PX25, 10/- each, 75/- per dozen. Type **P27/500**, practically identical with the PX25A, 10/- each, 75/- per dozen.

25 watt Pentodes. Type **PT 25H**. 4 v. 400 v., 3/- each, 24/- per dozen.

Miniature Valves **CV3830** (XH 1.5), 2/6 each, 20/- per dozen. **9002**, **9003**, 3/6 each.

Transmitting and Special Purpose Valves Special Offer. Types **8012**, **830B**, **878**, **705A**, **843**, **1625**, **1616**, **4C27**, **703A**, **EL266**. Any of the above 5/- each.

Type **E1148**, 1/6 each, 12/- per dozen. Type **CV52**, 4/6 each.

Bayonet Base (Side Contact) Low Noise H.F. Pentode. **CV1123** (EF8), (VR123), 6.3 v., 5/- each, 36/- per dozen.

T.R. Box. Type **CV115**, 5/- each. Magnetron, **CV186**, 10/- each.

ARP3 Valves, 13 v. .2A HF Pentodes, 3/- each, 24/- per dozen.

SPECIAL OFFER —NOW AVAILABLE

C.R. Tubes, Type ACR13 (CV1385). A perfect replacement without alteration for the VCR97. Guaranteed free from "cut-off," price 35/-. Send 3d. for latest valve list of hundreds of types at lowest prices.

TRANSMITTING VALVES

813	£3	707B	£3	715A	£3
723A/B	£5	U19	6/6	HF300	£3
1622	8/6	327A	£1	CV19	30/-
1B24	£3	357A	£3	VP58A	£3
3B24	£1	282A	£2	803	15/-
		2E22	6/6		

TERMS OF BUSINESS

Postage and Packing is free for orders over £2 in value unless otherwise stated. Under this amount, please include 1/- for orders up to 10/- and 1/6 for orders over 10/-. C.O.D. orders cannot be sent under 20/-.

152-153, FLEET STREET, E.C.4. *Phone: CENtral 2833*—**and at—207, EDGWARE RD., W.2.** *Phone: AMBassador 4033*

207, Edgware Road is open until 6 p.m. on Saturdays.

OUR CATALOGUE PRICE 6d. CONTAINS ALL THE NEWEST RADIO EQUIPMENT.

ELPREQ SPECIALS

TRANSFORMER SNIP

A Universal replacement by a very famous maker. Standard mains nput secondaries: 350-0-350 at 80 mA 6.3 tapped at 4 v. 4 amp. and 4 v. at 3 amps. Special price for one month only **13/6** plus 1/- post. Note this is a half shrouded drop through type.

SPECIAL MATCHING TRANSFORMER

For matching output valve such as the 3S4, 3V4, 1S4, etc., to normal 2½in. and 3in. speaker. Size less than 1 cubic inch. Ideal for personnel sets. Price **5/-** each.

INSTRUMENT RECTIFIER

Full wave 5 mA. Price **4/6** each.

12 v. ACCUMULATOR

25 amp hour, made for the Admiralty, new and unused—in ebonite case, size 10in. × 10in. × 4½in. Price **37/6**, carriage etc., 5/6.

TWO VOLT ACCUMULATORS

Made for the forces by one of the most famous firms in the World. 15 amp hour size approx. 6in. × 1½in. square in ebonite case, precharged, only need filling with acid, **4/9** each, plus 9d. post and nsurance. Six or more post free.

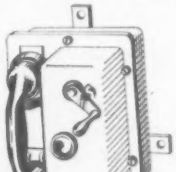

EX-ROYAL NAVY SOUND POWERED TELEPHONE

These require no batteries, and will go for long periods without attention. Complete with generator and sounder which gives a high pitched note, easily heard above any other noise. Also fitted with an indicator lamp which in quiet situations can be used instead of the sounder, or where several 'phones are used together, will indicate which one is being called. Size 7½in. × 9in. × 7½in., wall mounting, designed for ships use, but equally suitable for home, office, warehouse, factory, garage, etc., etc. Price **37/6** each, plus **3/6** carriage

METER FOR A.C. CURRENT

In all probability you have very often needed a meter to measure A.C. current. Due again to Government surplus, we are able to offer such a meter. It is a 2½in. movement, in bakelite case flush mounting. It reads 0-9 amps and is suitable for either A.C. or D.C. work. On checking A.C. current we found the accuracy compared very favourably with an expensive instrument. We have only a limited quantity of these, price **12/6** each.

POWER PACK FOR ALL-DRY RECEIVERS

Output 90 v. h.t. and 7.5 v. l.t. using metal rectifiers. Fitted into a bakelite case size only 3¾ × 2¾ × 1¼ complete with flex and mains input plug. Suitable for A.C. or D.C. mains. Price **19/6.**

3 PIN PLUG AND SOCKET

Very useful for connecting up gramophone pick-ups, extension loudspeakers, etc. We can offer this at a really knock-out price, namely **8d.** per pair.

SENTERCEL METAL RECTIFIER

Type MR1. 60 mA at 115 v. useful for valve replacements, etc. metal. Limited quantities, **4/6** each. 230 v.—80 mA, type **5/6.**

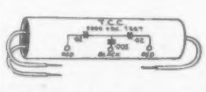

SUPPRESSOR

The multiple condenser illustrated is designed and made to suppress the sparks caused by devices such as vacuum cleaners, hair driers, motors, which cause interference with radio and television. Our price **1/6** each.

HEAVY DUTY STARTER SWITCH

This is the type fitted in many older motor cars, made in fact by the famous "O.A.V. Co." This will handle 50 to 100 amps. Few only—**1/6** each. Bin No. N6AL.

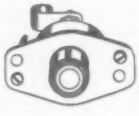

HOT AIR BLOWER

For drying out instruments, etc. This is an attachment which is fitted with a mains operated heating element and heat control, it is designed to fit on a vacuum cleaner tube at the blowing end of course. Price **17/6.**

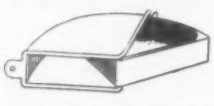

GRAMOPHONE ACCESSORIES

As illustrated to hold needles, etc. Price **1/6** each. Similar fitting but in the form of a small metal drawer. Price **1/10.**

MIDGET I.F. TRANSFORMERS

By famous maker, type No. M400B size only 1½in. × ¾in. × ¾in., 465 Kc/s, high "Q". Price **12/6** pair.

I.F. TRANSFORMERS (Pre-Tuned)

465 Kc/s, these have very high "Q." Standard size can with dust cores. Price while they last only **7/6** pair.

SLIDLOK FUSES

15 amp., very latest pattern for mounting on the front of instrument panels, etc. Price **1/6** each.

THIS MONTH'S SNIP

Due to a very large purchase, we are able to offer you 8 mfd. 600 v. working electrolytic condensers, aluminium can, upright mounting, made by one of our most famous Companies. These condensers will stand high surge voltages, and the normal list price is **7/-** each. All are unused, and in perfect working order but outside cases may be soiled. Price only **1/9** each or **10/-** per half dozen. Order by return because obviously once we have sold these we shan't be able to repeat.

JUMBO VALVE BASES

Ceramic 4 pin for transmitting valves. Price **3/6** each.

MONTH'S VALVE SNIP

Is a very useful Thyratron. These, as you probably know, are the most interesting of all valves for with them you can not only make time bases for scopes and televisors, but you can also use them as ultra sensitive relays, rectifiers, inverters, frequency changers, electronic switches, etc., etc.

The thyratrons we offer are brand new, Government Surplus. It will certainly be worth your while to get some of these while they are cheap. Details are: Heater volts 4, heater current 1.75 peak plate current 1,000 mA average plate current, 200 mA British 5 pin base. We offer these at **6/6** each or **£3** per dozen.

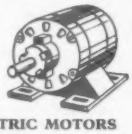

ELECTRIC MOTORS

Solid cast body, well wound, and impregnated. Heavy duty continuous rating.

¼ horse power	£5	5	0
½ horse power	£5	15	0
¾ horse power	£6	5	0

Carriage, etc., 7/6.

RECEIVER TYPE 21

Battery operated superhet covering 4.2 to 7.5 Mc/s and 19 to 31 Mc/s., on 10 metre band, this operates as a double superhet. In brand new condition, complete with 9 valves and circuit diagram.

Price **£2/5/-** plus 7/6 carriage, insurance and packing.

RECEIVER 3457

These cost over £100 each to build, they contain 15 valves type EF50 and one each of VR56, VR55, VR92, and 2 of types VR116 and VR54. These contain a host of valuable pot' meters, motors, relays, gear box, and components of all descriptions, and in addition they contain the famous "Pye" 45 Mc/s television strip. Brand new in transit boxes. Price **£5/19/6.**

ELECTRON MULTIPLIER

Type 931A. Direct equivalent of the 27M1, can be used for warning systems, locating foreign bodies, burglar alarms, etc., etc. Complete with base and a special light-proof chamber and resistance network. Price **27/6 each.**

ELECTROLYTICS

	s.	d.
2 mfd. 450 v.	1	4
4 mfd. 450 v.	1	6
8 mfd. 150 v.	1	3
8 mfd. 350 v.	1	6
8 mfd. 450 v.	1	11
8 mfd. 500 v.	2	6
16 mfd. 350 v	1	11
16 mfd. 450 v.	2	8
16 mfd. 500 v	3	6
32 mfd. 350 v.	2	8
32 mfd. 450 v.	3	6
10 mfd. 25 v.		10
25 mfd. 25 v.	1	3
50 mfd. 12 v.		10
8 mfd. × 8 mfd. at 450 v.	3	4
8 mfd. × 16 mfd. at 350 v.	2	6
8 mfd. × 16 mfd. at 450 v.	3	6
16 mfd. × 16 mfd. at 350 v.	3	0
16 mfd. × 16 mfd. at 450 v.	3	9
16 mfd. × 8 mfd. × 24 mfd. at 450 v.	4	2
25 mfd. × 25 mfd. at 200 v.	3	11
16 mfd. × 8 mfd. at 350 v.	2	6
16 mfd. × 8 mfd. at 500 v.	4	6
250 mfd. at 12 v.	2	3
16 mfd. × 32 mfd. at 350 v.	3	4
12 mfd. at 50 v.	1	3

LESS THAN HALF PRICE

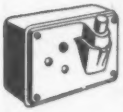

15 amp. shuttered switch plug, bakelite moulded surface, mounting type, made by very famous maker, made to B.S.S. 8/6 each.

STILL AVAILABLE—

At a non-repeatable price, the parts for a miniature tuning heart which will tune long and medium waves and which will not take up much more than 1 cubic inch of space. If you have planned to build a personal set or a tiny radio then here is an opportunity not to be missed. For only 8/6 we supply a two-gang tuning condenser and a pair of dust-cored dual-wave coils, ultra small but nevertheless very efficient. We will also supply free of charge circuit diagrams of a battery and a mains set using these parts and further, if you care to call, we will gladly demonstrate these sets. Limited stock, so order without delay.

B7G PLUG

With hard rubber body, fits into standard B7G valve holders, ideal for joining small chassis, etc., 1/4 each.

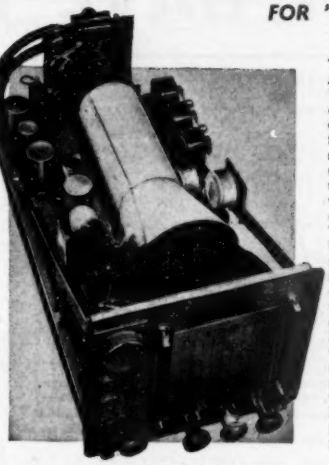

FOR 'SCOPES OR T.V. SETS

Type 6 Indicator. As specified for the *Wireless World* oscilloscope (reprint of data 9d.). Also for the "Inexpensive Televisor" (booklet 1/6), and the Mark I Televisor (Constructors' envelope 2/6). These indicators are brand new, packed and sealed in manufacturer's original crates, they contain VCR 97 Cathode Ray Tube, 4 EF50 valves, 3 other valves, and hundreds of useful components, including wire-wound pots. Price is only £3/19/6 plus carriage and packing case 10/-.

ONE MORE CHANCE—

To buy one of our R. & C. boxes (made originally for Government Laboratories) for we are fairly certain that they will be all sold before Easter. You have needed this in the past and you will continually need it in the future. With it you can put resistance into a circuit one ohm at a time up to 6,000 ohms. You can also put in capacity by equally small amounts. Further you can put in combinations of resistance and capacity and if you are keen on experimenting you can use the box for both arms of a wheatstone bridge, for each box has four sections that can be used separately. The price is only 19/6, plus 1/6 post. Which is less than the cost of the close tolerance resistors.

A DUAL PURPOSE RECEIVER

With the R.1155 Communications Receiver, you can either relax to the B.B.C. enjoying the same quality as with any good receiver, or when the mood suits you, you can don headphones and search out the weakest station on your favourite band. It is undoubtedly a dual purpose receiver. Its frequency range is 75 kc/s to 18 mc/s, it uses 10 valves and is fitted in a black crackle case. Made for the R.A.F. so obviously a robust receiver which will give years of service. We have available models as delivered from Ministry, unused at £8/19/6, used at £6/19/6. We have found even the unused models owing to long storage need certain components replacing, and need re-aligning and adjustments. We have serviced some of each and can guarantee them to be in perfect working order. Price unused £9/19/6 used, £7/19/6. If you cannot call to collect, please include an additional 10/- to cover cost of transit case and carriage. This is partly returnable to you if and when you return the transit case. The unit which you see standing on top of the R.1155 in the illustration is a combined mains power pack, control unit, output stage, and loudspeaker, buying one of these will save you having to make any fiddling alterations to your R.1155, you simply plug into the mains and your R.1155 is then mains operated, and will work right away without modification. The price of this unit is £7 and there is no additional carriage charge if it is ordered with an R.1155, otherwise send 2/6 extra.

POWER PACK TYPE 392

This is an extremely useful unit which works off A.C. without modification giving an output of 700 v. D.C. adequately smoothed. Here is a list of the components contained in the power unit: Mains Transformer for 200-250 v. 50 cycle, with secondaries of 700-0-700 v. at 70 mA., 4 v. at 2.5 amps., 12.5 v. at 1 amp. (Note these are Admiralty ratings, the transformers will stand at least twice these figures). Also 2 rectifier valves type CV54, 10-watt resistors, three 4 mfd. 100 v. condensers. L.F. choke, 10 henry 100 mA., 2 slydlok fuses. The power pack is unused and is contained in a louvred case size 12in. × 5½in. × 8½in. Price 67/6.

"SNIPERSCOPE"

Famous wartime "cats eye" used in conjunction with a lens system and h.t. for seeing in the dark. This is an infra-red image converter cell with a silver caesium screen which lights up (like a cathode ray tube) when the electrons released by the infra-red strike it. It follows that as light from an ordinary lamp is rich in infra-red these cells will work burglar alarms, counting circuits, smoke detectors and the hundred and one other devices as will the simpler type of photo cell. Here then is a golden opportunity for some interesting experiments. Price 9/6 each, or six for 52/6. Data will be supplied with cells if requested.

VALVE EQUIVALENTS CHARTS AND STOCK SHEETS

At more or less regular intervals you must waste a considerable amount of your valuable time either looking for the equivalent of an unusual valve or looking to see if you have such an equivalent in stock. To the best of our knowledge no firm has yet produced a really good combined valve equivalents manual and stock records book. We have however just completed ours and we think they will be a great help to all of you who repair domestic radios. We have had to put a lot of research and laborious work into these charts, we have tried to include all types ancient and modern and all makes. We are sure that our efforts have not been wasted however, because we think that once tried our charts will become very popular because they will save so much time and all the information will be under one cover. We invite you to give these charts a trial and if you don't honestly think they will save their cost many times over then please send them back for credit. The price is only 3/6 post free.

Orders under £2 add 1/6, under £1 add 1/-. Postable items can be sent C.O.D., additional charge approx. 1/-. Good stock of all items at time of going to press. List 6d. Closed Wed.—Open All Day Sat.

Telephone: Ruislip 5780

ELECTRONIC PRECISION EQUIPMENT (2) ELECTRON HOUSE, Windmill Hill, RUISLIP MANOR, MIDDX.

YOU MUST HAVE THESE!

INDICATOR UNIT TYPE 62. Contains VCR 97 tube, 16 valves VR65, 2 VR54, 2 VR92, and shoals of condensers, resistors, potentiometers, etc., etc. The last few to clear at ONLY **59/6** (carriage, etc., 12/6).

Also available are some chassis only of this indicator (no valves or tube) and they are a really " Happy hunting ground " for components, of which there are hundreds of condensers, resistors, potentiometers, etc. ONLY **17/6** (Carriage 5/-).

RECEIVER 25.73. Part of the TR.1196. Covers 4.3-6.7 Mc/s., and makes an ideal basis for an all-wave superhet. Complete with six valves, 2 each EF36 and EF39, and 1 each EK32 and EBC33, and modification data. ONLY **22/6** (postage, etc., 2/6).

OSMOR ALL WAVE COIL PACK, recommended for above, **4/6.**

RECEIVER 18. Part of the T.R18. Covers 6-9 Mc/s. and only requires normal battery supply to operate. Complete with 4 valves : 3 of VP23 and 1 of HL 23DD. ONLY **15/-** (postage, etc., 2/6). Suitable headphones fitted with jack plug. ONLY **6/6** (post 1/-).

BATTERY SUPERSEDER. With restrictions on the use of zinc those H.T. batteries are likely to be scarcer. Fit a superseder and forget. Operates from a 2 v. accumulator and delivers 67 volts at 4.7 ma., 130 volts at 13-25 ma., also 1.4 v. L.T. Originally designed for use with Canadian Walkie Talkie equipment, this American made unit can be easily adapted for use on any set, and full, illustrated details are supplied. ONLY **60/-** (postage 1/6), or with two 2-volt accumulators in metal case, **90/-** (carriage, etc., 5/-).

TELESCOPIC AERIALS, extending from 15in. to 102in. Just pulls out of steel tube. Very strong. BRAND NEW. ONLY **12/6** (postage 10d.).

HEADPHONE AND MICROPHONE SET. A pair of 4,000 ohms phones fitted with rubber noise excluders, and a high grade carbon microphone. BRAND NEW ONLY **12/6** (postage 10d.).

RECEIVER 3547. Contains the " Pye " 45 mc/s. I.F. strip, which is easily removable, and 15 valves : EF50, 3 EB34, 2 SP61, and 1 each EA50, EBC33, EF36. BRAND NEW IN MAKER'S CASES. ONLY **120/-.**

MINIATURE DYNAMOTOR UNIT. D.C. input 28 volts at 1.1 amps. D.C. output 250 volts at .06 amps. BRAND NEW. ONLY **12/6** (postage 1/-).

COMMUNICATIONS RECEIVER R.1155

Another purchase from the Ministry of Supply enables us to once again offer this superlative communications receiver at " give away " prices. A World Station Getter, this 10-valve set covers 5 wave ranges : 18.5-7.5 Mc/s., 7.5-3.0 Mc/s., 1500-600 kc/s., 500-200 kc/s., 200-75 kcs., and is easily adapted for normal mains use, full details being supplied. Prices to suit every pocket, as follows :

Used, good condition, and aerial tested	£7	19	6
Used, good condition, untested ...	£6	19	6
New, in maker's cases & aerial tested	£9	15	0
Used, good condition, untested, less valves...	£5	0	0

Carriage in all cases 10/- extra.

A few **R.1155.N** models are also available, which have similar wave ranges to above, with the exception of the 200-75 kc/s. band which is omitted, and a 3.0-1.5 mc/s. band fitted instead. These are used, but in good condition and aerial tested. **ONLY £14/10/-** (plus carriage).

MAKING AN OSCILLOSCOPE ?

Then you want the **INDICATOR UNIT TYPE 6,** as recommended for the " Wireless World General Purpose Oscilloscope." Fitted with 6in. C.R. Tube type VCR 97, 4 valves EF50 and 3 of EB34. Another purchase from the Ministry of Supply enables us to offer these units, which are BRAND NEW IN MAKER'S CRATES at ONLY **79/6** (carriage 7/6). Constructional data as above supplied free with each unit, or available **9d.**

The following component parts are in stock :

EHT Transformer for VCR 97 tube. ONLY **30/-** (postage 1/6).

4v EHT Rectifier, with ceramic base. ONLY **8/6** (post 9d.).

CHOKES 20 h. 80 ma. ONLY **6/6** (post 9d.).

AIRCRAFT CLOCKS

8 day movement and really precision made. Have mounting flange, and are ideal for Car, Boat, Workshop, etc. BRAND NEW. ONLY **30/-** (postage etc. 2/6).

T.1154 TRANSMITTER OUTPUT UNIT

The complete Output Section of this famous transmitter BRAND NEW IN MAKER'S CARTONS. Contains two heavy transmitting condensers, short wave coils, variable inductance pre-set tuning mechanism, etc., etc. A " must have " for everyone. ONLY **7/6** (Carriage 3/6).

W.6331 MODULATOR & MIXER

A very fine ex-Admiralty unit containing 8 valves : 1 each 5U4G, SP61, EB34, 2 of 6J5G, and 3 of P61. Ideal for the experimentar. ONLY **22/6** (Carriage etc., 7/6)

INDICATOR UNIT TYPE 184A. Contains two C.R. Tubes a 6in. VCR 517 and a 3in. VCR 139, 5 valves type EF50, 3 type EB34, 3 type SP61, and 5 diodes EA50. ONLY **75/-** (Carriage etc. 12/6).

RECEIVER TYPE 159. Contains 4 valves, 1 each EF50, SP61, EA50, CV66, and a small impulse motor. ONLY **11/6** (Postage 1/-)

RECEIVER R.3179. Contains 12 valves, 7 type EF50, 2 of RL37, 1 each EC52, HVR2, EA50, and a 30mc/s I.F. Strip. ONLY A FEW AVAILABLE AT **49/6** (Carriage 5/-).

COMMAND RECEIVER FOR 100-200 METRES. A 6 valve superhet containing all metal valves, 3 of 12SK7, 1 of 12K8, 1 of 12SR7, 1 of 12A6. I.Fs 1415 kcs. Ideal for Trawler Bands etc. BRAND NEW ONLY **59/6,** carriage paid.

PACKARD BELL PRE-AMPLIFIERS. A first class American job designed to increase the output of low gain microphones and pick-ups. Most efficient. Contains two double valves, push pull input, and push pull output transformers, a relay, a choke, etc., etc. BRAND NEW IN MAKER'S CARTONS. ONLY **14/6.** (Postage 1/3) or with 2 spare valves **22/6** (Postage 1/3).

INSULATION TESTERS (MEGGERS). Manufactured by Record. Readings up to 20 megs. at 500 v. pressure. A FEW ONLY AVAILABLE AT **£8/10/-,** carriage paid.

POWER UNIT TYPE 195. Converts 24 v. D.C. to 230 v. A.C. In grey metal case with leather carrying handle. ONLY **59/6** (Carriage etc. 10/-).

4in. C.R. TUBE VCR 138. Complete with holder and mu-metal screen, **22/6** (Postage etc. 5/-).

BATTERY AMPLIFIER. Ex-R.A.F. being used for inter communication system on aircraft. Ideal for use with a gramo pick-up or home intercom. etc. Works off normal battery, supply, 120 v. H.T., 2 v. L.T. complete with valves types QP21 and 210LF in metal case. IN MAKER'S TRANSIT CASES. ONLY **19/6.** (Postage etc. 2/6).

AMERICAN LORAN RECEIVER APN4. Contains 16 valves : 3 6B4, 2 2X2, 4 6SK7 and 1 each 5U4G, 6H6, 6SU7, 6SL7, 6SN7, VR105. Covers approx. 550-650 metres in 4 switched bands. ONLY **69/6** (carriage, etc., 5/-).

Cash with order please, and print name and address clearly

U.E.I. CORPORATION

Radio Corner, 138 Gray's Inn Road, London, W.C.1. *Phone:* TERMINUS 7937

(Open until 1 p.m. Saturdays. We are 2 mins. from High Holborn (Chancery Lane Station) and 5 mins. by bus from King's Cross)

CLYDESDALE

Bargains in Ex-Service Radio and Electronic Equipment

RCA TELEPHONY AND TELEGRAPHY TRANSMITTER ET-4336

THE ET-4336 TRANSMITTER operates with a maximum input of approx. 1 kW. on Phone (RT) or CW (Telegraphy) with an aerial output of 350/450 watts with respect to the frequency and antenna system used. The frequency range covers 2-20 Mc/s. with either a plug-in crystal controlled oscillator unit or an ECO (VFO) unit, these are interchangeable. Features of the ET-4336 are: Built-in power supplies for 110 - 250 v. A.C. mains, 2/813 valves for PA, 2/805 valves for class B modulation.

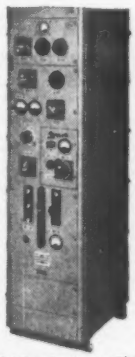

COMPLETE AND TESTED COMPRISES:—
RACK
plus
MASTER OSC.
plus
CRYSTAL MULTR.
plus
SPEECH AMPL.
plus
MICROPHONE
plus
MORSE KEY.
Packed in 4 wooden cases. Weight inclusive 5½ cwt. approx.

1/807 buffer stage 1/807 in each of the interchangeable osc. units. Separate speech amplifier with self-contained 110/250 v. A.C. mains power supply. Valves include 4/6J7 and 2/6L6—500 ohm match to the TX. All tuned circuits are metered. Safety switches on removable side and rear panels to obviate shock hazards during inspection. The transmitter is supplied complete with both types of oscillator units, valves, speech amplifier, microphone and morse key. Ready for immediate use on RT or CW. Rigidly crated for shipment. **Dimensions:** TX. 58 × 17 × 24in. Amplifier, 19 × 12 × 8in.
CLYDESDALE'S PRICE ONLY **£120** Carriage Paid G/t. Britain

T.1154 C.W., M.C.W. "FON" TRANSMITTER

This transmitter can be operated at an input of up to 100 watts on C.W. and 60 watts on "FON." Employs a parallel Final arrangement of Two PT15 pentodes, and an ECO driver stage using an ML6, a further ML6 provides GRID MODULATION (approx. 60%), this stage also provides a means for Side Tone monitoring when the transmitter is on C.W. A carbon or electro magnetic microphone can be used.
The controls include: Frequency Selector (ECO), P.A. tuning and Antenna loading. Stand-by/Transmit switch and plate current meter (MAG FEED), together with R.F. amps (output) meter.
Enclosed in a metal case, finished in black. 14 × 16½ × 8½in. 3 Waveband model.
CLYDESDALE'S PRICE ONLY **£7/18/6** POST PAID

V.H.F. RECEIVER

The Stratton P40 for conversion on to 2 metres. Crystal controlled 85/95 Mc/s. and includes 1/EF54 (RF), 1/EF54 (MIX), 1/EC92-2/EF54 (Osc. and Mult.), 2/EF39 (IF) 1/EB34 (DET/AVC), 16/J5 (1st Aud.). 6V6 output. The receiver is enclosed in a die-cast frame with louvred cover 11½ × 5½ × 4½in. Less crystal.
CLYDESDALE'S PRICE ONLY **£3/19/6** POST PAID

RECEIVER TYPE 4A

This is a Channel Checking receiver working on 49/100 metres which includes 3/VR91 (EF50), 1/6K8, 1/VR55 (EBC33) and 1/VR53 (EF9) valves. Included in the circuit is a terminal switch breaking at 86 Degrees F. Enclosed in a metal case.
CLYDESDALE'S PRICE ONLY **45/-** POST PAID

TELEVISION

EX-R.A.F. Indicator Unit 62 consists of a host of TV Components plus a VCR97 Cathode Ray Tube and various Valves 16/SP61s, 2/EB34s and 2 EA 50.
The Indicator Unit 62 circuit may be useful for your TV experiments in its existing state. Circuit details are available at 1/3 each.
Complete and enclosed in a metal case 18 × 8½ × 11½in.
CLYDESDALE'S PRICE ONLY **67/6**each POST PAID

VIEWING TUBES

VCR 97 CRT is an electrostatic tube with a 6 inch screen requiring a 4 v. filament.—the trace is green.
Individually examined and carefully packed.
CLYDESDALE'S PRICE ONLY **35/-** CARRIAGE PAID

3 BP1 CRT is an electrostatic tube with a 3 inch screen requiring a 6 v. filament supply.
Individually examined and carefully packed before dispatch.
CLYDESDALE'S PRICE ONLY **22/6**each POST PAID

T.V. COMPONENTS

The R.3515 provides a mass of TV components and various valves plus a 12.25 Mc/s I.F. strip by Pye. The valves include 10/SP61s 5/EF36s, 3/EB35s, 1/EB34, 1/EF39 and 1/EA50.
Components include relays, condensers, resistors and potentiometers. Enclosed in a metal case 18 × 11½ × 7½in.
CLYDESDALE'S PRICE ONLY **67/6**each POST PAID

IF/VIDEO RECEIVER

The EX-R.A.F. R. 1355 provides an excellent vision receiver and the RF section can be removed by sliding the complete unit free of the Receiver. An integral power pack for A.C. 200 v. Mains can be readily built in place of the existing 90 v. 2,000 C. pack.
The R.1355 is complete with valves: 5 stages of I.F. at 7.5 Mc/s. (8P61), Detector (EA50), Video Amplifier (8P61), and Cathode Follower (EF91), EHT rectifier (5U2150), and H.T. rectifier (5U4G.)
Complete in metal case 18 × 8½ × 7½in.
CLYDESDALE'S PRICE ONLY **67/6**each CARRIAGE PAID

Ex U.S. NAVY. AN/APA-I RADAR UNIT

Consists of an enclosed self-contained repeater amplifier unit with high frequency (400 cy.) power supplied, both E.H.T.- H.T.- and L.T.
11 valves include: 1/2x2 EHT rectifier, 1/6x5 Rectifier, 1/6G6 Power amplifier, 7/6SN7, R.F. Amplifier, 1/6H6 D/Diode, and 3 B.P.I. Cathode Ray Tube complete with base, metal shields mounting rack and 8 ft. core braided harness.
The unit is a wealth of components i.e., condensers, resistors, etc., Circuit supplied with each unit.
CLYDESDALE'S PRICE ONLY **£4/19/6**each CARRIAGE PAID

H38A CHASSIS

H38A CHASSIS, complete with valves.
CLYDESDALE'S PRICE ONLY **47/6**each POST PAID

R.F. STAGES FOR T.V.

The RV24 (30 to 20 Mc/s—10-15 metres) and RF25 (50 to 40 Mc/s—6-7.5 metres) are spot tuned converter units which are used with the R.1355 Receiver, but can be fed into any Receiver which tunes 7 Mc/s (42 Metres) Short Wave. 6 Channels are pre-tuned and switched. These units consist of an RF stage (8P61), Mixer (8P61) and Oscillator (8P61) stage. Enclosed in a metal case 9½in. × 7½in. × 4½in.
CLYDESDALE'S PRICE ONLY **12/6**each POST PAID

VIEWING UNITS

Indicator Type 6, Series B. These units are brand new in excellent condition and are all fitted with a VCR. 97 CRT, the tube which many constructors have put to T.V. use. Valves include 4/VR93 (EF50), 2/VR54 (EB34), plus a host of potentiometers and H.V. condensers, etc.
The complete unit is enclosed in a metal box 18in. × 8½in. × 7½in.
CLYDESDALE'S PRICE ONLY **£3/19/6** CARRIAGE PAID

Please include 10/- for transit case to ensure safe transit of unit. Refunded on return of case.

MISCELLANEOUS COMMUNICATIONS

TRAWLER BANDS

R1155N is the 1155 model that all operators would like. This superhet communications receiver is complete with valves: 2/VR29 (X66-X65), 3/VR100 (KTW62-KTW61), 2/VR101 (MHLD6-DH63), VR102 (BL63), VR103 (V63), and fitted with the type "E" geared reduction drive. The frequency ranges are in 5 wave-bands 18-7.5 Mc/s. (17-40 M.), 7.5-2.9 Mc/s. (40-100 M.), 3-1.5 Mc/s. (100-200 M.), 1500-600 Kc/s (200-500 M.), 500-200 Kc/s. (600-1500 M) AVC/Controlled R.F. switch, B.F.O., Filter and combined RF/AF gain control. Power requirements: 200 v. H.T./60 m/a and 6.3 v. L.T. Totally enclosed in a metal cabinet in black, 16½ × 9 × 9in.
CLYDESDALE'S PRICE ONLY **£14/14/0** CARRIAGE PAID

We supply this receiver modified for L.S. use and complete with A.C. Mains power supply, 8in. speaker.
CLYDESDALE'S PRICE ONLY **£21** CARRIAGE PAID

AS88 RECEIVER CAY44ACE

12 valve double superhet operating on 516 mc/s.
Containing an R.F. stage 446A lighthouse triode in a precision machined silver plated cavity.

955	1st oscillator 460 Mc/s.
955	Mixer.
2/6AC7	1st and 2nd I.F. 55 Mc/s.
6J5	2nd oscillator 39 Mc/s.
6AC8	Mixer.
2/6AC7	1st and 2nd I.F. Mc/s.
6H6	Diode detector.
6AC7	Video Amplifier.
6AC7	Cathode follower, 230 ohm. output.

Details can be supplied for fixing noise limiter, "S" meter and A.C. Power Pack.
Unit dimensions: 13½ × 5½ × 7½in.
CLYDESDALE'S PRICE ONLY **£4/10/0** CARRIAGE PAID

BRAND NEW. In Original Wood Case

Ex. Cdn. Army Supply Unit Rectifier for No. 43 Tx. This Unit is 3 complete power supplies, H.T., L.T. and Bias supply with an input of 110 v. A.C. 50/60 cyl. 1.7 KVAs. All smoothing is double-choke, condenser input circuits, H.T. starters, and stabilisers. Power-Transformers, 2,100-500-0-500-2,100 v. 400 m.A. 450-0-450 v. 12 v. ct. 6.3 v. 6.3 v. Fil. Trans. 2.5 v. ct. twice and 6.3 v. channel starter transformer.
Outputs: 2,100 v. H.T. 375 m.A., 500 H.T. 500 m.A., 385 v. regulated, 450 v. H.T. line, 415 v. neg. bias. 250 v. neg. bias, 150 v. neg. bias, 90 v. neg. bias.
The complete unit is mounted in a metal case with lid 2ft. 6in. × 1ft. 6in. × 1ft., finished in olive-drab crackle, and fitted with shock absorbing feet. Weight 429 lb.
CLYDESDALE'S PRICE ONLY **£16** CARRIAGE PAID

WS-18 RECEIVER

Ex-Army Wē-18 Receiver Unit, constituting a 4 valve superhet chassis with a frequency range of 6 to 9 Mc/s (50 to 33.3 Metres). I.F. Freq. 465 kc/s. employing an ARP12 (VP23) F/changer, 2/ARP12s IF/LF and AR8 (HL23DD) audio, 3 det. and AVC. Headphone output.
A very sensitive compact receiver with great possibilities. Chassis 8½ × 5 × 1in. Front panel 9½ × 6½in.
Unused, good condition.
Requires only 3 v./3 a. L.T. 120 v./15 mA. H.T. 1.5 v. Bias.
CLYDESDALE'S PRICE ONLY **17/6** CARRIAGE PAID
Circuits available for Mk. I, II and III, at 2/3 post paid, or 4/6 post paid, for complete Tx/Rx circuits.

FOR MARINE USE

The CRV 46151 is a 6 valve superhet, suitable for shipping, with a frequency coverage of 195-9050 kc/s, 1 R.F. and 3 I.F. stages, plus an audio output stage. The 3rd I.F. stage provides CW Osc.
VALVE LINE-UP: 4/12SF7, 1/12SA7, 1/12A6 and 1/991 stabilizer.
H.T. power is derived from a 28 v. dynamotor mounted sub-chassis, which has an output of 250 v./70 mA. The valves are wired in series/parallel providing a 24 v. heater circuit.
Complete in metal case 15½ × 8 × 7½in. Weight 26.8 lb.
CLYDESDALE'S PRICE ONLY **£5/19/6**each CARRIAGE PAID

HAND DRIVEN GENERATOR

H.409. Hand driven Generator 10K/12043 consisting of a 40:1 gearing unit driving a generator producing 6.3 v./5a. and 300 v. 50 mA. complete with ratchet handle. Dim.: 7in. long. Used but in good condition.
CLYDESDALE'S PRICE ONLY **13/6** POST PAID

H.408. Hand Driven Generator by BENDIX consisting of a 70:1 geared unit driving a generator producing 28 v. × .175 a. and 300 v. at 40 m.A. The Generator is detachable measuring 4½ × 2½in. The unit is complete with ratchet handle. Used but in good condition.
CLYDESDALE'S PRICE ONLY **13/6** POST PAID

MAGNETIC COMPASS

H.406 Magnetic marching compass MK I. for day or night use enclosed in a black bakelite case, 3 × 2½ × 1in., complete with instructions for use.
CLYDESDALE'S PRICE ONLY **21/-**each POST PAID

Order direct from:—

CLYDESDALE SUPPLY CO. LTD. 2 BRIDGE STREET GLASGOW - C.5

Phone: South 2706/9. Branches in Scotland, England and Northern Ireland.

GARLAND BROS

AMPLIFIER ACIII : As supplied to Universities, Institutes, Colleges, Factories, and a host of other satisfied users. Specification : 7 valves, including rectifier (6SH7, 6J5, 6J5, 6J5, 2 x 6V6, 5Z4). 10 watts push-pull output to 3 or 15 ohm speaker. High- and low-gain inputs. Separate bass and treble controls. High-quality components, including Varley Mains Transformer and Varley DP47 Hi-fi Output Transformer. Negative feedback. Overall dimensions : 12in. x 6½in. x 7½in. Supply available for tuner unit, etc. Complete kit, including punched chassis, all valves and components, with circuits and instructions, including circuit of suitable tuner unit, **£8/10/-.** Amplifier, wired and tested, **£10/10/-.**

AMPLIFIER ACII : For those who desire good quality reproduction at low cost. 4 valves, including rectifier. Output 5 watts. Volume, tone, and variable feedback controls. High-grade output transformer. Chassis completely isolated from mains. Complete kit, including punched chassis, all valves and components, with circuits and instructions, **£4/4/-.** Amplifier, wired and tested, **£5 5/-.**

DECCA TWO-SPEED GRAM MOTORS : For 33⅓ and 78 r.p.m records. Delivery from stock. Price (incl. P.T.) **£5 19/10.**

DECCA TURNOVER PICK-UP : A crystal pick-up with turnover head for use with above or other two-speed motors. Delivery from stock. Price (including P.T.) **£4/9/4.** Suitable for use with ACIII or ACII Amplifiers.

AERIAL RODS : Heavily copper-plated steel, one foot long. Fit into one another to make any length aerial. Per doz., **2/-.**

STABILIVOLTS : Type NS1. Voltage stabiliser and divider. Operating voltages 280 v., 210 v., 140 v., 70 v. ; max. electrode current, 80 mA. Again available. Each **10/-.** Type VS6B : same operating voltages, but max. electrode current, 60 mA. Each **9/6.**

" VIEWMASTER " TELEVISION : The ideal televisor for the home constructor. Instructions, including instruction booklet, circuits, photographs and point-to-point wiring diagrams, for London or Midland transmissions (state which), **5/-.** Component kits as follows : WB chassis, speaker, transformer, etc., **£6/5/-.** T.C.C. Condensers, London, **£6/15/-** ; Midlands, **£7.** Westinghouse Rectifiers, **£3/2/6.** Morganite Resistors, London, **£1/6/9** ; Midlands, **£1/6/-.** Morganite Type Q Variable Resistors, 4/6 each. Plessey Transformer, Focus Ring, etc., **£5/12/6.** Colvern W/W Pots, **19/3.** Bulgin Switches, etc., **12/6.** Belling-Lee Mains Panel, etc., **7/6.** Wearite Coils and Choke, London, **£1/2/-** ; Midlands, **£1/10/-.** Individual components included in above kits can be supplied separately if desired.

" Viewmaster " Pre-Amplifier : Wiring diagram, **1/-.** Complete kit, **23/6.**

" ELECTRONIC " TELEVISION : London handbook, **2/6.** Wiring diagram, **2/6.** Midlands handbook and wiring diagram, **4/6.** Chassis, with valveholders, coilformers, etc., mounted : Vision, **22/6.** Sound, **18/9.** T/Base, **17/6.** P/Unit, **25/-.** Gantries, etc., **9/-.** Designer-approved components : Coils and Chokes, London, **15/-** ; Midlands, **17/6.** Focus Coil, **30/-.** Scanning Coils, **25/6.** Line Transformer, **25/6.** Mains Transformer, **90/-.** 4 kv. Transformer, **67/6** ; 5 kv. Transformer, **72/6.**

" OSMOR " GLASS DIAL ASSEMBLY : 3-colour, 3-wave, 7in. x 7in., with drive mechanism, **25/-.**

" OSMOR " " Q " COILPACKS : A selective high-Q coilpack of miniature size (1⅝in. x 3⅛in. x 2¼in.), with easy one-hole fixing. Type HO, Long, Medium and Short, **33/-,** plus 7/4 P.T. Type LM, Long, Medium and Gram, **28/-,** plus 6/4 P.T. Type TB, Medium, Long and Shipping, **35/-,** plus 7/10 P.T. Type EX, Medium, Short and Short, **35/-,** plus 7/10 P.T. Type B, Long, Medium and Short Battery with frame aerial, **37/6,** plus 8/4 P.T. Type T.R.F., Long, Medium for T.R.F. Receivers, **30/-,** plus 6/8 P.T.

" OSMOR " HF STAGES : Designed for use with above coilpacks. For HO, TB and EX Coilpacks, **15/-,** plus 3/4 P.T. For LM Coilpack, **13/-,** plus 2/10 P.T.

I.F. TRANSFORMERS : 465 k/c., standard size, capacity-tuned. Made for us by a leading manufacturer. Per pair, **12/6.**

T.R.F. COILS : M. and L. wave with reaction winding. Per pair, **6/6.**

" CLEAREX " TELEVISION LENSES : For 9in. tube, **50/-,** with filter, **55/-.** For 12in. Tube, **70/-** ; with filter, **75/-.**

HIGH-CAPACITY PRECISION MICA CONDENSERS : By leading manufacturers. Accuracy plus or minus 0.5 (point five) per cent of stated value. Pure mica and copper foil.

(a) 0.017970 μF ... 1/3 (b) 0.023570 μF ... 1/3 (c) 0.035020 μF ... 1/6
(d) 0.040710 μF ... 1/6 (e) 0.055820 μF ... 1/6 (f) 0.065350 μF... 1/6
(g) 0.087460 μF ... 1/6 (h) 0.108435 μF ... 1/9 (i) 0.123750 μF... 1/9
(j) 0.147000 μF ... 1/9 (k) 0.205276 μF ... 2/-

Many close tolerance standard values may be made up by parallel or other combinations of above, e.g. : 4k+i+e=1 μF ; 2k+g=0.5 μF ; c+f=0.1 μF.

" POLASPEX " TELEVISION FILTERS : For viewing in daylight or artificial light without strain. Will fit your set without necessitating any alteration. For 9in. Tubes, **18/-** each. For 12in. Tubes, **21/-** each.

PLUGS AND SOCKETS : Pye angle, **1/-** ; Pye straight, **1/3** ; B. & L. 5-pin, **1/6** ; B. & L. 7-pin, **1/9** ; B. & L. 10-pin, **2/-** ; Jones 6-way, **1/6** ; Jones 8-way, **1/9** ; Jones 10-way, **2/-** ; Jones 12-way, **2/6** ; E.H.T. Single, **1/-.** The above prices include plug and socket in all cases. Octal Plug and Socket (Valveholder), black bakelite, **1/9.** Jack plug with Igranic socket, **2/6.** Pye T-pieces, **6d.** Pye connectors, **6d.**

Now in stock : Pye Angle P. & S. to fit ¼in. cable, **1/3** complete.

MOTORISED SWITCH ASSEMBLY : Type 10FB/556. Containing 24 v. miniature motor, 2⅛in. x 1⅛in. x 1⅛in., gearing, switch contacts, etc. Ex-Govt. Motor only tested. **10/-** each.

WAFER SWITCHES : S.P. 10 w., **1/9** each, **18/-** per doz. ; 3 p. 2 w., **1/6** each, **15/-** per doz.

MINIATURE 3-WAVE COILPACKS : By a leading manufacturer. Coverage 16-50 m., 200-550 m., 800-2000 m. Dimensions : 2½in. x 2⅛in. x 2in. **22/6.**

ACCUMULATORS : 2 v. 10 AH. Unfilled and uncharged, Bakelite-cased. **4/9** each.

ROTARY TRANSFORMERS : With permanent magnet field. Input 11/12 v., output 480 v. 40 mA. Each **10/6.**

UNIT OFFER : Ex-Govt Receiver type 3170A, approx. 2 metres, 13 mcs. I.F., containing 8 EF50s, 1 EF54, 2 CV66 grounded grid triodes, 7475 stabiliser, 1 VU39 full wave rectifier, 1 HVR2 EHT rectifier, 1 EC52 2 EA50, variable condensers, switches, pots and a host of other useful components. Brand new in original transit cases. Our price **£3/12/6,** carriage forward.

ANOTHER UNIT OFFER : Ex-Govt. Indicator Unit 6A. For T/v. or " W.W." Oscilloscope. Containing VCR97, 4 EF50, 3 EB34, 10 w/w pots, 2 carbon pots, 4-pole 3-way and other switches, condensers, resistors, etc., etc. Brand new in original transit cases. Our price **£3/12/6,** carriage forward.

CATHODE RAY TUBES : 5CP1 Electrostatic Intensifier, type C.R.T., diameter 5in., max. second anode voltage 2 kv., max. intensifier anode voltage 4 kv., medium persistence screen. Brand new in original crate or carton, **22/6** each.

CHARGER VARIABLE RESISTORS : 2.4 ohms at 6 amps. Worm-driven. **5/6** each.

SPEAKER CABINETS : In brown bakelite, to take 5in. speaker with 4-hole fixing. Complete with back. **6/-** each.

TX AND S.P. VALVES : 807, **7/6** ; CV1141 (Thyratron), **6/6** ; VT501 (TT11), **6/6** ; RL18, **4/6** ; CV3830 (XH 1.5), **4/6** ; VU111 (4 v. 5 kv. Rect.), **4/6** ; CV54 or VU133 (4 v. 2.5 kv. Rect.), **3/6** ; CV73 (4 v. Bm. Tet.), **3/6** ; 954, 955, 956 (set of 3), **5/6.**

MAT RESISTORS : 300 ohm 250 watt. **1/9.**

SELENIUM RECTIFIERS : 280 v. 75 mA. half-wave, **5/9** each ; 24 v. 1.2 A. bridge, **12/6** each ; 12 v. 4 A bridge, **15/-** each.

TOROIDAL POTENTIOMETERS : On ceramic former. 2,400 ohm at 50 w. Each **5/6.**

H/D VITREOUS W/W RESISTORS : 5 ohm, 7.5 k, 30 k at 15 w., **1/6** each ; 4 ohm, 24 ohm (tapped), 350 ohm, 5 k, 7.5 k, 10 k, 75 k at 25 w., **1/9** each ; 18 k, 75 k at 50 w., **2/3** each ; 850 ohm, 10 k, 12 k, 50 k, 100 k at 100 w., **3/-** each ; 430 ohm 200 w., **4/-** each.

BALANCED ARMATURE HEADPHONES : Type DLR2. With wide comfortable double metal headband, lead and plug. The most sensitive low resistance phones made. Per pair, **8/-.**

HEADPHONES, TYPE DLR1 : Low Resistance with headband, lead and plug. New and unused. Special offer at **3/9** per pair, or **42/-** per dozen pairs.

JUNEERO TOOL AND XACTO SLIDE GAUGE

CUTTING SHEARS FOR ROD
"XACTO" GAUGE BAR
BENDING JIG SIDE NOTCH
CUTTING SHEARS FOR STRIP
PROTRACTOR SLIDE PLATE
PUNCH FOR STRIP AND METAL
VICE TO HOLD ROD FOR SCREW CUTTING

Bends, shears, punches and threads. For all the little jobs that waste your time As reviewed in this journal. Each, **18/6.** Xacto Slide Gauge and Protractor. For use with above Juneero Tool, **7/6.**

ALL GOODS NEW AND UNUSED UNLESS OTHERWISE STATED. GOODS SHOWN AS EX-EQUIPMENT HAVE BEEN FULLY TESTED AND ARE IN GOOD WORKING ORDER. PLEASE ADD POST OR CARRIAGE ON ALL ITEMS.

We maintain a very complete and comprehensive stock of valves, cathode tubes and components for radio, television and electronics. Our shop hours are 9 a.m. to 6 p.m. on Monday, Tuesday, Wednesday, Friday and Saturday, and 9 a.m. to 1 p.m. on Thursday, during which times we are always pleased to welcome callers. Post orders to Garland Bros., Chesham House, Deptford Broadway, S.E.8.

GARLAND BROS

GARLAND RADIO
CHESHAM HOUSE, DEPTFORD BROADWAY, S.E.8
TELEPHONE : TIDEWAY 4412/3

ALLEN & GOULD
5, OBELISK PARADE, LEWISHAM, S.E.13
TELEPHONE : LEE GREEN 4038

Moving Coil Speakers. All new 2/3 ohms P.M., 8in., 11/6; Rola 16/6; 4in., 18/-; 5in. 10/-; (with Trans. 14/6); 6in. 11/6; 8in. 12/6 and 17/- (with Trans., 16/-); 10in. 23/6; 12in. Truvox 39/6 and Celestion 75/-.

Potentiometers. New Centralab: 2K, 5K, 10K, 25K, 50K, 100K, ½, 1, 1 and 2 meg., less switch, 3/9, with switch 6/-. Midget with switch, ½ and 1 meg., 6/-. Surplus Midget, 1in. dia. valves between 6 ohms and 2 meg., 2/6 each.

Surplus Potentiometers. All standard size with extended spindles: 5K, 10K, 15K, 20K, 25K, 50K, 100K, 250 K, 500K, 750K, 1 meg., 2/- each.

Coils. Denco Maxi "Q" High "Q" with miniature size Litz wound on Polystyrene Formers with adjustable Iron Dust Cores. Aerial, H.F., or Oscillator for 465 k/c. or 1.6 m/c. Range covers all wavebands from 3.6 to 2,000 metres. Wiring diagram. Prices: Chassis Mounting, 3/9 (with React. 4/9). Octal fitting pin base, 4/- (with React, 5/-). Denco T.R.F. Matched pair Medium and Long Waves, 6/6 pair. Weymouth T.R.F. Matched pair M. and L. Waves, 9/6 pair. Superhet Matched pair S.M. and L. Waves, 9/9 or 11/6 pair. All types Wearite "P" Coils, 3/- each in stock. Weymouth Midget 1¼in. × ¾in. dia., Iron Core, Aerial, H.F. or Osc., 3/6 each.

Electrolytic Condensers. B.E.C. Midget Can Tubular, 8 mfd. 450 v. (1¼in. × ¾in. dia.), 2/6; 8-8 mfd. 450 v. (1¾in. × 1in. dia.), 4/-; 16-8 mfd. 450 v. 1¾in. × 1in. dia.), 4/6; 32 mfd. 450 v., 5/-; 16-16 mfd. 450 v. (1¾in. × 1¼in. dia.), 4/6; Dubilier "Drilltic" Card Tubular, 4 mfd. 500 v., 3/6; 8 mfd. 500 v., 4/-; 16 mfd. 500 v., 5/6; B.I. Can, standard size, 8 mfd. 500 v., 3/9; 8-8 mfd. 500 v., 5/-; 16 mfd. 500 v., 4/3; 16-16 mfd. 500 v., 5/3; 32 mfd. 500 v., 5/-; All New Stock. Dubilier mica .001 mfd. 5,000 v., 2/6.

Denco I.F. Liner for accurately lining-up 465 k/c/s., or 1.6 m/c. I.F. channels. Pre-tuned circuits, battery operated and completely self-contained. Price 42/- (incl. P.T.).

Coil Packs. Osmor Midget Coil Pack. Size 3¼in. × 2¼in. × 1¾in. covering S. M. and L. Waves. Coils wound on Polystyrene Formers with adjustable Iron Cores, ensures efficient performance. Factory wired and aligned. Price, including full circuits for Superhet 465 k/c. Unit, 35/-. Pins 7/4 P.T. **Weymouth** Midget 3¼in. × 2¼in. × 1¾in. covering S.M.L. W/Bands, for 465 k/c., employing Matched Iron Cored Coils on each W/Band. 42/10. **Wearite** Superhet Type 703 and 706, size 4¼in. × 3¼in. × 1¾in., covering two Short Wave and one Medium W/Band or S-M-L. Warebands, 465 k/c., employs Iron Cored Coils, 37/10. All of the above Coil Packs include Switching, Padding and Trimmer Condensers.

You're SURE to get it at

STERN'S

ESTABLISHED 25 YEARS

Output Transformer—Stern's. Midget 1¼in. × ¾in. × 1in. ratio 60-1, 3/9 (or ratio 90-1, 3/9). Stern's Multi-ratio (over 12 ratios, some C.T.), 5/6 watts, 8/6. Stern's Heavy Duty Multi-ratio, all C.T.apped, handles 13 watts and suits P.X.4s, 6L6s, etc., 29/6. Rola Multi-ratio, 5/6 watts, 10/6.

L.F. Chokes. Midget 10 henry 250 ohm 40 m/a., 3/6; 20 hny. 250 ohm 60 m/a., 6/6; 20 hny. 300 ohm, 100 m/a., 11/9; 5 hny. 50 ohm 250 m/a., 18/6; 20 hny. 250 ohm 120 m/a., 18/6; 9 hny. 250 ohm, 120 m/a., 8/6.

Metal Chassis. Substantially made of gauge 16 S.W.G. with four sides. 7in. × 4in. × 2in., 3/3; 9in. × 5in. × 2½in., 4/-; 10in. × 6in. × 2½in., 4/11; 10in. × 8in. × 2½in., 5/6; 12in. × 9in. × 2½in., 6/8; 14in. × 9in. × 2½in., 6/11; 16in. × 8in. × 2½in., 7/3; 16in. × 8in. × 3½in., 8/6.

I.F. Transformer, 465 k/c. New well-known manufacturer's surplus ¾in. × ¾in. × 1¼in. Iron Core, 9/- each. Denco Iron Core, 465 k.c. or 1.6 m/c., 1¼in. × 1¼in. × 3¼in., 16/6 pair. Wearite Stand Cap, Tuned, 465 k/c., 20/- pr. New Surplus 465 k/c. Iron Core, 4in. × 1½in. sq., 10/- pair.

Meter Rectifiers. Westinghouse 250 micro/amp., 11/6; 1 m/a., 10/6; 5 m/a., 4/9.

Selenium Rectifiers. H.T./H. wave. 250 v. 50 m/a., 5/6; 250 v. 100 m/a., 7/6; 250 v. 170 m/a., 13/9.

F. Wave Bridge Rectifiers for Battery Charging or Models 2, 4 or 6 v., 1½ amp., 7/6; 6 or 12 v. 1½ amp., 11/6; 6 or 12 v. 3 amps., 19/6; 6 or 12 v. 5 amps., 23/6; 12 or 24 v. 3 amps., 23/6.

Variable Resistor to control charging (or model speed) up to 3 amps. rating, 13/6. Suitable METER, 5/9.

Charger Transformers. Suitable for use with preceding Rectifiers. Each has input of 230 volts. Outputs (a) 24 volts tapped 15 v., 9 v. and 6 v. at 3 amps., 22/9; (b) 30 volts tapped 15 v. and 9 v. at 3 amps., 23/9; (c) 15 volts tapped 9 v. at 3 amps., 16/6; (d) 12 volts, 1½ amps., 11/3; (e) 15 volts tapped 9 v. at 6 amps., 21/6; 15 volts tapped 9 v. at 1½ amps., 13/6. A Battery Charger Wiring Diagram is included with purchase of Charger Transformer and Rectifier.

NEW SURPLUS!! FOSTER TRANSFORMERS. PRIMARY 230 VOLTS. SECONDARY 12 VOLTS 9 AMPS. 21/-.

Filament Transformer. Inputs 230 volts, outputs 6.3 v. 1½ amp., 8/3; 4 v. 1½ amp., 7/6; Input 200/250 v., output 4 v. (C.T.) 1½ amp., 4 v. 2 amp., 6.3 v. 2 amps., 19/6. Input 230 v., output 6.3 v. (C.T.) 4 amp., 16/6.

Westinghouse Rectifiers (a) H.T.51. Rated 350-0-350 volts, 100 m/a., 35/-; (b) H.T.52 Rated 350-0-350 v., 200 m/a., 37/6; (c) H.T.53. Rated 500-0-500 v., 200 m/a., 50/-; (d) Type 16H.T.56, 17/9; (e) Type 36E.H.T.25, 11/9; (f) Type 36E.H.T.35. Rated 2.5 kV., 1 m/a., 17/6; (g) Type 36E.H.T.100. Pulse rating 5/6 kV., 26/8.

Mains Transformers. All New Stock with Primaries tapped for 200-250 volts. Secondaries (a) 250-0-250 volt, 80 m/a., 6.3 v. (tapped 4 v.) 4 amp. and 5 v. (tapped 4 v.) 2 amp., 18/6 (also available with 350-0-350 volt at 18/6). (b) Stern's 350-0-350 volt, 150 m.a., 6.3 v. (tapped 4 v.) 4 amp. and 5 v. (tapped 4 v.) 2 amp., 38/6; (c) 350-0-350 v. 250 m/a., 4 volt, 8 amp., 4 v. 2 amp. 6.3 v. (tapped 2 v.) 2 amp. and 6.3 v. 6 amp., 72/6, and many to other ratings.

Heater Auto Transformers: (a) tapped 2 v. 4 v., 5 v., and 6.3 volts 3 amp., 9/6; (b) 4 v. 3 amp. to 6.3 v. 2 amp. Reversible, 6/6; (c) 4 v. 3 amp. to 6.3 v. 2 amp. Reversible, 6/6.

Power Potentiometers. Bulgin adjustable slider type, max. 6 ohms 60 watt, or 14 ohms 60 watt, 13/6 each. Ex-Govt. Rotary Adjustable 50 ohms 60 watt, 5/9.

A 4-Station Pre-Set Tuner. A complete self-contained unit from which any 3 Medium W/band and 1 Long W/band Stations may be pre-selected, and then individually selected by turn of Rotary Switch. No Tuning Condenser required, only 4 connections are necessary, price 40/-.

Adjustable Mains Droppers. 1¼in. dia. × 2¾in. (a) .15 amp., 1500 ohms, 5/-; (b) .2 amp., 1,000 ohms, 4/3; (c) .3 amp. 600 ohms, 5/-.

6 Volt Vibrator Transformers, secondary 250-0-250 volts, 85 m/a., 8/6.

KITS OF PARTS AND CONSTRUCTORS' ASSEMBLY OUTFITS

Assembly Instructions and Circuit to build an

A.C. MAINS MIDGET 4-STATION "PRE-SET" RECEIVER

We now have available a complete set of detailed Assembly Instructions, showing Wiring Diagram, Practical Component Layout, Point-to-Point Connections, and individual Component Price List, for the construction of a 4-STATION "PRE-SET" 4 VALVE SUPERHET RECEIVER.

This Set is designed to receive three chosen stations on Medium Waveband and one on Long Wave, each station being then selected by the turn of a Rotary Switch, no tuning being necessary. It is of Midget size, being 8¼in. × 4¼in. × 7in. high, when fully assembled, and can be completely built, including Valves and Matched P.M. Speaker, for approximately £5/17/6.

These Assembly Instructions are available for 1/6 (plus 3d. post), and in addition to the normal Wiring Diagram, they include practical layouts to enable the inexperienced Constructor to build the Set.

"MAINS or BATTERY PERSONAL KIT"

A complete KIT OF PARTS to build our new MIDGET 4-VALVE SUPERHET PERSONAL SET, covering MEDIUM and LONG WAVES and designed for MAINS or BATTERY operation is now available.

This 2 Waveband Superhet Receiver is designed to operate on A.C. mains 200/240 volts, or by an "All-Dry" Battery, either method being selected by means of a Rotary Switch. It is so designed that the Mains Section (size 4¼in. × 1¾in. × 3¼in.) is supplied as a separate K.it, which may be added at any time. The kit therefore can be supplied either as an "All-Dry" Battery Personal Set, or as a Midget Receiver for combined Battery/Mains operation.

The circuit incorporates Delayed A.V.C. and Preselective Audio Feedback. A Rola 4in. P.M. Speaker with generous size Output Transformer ensures excellent quality reproduction. Rear-of-Panel Aerial, Fully aligned I.F. Transformers, and a Drilled Midget Chassis are included. Valve line-up:—1.R.5 (F.C.).1.T.4 (1.F. Amp.), 1.S.5 (Diode Det. and Audio Amp.) and 3S.4 (Output Tet.).

The Set is quite easily built from the very detailed assembly instructions supplied, which include a practical component layout, with point-to-Point wiring, and a circuit diagram for both the Set and the Mains Unit.

Price of COMPLETE KIT (less Mains Unit), £6/13/9. Price of COMPLETE MAINS UNIT KIT, £1/17/6. EVER READY Type B114 BATTERY, 10/3.

An attractive Walnut Finished Cabinet, size 9in. × 5¾in. × 5¼in., of the hinged-lid type and suitable to house the combined set is available for 19/9.

THE COMPLETE ASSEMBLY INSTRUCTIONS mentioned above can be supplied separately for 1/9.

A Midget T.R.F. Battery Portable "Personal" Kit. A complete Kit of Parts to build a Midget 4-valve All-dry Battery Personal Set. Consists of Regenerative T.R.F. Circuit employing Flat Tuned Frame Aerial, with Denco Iron Dust Cored Coil, thereby ensuring maximum gain for Single-Tuned Stage covering Medium Waveband.

Valve line-up: 1T4 (R.F. Ampl.), 1T4 (Detector), 1S5 (1st A.F.), and 3S4 (output). Includes latest Rola 5in. Moving Coil Speaker, and a Chassis already drilled and shaped. A consumption of only 7 m.a. ensures long battery life. The Kit is designed for a cabinet, minimum size 6¼in. × 4¼in. × 3in. Detailed Building Instructions, with Practical Layout and Circuit included with Kit make assembly easy. Price for Complete Kit, £3/18/9 (plus 16/7 P.T.). Suitable unpolished Cabinet 6¼in. × 4¼in. × 2¾in. 12/9. Ever Ready B114 Battery 10/3. Building Instructions, Circuits, etc., supplied separately, 1/-.

A Complete Kit of Parts to build a **Midget "All-Dry" Battery Eliminator,** giving approx 69 volts H.T. and 1.4 volts L.T. This Eliminator is suitable for any Personal Set requiring H.T. and L.T. voltages indicated above. The Kit is quite easily and quickly assembled and is housed in a Light Aluminium Case, size 4¼in. × 1¾in. × 3¼in. It can therefore be accommodated inside most makes of Personal Sets. Price of complete Kit, £1/17/6.

"Wireless World" Midget A.C. Mains 2-Valve Receiver. We can supply all the components, including Valves and M.Coil Speaker to build this set as specified in the March 1950 issue at a total cost of £3/5/-. Reprint of detailed assembly instructions and circuit supplied separately for 9d.

"Wireless World" Midget A.C. Mains 3-Valve Receiver. Covering Long and Medium Wavebands. We can supply all the Components, including Drilled Chassis, Valves, Moving Coil Speaker, etc., to build this Set, as specified in the Feb. 1950 issue at a total cost of £4/10/- including a reprint of the complete Assembly Instructions and Circuit (this is available separately for 9d.) and Practical Components Layout with "point-to-point" connections. An attractive **Walnut Finished Cabinet** is now available for this W/World 3-Valve Set at 21/-, or it can be supplied with a complete Dial and Drive Assembly which includes the latest Station Name Dial and Dial Escutcheon, and a Combined Switch/Volume Control to effect very slight modification. Inclusive price, 35/- (Dial and Drive Assembly with Switch/V. Control supplied separately for 14/-).

We can supply all the Components, including Valves, M/Coil Speaker, etc., to build a **Midget A.C./D.C. Mains T.R.F. 3-Valve (Plus Metal Rectifier) Receiver** as designed and specified by a popular Technical Magazine, at a total cost of £4/17/6. A reprint of the assembly instructions, and layout available for 9d.

An Entirely Complete 3-Valve Amplifier Kit of Parts. Operating on A.C. or D.C. mains 200-250 volts. Has an output of max. 4 watts, with valve line-up 2A6, 6J7 and U31. A matched 6in. Moving Coil Speaker is supplied. Price, including Wiring Diagrams 75/- (or less M/Coil Speaker, 59/6).

FOR UNDER £6!! A complete **KIT OF PARTS,** including Drilled Chassis and Valves, to build a **6 to 8 Watt Push-Pull Amplifier,** for operation on A.C. mains. Is suitable for use with Magnetic, Crystal or Light-weight Pick-up and incorporates Tone Control. Theoretical and Practical diagrams supplied. Price of Complete Kit, £5/18/9. Price of Amplifier Chassis, completely assembled, £7/10/0. Circuit and component list separately 9d.

TELEVISION!! The **"Viewmaster" Televisor,** assembly instructions showing Wiring Diagram and Practical Component Layout available for 5/-. We have the specified Components, including the T.C.C.—Bulgin—Morganite—W.B.—Westinghouse—Plessey—Colvern, etc., outfits in stock. We can supply this Televisor by the individual stages (as published with the instructions) or by separate Components. Complete price details can be obtained on application.

DECCA DUAL SPEED GRAM UNIT. Complete with Dual Speed Motor and Dual Pick-up for 33⅓ and 78r.p.m., £9/19/2. Motor only supplied separately for £5/19/10, and Dual Pick-up for £3/19/4.

THE "CONNOISSEUR" SUPER LIGHTWEIGHT PICK-UP, with interchangeable Heads for Standard and Long Playing Records, £9/6/4.

We have a limited number of COSMOCORD G-P.26 PICK-UPS in stock, price £3/11/5

★ Send 6d. P.O. or our NEW STOCK LIST, showing many KITS OF PARTS for Sets and Battery Chargers and "hundreds" of Wireless Components. When ordering please include postage and packing.

STERN RADIO LTD., 109 and 115 FLEET STREET, E.C.4

Telephone: CENtral 5814 and 2280

D. COHEN

RADIO & TELEVISION COMPONENTS

MAINS TRANSFORMERS

Primary 200-250 v. P. & P. on each 1/6 extra.

250-0-250 100 mA., 6 v. 3 amp., 5 v. 2 amp. Upright mounting. 17/6.

250-0-250, 60 mA., 6 v. 4 amp. (to be used on common heater chain with 6 x 5 rectifier), 13/6.

280-0-280, 80 mA., 6 v. 3 amp., 4 v. 2 amp., drop-through, 14/-. Same as above, but 350-0-350 14/-.

Drop thro' 350-0-350 v. 70 mA., 6 v. 2.5 amp., 5 v. 2 amp., 14/6.

Semi-shrouded, drop-thro' 280-0-280, 6 v. 3 amp., 5 v. 2 amp., 16/-

Semi-shrouded, drop-thru' or upright mounting 280-0-280 80 mA., 4 v. 6 amp., 4 v. 2 amp., 12/6.

Auto-wound H.T. 280 volts at 360 mA., 4 v. 3 amp., 2 v. 3 amp., or 6 v. 3 amp. Separate 4 v. 3 amp. rectifier winding (upright or drop-thro'), 18/6.

320-0-320 v. 120 mA., 6 v. 4 amp., 5 v. 3 amp., drop-through, 22/6.

350-0-350 v. 120 mA., 4 v. 6 amp., 4 v. 3 amp., drop-through, 21/-.

Auto-transformer, various combinations of voltages including 110 v. 70 watt, and 3/4 volts windings at 1 amp., 2 volt 1 amp., drop-through or upright mounting. 10/6.

Heater Transformers Pri. 200-250 v., 6 v. 1½ amp., 6/- ; 2, 4 or 6 v. 2 amp., 7/6. P. & P., each 9d.

ELECTROLYTIC CONDENSERS

50 mfd. 50 work. 1/9.
100 mfd. 12 v. work, 1/3.
16-16 mfd. 450 work, 4/-.
50 mfd. 12 v. work, 1/-.
25 mfd. 25 v. work, 1/2.
16 x 8 mfd. 450 work. 3/9.
8 mfd. 450 v. work, 1/11.
250 mfd. 12 v. work, 1/3.
16 mfd. 500 v., 3/6.
8 x 8 mfd. 450 work, 3/6.
32 mfd. 350 work, 2/-.
32 + 32 mfd. small tube tag ends 200 v. work at 2/-.

P.M. SPEAKERS

	with trans.	less trans.
3½in.	—	10/-
5in.	13/6	—
6½in.	13/6	10/-
8in.	15/6	13/6
10in.	19/6	17/6

P. & P. on each of above 1/- extra.

ENERGISED SPEAKERS

8in. 2,000 ohm field with O.P. trans. 5,000 ohm imp., 15/6.
5in. 750 ohm field with O.P. trans., 13/6.
Post and packing 1/-.

WAVE CHANGE SWITCHES

6-pole 3-way, 2/-.
3-pole 2-way, 1/2.
4-pole 3-way, 1/9.
1-pole 12-way, 2/6.
3-pole 12-way, 4/6.
5-pole 2-way midget. 1/9.
Post and packing 3d each.

MIDGET COMPONENTS. Twin gang ⅞in. diameter, ⅞in. long. (The dimensions of this gang are slightly deeper than a standard volume control.) Pair Medium and Long iron cored T.R.F. Coils ⅞in. long x ⅞in. wide complete with a 4-valve all dry circuit. Both above items 8/6, post paid.

A NOVEL MIDGET CABINET 6in. high x 4in. diameter (takes 3in. speaker in base), 10/- post paid.

ALL-DRY A.C. MAINS SUPPLY UNIT, size 3½in. long x 2⅞in. wide x 1½in. deep. We can supply a complete all-dry circuit, using the above Midget Components to incorporate the above Power Unit, 19/6, post paid with circuit.

SCALE AND POINTER KNOB to fit the above 1/6.

3in. P.M. SPEAKER to fit above 10/- post paid.

MIDGET O.P. TRANSFORMER to suit above 1in. x ⅞in., 5/-. We can supply all the midget condensers and resistors to suit the above circuit.

MIDGET BAKELITE CABINET, 7in. x 5½in. x 5in. c/w. 5-valve S/H. chassis med./long wave scale and back (takes std. twin gang condenser and 3½in. speaker), 15/-.

LINE AND FRAME COIL ASSEMBLY. Frame coils wound but not fitted (full instructions supplied). High impedance frame; low impedance line, matching 5-1, 8/6.

6½in. SPEAKER (P.M.) specially made for Television with closed field, complete with O.P. transformer, 12/6, plus 1/- post and packing.

PRE-ALIGNED MIDGET 465 Kc. Q.120, 8/6 per pair, post 6d.

MINIATURE 465 Kc. I.F.s. Type M400B. 12/6, plus 6d. post and packing.

MINIATURE 465 Kc. I.F.s (slightly larger than the above item), Q.120, per pair 10/-.

IRON CORED 465 Kc. I.F.s. Q.130, 2½in. x 1½in., per pair 6/-.

IRON CORED 465 Kc. WHISTLE FILTER, screened, each 2/-.

VALVE HOLDERS. Paxolin International octal, 4d. each. Moulded International octal, 6d. each. EF50 ceramic 7d. each. Moulded B7G slightly soiled 6d. each.

LINE CORD. 3-way 0.3 amp., 180 ohm per yard. 1/- per yard.

CERAMIC P.F.S. 3 each of the following : 330, 220, 180 and 82, 2/6.

VOLUME CONTROLS, by famous manufacturer. Long spindle and switch, ¼, ½, 1 and 2 meg., 3/6 each. 20, 25 and 50 k., 3/- each. Post and packing 3d. each.

VOLUME CONTROLS, by famous manufacturer. Long spindle less switch, 5 k., 50 k., 500k., 1 meg., 1/9 each. Post and packing 3d. each.

5-VALVE A.C. MAINS, 200-250 v., 3 wave-band superhet chassis. 1,000-2,000, 200-500 and 16-50 metres. By very good manufacturer, complete with valves. 6K8, 6K7, 6Q7, 6V6 and 5Z4. Size of chassis 11¼ x 7½ x 2in. Size of glass scale 8⅜in. x 7½in. with pick-up sockets (takes 8in. P.M. with trans.). TAX PAID, £8/18/6. Post and packing 2/6.

GOVERNMENT SURPLUS. Removed from equipment but guaranteed :
Metal Rectifier, 230 v. 60 mA, 4/-.
Metal Rectifier, 230 v. 80 mA., 5/-.
Post and packing on each, 6d.
8 mfd. metal cased, 450 v. work, with clip, 1/- each.

Stamp for list.

TELEVISION MASKS

White Rubber. 9in. with glass 10/6. White Rubber. 12in. with glass, 15/-, plus 1/- post and packing.

CONSTRUCTOR'S PARCEL comprising : 5-valve superhet chassis with I.F. trans. and V/H. cut-outs, 13⅜in. x 6in. x 2in. with L.M.S. scale 7in. x 5in., back plate and two supporting brackets. Drive drum, spindle and pointer, mains trans. G.E.C. 350-0-350 70 mA., 6 v. 2.5 amp., 5 v. 2 amp., and Plessey 8in. M. energised 2,000 ohm field with 5,000 ohm impedance, O.P. trans., 29/6. Post and packing, 2/-.

CONSTRUCTOR'S PARCEL comprising : 5-valve superhet chassis with I.F. trans., and V/H. cut-outs, 13⅜in. x 6in. x 2in. with L.M.S. scale 7in. x 5in., back plate and two supporting brackets. Drive drum spindle and pointer, 6/6. Post and packing 1/6.

CONSTRUCTOR'S PARCEL comprising : twin gang with feet, pair long and medium iron cored T.R.F. coils, 4 octal V/H., 3 pole 2-way switch Erie 20k. pot. w/s., heater trans. 220-240 v. 1 amp., 2 yds. flat silk flex, 3 black knobs, chassis 10½in. x 5½in. x 2in. with speaker and V/H cut-outs, metal rectifier 60 mA., 230 v. and 32 + 32 mfd. 200 v., 19/6, post paid.

CONSTRUCTOR'S PARCEL comprising : Chassis 10½ x 5½in. x 2in. with speaker and valve holder cut-outs, R. and A. 6½in. P.M. with transformer, twin gang with feet, pair medium and long wave iron cored T.R.F. coils. Four International Octal valve holders, wave-change switch and Erie 20k pot with switch, 25/-, plus 1/6 post and packing.

CONSTRUCTOR'S PARCEL comprising chassis 10½in. x 5½in. x 2in. with speaker and valve holder cut-outs ; Rola 5in. P.M. with O.P. trans. ; twin-gang with trimmers ; pair of T.R.F. coils ; Four international Octal valve holders ; wave change switch and Erie 20k pot. with switch, 19/6, plus 1/6 post and packing.

CONSTRUCTOR'S PARCEL comprising : Midget twin-gang with slow-motion drive ; pair midget 465 Kc. I.F.s ; frame aerial ; medium wave osc. coil and layer type H.T. and L.T. batteries 90 v. + 1½ v., 21/-, plus 2/- post and packing.

CONSTRUCTOR'S PARCEL comprising : 5-valve superhet chassis with transformer cut-out, size 13⅜in. x 6in. x 2in., with L.M. and S. scale, size 7in. x 5in. Back plate, two supporting brackets, drive drum, pointer, two-speed spindle, twin gang condenser. Mains transformer 250-0-250 v. 60 mA., 6 v. 4 amp. Pri. 200-250, 6½in. speaker and 6 x 5 rect. 28/-, plus 2/- post and packing.

POST ORDERS ONLY

67 RALEIGH AVENUE, HAYES, MIDDLESEX

The M.O.S. "EASY-TO-BUILD" SERIES of HOME CONSTRUCTOR KITS

(Including recommended accessories)

A.C. AMPLIFIER, TYPE A1. COMPLETE KIT

including pre-drilled chassis, pre-wired groupboard, valves and all items including nuts, bolts, solder tags and solder. With Instruction Manual. FOR A.C. ONLY. 200-250 v. **£4.2.6**
As previously advertised.

INSTRUCTION MANUAL if purchased separately. (Contains full construction details). **3.6**

A.C./D.C. AMPLIFIER, TYPE A2.

The amplifier type A2 is based on the same fundamental design as its successful predecessor, the A.1., but while the A1 can be used only on A.C. mains, the A2 may be used on A.C. or D.C. The A2 is introduced to meet the demands of those who are on D.C. To those on A.C. the A1 is to be preferred since the safety factor is so much higher.
Owing to the use of a transformer-less power supply the A2 amplifier is offered at a price which is extremely competitive, and places good equipment in a price range so far unheard of.
All the components which form the A2 amplifier are tested and of first grade. Moreover each kit is fully guaranteed.
The kit is supplied complete in every detail right down to nuts, bolts, solder tags, and solder. A pre-drilled chassis is supplied. A comprehensive instruction manual gives the fullest construction details, the instructions being written in such a way that those without previous knowledge can construct the A2 amplifier with the sure knowledge that it will operate, without trouble, from the time of first switching on. The instructions are supplemented with many clear diagrams.
The circuit is simple and straight forward, but by the careful choice of component values the performance is outstanding. Primarily designed for crystal pick-ups, the amplifier can be used with magnetic pick-ups if desired. Output 2.5 to 3 watts.

Complete kit with valves for A.C./D.C. Mains **£2.19.6**

Instruction Manual. ONLY **3.0**

HIGH QUALITY 10" SPEAKER.

Specially selected for use with our amplifiers. This offer is only available to those purchasing one of the amplifier kits. **17.11**

HOME BROADCASTER MICROPHONE.

Complete with matching transformer, mounted on neat bakelite desk stand. Highly sensitive **7.6**

ACOS. GP20 MICROCELL PICK-UP.

Extremely low needle pressure—13 grams—and a flexible stylus mounting, virtually eliminating record wear. The GP20 has a rising bass characteristic which enables it to be used without equalisers. The crystal element is non-hygroscopic and unbreakable. We recommend this pick-up as first choice for use with the A1 amplifier. **£3.11.5**

A.C. 504GB COLLARO MOTOR UNIT.

Single speed 78 r.p.m. Well constructed for long life and reliability. Turntable rim driven. Crystal pick-up, mounted in neat balanced bakelite arm. New and boxed, with full size mounting template. A.C. ONLY. 200-250 v. **£6.4.4**

A.C. 504MB COLLARO MOTOR UNIT.

Specification as above except that a magnetic pick-up is employed. A.C. ONLY 200-250 v. **£5.19.2**

DECCA PLAYING DESKS.

33A. Single speed player for 33⅓ r.p.m. records. Light-weight crystal pick-up with sapphire stylus in spring balanced arm. Mounted on heavy pressed steel base. A.C. ONLY 200-250 v. **£9.9.0**

33B. Specification as per 33A but enclosed in strong leathercloth covered wooden case with lid. **£12.1.6**

RADIO FEEDER UNIT, TYPE RFI.

This radio feeder unit has been designed for use with the A1 amplifier in response to many requests. Please note it is not suitable for use with the A2 amplifiers.
As with the A1 amplifier itself, simplicity, coupled with good performance, has been the keynote. The tuning unit uses a "straight" TRF circuit tuning the Medium Wave Band only and the power to operate it is drawn from the A1 amplifier. *If provided with its own power unit*, it can be used with the A2 or any other amplifier.
Although a TRF circuit is employed, the unit is exceptionally sensitive; enough to be used in areas of only moderate signal strength from the transmitter. Its selectivity however debars its use in areas of low signal strength.
By the use of a TRF circuit the bandpass is such that the output fed into the A1 amplifier is of very high fidelity, and full advantage can be taken of the transmitted quality.
The unit is provided with only two controls—Tuning and Sensitivity—and consequently is very simple to operate. No tuning scale is provided as it is thought that the great majority of constructors will prefer to fit the unit into a cabinet and so be able to choose an assembly to suit the housing. Adequate spindle length is provided in all cases.
In line with the other "easy-to-build" series the kit is complete in every detail, and the instruction manual fully detailed and illustrated.

Complete Kit with Valves **£2.5.0**

Instruction Manual only **2.0**

HIRE PURCHASE TERMS ARE AVAILABLE ON ORDERS OF £10 OR OVER.

Terms: one third of total cash price as deposit. Balance, *plus* 10% *interest*, spread over six months to make *six equal payments*.

A REVOLUTION IN SOLDERING METHODS!

52/6
Post Free.

We can offer immediate delivery of the BURGOYNE SEVEN-SECOND SOLDER GUN, and all guns which WE SUPPLY are GUARANTEED for TWO YEARS. How often do you leave your soldering iron on all evening, or all day, so that it will be ready for use when wanted? How often do you have to re-tin the bit? How much electricity DO YOU waste? The Burgoyne Solder Gun gives you heat in seven seconds, and all the heat where you want it. Cold when not in use, no waste of electricity, no danger from picking up the "wrong end." No constant re-tinning.
The Burgoyne Solder Gun is a balanced instrument easy to handle. It is robust, has no elements to burn out, no mica to crack and make the bit "live."
We have nearly exhausted our stocks of "cancelled export order" guns which we have been able to offer at the reduced price of 52/6, and must therefore advise our customers that there will be an increase to the list price of 75/6 as from April 1st.
ORDER NOW TO SECURE AT THE REDUCED PRICE.

For RELIABILITY plus EFFICIENCY you must have a BURGOYNE AERIAL CONNECTOR

This is the ONE and ONLY unit available which enables a really efficient and reliable weather-proof connection to be made between dipole and feeder. Why continue to worry about your dipole? Come gale or hail, rain in drops or by the bucket, this connector will never let you down. **ORDER NOW!** Price increases April 1st.

12/3
Plus 9d. postage.

BRAND NEW IN ORIGINAL CARTONS

REMINGTON "Blue Streak" ELECTRIC DRY SHAVER

The World's finest Multiple Head Shaver.
Shave anywhere without fuss. No brush, soap or hot water needed. Even the toughest beard and tenderest skin respond to the Remington.
The FOURSOME (4 shaving heads). **£7/16/5**
The FIVESOME (5 shaving heads). **£8/17/7**
Hire purchase terms available.

7 DAYS FREE TRIAL ON CASH DEPOSIT

Miniature SPORTS BINOCULARS

A pair of small binoculars with superficial magnification x5 Finished in pastel plastic. Extra light-weight
Plus 6d. postage and packing. ONLY **14/6**

B.S.R. TAPE AND WIRE RECORDER MOTORS

This small induction motor is specially designed for magnetic tape and wire recorders. Absolutely silent in operation and virtually free from vibration. Minimum stray magnetic field for A.C. mains 100-250 volts 50 cycles. **30/-**
Post Free.

"IVALEK" CRYSTAL SET

A radio set in the palm of your hand! A beautifully made receiver, that looks good and IS GOOD. The receiver is constructed on an aluminium chassis and the circuit used, although simple, is highly efficient. All that is required is an aerial and earth, and a pair of high-resistance headphones for good trouble-free reception. **17/6**
Post and packing 9d. Standard Model, without tuning dial 12/6, postage and packing 9d.

M-O-S **MAIL ORDER SUPPLY CO., THE RADIO CENTRE**
33 Tottenham Court Road, London, W.1. Museum 6667

T.V. SCAN COILS FOR LINE AND FRAME. Brand new, manufacturer's surplus. For 9in. or 12in. c.r. tubes.
LASKY'S PRICE 14/6 Post 1/-.

RADAR RECEIVER UNITS TYPE 3584. Brand new, in original wood transit case. Contains 23 valves: 15 EF50; 3 EB34; 2 VR65; 1 VR55; 1 VR56; 1 EA50. Also incorporated in this unit, is the Receiver Unit 153 (45 Mc/s Pye strip), which contains 6 EF50 and 1 EA50 valves included in the above line up. Hundreds of components of all descriptions, including pot/meters, resistances, condensers, etc. Built on large size chassis: 18in. × 13½in. × 8in. Weight 45lb.
LASKY'S PRICE £5.19.6
Carriage 10/- extra.

PLESSEY TELEVISION

Line EHT Trans. ...	21/3
Focus Ring	19/6
Line width coil	8/9
Boost choke	5/-

6 VOLT VIBRATOR POWER PACKS. Output 300 volts, 80-100 m/a. Suitable for operating an A.C. mains radio from a 6 volt source with the minimum of conversion. Supplied with vibrator and 6X5 rectifier. In black metal case, size: 6in. × 5in. × 4in.
LASKY'S PRICE 29/6
Carriage 2/6 extra.

THE FAMOUS TYPE 6 INDICATOR UNIT. BRAND NEW AND UNUSED. IN MAKER'S ORIGINAL CARTON. Contains 1 6in. c.r. tube type VCR97 and 7 valves: 4 EF50; 3 EB34. Also 12 pot/meters, and hundreds of assorted components, resistances, condensers, etc. In metal case, grey enamelled, size: 18in. × 8½in. × 7½in. Weight 28lb.
LASKY'S PRICE 90/-
Carriage 10/- extra.

DE LUXE TELEVISION CABINETS. For 9, 10 or 12in. cathode ray tubes. Beautiful figured medium walnut finish, with high polish. Fitted with shelf for receiver, glass, speaker baffle and fret, rear tube protector, and castors for easy movement. Undrilled.
LASKY'S PRICE £8.10.0
Carriage 12/6 extra.
Outside dimensions of cabinet: 16½in. × 16½in. × 32in. high.

Limited Quantity
L.S.L. PORTABLE VALVE AND CIRCUIT ANALYSER.
LASKY'S PRICE £10.19.6
Complete. Carriage 10/- extra. Brand new and unused. Details available.

RADAR RECEIVER TYPE 3179A. Contains: 17 valves: 8 EF50; 2 RL37; 1 HVR2; 1 R3; 2 EA50; 1 EC52; 1 CV-188; 1 VR507. Also dozens of other components. including condensers, coils, resistances, etc. Totally enclosed in metal cabinet, size: 18in. × 7½in. × 8½in. Weight 35lb.
LASKY'S PRICE 59/6
Carriage 7/6 extra.

PACKARD BELL TYPE K. MICROPHONE PRE-AMPLIFIERS. BRAND NEW AND UNUSED. Contains 2 valves 1 6SL7 twin triode, and 1 28D7 twin pentode. Also associated components, input and output transformers, etc. Contained in lightweight metal case, Size: 4½in. × 5in. × 4in. Designed to increase the output of low gain pick-ups and microphones. Supplied with full circuit and details.
LASKY'S PRICE 16/6
Postage 1/6 extra.

RADAR INDICATOR UNITS TYPE 162C. BRAND NEW IN MAKER'S ORIGINAL WOOD CASE. Contains 2 cathode ray tubes, one 6in. VCR517 and one 3in. VCR139. Also the following valves: three SP61, one 6J5, three EA50, one D1. Dozens of components, coils, resistances, condensers, seven pot. meters, etc. Enclosed in metal case, size 12in. × 9in. × 19in. Weight 40lb.
LASKY'S PRICE 79/6
Carriage 7/6 extra.
The 162C Indicator, Less the VCR139.
LASKY'S PRICE 59/6
Carriage 7/6 extra.

CONDENSERS. ALL BRAND NEW.

8 mfd. 500 v. w.	3/-
8 mfd. 450 v.w.	2/9
16 mfd. 500 v. w. ...	3/9
16 × 16 mfd. 450 v.w.	4/6
25 mfd. 25 v.w.	1/6
8 × 16 mfd. 500 v.w.	4/3
60 × 100mfd. 350 v.w.	8/6
64 mfd. 500 v.w. ...	6/9

Postage extra.

EX. A.M. RECEIVER TYPE R1132A. BRAND NEW AND UNUSED. IN MAKER'S ORIGINAL WOOD CASE. High frequency receiver. 100-124 Mc/s. Contains 11 valves: one VR65, one VR66, four VR53, two VR54, one 6J5, one VS70 (voltage stabiliser), one VR57. Large tuning scale, with slow motion drive. 0-5 m/a. tuning meter, R.F. and L.F., gain controls, jack sockets for line and 'phone. Totally enclosed in metal case, grey enamelled with plated handles. Size: 18in. × 10in. × 11in. Weight packed 54lb.
Supplied with circuit and calibration chart.
LASKY'S PRICE 99/6 Carriage 10/- extra.

I.F.F. RECEIVER TYPE R3108. BRAND NEW AND UNUSED. IN ORIGINAL CARTONS. Contains 8 new valves: 4 SP41, 1 EA50, 1 VR78, 2 CV6. Also a host of components, coils, condensers, resistances, etc. A motor generator with input of 24 volts, and output of 480 volts.
LASKY'S PRICE 25/-
Carriage 3/6 extra.

RECEIVER UNIT TYPE 153 (45 Mc/s Pye Strip). BRAND NEW AND UNUSED. Contains 4 RF. stages, detector, video amplifier, phase splitter. Uses 6 EF50 and 1 EA50 valves. Stripped from brand new equipment. Supplied with valves. Full circuit and connecting details free with each unit.
LASKY'S PRICE 63/-
Post free.

COMMUNICATIONS RECEIVER. TYPE P.C.R. By Philips. Perfect condition. Aerial tested before despatch. 6 valve superhet circuit: R.F., F.C., two I.F.s, D.D.T., pentode output. Frequency coverage: 16-50 mtrs.; 200-550 mtrs.: 800-2,500 mtrs. Fitted in metal case, black crackle finish, with built-in loudspeaker. Flywheel tuning. May be used with any suitable power pack. Supplied complete with 6 brand new Mullard valves: 3 EF39; 1 ECH35; 1 EBC33; 1 EL 32.
LASKY'S PRICE £10.10.0 Carriage 10/- extra.
Power pack for P.C.R. Receiver. 12 volt.
LASKY'S PRICE 39/6 Carriage 5/- extra.

CAR RADIO PLUG SUPPRESSORS. Brand new Ex-Gov. Normally listed at 1/6 each.
LASKY'S PRICE 1/- each, 10/- per dozen. Post Free.

AMERICAN AIR CORPS RECEIVER TYPE BC454. Brand new in original cartons. Frequency range 3-6 Mc/s. Contains 6 valves: 3 12SK7; 1 12K8; 1 12A6; 1 12SR7. Also dozens of miniature components, resistances, condensers, etc. Built in black crackle metal case, lightweight, size: 11in. × 5in. × 5¼in. Weight 10lb.
LASKY'S PRICE 55/- Carriage 3/6 extra.

EX-A.M. COMMUNICATION RECEIVER TYPE R1155. BRAND NEW IN WOOD TRANSIT CASE. Aerial tested before despatch. Supplied complete with 10 valves. Circuit: B.F.O., A.V.C., R.F. Amp., two I.F. stages, magic eye, etc. 5 frequency ranges: 18.5-7.5 Mc/s.; 7.5-3.0 Mc/s.; 1,500-600 kc/s.; 500-200 kc/s.; 200-75 kc/s.

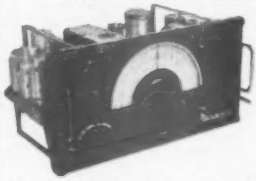

LASKY'S PRICE £12.10.0
Carriage (in wood case), 7/6 extra.
Full modification data and circuit details supplied free with each receiver. Power pack and output stage for the R1155, as described in the modification instructions. Fully assembled, and supplied with output valve and rectifier. In black enamelled case ready for use.
LASKY'S PRICE 79/6 Carriage 5/- extra.

SAFETY FIRST. Fused test prods. Fully insulated pencil type with retractable point. Contact is only made when desired by pressing top. Each prod contains a cartridge type fuse and spring.
LASKY'S PRICE 4/11 per pair (one red, one black). Post 6d. extra.

LASKY'S RADIO

370 HARROW ROAD, PADDINGTON, LONDON, W.9

(Opposite Paddington Hospital) *Telephones:* CUNningham 1979 and 7214
Hours: Mon. to Sat. 9.30 a.m. to 6 p.m., Thurs, half day 1 p.m. Send a 2½d. stamp with your name and address (in block letters please) for a copy of our current stock list, giving details of our supplies of new manufacturers' surplus equipment and ex-Government radio, radar and valves, etc.

TELEVISION

SOUND & VISION ON A SINGLE CHASSIS

SIZE: 10" LONG, 4½" WIDE, 1" DEEP

MADE POSSIBLE BY USING THE LATEST MINIATURE VALVES

LASKY'S RADIO
World Renowned for Service & Reliability

LONDON & BIRMINGHAM FREQUENCIES

10 VALVES

VALVE LINE UP.

V1.	6AM6.	Sound and vision R.F. amp.
V2.	6AM6.	Sound 2nd RF. amp.
V3.	6AM6.	Vision 2nd RF. amp.
V4.	6AM6.	Sound 3rd RF. amp.
V5.	6AM6.	Vision 3rd RF. amp.
V6.	6AL5.	Sound detector and noise limiter.
V7.	6AL5.	Vision detector and noise limiter.
V8.	6AM6.	Sound output.
V9.	6AM6.	Sync. pulse separator.
V10.	6AM6.	Video output.

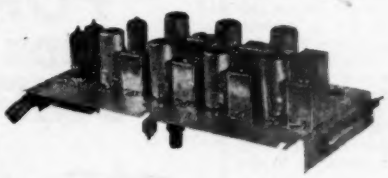

LASKY'S PRICE £6 19 6

Carriage 3/6 extra.

Complete with all valves. NO EXTRAS.

LONDON CHASSIS CONVERTS EASILY TO HOLME MOSS

These units are not ex-Government, but brand new manufacturer's surplus. May be used with any type time base and c.r. tube. The unit is fully assembled and wired, supplied with all valves and ready for fitting. Voltages required: 6.3 v. at 3 amps. and 270 v. at 80 m/a.

Send 6d. for a copy of the full data, circuits and photographs dealing with this unit. SAVES—SPACE, TIME, CASH.

Sold only at

LASKY'S RADIO

370 HARROW ROAD, PADDINGTON, LONDON, W.9.
(opposite Paddington Hospital)

Telephones: CUNningham 1979 & 7214. *Hours:* Mon. to Sat. 9.30 a.m. to 6 p.m. Thurs. Half Day 1 p.m.

GALPIN'S ELECTRICAL STORES

408 High Street, Lewisham, London, S.E.13

Telephone: Lee Green 0309 *Near Lewisham Hospital*

Terms:

CASH WITH ORDER. NO C.O.D.

EARLY CLOSING DAY THURSDAY

ALL GOODS SENT ON 7 DAYS' APPROVAL AGAINST CASH

EX-NAVAL CATHODE RAY UNITS, as new, containing loads of useful parts, Chokes/Transformers etc., weight 92 lbs. a few only to clear 25/- each, carriage 7/6. I.F.F. Units ex-R.A.F., containing ROTARY Generator 24 volts D.C. input 450 volts 50 M/amps. output. VALVES and many other useful parts to clear 22/6 each. Carriage paid.

MAINS BOOSTER TRANSFORMERS. 1,500 watts tapped 0, 6, 10, 19, 175, 200, 225, 240 and 250 volts, good condition, electrically guaranteed, £4/15/- each. Carriage 5/-.

HIGH CYCLE ROTARY CONVERTORS. 24 volts D.C. Input 100 volts, 3 phase, 400 cycles, approx. 60watts output, as new 35/- each. Carriage 3/6.

DOUBLE WOUND 3,000 WATT VOLTAGE CHANGER TRANSFORMERS. 130 to 250 volts or vice versa, weight 100 lbs., £10 each. Carriage 10/-.

REPULSION-INDUCTION ¼ H.P. MOTORS. 230 volt, 50 cycles 1 phase, complete with reduction gear, 50 r.p.m., by well known makers, a few only to clear, £8/10/- each. Carriage 10/-.

DOUBLE-WOUND TRANSFORMERS. Suitable for Welding etc. Input 230 volts, 50 cycles 1 phase. Output 50 volts, 100 amps., £15/10/- each. Carriage 10/-.

X-R.A.F. CRYSTAL MONITORS. Less Xtals and valves, these units contain many useful parts, Transformers/Condensers/Resistances etc., the basis of a midget receiver. To clear 5/- each. Post 1/-.

SWITCH-BOARD METERS. 4in. scale 0 to 14 amp. D.C., 17/6 each. 0 to 30 amp. AC/DC, 22/6. 0 to 14 amps. AC/DC, 22/6 each. All fully guaranteed.

MAINS TRANSFORMERS (New), all 200/250 volt primaries in steps of 10 volts. Output 350/0/350 volts, 450 m/a., 6.3 v. 8 a., 6.3 v. 8 a., 4 v. 4 a., 5 v. 4 a., 62/6 each · 500/0/450 volts 300 m/a, 6.3 v. 8 a., 6.3 v. 8 a., 4 v. 4 a., 5 v. 4 a., 62/6 each ; 500/0/500 volts, 300 m/a., 6.3 v. 8 a., 6.3 v. 8 a., 6.3 v. 4a., 5 v. 4 a., 3 v. 4 a., 67/6 each ; 350/0/350 volts, 250 m a., 6.3 v. 8 a., 4 v. 8 a., 4 v. 4 a., 6.3 tapped 2 v. 2 amps. (Electronic), 57/6 each. Carr. 3/6.

MAINS TRANSFORMERS (New), all with 200/250 volt primaries in steps of 10 volts ; output 350/0/350 volts, 180 m/a., 6.3 v. 8 a., 5 v. 3 a., 37/6 each ; 350/0/350 volts, 180 m/a., 6.3 v. 4 a., 5 v. 3 a., 4 v. 4 a., 37/6 each ; 500/0/500 volts, 150 m/a., 6.3 v. 4 a., 4 v. 4 a., 5 v. 3 a., 42/6 each ; 425/0/425 volts, 160 m/a., 6.3 v. 3 a., 6.3 v. 3 a., 5.3 a., 39/6 each. Carriage extra 1/6.

MAINS TRANSFORMERS. 230 volts, 50 cys., 1 ph. input, tapped output. 0, 6, 12, 18 volts at 4 amps., at 17/6 each, post 1/6; another 230 volt input, 700/0/700 volt, 70 m/amp., 12 v. 1 a., 4 v. 2½ a., 27/6 each, post 1/6.

METERS EX-W.D. SURPLUS (New), 2in. scale, moving coil 0 to 20 volts, 6/- each, post 9d. ; another 0 to 40 volts, 7/6 each, post 9d. ; another 0 to 10 amp., 12/6 each, post 9d.

EX-GOVERNMENT AUTO WOUND TRANSFORMERS (as new), 1,000 watts output, 115/230 volts or vice versa, £4/10/0 each, carriage 5/- ; another 1,000 watts, from 5 to 230 volts, with various tappings inclusive of 110, 150, 60, 90, etc., etc., all tappings at 1,000 watts, £5/10/0 each, carriage paid.

DUCOIN VARIABLE TARIFF ELECTRIC LIGHT Id./1s. SLOT METERS, all fully guaranteed 200/250 volt A.C. mains 5 amp. load, 42/6 each, carriage 2/6 ; 20 amp. load, 57/6 each, carriage 2/6.

SMALL SIZE CREDIT TYPE ELECTRIC METERS, 200/250 volt A.C. mains, overall size 4½in. x 3½in. x 3½in., weight 4 lbs., 10 amp. load, 25/-, post 1/- ; 20 amp. load, 30/-, post 1/- ; 25 amp. load, 35/-, post 1/-, fully guaranteed electrically.

BRIDGE MEGGERS, by well-known makers, 250 volt type, complete in leather carrying case, as new, £12/10/0 each, carriage and packing 7/6.

MAINS VARIABLE SLIDE RESISTANCES, protected type, by well-known makers, 450 ohms., 9 amps, 22/6 each ; ditto, 1,500 ohms to carry .45 amps, 22/6 each ; not protected, 0.4 ohms, to carry 25 amps, 10/- each ; 14 ohms to carry 1/4 amps, 12/6 each.

ROTARY CONVERTERS, 24 volts D.C. input, 50 volts 50 cycles, 1 ph. at 450 watts output, complete with step-up Transformer from 50 to 230 volts, £7/10/0 each, carriage 10/-, condition as new.

ROTARY CONVERTERS, EX-NAVAL, well-known makers, 100 volts D.C. input, 230 volts 50 cys. 1 phase at 250 watts output, capable of 100 per cent. overload, weight 100 lbs., condition as new, £10/10/0 each, carr. paid.

POWER TRANSFORMER AUTO WOUND, voltage changer tapped 0, 110, 150, 180 and 230 volts at 1,600 watts, £5/5/0 each, carriage 3/6 ; ditto, 2,000 watts, £6/5/0 each, carriage 3/6 ; another tapped 0 110, 200, 230 volts at 350 watts, at 48/6 each, carriage 2/-.

EXTENSION P.M. SPEAKERS. Makers, Johnson & Phillips, 3½in., 2/3 ohm., speech coil will handle 1½ watts (new, boxed), 8/6 each. Rotary Transformers, ex-R.A.F., D.C. to D.C., 28 volts to 1,200 volts at 70 m/amps., 7/6 each, carriage 1/6.

EX-R.A.F. MICROPHONE TESTERS. These contain a 2½in. scale 0 to 450 micro-amp. meter shunted to 1 m/amp., calibrated 0 to 10 volts, moving coil, complete w.th 1 m/a rectifier, "mike transformer," etc., all contained in polished wood box, as new, 17/6 each.

ELECTRIC LIGHT CHECK METERS, quarterly type, for sub-letting garages, apartments, etc., all fully guaranteed electrically for 200/250 volts A.C. mains, 50 cycs., 1 ph., 5 amp. load, 17/6 each ; 10 amp. load, 20/- ; 20 amp. load, 25/- each, 50 amp. load, 37/6 each ; carriage 2/- extra on each ; special discount of 10 per cent. on quantities of one dozen or more.

MAINS TRANSFORMERS (New). All 200/250 volts input in steps of 10 volts. Outputs, 0, 6, 12 and 24 volts at 10/12 amps., 47/- each ; 0, 18, 30, 36 volts at 5/6 amps., 42/6 each ; 0, 6, 12 and 24 volts at 25/30 amps., 48/6 each ; 0, 6, 12 and 24 volts at 5/6 amps., 35/- each.

CONDENSERS by well-known makers (new, boxed), 2,500 mfd., 50 v./wkg., 7/6 each. Smoothing Chokes, 3/5 Henries at 250 m/amps., as new, by well-known makers, weight 7 lbs., 12/6 each.

LAWRENCES
NEW RADAR EQUIPMENT

PROJECTION RADAR INDICATING EQUIPMENT MODEL V.G. TYPE CG-55AEB

Designed and produced by the General Electric Co., U.S.A., for installation in ships, shore stations, aerodromes or research establishments. This Projection Type Plan Position Repeater performs a duty similar to the conventional P.P.I., except that the pattern is optically projected on to a large flat horizontal surface, instead of being observed directly on a cathode ray tube face. The complete unit is approximately the size of a desk, 35in. high, with the viewing screen occupying half of the top surface, and is operated as a plotting table, on which the actual map-in-motion is portrayed. Navigational calculations are made directly on the paper viewing screen which can be replaced at will from a concealed 30 yard roll supply.

The full screen may be employed to map an area of 4, 10, 20, 80, or 200 miles radius, the choice of range being made by a range selector switch. Electronically generated range marks divide the screen into concentric rings for ranging purposes. In addition, two bearing scales are projected on to the screen, one being fixed to present true or relative bearing, the other rotating to present heading. The radar pattern is therefore far more significant, because it can be observed simultaneously with the pattern of actual bearing.

The equipment is designed for operation with any radar system, of repetition rates of from 60 to 1,000 per second, and only very limited arrangements are necessary to provide the video, trigger and synchro inputs.

BRIEF TECHNICAL SPECIFICATION

Power requirements : 115 v. A.C. Single phase, or 230 v. with auxiliary transformer. Total consumption 1765 watts.

Input requirements : Trigger voltage 5-40 volts peak. Video voltage 3 volts peak max.

Ambient Temperature Limits of Operation : 0°C to +50°C.

Screen Diameter : 25½in.

Picture Diameter : 24in.

Image Visibility : Image on Projection Screen may be observed in the presence of approx. 1 foot candle of indirect lighting.

Optical System : Highest grade lenses and components by Bausch & Lomb.

Range Accuracy : ± 1% of total designated range.

Bearing Accuracy : Within .75 degrees.

Overall Dimensions : 59in. x 34in. x 35in.

Weight unpacked : 1,000 lb.

The exceptional quality of construction, together with the numerous operational advantages, are several of many features which make this advanced equipment of outstanding interest in the field of Radar Engineering.

RADAR INDICATING EQUIPMENT MODEL VE. TYPE CAY-55ADV

Manufactured by The Westinghouse Mfg. Co., U.S.A. A Plan Position Indicator Repeater of conventional type employing a seven inch electro-magnetic cathode ray tube. Instrument is fully enclosed in console type housing.

BRIEF TECHNICAL SPECIFICATION.

Power requirements : 115 v. A.C. Single phase, or 230 v. with auxiliary transformer.

Range Calibrations : Electronic, with switched selection of ranges 4, 20, 80, 200 miles radius.

Overall Dimensions : 13in. x 24in. x 26in.

Full technical details of the above equipments available on request.

LAWRENCES, 61 BYROM ST., LIVERPOOL, 3

Phone: CENtral 4430

CONSTRUCTORS!!
HERE'S A BARGAIN FOR YOU!
POUNDS WORTH OF COMPONENTS
FOR ONLY 5/-

The home constructor should derive a lot of satisfaction from this chassis—it contains so much of value to him. It might even have the very component he has been looking for.

The light but immensely strong steel framework, paxolin and aluminium panels, stand-off insulators and the innumerable lengths of high-quality, beautifully insulated leads are all worth far more than is being asked for the whole chassis.

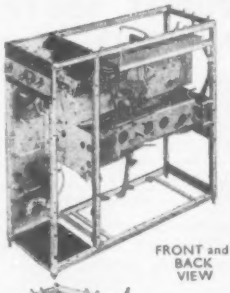

FRONT and BACK VIEW

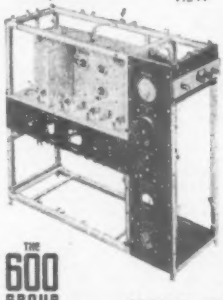

THE 600 GROUP OF COMPANIES

READ THIS :—

Average Contents (all new and unused).

- 5 250 K. 1-watt Resistors.
- 4 100 ohm. 1-watt Resistors.
- 2 600 v. 1 mf. Condensers.
- 9 High-voltage Condensers, .0001 to .01.
- 1 3-way Switch.
- 2 H.F. Chokes.
- 1 Relay Switch.
- 1 Ceramic Valve Holder.
- Lamp fuse with holder.
- Spring Terminals.
- Paxolin Panel 6½in. x 5in.
- Aluminium Panel, black finished.
- Large number Multi-coloured sleeved leads.
- Very strong steel framing.
- Innumerable Nuts and Bolts, Soldering points.
- Stand-off Insulators, etc., etc.

The whole outfit, weight 18 lbs, sent to any address for only 5/-. plus 2/3 part cost of packing and carriage.

SPECIAL OFFER: 4 for £1, carriage paid.

THE NEW LONDON ELECTRON WORKS, Ltd.

Dept. 92, EAST HAM, LONDON, E. 6.

Telephone: Grangewood 0044-1363

Measure those Millivolts

with the

Furzehill

SENSITIVE VALVE VOLTMETER

This instrument enables measurements from 1mV to 100 volts to be made within the frequency range of 10 c/s to 500 kc/s. The meter is calibrated with a logarithmic scale for voltage readings, and a linear scale for decibel readings together with a constant reading accuracy of 5% at all points.

FURZEHILL LABORATORIES LTD.
BOREHAM WOOD, HERTS. ELStree 3940

Audix SCHOOL RADIO

THE NEW MODEL – R.A. II.

for Schools, Institutions, Hospitals, etc.

- POWER OUTPUT 10 WATTS (3 Ω PUSH-PULL)
- INPUT FOR GRAMOPHONE
- TUNING INDICATOR and MONITOR SPEAKER
- MAINS KEY SWITCH
- SPEECH-MUSIC TONE CONTROL
- POLISHED OAK CABINET

Price
£24 . 3 . 8 Inc. Tax.

Audix B.B. Ltd.

HOCKERILL WORKS · BISHOP'S STORTFORD · HERTS.
'Phone : Bishop's Stortford 1394

RADIO SUPPLY CO.

34, HANOVER STREET, PARK LANE, LEEDS, 1. *(Telephone 22153)*

Post Terms C.W.O. or C.O.D. No C.O.D. under £1. Postage 1/2 charged on orders under £2. Open to callers 9 a.m. to 5.30 p.m., Sats., until 1.0 p.m. Full list 3d. Special list for Trade 3d.

R.S.C. MAINS TRANSFORMERS

Fully Guaranteed, Interleaved, and Impregnated. Primaries 200-230-250v., 50 c/s.

DROP THROUGH TYPES WITH TOP SHROUD

260-0-260 v. 70 ma., 6.3 v. 2 a., 5 v. 2 a.... 12/11
350-0-350 v. 70 ma., 6.3 v. 2 a., 5 v. 2 a.... 14/11
350-0-350 v. 80 ma., 0-4-6.3 v. 2 a., 0-4-5 v. 2 a. 18/9
260-0-260 v. 90 ma., 6.3 v. 3 a., 5 v. 2 a. 17/6
350-0-350 v. 90 ma., 6.3 v. 3 a., 5 v. 2 a.... 18/9
250-0-250 v. 100 ma., 6.3 v. 4 a., 5 v. 3 a. 21/9
250-0-250 v. 100 ma., 6.3 v. 6 a., 5 v. 3 a., for R1355 conversion 23/11
350-0-350 v. 100 ma., 6.3 v.-4 v. 4 a. C.T., 0-4-5 v. 3a. 21/11
350-0-350 v. 120 ma., 6.3 v. 4 a., 5 v. 3 a. 25/9
350-0-350 v. 150 ma., 6.3 v. 4 a., 5 v. 3 a. 27/11

FULLY SHROUDED UPRIGHT MOUNTING

250-0-250 v. 60 ma., 6.3 v. 2 a., 5 v. 2 a., Midget type 2½-3-3in. 16/11
350-0-350 v. 70 ma., 6.3 v. 2 a., 5 v. 2 a.... 18/9
250-0-250 v. 100 ma., 6.3 v.-4 v.-4 a. C.T., 0-4-5 v. 3 a. 23/9
250-0-250 v. 100 ma., 6.3 v. 6 a., 5 v. 3 a., for 1355 Conversion 26/9
300-0-300 v. 100 ma., 6.3 v.-4 v. 4 a., C.T., 0-4-5 v. 3 a. 23/9
350-0-350 v. 100 ma., 6.3 v.-4 v. 4 a. C.T., 0-4-5 v. 3 a. 23/9
350-0-350 v. 120 ma., 6.3 v. 4 a., 5 v. 3 a. 27/9
350-0-350 v. 150 ma., 6.3 v. 2 a., 6.3 v. 2 a., 5 v. 3 a. 29/11
350-0-350 v. 250 ma., 6.3 v. 6 a., 4 v. 8 a., 0-2-6 v. 2 a., 4 v. 3 a., for Electronic Eng. Televisor 63/-
425-0-425 v. 200 ma., 6.3 v.-4 v. 4 a. C.T., 6.3 v.-4 v. 4 a. C.T., 0-4-5 v. 3 a., suitable Williamson Amplifier 47/6
325-0-325 v. 20 ma., 6.3 v. 0.6 a., 6.3 v. 1.5 a., for Williamson Preamplifier..... 15/11

FILAMENT TRANSFORMERS

All with 200-250 v. 50c/s. primaries : 6.3 v. 2 a., 7/6 ; 0-4-6.3 v. 2 a., 7/9 ; 12 v. 1 a., 7/11 ; 6.3 v. 4 a., 14/9 ; 6.3 v. 6 a., 16/9 ; 0-2-4-5-6.3 v. 4 a., 16/9 ; 24 v. 1.5 a. or 24 v. 3 a..... 16/9

CHARGER TRANSFORMERS

All with 200-230-250 v. 50c/s. Primaries : 0-9-15 v. 1.5 a., 12/9 ; 0-9-15 v. 3 a., 15/9 ; 0-9-15 v. 6 a., 21/9 ; 0-4-9-15-24 v. 3 a., 21/9 ; 0-9-15-30 v. 3 a. 22/9

SMOOTHING CHOKES

200 ma. 5 h. 100 ohms..... 7/6
100 ma. 10 h. 100 ohms..... 7/6
80 ma. 12 h. 350 ohms..... 5/3
60 ma. 15 h. 400 ohms..... 4/6
40 ma. 10 h. 350 ohms..... 3/3

FILAMENT AUTO TRANSFORMERS

6.3 v. to 4 v. 3 a., or 4 v. to 6.3 v. 3 a.... 7/11

ELIMINATOR TRANSFORMERS

200-250 v. 50 c/s. input, 120 v. 40 ma. output 7/9

OUTPUT TRANSFORMERS

Midget Pentode 35 ma. for 25A6, 25L6, etc. 2/3
Midget Battery, Pentode 66 : 1 for 354, etc. 3/6
Medium Pentode, 5,000 ohms to 3 ohms 2/9
Standard Pentode 5,000 ohms to 3 ohms 4/6
Multi ratio 40 ma., 30 : 1, 45 : 1, 60 : 1, 90 : 1 Class B Push-Pull 5/3
Push-Pull 10-12 watt 6V6s to 3 or 15 ohms 15/11
Push-Pull 10-12 watt to match 6L6, PX4, 6V6, etc., to 3-5-8 or 15 ohm speaker ... 15/11
Push-Pull 15-18 watt to match 6L6, etc., to 3 or 15 ohm speaker 19/9
Williamson type exact to author's spec. 72/-

RECEIVER CHASSIS, 16 s.w.g., Aluminium : 10-5½-2in., 3/3 ; 11-6-2½in., 3/9 ; 12-8-2½in., 4/6 ; 16-8-2½in. 5/6

AMPLIFIER CHASSIS, 16 s.w.g., Aluminium : 12-8-2½in., 6/6 ; 16-8-2½in., 7/11 ; 20-8-2½in. 10/6

ELECTROLYTICS, 4 mfd. 200 v. Tubs : 9d. ea., 6/- doz. ; 8-8 mfd. 500 v. cans 2/11 ea. ; 8-16 mfd. 450 v. cans ..... each 3/9

MISC. ITEMS, ex-Govt. Aladdin Coil Formers, Slug Tuned, 4/- doz. T.V. Masks, 12in., White, 12/9. Receiver Cabinets, 16½ x 9½ x 7½in. approx. cut for Dial and Speaker. Complete with Speaker, Fabric and Back, Cream Cellulose finish, 12/6 ea. Ex-Govt. Receiver Units, type 71, less valves, 6/9. Ex-Govt. Condensers, block paper, 1 mfd. 1,000 v., 4/9 doz. Vol. controls with D.P. switch, spindle, 1in., 25K, 100K, 2/9 ea.

BRAND NEW GOVT. SURPLUS VALVES (boxed), 954, 955, 956, 2/9 ; 9004, 1/11 ; VR91, 5/11.

TRIMMERS AND PADDERS

4-40 pfd., 3/11 doz. ; 5-50 pfd., 5/- doz. Twin types 50-150 pfd., plus 50-150 pfd., 11/- doz. ; 10-100 pfd., plus 100-500 pfd., 10/6 doz. ; 100-600 pfd., plus 100-600 pfd., 14/- doz.

EX-GOVT. ELECTROLYTICS

50 mfd. 12 v. Solar Cans, 6/9 doz. ; 16 mfd. 175 v. cans, 5/3 doz. ; 250 mfd. 12 v. cans, 5/3 doz.

FULL RANGE OF STANDARD COMPONENTS AVAILABLE AT KEEN PRICES. ALL GOODS GUARANTEED AND NEW, UNLESS OTHERWISE STATED.

"You're CERTAIN to get it at ARTHURS!"

★ **VALVES:** We have probably the largest stock of valves in the country. Send your enquiries.

AVO METERS IN STOCK

Avo Model 7 ..... £19 10 0
Avo Model 7, high resistance..... £19 10 0
Avo Model 40 ..... £17 10 0
Valve Tester £16 10 0
Avo Minor, AC/DC model £8 10 0
Electronic Test Meter £35 0 0
Signal Generator £25 0 0
Valve Characteristic Meter..... £50 0 0

★ Demonstration of Philips Projection Television sets in our showrooms.

TAYLORS METERS. List on request
DECCA PICK-UPS..... £3 15 5
DECCA HEAD..... £2 19 2
ADAPTOR for Garrard 3 8
COSSOR DOUBLE BEAM OSCILLOSCOPE £85 10 0

"Viewmaster" Television Kits in stock for Birmingham and London areas. Please state which required.

LONDON'S OLDEST LEADING RADIO DEALERS

LATEST VALVE MANUALS
Mullard - 1/- & 2/- ea.
Mazda - 5/- ea.
Brimar - Teletube and Radio - 4/-
Mullard Valve Replacement Guide 1953-49 - 2/6
Post 6d. each extra.
Send for catalogue.

Arthurs EST. 1919

PROPS: ARTHUR GRAY, LTD. *Terms C.O.D. or cash with order*

Our Only Address. **Gray House, 150/152 Charing Cross Rd., London, W.C.2** *TEMple Bar 5833/4 and 4765*

ELECTRICAL, TELEVISION & RADIO ENGINEERS

R.C.A. TRANSMITTER

ET4336 COMPLETE

NEW AIR TESTED

Available in quantity for export.

SPECIAL TERMS TO LICENSED AMATEURS.

FREQ. METERS BC 221
few still available.

TRANSMITTING TUBES — ALL TYPES.

SQR 522, VHF Trans/Rec.

BC 375E TUNING UNITS
New, with cases, TU 7/8/9/10 and 26B. 12/6 each, + 2/- carriage. TU 5 and 6, 22/- each, + 2/- carriage.

IDEAL 25 WATT TRANSMITTER
Army Type No. 12, Frequency Coverage 1.2 to 17.5 mc/s, in Four Switched Bands. C.W. and Phone, Built-in Modulator, A.C. Mains, 100 Volt or 250 Volt, Complete with all Tubes and Delivered. £18.

Send for details of our compact EX/TX F-U-40. 40 watts.

HALLICRAFTER U.K. AGENTS

McELROY-ADAMS MFG. GROUP LTD.

46 GREYHOUND ROAD, LONDON, W.6.

Cables: Hallicraft, London. Phone: FULham 1802.

SOME INTERESTING OFFERS THIS MONTH

1 EACH ONLY OF THE FOLLOWING COMMUNICATION RECEIVERS:

HALLICRAFTER SUPER SKYRIDER. Black Crackle Case. 10 valves and magic eye. 110-220 v. A.C. Crystal Phasing. 5 bands. 550 Kc/s-38 Mc/s. Excellent condition, **£25.**

H.R.O. 9 valves. As new. With 1 coil. .9-2.05 Mc/s, **£25.**

JUST ARRIVED. A new consignment of **1155 RECEIVERS.** Brand new in transit cases. Aerial tested before despatch. **£10/10/-**, carr. 7/6.

THE FOLLOWING ARE TWO RARELY OBTAINABLE BARGAINS.

BC375 TRANSMITTER. Complete with 4 Tuning Units and Motor Generator. First-class order and condition, **£25.**

NO. 48 EQUIPMENT. 1 only entirely complete. Brand new and unused. Briefly comprises Sender, Receiver, 11 valves and 11 spares, microphone, key, pedal generator, cases, cables, aerial, etc. First **£30** secures.

ET4336 TRANSMITTERS. Rough condition. Need minor repairs. 10 only to clear at ridiculous price. **£13/10/-** each, carr. paid.

BRAND NEW SPARES FOR ET4336 AS FOLLOWS

CHOKES R.C.A. 110C/2673. Heavy duty smoothing. Weight 19lb. Size 6in. x 6in. x 4in. Suitable for any purpose requiring heavy duty unit. Brand new, **5/-** each, carr. 2/6.

MODULATION TRANSFORMERS, RCA 110K/117 working into 2 805's. Weight over 5 lb. 4½in. x 3½in. x 3in. Brand new. **5/-**, carr. 1/-.

CRYSTAL MULTIPLIERS, brand new and unused. Complete with 2/807 valves, **45/-**, carr. 5/-.

WE HAVE THOSE HARD TO GET RESISTORS FOR THE ET4336.

100 watts. 3.150 k. (3), 40 k. (suitable substitute for 31), 5 k. (1), 2 Screw-in Resistors 660 watts. 4 fuses. The Kit **55/-**, carr. paid.

VOLTAGE CONTROL UNITS. Type C3. Has On/Off Switch, Pilot light, 6 Bank fuse panel, 5 and 3 mfd. Condenser. Heavy duty mains noise filter, excellent case. **12/6**, carr. 1/6.

CAY 471S1A TUNING UNITS. 800-1500 Kc/s. Brand new with case and lid. **15/-**, less case **10/-**, carr. 2/6.

CATHODE RAY TUBES. 3BP1. Brand new, boxed. **19/6**, postage 1/-.

BC357 MARKER BEACON RECEIVERS. 2 valves. 12C8 and 12SQ7, Super Sensitive Relay. **12/6**, post 1/-.

RF 24 UNITS. Complete with 3 valves. 5 spot Frequencies. 20-30 Mc/s. **21/-**, post 1/6.

COLLARO GRAM UNITS. AC504. Latest type. Rim Drive Complete with Pickup (not auto change), **£6/11/-**, carr. 1/6 (6 only).

AMPLION CRYSTAL PICKUPS. Brand new. In Cartons, **26/9**, post paid.

TELEVISION PRE-AMPLIFIERS. Fitted with EF50. Very compact. Available for London and Birmingham. Needs 6 v. L.T. and 200/275 H.T. as previously advertised. Now selling the last 1,000. **15/-**, post 1/-. Enquiries must be accompanied by 2½d. stamp.

H.P. RADIO SERVICES LTD.

Britain's Leading Radio Mail Order House

Est. 1935

55, COUNTY ROAD, WALTON, LIVERPOOL, 4

ALEC Davis SUPPLIES Ltd.

Dept. W.W.

18 TOTTENHAM COURT ROAD, LONDON, W.1

Tel.: MUSeum 2453/4539

Shop hours: Monday - Friday 9—5.30 *Saturday* 9—1

FULL MAIL ORDER FACILITIES. ***Please add postage***

THE FAMOUS R.1155 RECEIVER. Needs no introduction. Supplied in original transit case, in perfect condition. Each Receiver aerial tested before despatch. Our price, **£8/19/6** (plus 10/- packing and carriage).

RECEIVER UNIT TYPE 184. Absolutely brand new, comprising four EF50, seven SP61, one Klystron CV67, three Neons, motor, I.F. Strip, etc., etc., less a relay which has been removed from under the chassis. Price **55/-**, plus 3/6 packing and carriage.

R.3584 RECEIVERS. Absolutely brand new in sealed manufacturer's packing case, including complete 45 mc/s. I.F. strip 15 valves type EF50, EF36, EBC33, two SP61, three EB34, relays motor, dial, drive, pots., and hundreds of resistors and condensers Only **£6** each (plus 10/- packing and carriage).

STROBE UNIT TYPE 68. Absolutely brand new in sealed cartons including six valves type EF50, five type EA50, 5Z4G, SP61, relays, transformers, potentiometers, slow-motion dial and drive, hundreds of resistors and condensers. Price **69/6**, plus 5/- carriage and packing.

INDICATOR TYPE 6. Needs no introduction. Absolutely new in manufacturer's packing case. As recommended for ex-Govt. T.V. construction, and "Wireless World" Oscilloscope. Incorporates VCR97 and mu-metal shield, 4 valves EF50, three of EB34, etc., Only **75/-** (plus 7/6 carriage and packing).

BAKELITE RECEIVER CABINET. Size 12in. x 5in. x 6in. high. In Brown or Ivory. Supplied complete with ready-drilled 4-valve T.R.F. chassis, with cut-out for 5in. speaker. 2-wave glass dial, back plate, mounting brackets and back. Only **25/-** plus 1/- packing and postage. A very handsome cabinet. Drum, drive and pointer to suit, **3/-** extra.

MODULATOR UNIT TYPE 169. Absolutely brand new includes Klystron type CV67, EF50, 5U4G, three Neons type CV71, rectifiers, transformers, and shoals of condensers and resistors. At 35/- plus 5/- packing and carriage.

COMMAND RECEIVERS. Absolutely brand new, valve line-up, three 12SK7, 12K8, 12SR7, and 12A6, for 1.5-3 mc/s. for 28 volt input, including dynamotor, **69/6**, plus 3/6 packing and carriage.

RELAYS. We can supply all 600 and 3,000 G.P.O. types, with resistance from 1.9-42,000 ohms. Multi-contacts, Siemens high-speed, etc., etc. Price list on request. Manufacturers' enquiries invited.

UNIT TYPE 207A. Absolutely brand new, complete with Klystron CV67, 5Z4, three Neons type CV71, etc. **19/6**, plus 1/6 carriage.

SWITCHING RELAY UNIT TYPE CZR. Operation double coil 2 makes, one change-over, locking relay, 12 volt 1½ amps., contacts rated 6 amps. at 16 volts, etc., etc., in black crackle case. **15/-**, post free.

SPECIAL OFFER. Manufacturer's Surplus ultra-midget superhet coil pack for 465 kc/s. and .0005 mfd. tuning. For Medium and Short-waves only. Size only 3in. × 2¼in. × 1¼in. deep. Iron-cored coils, complete with circuit. Price **19/6** only, plus 9d. post.

I.F. TRANSFORMERS. Manufacturer's surplus. Iron-cored. 465 kc/s. Size 4in. × 1¼in. × 1¼in. Per pair **8/6** only.

"DENCO" ALIGNMENT OSCILLATOR D.A.O.I. This unit provides a modulated signal for the alignment of I.F. amplifiers and associated circuits.
The two standard frequencies of 465 kc/s. and 1,600 kc/s. are selected at the turn of a switch.
All supplies are derived from one U.10 cell and one 1289 battery inside the unit. Consumption of 50 m/a. single valve type DL92 is used. Dimensions of case: width 3¾in., depth 2¼in., height 4¼in. Price only **39/6**, post free.

A.D.S. QUALITY AMPLIFIERS. Full constructional details of our 4½-watt inexpensive quality amplifier are now available including circuit diagram and layout pictures. Post free, **10d.**
Complete set of components for above amplifier, including cabinet, chassis, knobs, etc. Carriage free, only **£7/15/-**.
Complete amplifier, constructed and tested. Carriage free, only **£9/17/6.**

We are situated 100 yds. only from Tottenham Court Road Underground Station. A visit will prove well worth while.

Henry's

RADIO COMPONENTS
ELECTRONIC & TELEPHONE EQUIPMENT

931A PHOTO-CELL MULTIPLIER AMPLIFIER UNIT COMPLETE. Incorporating 931A photo-cell, 2 valves type 6AC7, 6AG7, etc., etc. Can be adapted for use in window lighting, warning systems, locating foreign bodies in liquids, flaws in textiles, burglar alarms, circuit switching by relays, etc., etc. Panel size 9½in. x 3½in. Circuit diagram not available. Price 45/- complete, post free.

R.3515 I.F. STRIP. A complete I.F. Unit, comprising 6 SP61 I.F. Stages, tuned to 13.5 Mc/s., 1 EA50 diode detector, and 1 EF35 or EF39 output or video stage. A few modifications only are required to adapt this unit, which will give pictures of extremely good quality. Price, complete with valves, and foolproof modification instructions, is 45/-, plus 5/- carriage and packing. Limited quantity only.

R3547 RECEIVERS. Absolutely brand new, in sealed manufacturers' packing cases. Incorporating 15 valves type EF50, 2 of SP61, EF36, EBC33, 3 of EB34. Complete 45 Mc/s. I.F. Strip, motor dial and drive, pots, etc., etc. £6 only, plus 10/- packing and carriage. Whilst they last!

EX-R.A.F. INDICATOR UNIT TYPE 62. Containing VCR-97 CRT with mu-metal screen; Xtal Unit and valves 16/VR65 (SP61) 2/VR54 (EB34) 2/VR92 (EA50), etc., etc., two deck chassis in metal case. 18 x 18½ x 11½in. New condition. 67/6 each. Plus 7/6 packing.

INDICATOR TYPE 6. These units are brand new, in excellent condition, and are all fitted with a VCR97 CRT, the tube which many constructors have put to T.V. use. Valves include 4/VR9 (EF50), 3/VR54 (EB34), plus a host of potentiometers and H.V. condensers, etc. The complete unit is enclosed in a metal box 18 x 8½ x 7½in.
PRICE ONLY £3/19/6 POST PAID
Please include 10/- for transit case to ensure safe transit of unit. Refunded on return of case.

RECEIVER TYPE 21. The receiver portion of the W/S 21 operating from 4.2-7.5 Mc/s. Double superhet from 18-30 Mc/s. Incorporating B.F.O. and crash limiter. Valve line-up 7-ARP12 (VP23) and 2-AR8 (HL23DD). Absolutely brand new, complete with circuit. Only 45/- complete. Vibrator Power Unit for above, brand new, 17/6 only.

NO. 38 "WALKIE TALKIE" TRANS-RECEIVERS. Complete with Throat Mike, 'Phones, Aerial Rods, and Data Sheet. Freq. Range: 7.4 to 9 m/cs. Brand new and guaranteed, £4/19/6. Carr. 2/6.

RECEIVER R. 1355 as specified for "Inexpensive Television." Complete with 8 valves VR65, and 1 ea. 5U4G, VU120, VR92, and a copy of "Inexpensive TV." ONLY 55/- (carriage, etc., 7/6).

METAL RECTIFIERS. S.T.C. 300 volt 75 mA, 5/-, 24 volt 2½ amp., 17/6; G.E.C. 6 v. 1 a., 4/-; J 50, 7/6; H 4/200 2,400 v., 3 mA, 15/-; WX6, W6, 1/6; CV102 crystal rect., 3/6.

6½in. WAFER SPEAKERS. Special offer of the above well-known speaker, listed at 25/-. Limited quantity available, brand new, at 15/- each. Post Free.

DUAL PURPOSE MAINS-TRANSFORMERS. Special 350-0-350 v. 80 mA, 6.3 v. tapped 4 v. at 3 a., 5 v. tapped 4 v. at 2 a. Top chassis mounting and fully guaranteed. 18/6 only, plus 9d. post.

ELECTROLYTIC OFFER. By leading manufacturers. All metal can. 16 x 8 mfd. 500 v.w., can size 3½in. x 1⅝in., 3 for 10/-. 32 mfd. 450 v.w. (550 v. Surge) BE37P, can size 4½in. x 1⅝in., 3 for 13/6. Also 16 mfd. 500 v.w. size 2in. x 1in., 3 for 7/6, 8 mfd. 500 v.w. type CT850, can size 2½in. x ¾in., 3 for 7/-. Post paid.

FREQUENCY CONTROL CRYSTALS. By American G.E. Co., Octal base fixing. Following frequencies only: 2,500 Kc/s, 3,500 Kc/s, 4,600 Kc/s, 8,000 Kc/s, at 7/6 each only. NEW.

MILLIAMMETERS. 0-1 mA, 2in. scale, square, moving coil, panel mounting, only 10/- each.
0-1 mA, 2½in. scale, moving coil, panel-mounting, 15/- each.
0-5 mA, 2½in. scale, moving coil, two mounted on panel, 12/6 pair

MICROAMMETER. 0-500 micro a., 2in. scale, moving coil, panel-mounting, 7/6 each.

MIDGET .0005 mfd. TWO-GANG TUNING CONDENSER. Size only 2⅜in. x 1⅜in. x 1⅜in. Capacity guaranteed, standard length ¼-in. spindle, complete with mounting bracket, less trimmers, 6/6 or, complete with "built-in" trimmers, 7/6 each plus 6d. post.

MAINS TRANSFORMERS. 250-0-250, 90 mA, 6.3 v. 3 a., 5 v. 2 a., half shrouded, drop through type. Electrostatic screen. Price 15/- only, plus 9d. post. Limited quantity.

I.F. TRANSFORMERS. Manufacturers' surplus. Iron-cored. 465 Kc/s. Size 4in. x 1⅛in. x 1⅛in. Per pair 8/6 whilst they last.

Send stamp for current Component List—
Probably the most comprehensive in the trade

5, HARROW ROAD, LONDON, W.2
PADdington 1008/9 and 0401

Used and recommended by the Leading Set Manufacturers for use by their Authorised Service Dealers

The Radar Video & Sync Generator provides a fully synchronised and correctly proportioned television test pattern together with sound to allow any receiver to be checked and adjusted outside of transmission hours, leaving the set in perfect order so that the viewer can switch on, when the programmes are being transmitted, with the certain knowledge that the set will not require any further adjustment—hence the use of this unique instrument both by leading manufacturers and authorised dealers throughout the transmission areas. Enquire to-day for details of models for London, Midland or Northern frequencies.

ENSURE A FULL 8-HOUR SERVICING DAY
with the
Radar
video & sync generator

TEL., ENT 5967

RADAR, RADIO & TELEVISION
26, Oakleigh Rd., New Southgate, London N.11

U.H.F. TRANSMITTER-RECEIVERS
of special interest to all enthusiasts on 420 Mc/s.

We still have a very limited number of complete Transmitter-Receivers Type RT-3A/ARN-1. These consist of an F.M. Transmitter and Receiver (a total of 13 valves are included), each containing a built-in Power Pack for direct operation from a 24-volt supply. Black Crackle cases slightly store soiled.

SPECIAL PRICE **79/6.**
Carr. and Packing paid.

Send stamp today for our NEW YEAR BULLETIN.

WALTON'S WIRELESS STORES,
203, STAVELEY ROAD, WOLVERHAMPTON

COILS • COILS • COILS

T.R.F. • SUPERHET • FILTERS • PACKS
TELEVISION COILS • I.F. TRANSFORMERS

FOR DEPENDABLE COMPONENTS CONTACT

OLYMPIC RADIO COMPONENTS
COIL WINDING SPECIALISTS & MANUFACTURERS
224, HORNSEY RD., N.7. NORTH 2914

Recognised as the Most Reliable Valveholders

Now in full production
NOVAL and B7G
Valveholders
of all types in
NYLON LOADED BAKELITE

B9A—NOVAL

B 7 G

We make all types of Valveholders

THE McMURDO INSTRUMENT CO., LTD., VICTORIA WORKS, ASHTEAD, SURREY · ASHTEAD 3401

PERFORMANCE PROOF OF FELICITY AMPLIFIERS

WARREN'S RADIO
88b WELLINGTON STREET
LUTON, BEDS.

Felicity Amplifiers S.W.15. 28/12/50.

Dear Sirs

We thank you for your prompt attention to our 'frantic' order of last week. Both the customer and ourselves are delighted with the amplifier's performance; it has in fact already sold another.

Quite frankly we have up to now only sold high fidelity amplifiers of high output and high cost with naturally limited sales. It would seem that there is quite a big demand for a low power but good quality amplifier, therefore we intend to stock and demonstrate your amplifiers; accordingly we enclose an order for two Minor amplifiers and RC/1 units. We shall undoubtedly be ordering other models and tuner units in the near future.

Yours, etc.,
p.p. WARREN'S RADIO,
Haydon G. Warren (Signed).

Start catering NOW for high fidelity with this new amplifier Incorporates all the essentials for first-class reproduction.

● Wide frequency range, 40-15,000 cps., with adequate variable bass lift and treble cut ● Hum-free at full output. ● Harmonic distortion below 1%. ● Attractive finish and layout. ● 33⅓% discount. ● Immediate delivery.

Microphone stage can be supplied as extra at £3/15/- list.

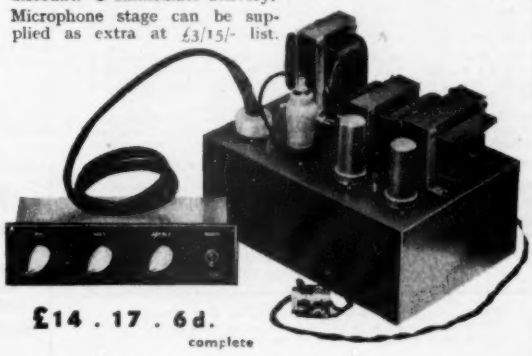

£14 . 17 . 6d.
complete

Also 10 watt Power Amplifier. Response 20-20,000 ~ Distortion under .5%. Push-pull output of 10 watts. Price **£21 . 10 . 0** list.

Tuner Units. Model SH6 3-waveband superhet with RF Stage.
Model PB5 TRF 4-station push-button.

FURTHER DETAILS AND LITERATURE FROM

FELICITY AMPLIFIERS, 26a, Wadham Rd., Putney, London, S.W.15. *Tel.: VANdyke 7533*

For Quality Bargains Always

—Best Buy at Britain's

Receiver R3584. Contains 15 of EF50, 1 of VR56 (EF36), 1 of VR55 (EBC33), 2 of VR116, 3 of VR54 (EB34), 1 of VR92 (EA50), and a 45 Mc/s. "Pye" Strip; also included are 11 pot'meters, a motor with gear box, relays and numerous other small components all mounted on an extremely useful chassis. BRAND NEW IN TRANSIT BOXES. ONLY £5.19.6. Carriage paid to your door.

Oscillator Type 217. Contains 2 of EF50, 2 micropack condensers, 25 mfd. 25 v. heavy duty resistors, 3 relays, 3 pot'meters, etc. A small unit with a large content at less than the price of the two EF50s. NEW AND BOXED 14/6 post paid.

45 Mc/s. "Pye" Strip. A ready made vision receiver. (London frequency). Uses 6 of EF50 and an EA50. Complete circuit data provided. In brand new condition. Less valves, 39/6, with all valves, 62/6.

Receiver Type 21. A battery operated superhet receiver covering 4.2-7.5 Mc/s. and 19-31 Mc/s. Operates as a double superhet on the 10 metre band. Complete with nine 2v. valves and circuit diagram. In new condition, 45/-. Carriage paid.

Indicator Unit 6H or 116H. Brand new and contained in manufacturers' original wooden crate. A more up to date version of the famous 6A. Contents include a VCR97 tube, 4 or EF50, 3 of EB34 and very many other useful components. Priced at only 79/6 plus 7/6 carriage.

Communications Receiver Type R1155. Now world renowned as one of the finest receivers obtainable. For those not familiar with the set we can supply an authoritative *Wireless World* circuit and descriptive leaflet at 9d. post free. All our receivers are air-tested before despatch and supplied complete with 10 valves. Any receiver gladly demonstrated to callers. The price is £9.10/- and for an additional 10/- the set is despatched in its original transit case. IN BRAND NEW CONDITION.

Shipping and Top Band. Listeners to these bands will be pleased to hear that we can now offer a Command Set with a frequency coverage of 1.5 to 3 Mc/s. (100-200 metres). These follow the same specification as the other types of Command Sets advertised below and are supplied complete with circuit diagram. The price is 59/6 post paid. In brand new condition and contained in black crackle cases.

Command Receiver Type BC454. A 6 valve superhet covering 3-6 Mc/s. Valve line-up: 3 of 12SK7, 1 of 12K8, 1 of 12SR7, 1 of 12A6—all metal valves. I.F. Value 1415 Kc/s. In brand new condition. Circuit data provided. Only 45/- carriage paid.

Command Receiver Type BC455. Frequency range of this set is 6-9 Mc/s. and the specification is exactly the same as the BC454 above. The price complete with circuit is 55/-. In brand new condition and contained in black crackle cases.

Receiver Type 159. Valve line-up: 1 of CV66 (grounded grid triode), 1 of EF50, 1 of VR65 (SP61), 1 of VR92 (EA50), small impulse motor, all in case size 8½ x 4½ x 6½ ins. A real bargain at only 12/6 post paid.

Amplifier Unit Type 18/165. A neat and compact equipment incorporating the following valves: 2 of EF36, 1 of EBC33, and 2 of EL32. Also included are microphone transformers, intervalve transformers, numerous condensers and resistors, etc. Are you looking for something to break down? Then here's your chance. An experimenter's gold mine for only 22/6. Post paid.

SCPI C.R. Tubes. Our stock now rapidly diminishing. Brand new and boxed. Only 25/- each post paid.

Blower Motors. For operation from 12 or 24v. A.C./D.C. but will run from mains when fitted with suitable dropper resistance. Has many uses—ventilation purposes, as a hairdryer, etc. AS NEW. Only 12/6 post free. We also offer a smaller model for operation on 24v. only, at 6/6 post free.

Meters. A.C. Voltmeter 0-100 Thermocouple 2½in. dial, in bakelite case size 4 x 4 x 2in. 12/6. A.C. Voltmeter 0-2 V. Basic movement 500 microamps 3in. face. Contains bridge metal rectifier. 12/6. Pocket Voltmeter, 0-250 v. and 0-15 v. 10/-. 0-20 Voltmeter, 2in. dial, 4/9.

Small 24 v. Motor. A.C./D.C. operation and complete with gear box. Will also work on 12 v. About 140 to 1 double reduction drive giving very high torque at slow speeds. New condition. Only 12/6 post paid.

INDICATOR UNIT TYPE 97. LESS VALVES & TUBE. A WEALTH OF COMPONENTS AT A TRULY RIDICULOUS PRICE. 64 RESISTORS, 13 POT'METERS, 27 CONDENSERS, A VCR97 HOLDER, EF50 and INTERNATIONAL OCTAL HOLDERS, etc. etc. ALL CONTAINED IN A USEFUL CASE SIZE 19 × 9 × 9 ins. ONLY 12/6 CARRIAGE PAID.

Our usual comprehensive range of valves, C.R. Tubes, components and specialised equipment in huge variety and at keen prices. Many, many bargains for the caller.

CHARLES BRITAIN (Radio) Ltd.
11, UPPER SAINT MARTIN'S LANE
LONDON, W.C.2 TEM. 0545

3 minutes from Leicester Square Station (up Cranbourn Street)
Shop Hours: 9-6 p.m. (9-1 p.m. *Thursday*). *Open all day Saturday*

1 KW TELEGRAPH TRANSMITTERS. Two HF 300's output. Operation 3.5 mc to 16 mc.

HALLICRAFTERS BC 610's. Complete with speech amplifier, antenna tuning unit; exciter units and coils for all bands.

RCA TRANSMITTERS. Type ET-4336. Complete with matched speech amplifier, crystal multiplier and VFO units. Brand new.

LM-300 TRANSMITTERS. (U.S.A.). 140 kc to 400 kc and 650 kc to 1,600 kc, 300 Watt output.

No. 12 TRANSMITTERS With coupling units, remote control etc.

AUTOMATIC HIGH SPEED TELEGRAPH EQUIPMENT. "BOEHME" (U.S.A.). Up to 400 signs per minute on line and wireless.

AR-88's, AR-77's, S-27's, HRO'S with coils and power pack, 1155's

SKYRIDER DIVERSITY HALLICRAFTERS RECEIVERS. Complete with console, power units and loudspeaker.

All above items in excellent working condition.
Working demonstration upon request.

TX VALVES 803, 805, 807, 813, 814, 832, 861, 866A, DET-16; 6L6 Met. and many others.

Large stock of Tx condensers, crystals and other components. Alignment and repair of communication receivers and all other short-wave equipment undertaken.

P.C.A. RADIO

Transmitter Division :—
The Arches, Cambridge Grove, London, W.6. *Tel. RIV 3279*

Receiver Division :—
170 Goldhawk Road, London, W.12. *Tel. SHE 4946*

NEON TEST PROD

Suitable for testing up to 250 V. supplies. Will indicate polarity and detect leakage. Housed in moulded rubber black case. Totally shockproof and safe.

A.F. BULGIN & CO., LTD.
BYE PASS RD., BARKING, ESSEX

RADIOMENDERS LIMITED

FOR SPECIAL TRANSFORMERS AND REWINDS

We specialise in
AMATEURS' WINDINGS, TRANSFORMERS ALL TYPES, CHOKES, PICK-UP COILS, INSTRUMENT COILS, Etc.

Highest workmanship **Good Delivery**

★

RADIOMENDERS, LTD.
Television & Radio Apparatus, Transformer & Coilwinders.
123-5-7 Parchmore Road,
THORNTON HEATH, SURREY
LIV 2261. Trade enquiries invited. Established 16 years.

MYCALEX
(REGD. TRADE MARK)
THE INSULATOR

MYCALEX TELEVISION DIPOLE and REFLECTOR AERIAL MOULDINGS

- Watertight assembly.
- Long leakage path.
- Element rods reinforced by the inserted metal tubes, at a point where fracture is liable to occur.
- Mycalex has high surface resistivity to moisture under damp conditions.
- Great physical strength due to nature of Mycalex which is a bond of Mica and Glass.

'Phone : CIRENCESTER 400 or send enquiries to

MYCALEX COMPANY LTD · ASHCROFT ROAD · CIRENCESTER GLOS

ENCLOSED RACKS

Imhof rack units are the most up-to-date enclosed racks available. They are made as standard in 6ft. and 4ft. sizes, to take 19in. panels and are 19in. deep. Semi-standard variations are depths of 24in. and widths to take 22½in. panels. Multiple assemblies of any number of racks can be built up requiring only two of the hinged end doors per assembly. The illustration is of a 3-unit assembly, showing one panel half extended on telescopic runners, the desk unit, and the gram unit which are standard extras. Also available are mobile bases for single units, and a large selection of panels, handles, chassis, brackets, etc. Special quotations can be given for non standard variations. Write for illustrated leaflet giving full information.

IMHOF'S

Regd. Design No. 855451.

ALFRED IMHOF LTD., 112-116, NEW OXFORD STREET, LONDON, W.C.1

Telephone : MUS 7878 (20 lines).

T.V. in the FRINGE AREAS

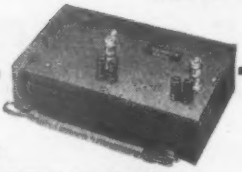

★

A Superior

PRE-AMPLIFIER

By 'RAINBOW'

For use with CO-AXIAL *or* BALANCED FEEDER

Built-in Power Pack, with Metal Rectifier, E.F.91 valve, exclusive Rainbow Coils. Complete with all Plugs, Crackle Finish, Steel Case $8\frac{3}{8}'' \times 4\frac{1}{4}'' \times 2\frac{1}{8}''$.

Alexandra Palace or Sutton Coldfield Model **Price £5 17 6**

is giving excellent results with Receivers by Bush, Pye, H.M.V., Marconi, Philips, etc.

Also available: 2-valve model for extreme fringe areas **£7 10 0**

It's to your advantage to write for fuller details.

RAINBOW RADIO MANUFACTURING CO. LTD.

Mincing Lane, Blackburn, Lancs., England

CONDENSERS	Silver Mica · Tubular · Mansbridge
CRYSTALS	American · British
HEADPHONES	High and Low Impedance
METERS	Thermo · Moving Coil · Moving Iron
PLUG & SOCKETS	All Types
RESISTORS	Carbon and wire wound
VOLUME CONTROLS	Carbon and wire wound

We hold large and comprehensive stocks of new components and units, both Government and Manufacturers' Surplus

No. 19 Set, Equipment Available.

Wholesale and Export Only.

ANDERS RADIO LTD.

167, HAMPSTEAD ROAD, LONDON, N.W.1
EUS. 1639 EST. 1928

LYONS RADIO Ltd.

RECEIVERS TYPE R3132. Easily modified for Television sound or vision or as a 2 metre receiver. This unit is almost identical to the R3084. Is fitted with seven VR91s, two VR136s, one VR137, one VR92, one VU134, one VU39, I.F. Amplifier strip, aerial switching motor, etc. In good used condition. **PRICE 50/-, carriage 5/6.**

MODULATOR UNITS TYPE 169. Contains one each of VR91, SU4, CV85, CV67 (Klystron), two Selenium rectifiers, about 330 v. max. input for 230 v. out at 30 m.a., tuning motor, high voltage condenser, etc. Built on neat metal chassis and housed in case, 18in. x 9in. x 7¼in. BRAND NEW and Unused. **PRICE 29/6, carriage 6/6.**

INDICATOR UNITS TYPE 62. These units are fitted with C.R. tube VCR97, sixteen VR65s, two VR54s, two VR92s, wire-wound pots., switches, condensers, crystal unit, resistors, etc. The whole built on metal chassis and fits into case 18 x 8½ x 11¼in. In good condition and C.R. tube tested before despatch. **PRICE £3 17 6, carriage 7/6.**

0-30 V. MAINS TRANSFORMERS. Primary 200-250 v. 50 c.p.s. Secondary tapped to give the following voltages: 3, 4, 5, 6, 8, 9, 10, 12, 15, 18, 20, 24 and 30 v. at 2 amps. total loading. Brand new and guaranteed. **PRICE 17/6, post 1/3.**

"PRACTICAL RADIO." For beginners wishing to commence the construction of Receivers. **PRICE 3/2, post paid.**

3, GOLDHAWK RD. (Dept. M.W.), SHEPHERDS BUSH, LONDON, W.12
Telephone: SHEpherds Bush 1729

G2AK *This Month's Bargains* G2AK

AR88D SPARE CRYSTALS. 455 Kc/s. 15/- each.

RECEIVERS. Type 18. Cover 6-9 Mc/s, and are for battery operation. New condition. Only 17/6 each. Phones to suit 4/6.

MOVING COIL HEADPHONES with moving coil microphone. Price 6/-. Post 1/-. Transformer to match 2/-. High resistance headphones, 4,000 ohms, 8/6 per pair. Post 1/-.

CABLE. 10ft. length flexible T.R.S. 3-core. Fitted with 3 position switch and plug. 1/6 post free.

VIBRATOR PACKS. 6 volt input. Output 180 volts 50 m/a., fully smoothed. Price 19/6, plus post 1/6.

TWIN RIBBON FEEDER. Heavy duty 300 ohm, 5d. per yd. Standard K25 300 ohm ribbon, 9d. per yd. Co-ax. cable, ¼in. dia. 70 ohm, 8d. per yd. ½in. dia., 1/- per yd. 7ft. length ½in. dia. Co-ax. with Pye plug one end, 1/6, post free. All other Co-ax., and feeder, plus 1/6 post any length.

POTENTIOMETERS. 5 watt wire-wound 20 k., 25 k., 2/-. 500 ohm and 2,000 ohm 50 watt wire wound on 3in. dia. Ceramic former, 3/6 each. Carbon Type Potentiometers, 50 k., 100 k., 1 meg., 2 meg., 1/6.

BRAND NEW 807 VALVES. 7/- each or 4 for 25/-.

AERIAL INSULATORS. Pyrex 7in. ribbed glass, 3/6 per pair, plus 1/- post.

STATION LOG BOOKS. 200 pages printed one side only. Size 8½in. x 11in. First class paper and bound with heavy cover. Price 17/6.

Carriage paid on all orders over £1 except where stated. Please include small amount for orders under £1.

Please print your name and address.

CHAS. H. YOUNG, G2AK

All Callers to ***110 DALE END, BIRMINGHAM***

Phone: CENTRAL 1635

Mail Orders to ***102 HOLLOWAY HEAD, BIRMINGHAM***

Phone: MIDLAND 3254

PRATTS RADIO

1070 Harrow Road, London, N.W.10

(Nr. SCRUBBS LANE) Tel. LADbroke 1734

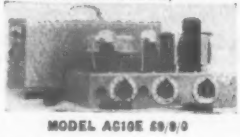

MODEL AC10E £9/9/0

AMPLIFIERS. College General purpose units. **MODEL AC10E,** 4 valve 10 watts neg. feedback, **£9/9/-. MODEL AC12E,** 6 valve, 12½ watt P/P Output. Feedback over 3 stages. **£13/19/6. MODEL U.10.E.** For DC/AC mains. 6 valve 10 watts P/P output. Feedback over 3 stages, **£11/11/-.** All the above are supplied with cases and chrome handles. They have **separate** microphone stage. Separate inputs for mike or gram, allowing individual fading, etc. Outputs match 3, 5 or 15 ohm speakers. Max. input volts required for stated output average .003 microphone, .3 v. gram. H.P. terms available. **MODEL AC8C,** 5 valve P/P 8-10-watt unit for records or radio, feedback over 3 stages, output to 3, 6, 15 ohms, **£9/19/6. MODEL AC4C,** 3 valve record/radio amplifier, 4 watts to 3 ohms, **£5/5/-,** ditto U4C for AC/DC mains **£5/5/-.** Stamp for list. Available from mid-March: **MODEL AC12E,** 32-watt version of AC12E. Delivery in strict rotation. Price **£17/17/-.** Full list of accessories for above available. May we send you our valve and transformer list?

All goods offered are new and unused. Nearest tube, Kensal Green.

HOME and OVERSEAS

RADIO DEALERS & SERVICE ENGINEERS

Write for our 1951 Wholesale Price List, giving details of A. W. F. Loudspeaker cone assemblies, for fast, economical repairs in your own workshops. A. W. F. Range of Transformers for nearly all replacements. T. C. C. Capacitors, Tungsram Valves, Erie Resistors & Potentiometers. "View Master" & "Electronic Engineering" Televisor Components & Cabinets. Brass B. A. Screws, etc., and hundreds of other lines. **Postage 3d.** Inland. 2/- Overseas Air Mail.

A. W. F. RADIO PRODUCTS

TATLER CHAMBERS · THORNTON ROAD

BRADFORD · YORKS.

SELECTED FOR THE FESTIVAL OF GREAT BRITAIN

. . . and this is what a "Ham" writes:—

"I am very pleased with this receiver and its selectivity is really wonderful. I would recommend this receiver to anyone desiring a receiver of high communication qualities."

"Q-MAX" Q5 10X COMMUNICATIONS RECEIVER

- 10 Valves
- Double Superhet
- 1·8-30 Mc/s.
- 6 Bands
- Crystal Gate
- 6 degrees of variable selectivity
- "S" Meter
- B.F.O.
- Noise Limiter

Price **55 Gns.**

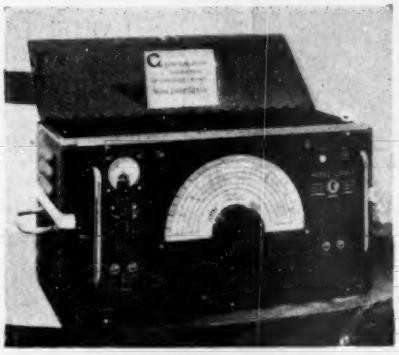

IN STOCK

DECCA twin speed motor	£5 19 10
Twin head	£3 10 4
CONNOISSEUR twin speed motor	£20 19 3
Pickup with Microgroove head	£5 14 8
Standard head (extra)	£3 11 8
WILLIAMSON AMPLIFIER: Components incl. full range of precision condensers, resistors, etc., and **OUTPUT TRANSFORMERS** by:	
WODEN	£5 7 3
VORTEXION (metal core)	£7 7 0
(Silicor 1 core)	£4 4 0
PARTRIDGE (unpotted)	£5 13 0
(Potted)	£6 6 0
LEAK "Point One" Amplifier	£25 15 0
PC/PA/U remote control Pre-amplifier	£8 15 0
BARKER Natural Sound Speakers:	
Model 148a	£15 15 0
Model 150	£18 18 0
W.B. Concentric Duplex:	
10in.	£7 7 0
12in.	£15 15 0
GOODMANS TWIN AXIOM	£8 8 0
WHARFEDALE:	
GOLDEN 10in.	£4 5 0
W10/CS 10in.	£7 10 0
W12/CS 12in.	£8 0 0
Speaker switch	11 6
Crossover network	£3 5 0
Microgroove Equaliser	£2 10 0

ILLUSTRATED CATALOGUE 6d. POST FREE

BERRY'S (SHORT WAVE) LTD.

25, HIGH HOLBORN, LONDON, W.C.1

THE HOUSE FOR QUALITY COMPONENTS

UNIVERSITY RADIO

Offer Guaranteed Used Equipment at Attractive Prices

AR88D, complete with valves. In perfect condition and working order £35 0 0

AR88LF, as above..... £45 0 0

SX 17 Receiver, complete. Perfect condition and working order £30 0 0

Wirek Wire Recorder, complete with mike, etc. As new... £35 0 0

Amour Wire Recorder, complete with mike and spare reel of wire £32 10 0

Wharfedale Corner Cabinets, complete with twin speakers and crossover units. As new... £38 10 0

Scott 13-valve Communication Receiver, complete with built-in A.C. power pack, 55 Kcs. to 160 Kcs.-5.6 to 16 mgs..... £19 0 0

Philips PCR1 Receiver, complete with power pack. As new £13 0 0

Eddystone 640 Receiver. As new £21 10 0

Avo Meter Model 40. As new... £13 10 0

Avo Model 7. As new £15 10 0

Avo Valve Tester, roller panel. As new £12 0 0

WE NEED GOOD USED EQUIPMENT URGENTLY. PLEASE SEND, BRING OR PHONE FOR OFFER

Taylor 85A £15 0 0

Avo Signal Gen. As new..... £11 10 0

Taylor 65B. As new £11 10 0

Advance El. Sig. Gen. As new... £16 10 0

Taylor Circuit Analyser. As new £11 10 0

Avo Universal Avo Minor. As new £6 10 0

Taylor Model 70A. As new..... £8 0 0

Taylor Valve Tester Model 45A. As new £15 0 0

Taylor Valve Tester Model 47AP. As new £19 10 0

Cossor Double Beam 'Scope Model 339. As new £40 0 0

As above, Model 3339. Perfect at £32 10 0

Cossor Model 343 Ganging Oscillator. As new £15 0 0

As above, Model 3343 As new... £10 10 0

Various other 'Scopes in stock from £7 to £22 0 0

Taylor Res. Cap Bridge Model 110B. As new £7 10 0

Romac 25 watt Amplifier, mic. and gram inputs A.C. 200-250, complete with valves. As new... £19 10 0

Pam Amplifier as above, with two Pam speakers, A.C. 200-250 v. As new £26 0 0

THESE ITEMS ARE ONLY A SMALL SELECTION FROM OUR STOCK OF EQUIPMENT. YOUR ENQUIRIES FOR ANYTHING THAT YOU MAY NEED WILL BE WELCOME. WE HAVE OTHER EQUIPMENT ARRIVING DAILY!

CASH OR CHEQUE WITH ORDERS. ALL ITEMS LISTED ARE CARRIAGE PAID UP TO 50 MILES

22 LISLE STREET, LEICESTER SQUARE, LONDON, W.C.2

Phone GERrard 4447 and 8582. Hours 9 to 6. Thursdays 9 to 1.

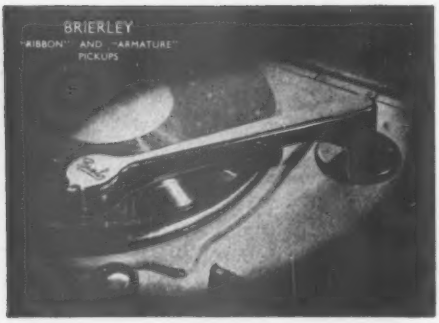

Idealism

Concepts may be divided into 3 categories—from the lowest to the highest—Concrete, Functional and Abstract.

Designs and policies may also have similar propensities. In a sadly materialistic world, our products are the result of an unshakable belief that progress is *earned* by the pursuit of things as they should be and is not the fruit of the limitations of things as they are.

Our wish for 1951 is that the number of those sharing our belief will increase.

J. H. BRIERLEY (Gramophones & Recordings) LTD.
KIRKBY TRADING ESTATE, LIVERPOOL

VALVES!! VALVES!!
RECEIVING, TRANSMITTING, MAGNETRONS, KLYSTRONS, CATHODE-RAY TUBES, PHOTOCELLS, ETC.
LARGE QUANTITIES & GREAT VARIETIES
IMMEDIATE DELIVERIES FROM STOCK
WRITE OR 'PHONE:—

S. Szymanski
(pronounced SHE-MAN-SKEE)
ELECTRONIC ENGINEER & STOCKIST
95 STRODES CRESCENT
STAINES - MIDDLESEX
TELEPHONE: STAINES 3971
PROBABLY THE LARGEST ACTUAL STOCKIST IN ENGLAND
WHOLESALE & EXPORT ONLY

TUNERS

Our Type 84 is the ideal Quality Tuner for your high quality amplifier. This four valve Super-Het Unit has a lively performance with very low distortion. Fitted variable selectivity 7K.C. and 10K.C. Wave-band coverage 16-50m., 190-550m., 900-2,000m. Using latest Mullard Valves ECH42, 2xEF41, EB91.

PRICE £12
+£2.13.4 P.T.
Manufacturers of Ventex Cabinets.

C. T. CHAPMAN (Reproducers) Ltd. FLAxman 3217
RILEY WORKS, RILEY STREET, CHELSEA, S.W.10
Daily demonstrations at Webb's Radio

"ADCOLA" SOLDERING INSTRUMENTS
Reg. Trade Mark

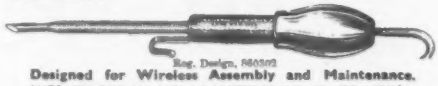

Reg. Design, 860302
Designed for Wireless Assembly and Maintenance.
SUPPLIED FOR ALL VOLT RANGES FROM 6/7v. TO 230/50v.
The three Adcola Models cover the requirements of the **Television, Telecommunication and Radar Engineers** and assure thorough jointing.
1/8in. dia. Bit. Standard Model — 22/6
1/4in. dia. Bit. Standard Model — 25/-
5/16in. dia. Detachable Bit— — — 30/-
Patented in England and Abroad.
Sole Manufacturers:
ADCOLA PRODUCTS LIMITED
Sales and Service: 50, CLAPHAM HIGH STREET, LONDON, S.W.4
Tele.: MACaulay 4272.

RELAYS AND KEY SWITCHES
LARGEST EX-GOVT. STOCK IN GT. BRITAIN
Types 600-3000 Relays — Siemens High Speed
Also A. C. 250 volts 50 cycles
Uniselector Switches, Telephone Switch-boards, Telephone Components, Plugs, Jacks, Handsets — **Government Contractors.**

JACK DAVIS (RELAYS) LTD. (Dept. W.)
36 PERCY STREET, LONDON, W.1
Phones: MUSeum 7940, LANgham 4321

MANUFACTURERS, RETAILERS AND SERVICE ENGINEERS AT HOME AND OVERSEAS
We can supply from stock
P.M. SPEAKERS · CONDENSERS · CHOKES · MAINS and OUTPUT TRANSFORMERS · RESISTORS
and many other attractive items at low prices
SEND FOR OUR MONTHLY BULLETIN
which includes special bargain lines. We can save you money!
— *TRADE ONLY SUPPLIED* —
V.E.S. WHOLESALE SERVICES LTD.
11, GUNNERSBURY LANE, ACTON, W.3
'Phone: ACOrn 5027

Wireless World Classified Advertisements

Rate 6/- for 2 lines or less and 3/- for every additional line or part thereof, average lines 6 words. Box Numbers 2 words plus 1/-. (Address replies: Box 0000 c/o "Wireless World," Dorset House, Stamford St., London, S.E.1.). Trade discount details available on application. Press Day: April 1951 issue, Thursday March 1st. No responsibility accepted for errors.

WARNING

Readers are warned that Government surplus components which may be offered for sale through our columns carry no manufacturers' guarantee: Many of these components will have been designed for special purposes making them unsuitable for civilian use, or may have deteriorated as a result of the conditions under which they have been stored. We cannot undertake to deal with any complaints regarding any such components purchased.

NEW RECEIVERS AND AMPLIFIERS

UNIVERSAL ELECTRONIC PRODUCTS, 36, Marylebone High St., London, W.1. Welbeck 4058.

SPECIALISTS in the design and manufacture of high fidelity reproducing equipment from 5-100 watts for domestic or industrial purposes. Our new twin channel amplifier (type U.E.57), with independent bass and treble outputs, provides the most satisfying standard of reproduction we have yet experienced. It is now being demonstrated in our showrooms daily (we close Thursday 1 p.m., Saturday 4.30 p.m.), and we invite those who seek perfection from recorded music to hear this superb instrument. We also offer tuning units or complete chassis designed and constructed to individual requirements.

MIDLAND RADIO COIL PRODUCTS offer a service for the production of high quality amplifiers and radio equipment to specification; list of standard products is available; suppliers of audio and radio equipment to the Northamptonshire Education Authority.—Enquiries to 28 Winstanly Rd., Wellingborough. [6336

BERNARDS, manufacturers of television, radio and amplifying equipment, can now offer good deliveries of hand-built equipment; let us quote you and save yourself £££££s by buying direct from actual manufacturers; 12 months' written guarantee; we supply complete television receivers; time-bases, vision strips, amplifiers 5-1,000 watts, radio receivers; quotations by return post.
BERNARDS, Radio Engineers, 12, Chelverton Rd., Putney, London, S.W.15. [0097

CONNOISSEUR'S receiver, acclaimed by its users as the finest receiver for the enthusiast and the only one with the following facilities: 9-1,500-metre, world-wide results on highly sensitive 10-valve receiver, comparable with any good communication set, or by change of switch, maximum fidelity reception of local stations on non-superhet receiver with high quality 2-PX4 push-pull amplifier incorporating all refinements, bass and treble tone control (boost to cut), whistle filter and gram input, etc.; basis rebuilt R1155; write for details or call for demonstration. FEEDER units as above, for use with external high-quality amplifiers; R1155 specialists, receivers repaired and re-aligned, also modified as above, or to your requirements; R1155 circuit and values 2/- post free.—R.T.S., Ltd., 5, Gladstone Rd., Wimbledon, S.W.19. Tel. Lib. 3303.

TELRAD ELECTRONICS, 70, Church Rd., Upper Norwood, London, S.E.19.—Designers and manufacturers of Telrad quality amplifiers; established as the most outstanding value in high-quality amplifiers, thanks to faithful reproduction at unrivalled price, these unique amplifiers are the first choice of the enthusiast; built to satisfy the discriminating ear; bass and treble independent controls, providing widest possible variation to suit all recordings and varying acoustic properties of one room with another; £18 complete; full details on request.—Write, call or 'phone Livingstone 4879. [0019

MANY people strive after quality reproduction but in most cases the price of associated equipment makes this impossible; however, with the R.T.M.C. Williamson amplifier you can attain your ideal at a reasonable price as superb quality can be obtained with reasonably priced speakers and pick-ups and there is no need to use expensive apparatus; the R.T.M.C. version of the now world-famous Williamson amplifier (which incidentally cannot be improved upon and is still pre-eminent in its class) is still the best reproducer you could possibly buy and before purchasing a quality reproducer we invite you to hear the Williamson but it must be a R.T.M.C. model; superb quality parts only used with outstanding finish and results; many have tried to equal the Williamson and extravagant claims are made but seeing and hearing are the best advertisement and we therefore offer you the opportunity of coming to actually hear the R.T.M.C. version of this wonderful amplifier which is superlative in its class; you are, however, quite safe in ordering by mail and the results obtained will astound even the most critical; 7-valve model £25/10, 9-valve model with built-in pre-amp £28/10 (ex covers); tuners, etc., supplied; write for details (3d stamp) to—R.T.M.C. (Ealing), Ltd., 141, Little Ealing Lane, W.5. Tel. Ealing 0962.

Partridge News

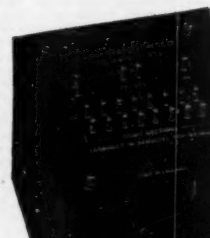

—for the

WILLIAMSON AMPLIFIER

THE widest possible audio range —the lowest possible distortion and an output of 20 watts . . . these critical demands of the designer of this now famous Amplifier implied the finest that technical skill and craftsmanship could provide for every component. From the inception of the Williamson Amplifier in 1947 Partridge have specialised in the transformers and chokes. The all-important output transformer was the special care of Partridge, and this "Williamson specification" component is now available for a varied range of impedance. Secondary windings are brought out as eight separate sections of equal impedance. Stock types comprise 0.95 ohm, 1.7 ohm, 3.6 ohm and 7.5 ohm sections.

The Partridge "Williamson" Output Transformer is acknowledged the most efficient of its type

FULL DATA ON REQUEST

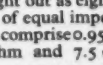

PARTRIDGE TRANSFORMERS LTD

ROEBUCK ROAD, KINGSTON BY-PASS
TOLWORTH SURREY
Telephone: ELMbridge 6737-8

9 KC Rejector, effectively removes the 9 kcs whistle, rejection at 9 kcs better than 35 DB; price 65/- each; response curve on application.
ROGERS DEVELOPMENTS Co., (M.O. Dept.), 116, Blackheath Rd., S.E.10. [6316

12-watt high quality amplifiers, bass and treble boost; £12/10; lists.—Broadcast & Acoustic Equipment Co., Ltd., Tombland, Norwich. [0065

CHARLES AMPLIFIERS, Ltd., are now able to produce amplifiers, radio units and electronic equipment to specification; enquiries invited for development work and for short production runs.—Charles Amplifiers, Ltd., 40, Kensal Rd., W.10. [0173

C.J.R. ELECTRICAL & ELECTRONIC DEVELOPMENT, Ltd., Hubert St., Birmingham, 6 (Aston Cross 2440), the Midlands specialist manufacturers of high fidelity sound reproduction equipment, for the world-famous Williamson amplifier and associated accessories including tone control stages, loudspeaker crossover units, distortionless contrast expanders and radio feeders; send for details and prices. [0105

OUTSTANDING value in radio to-day, our SL.35 three wave-band 5-valve superhet, radiogram chassis is, we believe, the best value for money obtainable anywhere; large, fully illuminated glass dial in pleasing colours, fully aligned and tested, ready for installation at 12-8-0 with 8in P.M. speaker or 12-18-0 with 10in P.M.; the all round performance of this model is truly remarkable; 2½d stamp for illustrated leaflets; trade enquiries invited.—Rayly Bros., 46, Pavilion Drive, Leigh-on-Sea, Essex. [6500

RECEIVERS, AMPLIFIERS—SURPLUS AND SECONDHAND

C. J. EMMS, Ltd.

RCA AR88, D radio, fully modified, as new, complete with instruction manual; £40.
26A, COLHERNE Mews, S.W.10. Fremantle 8941. [0061

AR88 receiver, perfect, seen Middlesex; any reasonable offer.—Box 8282. [6468

ARMSTRONG 14v all-wave radiogram chassis, 125in. for sale; £20.—E. Brightmore, 93, Fellbridge Rd., Sheffield, 2. [6433

BC454, few only to clear, 35/-; 28v plug-on dynomotor for above, 17/6; both carriage paid.—Clarks, 103, High St., Sandown, I.W. [6437

HARTLEY-TURNER radio tuner, 25-watt amplifier, power unit and pick-up complete, £30; also 16in cube Bottle, £3.—Box 7989. [6384

HALLICRAFTER BC614 speech amplifiers complete all tubes, perfect condition; £18.
BENDIX BC221 frequency meters, complete, perfect; £25.
SCR 522 freq. 100-156 mcs, complete transmitter/receiver in new condition with all tubes; £30.
TUNING units, types TU6 to TU26B, new with covers, 12/6; BC610 tuning units, P.A. coils and spares available. WS19 Mk II and installation kits, spares, etc., large quantities.
EXPORT enquiries for ex-Govt. American spares promptly attended.
McELROY ADAMS MFG. GROUP, Ltd., 46, Greybound Rd., London, W.6. Tel. Fulham 1902. Cables, Hallicraft, London. [0194

HRO Rx's and coils in stock, also AR88, BC348R, CR100, etc.—Requirements please to R.T. & I. Service, 254, Grove Green Rd., London, E.11. Ley. 4986. [0053

SUPER-Pro-Hammerlund, 22-valve, all-wave super radio receiver, that has everything and can get anything on the air; set includes speaker and power pack; sacrifice, £40.—Duke & Co., 219, Ilford Lane, Ilford, Essex. [6484

COMMAND receivers BC453, 42/-; BC454, BC455, 32/-; 10-way push-button units, 2 LW, 4 MW, 4 manual, I.F., 465kc/s, escutcheon, buttons, circuit supplied, 21/-; all above in new condition and carr. paid.—J. Henderson, 94, Eastern Ave., Largs, Ayrshire. [6492

ASTRA standard reproducer comprising modified W-W amplifier PX4 push-pull separate bass treble controls, Collaro motor turntable Connoisseur pick-up, mahogany cabinet, £20 or near offer.—Hollyer, 20, Cheyne Gardens, S.W.3. Flaxman 9622. [6515

BIRMINGHAM television, two 1355's one vision, one sound, time base and VCR97, all complete and working, with 3-stage preamplifier, £25; fully smoothed rotary convertor 300w., 220v. d.c. in, 230 a.c. out; £12.—Davis, 7, West Grove, Merthyr Tydfil, S. Wales. [6514

NEW LOUDSPEAKERS

BARKER model 150 £18/18; model 148A £15/15; Goodmans Axiom 22 £12/13; Axiom 150 £8/8; Wharfedale Super 12/CS/AL £12/10; W10/CS or CSB £7/10; Golden £4/5; Golden CSB £4/15; Super 8 £3/10; 8 CS £4/6; CS/AL £4/5; WB Concentric Duplex with O.T. £7/7; without O.T. £6/6; high grade Bass Reflex and Corner loudspeaker cabinets. Illustrated leaflet on request; all speakers post free.
ROGERS DEVELOPMENTS Co., (M.O. Dept.), 116, Blackheath Rd., S.E.10. [6315

LOUDSPEAKERS—SURPLUS AND SECONDHAND

VOIGHT unit with new spare cone; £10.—88, Stag-Leys, Ashtead, Surrey. [6419

12in Goodmans loudspeaker, type T2, 15 ohms. As new, unused, boxed in carton; £6.—Box 8314.

WHARFEDALE W.12/CS and W.10/CS 3-ohm speakers with crossover unit; £15.—Box 8291. [6486

NEW DYNAMOS, MOTORS, ETC.

CHARGING and lighting plants, ac and dc; please note items 1 and 2 are not surplus, but current products of well-known British manufacturer.
ALTERNATOR 230/1/50, 3kva, belt driven by Petters very latest type diesel engine A.V.1.; self-energised automatic voltage control, handle starter and press-button, also remote control, one press button remote control start and stop supplied; extra control units, £1; complete with H. duty starter battery and battery charger; full load 5 hrs. on 1 gall. of fuel; engine covered by Petters' inspection service; tested on full load before dispatch; delivered ready for use; £195.
250/1/50 ALTERNATOR, 400va with voltage regulator, self-energised, clock, or anti-clock, 3,000rpm; suitable television; £18 del.
6v BATTS., car-type 72amp/hr, 65/-; wooden cased, 85amp/hr, 70/- del.
H. DUTY rubber-covered flexible cable, 100amp, 2/- per yard.
SOME 12 and 24v lighting plants, dc.
PLEASE do not ask for general catalogue, state exactly your requirements; see displayed advert page 90 for S.T.C. selenium rectifiers; terms c.w.o., pro-forma invoice, c.o.d. (post goods only).
PEARCE, 66, Great Percy St., W.C.1. (Near Angel.) [0014

BATTERY chargers, 4 models, 2-6-12v, 1-2-4 amp D.C.; any mains voltage; also larger types special transformers, chokes, test gear, interior car heaters, etc.—The Banner Electric Co., Ltd., Hoddesdon, Herts. [0122

ALL types of rotating electrical machinery 1kva to 20kva available, including rotary converters, rotary transformers, motors, petrol and diesel-engined generating plants, alternators and d.c. generators. We are also in a position to quote for power transformers; as actual manufacturers we will be glad to quote for any quantity for home or export.
DIESEL Electric generating plants, 3kva, 230v with push-button remote control, starting equipment, ready for use, £195.
ROTARY transformers, input 20v d.c., outputs 6.5v d.c. and 300v d.c., permanent magnet field, 20/-; ditto, input 28v d.c. and 1,200v 70ma d.c. output; energised field, 35/-; ditto, input 12v d.c., output 500v, 90ma d.c., energised fields, 35/-.
PETROL electric generator plants, comprising a J.A.P. No. 2a single cyl. engine coupled by vee rope drive to a 1kva alternator, giving an output of 250v 50 cycles, 400 v.a., with screened ignition and filtering on generator, eminently suitable for operating television and radio on farms, etc., price £40; such plants can be supplied with various outputs, a.c. or d.c. for other applications.
CHAS. F. WARD, Lordscroft Works, Haverhill, Suffolk. Tel. 253. [0039

DYNAMOS, MOTORS, ETC.—SURPLUS AND SECONDHAND

ROTARY converter, 240v d.c., 163v a.c., 350w; £5.—37, City Rd., Norwich. [6450

TEST EQUIPMENT—SURPLUS AND SECONDHAND

COSSOR A.339 D.B. scope with S.B. tube as spare; £52, or near offer.—Box 8270. [6440
AVO and Taylor meters ,less 8% list.—Radilect, 2b, Ot Western St., Manchester, 16. [6454

ERSKINE oscilloscope-wobbulator, almost unused; offers over £12.—Josling, Heamoore Institute, Penzance. [6434
EVERETT Edgcumbe type M.S.R. recording millammeter, 0-2 ma. spare charts; £12.—88, Stag-Leys, Ashtead, Surrey. [6420
SIGNAL generators, oscilloscopes, output meters, valve voltmeters, frequency meters, multi-range meters in stock; your enquiries are invited.—Requirements to R.T. & I. Service, 254, Grove Green Rd., London, E.11. Ley. 4986.

NEW GRAMOPHONE AND SOUND EQUIPMENT

TAPE recorder motors, 230v a.c., powerful, quiet, brand new, 13/11; post, etc., 1/1.—K. W. Logan, Westalley, Hitchin, Herts. [6469
RUBY Stylii for E.M.I. lightweight pick-up, 4/8, plus 1/10 P.T.; cash with order.—Bradmatic, Ltd., 10, Station Rd., Aston, Birmingham, 6. [6477
MAGNETIC Tape.—Emitape on 1,200ft spool, 25/-; G.E.C. A tape, 30/-; blank recording discs, 10in d/sided, 3/-; all from stock; full trade terms available.
SOUND DISCS (SUPPLIES) Ltd., 178, Bispham Rd., Southport, Lancs. Tel. 88153. [5335
INFINITE baffle corner deflectors, scientifically designed acoustic chambers for 8 to 15in speakers; lists.—Broadcast & Acoustic Equipment Co., Ltd., Tombland, Norwich. [0064
EXPORT only, BSR 2-speed gram motors, 33⅓ and 78rpm for microgroove or standard records, simple speed change, 10in turntable, 100-120/200-250v 50c/s, tax free price £3/10 including packing and postage to any part of the world.
FRITH RADIOCRAFT, Ltd., Churchgate, Leicester. [0024
AVAILABLE from stock; good quality 33⅓-rpm motors, including turntable and rubber mat, £4/11; Decca 3378 playing-desk, £16/16; Decca 33B and 33C playing-desks, £12/1/6; Connoisseur twin-speed motors, £19/4/2; Acos GP20 pick-up, £3/11/4; Decca l.p. records; despatched post free.—Rogers Developments Co., (M.O. Dept.) 116, Blackheath Rd., S.E.10.

A NEWCOMER'S OPINION

"Yesterday I took delivery of my first Hartley-Turner speaker. I had never heard one and purchased purely on recommendation. What did I find in the box? Rather a large magnet for the chassis size, an iron frame, and a most unusual cone arrangement. Being myself a manufacturer I was impressed with the finish and accuracy of the unit.

"By the time I had screwed the unit into my cabinet the orchestra at the Albert Hall was tuning up for the Promenade Concert. Before the concert commenced I was more than satisfied with my new reproducer.

"Candidly, I heard top I had never heard before. A music stand was shifted—and some steel strip was moved within my lounge. Within a few moments, very quietly, a man ran off a few notes on an oboe—just behind my chair. He definitely had a real oboe in the room with me.

"Then the concert. This is quite beyond my description. The timps were just perfect—not too heavy, but they were there. The slight adjustments to their pitch were all so apparent. The flutes and horns were magnificent. And then the applause! The whole thing was something quite new to me after having searched for years for quality. The research that was packed into that carton is something I shall never know about.

"It is not a speaker. It is surely a reproducer. It is a very beautiful musical instrument. It is a human voice. It is a really amazing achievement."

B.T.S., London.

The Hartley-Turner 215 speaker costs £10/10/-. By all means hear the others first—at any price you like. But, sooner or later, your choice will be—the 215.

Catalogue free on request.

H. A. HARTLEY CO. LTD.
152 HAMMERSMITH ROAD
LONDON, W.6. *RIVerside 7387*

THE MODERN BOOK CO.

Sound Reproduction. By G. A. Briggs. **10s. 6d.** Postage 9d.
Television Receiving Equipment. By W. T. Cocking. **18s.** Postage 9d.
Voltage Stabilizers. By F. A. Benson **12s. 6d.** Postage 6d.
Wireless Servicing Manual. By W. T. Cocking. **12s. 6d.** Postage 4d.
Basic Mathematics for Radio Students. By F. M. Colebrook. **10s. 6d.** Postage 4d.
Television Servicing. By Héller & Shulman. **47s.** Postage 9d.
Outline of Radio. By Penrose. **21s.** Postage 9d.
Testing Radio Sets. By J. H. Reyner **22s. 6d.** Postage 9d.
Electronics Manual for Radio Engineers. By vin Zeluff and J. Markus. **63s.** Post Free.
Telephony. By J. Atkinson. Vol. I. **35s.** Vol. 2 **50s.** Postage 1s.
The Technique of Radio Design. By E. E. Zepler. **25s.** Postage 9d.
High-Quality Audio Amplifiers. Reprints from "Wireless World." **2s. 6d.** Postage 2d.
Admiralty Handbook of Wireless Telegraphy. Vol. I **5s.** Vol. 2. **7s. 6d.** Postage 1s.
The Williamson Amplifier. Reprints from "Wireless World." **3s. 6d.** Postage 2d.
Radio Valve Data. Compiled by "Wireless World." **3s. 6d.** Post 3d.

We have the finest selection of radio books in the Country. Complete list on application.

19-23 PRAED STREET
(Dept. W.3)
LONDON, W.2
PADdington 4185

GRAMOPHONE AND SOUND EQUIPMENT —SURPLUS AND SECONDHAND

COLLARO microgram, 55 records, £20; exchange for 9in television; cash adjustment.—Bostock, 4, Seddon St., Middlewich, Ches. [6421

R.G.D. a.c. autoradiogram, 4-band (model 1221), 13 valves, clock, every refinement, walnut cabinet, excellent condition; £95, offer.—33, Byron Rd., Earley, Reading. [6501
MAGNETIC sound recording wire, stainless steel, temporary wooden spools, approx 1½ hours' running time at 2ft per sec.; 14/- per spool.—A. Smart, 40, Grange Rd., Halesowen. [6491

M.S.S. complete disc recording outfit with 2 recorders, 3 mikes, high quality amplifier stocks, blank discs; full particulars on request.—Cook, 163, Stourbridge Rd., Holly Hall, Dudley, Worcs. [6398
H.M.V. portable disc recorder, amplifier, ribbon microphone and stand, speaker, quantity of discs, stylii, etc., last year's model, as new; demonstration by appointment; £140 complete, or near offer.—Neal's, 18, Sheffield Rd., Barnsley. Tel. 3909. [6381
MARCONI high-speed morse tape recorders MA with 250v a.c. motors variable speed control; type U.G.8 (Inker), post-war model, apparently unused; also type 180 (punches holes), with speed indicator to 400 w.p.m.; both types complete, £18 each.—P. B. Crawshay, 166, Pixmore Way, Letchworth, Herts. [6277
B.S.R. DR662, direct disc recording outfit, comprising amplifier AR15C in leatherette case, 2 disc recorders type AR33C, and interconnecting leads, 2 Monitor loudspeakers, extension leads, etc.; 1 B.S.R. ribbon microphone, 1 B.S.R. moving coil microphone, 2 floor microphone stands, 1 table microphone stand, 2 B.S.R. microphone matching transformers, approx. 100 blank discs, B.S.R. and E.M.I., 8in, 10in, 12in, 13in, with full equipment, sapphire cutting Stylus, etc.; 1 pr. B. G. Brown moving coil Monitor headphones, scarcely used, original cost £400; offered at £320 or near offer.
WILSON, 23, Mountbatten Close, Hastings. Tel. 1725. [6399

NEW COMPONENTS

HANNEY OF BATH offers:—
WILLIAMSON amplifier, complete kit of 25 resistors and pots for the main amplifier, with matched pairs where necessary, 27/-; kit of 9 high stability and carbon resistors for the pre-amp (fig. 15), 8/7; kit of 23 H.S. and carbon resistors for the 3-valve pre-amp (fig. 15), 19/9; kit of 18 H.S. and carbon resistors and 4 pots (fig. 19), 30/-; kit of 15 condensers for fig. 15, 47/-; kit of 33 condensers for fig. 19, 54/6.
COMPLETE Williamson tone compensation unit, wired and tested (fig. 19) a laboratory job, £11/11 (less valves); matched pairs of resistors, 47K 2 watt 3/-, 22K 1½ watt 2/- pair; Dubilier high stability resistors, all Williamson values, ½ watt ±5% 1/3, ±1% 2/3, 1 watt ±5% 1/-, ±1% 2/-; silver mica condensers, finest quality only, no surplus, 25 to 500 pfd, ±5% 1/-, ±1% 1/3, 1,000 pfd ±20% 1/-, 4,000 pfd 2/-; 5-bank 6-position switch, a few left at 7/6; matched pair KT66 valves, 42/8; PX4 ditto, 36/8; 6V6 ditto, 31/8; KT63 ditto, 31/8; complete kit of parts for 4 watt amplifier, with bass and treble tone controls, £6/6, or complete with instrument case, £6/19/6; band pass converter coils (Oct. W.W.), set of 4, 10/6; Eddystone 759 split stator, 7/9; wobbulator coils, 5/6 pair; also 16HT 28 rectifiers, resistors and reliance pots, etc., for the above 2 designs. Goodmans Audium 60 155/-, axiom 150 168/-; Wearite "P" coils, 3/- each; Denco type "C" coils, 6/6 pair.
WIRELESS World TV Superhet, complete set of 20 coils wound exactly to designers' specifications; 45/-.
POLYSTYRENE formers, 1¼in×¾in, tapped 6BA for slug, with fixing hole, 1/-; 2¼in×¾in, 6d.
PAXOLIN formers, 1¼in×¾in, tapped 0BA for slug, 9d; 1½in or 2in×½in, 8d; 1⅝in×⅝in, 9d; polystyrene varnish, large bottle, 1/10; 0BA screwed rod, copper 2/- ft, brass 1/- ft; all other components and accessories ex-stock as previously advertised.
ALL Avo and Taylor instruments supplied, list on request. We supply everything for W.W., P.W., E.E. and Berards designs . . . get our quotation, retail only; send 3d stamp for lists.
L. F. HANNEY, 77, Lower Bristol Rd., Bath. Tel. Bath 3811. [6503
CRYSTAL microphone inserts (Cosmocord Mic-6), guaranteed brand new, 15/6, post free.
RADIO-AID, Ltd., 29, Market St. Watford. 'Phone Watford 5968. [0036
NEW push pull crystal set, double wound coil, special high Q, each 6/6.—Bel, Marlborough Yard, Lond., N.19. [0184
GARLAND RADIO, Chesham House Deptford Broadway, S.E.8. Please see our displayed advertisement under name Garland Brothers on page 68. [0192
ALLEN & GOULD, 5, Obelisk Parade, Lewisham, S.E.13. Please see our displayed advertisement under name Garland Brothers on page 68. [0191
EHT Transformers, mains transformers, output transformers and chokes; open or potted types; transformers designed to individual specification; singles or in quantity.
WILLESDEN TRANSFORMER COMPANY, Ltd., 781, Harrow Rd., N.W.10. Ladbroke 2846. [0075
YOU are bound to try an Osmor "Q" Coil-pack eventually and be delighted with the results; why not save time and money now? Send a stamp for free circuits and latest lists of coils coilpacks, dials, etc., etc.
OSMOR RADIO PRODUCTS, Ltd. (Dept. W.C.A.) Borough Hill, Croydon, Surrey. (Tel. Croydon 1220) [0046

—if yours is a (rare) VALVE problem

CATHODE RAY TUBES.
EIMAC. — C9B. C12B.
COSSOR.—65K. 75K. 85K. 105K.
FERRANTI.—T12/44.
G.E.C. — 6504A. 6505A.
MAZDA.—CRM 91. 92.
MARCONI.—3/3, 3/4, 3/16, 3/20, TA10, TA15.
MULLARD.—MW22/14, MW22/14C, MW22/17, MW22/18, MW31/17, MW31/18.

AMERICAN (RVA) TYPES.—OZ4, 1A3GT, 1C5GT, 1LA6, 1LD5, 1LH4, 1LN5, 1N5G, 1R5, 1S4, 1S5, 1T4, 1U5, 2A2, 3D6, 3Q4, 3S4, 3V4, 5R4GY, 5U4G, 5V4G, 5X4G, 5Y3GT, 5Y4G, 5Z3, 5Z4, 5Z4G, 6A6, 6A8GT, 6AB7, 6A8, 6AC7, 6AG6, 6AL5, 6AM5, 6AM6, 6AQ5, 6AT6, 6AU6, 6BG6G, 6B7, 6B8G, 6BA6, 6BE6, 6C3G, 6C5GT, 6C6, 6D6, 6F6, 6F6G, 6F7, 6F8G, 6G5G, 6G6G, 6H6, 6H6GT, 6J5, 6J5G, 6J5GT, 6J7, 6J7G, 6J7GT, 6K8GT, 6K7, 6K7G, 6K7GT, 6K8GT, 6L6, 6L6G, 6L7, 6N7, 6Q7G, 6Q7GT, 6R7, 6R7GT, 6SF5, 6SG7, 6SH7, 6SJ7, 6SK7, 6SL7GT, 6SN7GT, 6S87, 6U5G, 6U7G, 6V6G, 6V6GT, 6X5GT, 7B6, 7B7, 7C7, 7C5, 7C6, 7H7, 7K7, 7Q7, 7R7, 7S7, 7Y4, 12A6, 12A7, 12AT6, 12AT7, 12AU6, 12BA6, 12BE6, 12C8, 12H6, 12J5GT, 12J7GT, 12K7GT, 12K8, 12K8GT, 12Q7GT, 12S07, 12SG7, 12SH7, 12SK7, 12SL7, 12SR7, 14A7/12B7, 14B6, 14H7, 14R7, 1487, 18, 35A6G, 35BN7, 35A5, 35W4, 35Z3, 35Z4GT, 39/44, 41, 43, 50L6GT, 75, 76, 77, 78, 80, 84, 807/3B/250A.
BRIMAR.—1D5, 1D6, 4D1, 7D3, 7D5, 7D6, 7D8, 8A1 (5 & 7), 8D2, 8D3, 9A1, 9D2, 9D6, 10D1, 11D3, 11D5, 15A2, 15D1, 15D2, E3, R3, 8B2, 8B3, RM1, RM2, RM3. **BRIMISTERS.**—CZ1, CZ2, CZ3, CZ6.
COSSOR.—DDL4, DDT, GDT4B, MP/PEN, M8/PEN, M8/PENB, MV8/PEN, MV8/PENB, OM4, OM6, PT41, 8I30, 8D6, 8U25, 8U61, 8U2150, 8U2150A, 2P, 4THA, 4TPB, 4TSA, 4VPB, 13PPA, 13VPA, 27SU, 40SUA, 41MHL, 41MP, 41MPG, 41MPT, 41MTL, 41MTS, 41MXP, 4187H, 42MPT, 42OT, 42OTDD, 42SPT, 451U32KU, 53KU, 61BT, 618PT, 63ME, 63PPT, 142BT, 185BT, 202DDT, 202STH, 202VP, 202VPB, 203THA, 210DDT, 210HF, 210LP, 210PG, 210SPT, 210VPA, 210VPT, 215P, 215SG, 220OT, 220PA, 220PT, 220TH, 230XP, 240QP, 302THA, 402PENA, 405BU.
MULLARD.—ACO42, ACO44, AZ1, AZ31, AZ50, C1, C1C, CBL1, CBL31, CL4, CL33, CY1, CY1C, CY31, DA5, DAC32, DAF91, DCC90, DF51, DF70, DF91, DF92, DK32, DK91, DL33, DL35, DL71, DL72, DL92, DLL21, DLL24, DW2, DW4/350, EA50, EA76, EABC80, EA50, EAC91, EAF42, EAF92, EB34, EB41, EB91, EBC3, EBC41, EBF80, EBL21, EC31, EC52, EC53, EC54, EC91, ECC31, ECC33, ECC34, ECC35, ECC40, ECC81, ECH21, ECH42, ECL80, EF22, EF32, EF36, EF39, EF40, EF41, EF42, EF50, EF54, EF55, EF80, EF91, EF92, EK2, EK32, EL2, EL3, EL31, EL32, EL33, EL35, EL37, EL38, EL38M, EL41, EL42, EL50, EL91, EM1, EM4, EM34, EY51, EY81, EY91, EZ35, EZ40, EZ41, FC2, FC2A, FC4, FC13, FC13C, FW4/500, GZ32, HL13, HL13C, HVR2, HVR2A, 1W4/350, KBC32, KF35, KK32, KL35, KLL32, PEN4A, PEN9A, PEN44, PEN44VA, PEN36C, PEN40DD, PEN428, PL33, PL36, PL38M, PL83, PM2HL, PM12M, PM22A, PM22D, PM24A, PM24M, PM202, PY31, PZ30, QP22B, 8P2, 8P4 (5 & 7), 8P4B, 8P13, 8P13C, TD02A, TDD4, TDD13C, TH4B, TH15C, TH30C, UAF42, UAF42A, UB41, UBC41, UBF80, UBL21, UCH21, UCH42, UF41, UF42, UL41, UL44, UL46, UM34, UR3C, UY21, UY41, VP2, VP2B, VP4 (5 & 7), VP4A (5 & 7), VP13A, VP13C, 2D4A, 954V, 8DA1, 4687A, 7475, L2D3, PHOTO FLASH TUBE.
MAZDA.—ACR1, ACH1DD, ACP, ACP4, ACPEN (5 & 7), AC/6GVM, ACTH1, ACPT, AC2HL, AC2PENDD, AC4PEN, AC6PEN, AC8PENDD, ACVP1(5), D1, DD41, DD620, DL810 HL21DD, HL23, HL23DD, HL41 HL41DD, HL42DD, HL133DD, ME41, ME91, P61, PA20, PEN25, PEN44, PEN45, PEN45DD, PEN46, PEN220A/PEN383, PEN/453DD, PEN/DD4020, PP3/250, QP25, QP230, 8P41, 8P42, 8P61, 8P181, TH41, TH233, TH3221, TP23, TP23, TP2620, U21, U22, U301, U781, U404, U801, U4020, UU5, UU7, UU9, VP14, VP25, VP41, VP133, VP210, VP1322, 1C1, 1P2, 1P3, 1PD9, 1P10, 6C9, 6C31, 6D1, 6D2, 6F1, 6F11, 6F12, 6F13, 6F14, 6F15, 6F32, 6L18, 6L19, 6LD20, 6M1, 10F1, 10F3, 10F9, 10LD11, 10P13, 10P14, 20D1, 200P1.
MARCONI-OSRAM.—B65, D41M, D42, D43, D63M, D77, DH63, DH63M, DH76, DH77, DH81, DH101, DH147, DH149, DH150, DL63, DL74M, DL82, DL145, DN41, DN143, GT1C, GU50, H63, HD14, HD24, HL2M, KT2, KT22, KT32C, KT36, KT41, KT44, KT45, KT63, KT66, KT74, KT76, KT81, K.101, KTW61, KTW63, KT241, KT263, L63, L77, LP2, M34, MH41, MHD4, MHL4, MKT4 (5 & 7), ML4 M8P4 (5 & 7), M8P41, M84B, MU14, MX40, N14, N16, N17, N18, N37, N77, N78, N142, N145, N147, N148.
FERRANTI RECEIVER TUBES TYPE 8SP1.

Subject to stock. We may send equivalents. Kindly mark envelope (WW). Order C.Q.D. or C.W.O. POSTAGE 1/-.

RADIO **BULLS** VALVES
246 HIGH ST. HARLESDEN NW10

EVERYTHING for home constructor, chassis, condensers, coils, valves, resistors, gram units, speakers, test gear, Viewmaster kits, etc., cash or H.P.; stamp for lists; quick service, no Govt. surplus offered.—BCM/EDHWA, London, W.C.1. [6227

TRF coilpack kits. 2 stage 3 station (1 lw, 2 mw), newest, amazing performance, only wiring to complete, size 3¼in×2in, full instructions, circuit diagrams, etc.; please note new price 15/-, post paid, c.w.o.—A. P. Cretton (W), 349, Connor Rd., Portsmouth. [6328

TELEVISION. "Wireless World" superhet receiver for long range at full bandwidth, simple conversion to any channel, straightforward construction on shallow tray RF chassis, very instructive booklets containing much general tele. information; 5/-.
ALL necessary special items listed below, remaining conventional parts also available.
COIL set, all channels, 20 pieces; 42/6.
SCAN coils, mounted, perf. linearity; 35/-.
FOCUS, lk, potted, heavy constr. flanges; 37/6.
BLOCKING trans., to spec. as rest; 15/-.
MAINS trans., 500, 6.3, 4, 2v, excl. value at 77/6.
MAINS trans., fully earthing, shrouded; 98/-.
MAINS choke, 20H at 250MA, heavy; 50/-.
LINE trans., flyback EHT, 4:1; 42/6.
WESTHET EHT, latest, 5.5kv, 2in long; pr. 32/-.
EHT unit complete, treblers, at 7kv; 77/6.
CONDENSERS, pots, resistors, in sets, EF50, EA50, EC52, 6J7, 6V6, 807 viva.
CHASSISWORK, complete, mounted V/H, etc.; 99/-.
COPPER RF, strips, boxes and v/holders; 52/6.
RADIO:—
"WILLIAMSON" type MW, LW tuner coils, Polysterene former, iron core, litz winding and small dimensions, ensures normal easily tuned RF; HF, DET 7/6 pair, specially wound 4/6 ea.; Wobbulator coils, set 7/6 (December issue); 10M convertor coils, set 10/6 (Dec.); 200M convertor, set 4, 9/6 (Feb.); Band-in coils, 3- & 6-v, HF horn metalwork; 4/set 3-band coils, 2 small formers, 8/6; miniature s'het coils, 1in high, cct, all bands at 2/6 ea.; Polysterene tube, cement; 8mm poly coilformers, 10d with core; March bargain, limited qty 2-band coilpacks, unwired cct. supplied, 16/6, exc. performance; trade supplied.
BEL SOUND PRODUCTS CO., Marlborough Yard, London, Archway, N.19. [0183
AUTO transformers, 110/230v, 80watt, 19/-; Westalite 12v 3amp rectifiers, new, 17/-; L.T. chokes, 3½lb 16ohms, 17/-; Selenium h.t. rects., 130v 40ma for mains, 5/-; 350-0-350v 80ma 6.3v 3a trans. with c.t. selenium h.t. rect. 80ma, 26/- the two; add postage, 1/-.—Champion Products, 43, Uplands Way, N.21. Lab. 4457.

15/- pair only; we can now supply the world-famous "MM" I.F. transformers (variable iron dust cored, high "Q," high stability) pre-aligned to 465 Kc/s at only 15/- pair; iron dust cored coils for standard wavelengths available at 3/- each; Coil Group A consisting of 6 Supacoils (your own selection from our range), 1 four pole three way switch, 2 fixed padders, suitable for coils selected, and 6 variable trimmers, all for 26/9; Coil Group B, similar to above but with 9 coils (your choice), six pole three way switch, 2 padders and 9 trimmers, all for 43/9; Home Constructor's Handbook, 1/6; see also our display advertisement in this issue.—SUPACOILS, 98, Greenway Ave., London, E.17.

COMPONENTS—SURPLUS AND SECONDHAND

C. J. EMMS, Ltd.

BRIDGE full wave metal rectifiers. 6 or 12-volt 1 amp. 5/6; 6 or 12-volt 3amp. 10/-; 6 or 12-volt 7amp. 17/6; 6 or 12-volt 10amp 25/-; 24-volt 1amp. 11/-; 24-volt 3amp. 20/-.
SLIDING resistance, 12amp 1ohm. 6/-; 12amp 1ohm, non-slider, 3/6.
26a, Colherne Mews, London, S.W.10. Fremantle 6941. [0201

MAGSLIPS at 1/10 to 1/20 of list prices. huge stocks, please state requirements.—K. LOGAN, Westalley, Hitchin, Herts. [6369

230,000 Simmonds fibre collar, type 6BA brass hex full nuts, 8/6 per 1,000, carr. paid 20,000.
D. C. WOODBERRY, Engineers Supplies, Treforest Estate, Glam. [6367

SUPREME RADIO, 746b, Romford Rd., Manor Park, London, E.12. Tel 11f. 1260. Est. 16 years. New bargains!
E.F.50 valve holders, 6d each; retaining rings for same, 6d each; B7G valve holders, Amphinol type, 9d each; Alladin coil formers with cores, 8mm, 8d each; 6mm 6d each; 3 m·e·c carbon vol. controls, 7½d each; 100 KΩ vol. controls, with long spindle and s/p switch, 2/6 each; 0.25 MΩ vol. control, long spindle, less switch, 2/- each; noise suppressor units, consisting of 2, 0.1mfd cond and iron cored choke, 6d each; C.V.102 crystal diodes, 2/6 each; Westinghouse type metal rectifiers, 250v, r.m.s. 65 m/A, 4/- ea; 650 Ω, 0.2amp flat type mains dropper, tapped for 200-250v, 1/6 each; 2-pole 2-way small switches, 8d each; fly-back type mains trans. with provision for EY51 valve, 22/6 each; 16mfd 350v Dryliic cond, 1/9 each; 50mfd 50v or 25mfd 25v tub. cardboard bias cond., 1/- each, 11/- doz. or ass.; 1.f.t./s. 465 Kc/s, small type, 12/6 pr.; Special lines—just arrived! Mains trans. drop through type primary tapped 0 to 250v, sec. 275-0-275v 100 m/a, 6.3v 3 amp, 5v 2amp, with screen, bargain price 14/11 each; also 465 kc/s standard size l.f.t./s 8/6 pr.
COMPONENT parts for constructor television and radio circuits our speciality.
TERMS c.w.o., no c.o.d.; send 6d. extra for postage orders under £5; 2½d. s.a.e. all enquiries and list. [0021

SOUTHERN RADIO SUPPLY, Ltd., 11, Little Newport Street, London, W.C.2. See our displayed advertisement page 88. [0016

The NEW 1355 CONVERSION!

SOUND, VISION, TIME BASES, POWER PACK AND SPEAKER ON ONE 1355 CHASSIS.
Data for London or Birmingham, 3/- per copy.

POWER UNIT S441B. Separate individually controlled H.T. and L.T. transformers, jewelled indicator lights, attractive grey crackle case, and modest size (14in. x 7½in. x 7in.), 300 v. at 200 mA fully smoothed, 12 v. at 3 a. A.C. and 5 v. D.C., make this one of to-day's best bargains. ONLY 65/-. A few soiled at 50/-.

AMPLIFIER 1135A with EBC33, EK32 and EL32; our "10 min. conversion" data and circuit, provided with the unit, will turn this into a really fine little amplifier. ONLY 15/-.

RECEIVER P40. Covering 85-95 mc/s, these may be converted for "2" or for the B.B.C. U.H.F. F.M. crystal controlled oscillator with subsequent multiplication ensures stability. With 4 EF54s (RF, mixer and multiplier), EC32 (L.O.), 2 EF39s (2.9 mc/s IFs), EB34 (det.) and 6J5 and 6V6 (audio), they are housed in robust attractive grey cases. ONLY 65/- in original cartons.

RECEIVER 21. 4.2-7.5 mc/s and 18-31 mc/s, with BFO, interference limiter and 9 valves, these have slightly damaged knob spindles. ONLY 25/-.

VIBRATOR 21. 6 v. input, approx. 140 v. at 40 mA. output, these were designed to supply the above receiver and its associated transmitter. 15/6.
Badly store soiled, but suitable for stripping 7/6.

TRANSMITTER 21. The remaining section of the above, this will send CW, MCW, or speech on the same frequencies as the receiver. Complete with valves, control box, key front panel (for mounting all three sections together) and circuit. In excellent condition. 25/-.

RECEIVER 3547. With 15 EF50s, eight other useful valves and hundreds of components, this contains a "Pye 45 mc/s Strip" which is ideal for London TV. Brand new in original makers' crates. ONLY £5/12/6.

INDICATOR 198 contains a 3in. VCR 138A short persistence tube and eight useful valves. Ideal case for test gear construction. In original maker's cartons. OUR PRICE £2.

ACCUMULATORS. Brand new, multiplate, in unspillable celluloid cases (3¼in. x 1¼in. x 4in.); 7 A.H. 2 v. 5/11.

Ex-U.S. BLOWERS. Ideal for cooling purposes, or as small motors: 1¾in. dia. x 2¼in. long, they require 24/28 v. A.C. or D.C. 7/6.

RADIO EXCHANGE CO.,
9, Cauldwell Street,
BEDFORD. Phone 5548.

SOUTHERN RADIO'S WIRELESS BARGAINS

R.3515 TELEVISION UNITS. 21 valves with 6-stage 14 Mc. I.F. strip, recommended for ideal TV conversion by all experts. Brand new in original wooden cases. **£3/10/-.**

R.1355 RECEIVERS. Brand new and unused, as specified for inexpensive television. **£3/5/-.**

T.R.1196 6-VALVE SUPERHET RECEIVERS. Perfect and guaranteed. **22/6**, plus 1/4.

BENDIX COMMAND RECEIVERS. B.C.454 (49-100 metres), B.C.455 (39-49 metres). Complete with 6 valves. Perfect condition. **35/-** each, plus 1/4.

WALKIE-TALKIE (TRANSRECEIVER), type 38, Mark II. Complete with 5 valves, throat mike, headphones and aerial. Tested and working. **£3/10/-** carr. paid, less batteries.

ATP4 VALVES. 7/6 each.

THROAT MICROPHONES. With lead and plug—magnetic. **4/6.**

CONTROL CABLES, 14ft., with adaptors or B.C.453/4/5. **9/6** each.

R.A.F. BOMBSIGHT COMPUTERS. Complete, brand new, with motors, gyro gears, blowers, etc., etc. Ideal for model makers, etc. The best component value ever offered. **35/-** each, plus 5/-.

LUFBRA HOLE CUTTERS. Adjustable from ⅜in. to 3½in. for use on wood, metal, plastics, etc. **5/6.**

HAND GENERATORS. 6 volts at 5 amps. Complete with crank. **21/-.**

RADIO COMPASS INDICATORS, with internal Selsyn motor, 3in. dial, **13/6**; 5in. dial, **15/6.**

INVERTER UNITS, type (PE 206A) 206-A. D.C. input, 27 volts at 38 amps., 6,000 r.p.m.; A.C. output, 80 volts, 800 cycles. Complete, brand new, with spares. **£3/10/-** each.

MAP CASES. Transparent plastic, 10½in. x 15in., with spring cover, suitable for documents, photographic display, etc. **5/6.**

Full list of Radio Publications, **2½d.**

SOUTHERN RADIO SUPPLY LTD.
11 Little Newport St., London, W.C.2.
Gerrard 6653.

PITMAN
Radio Books

Short-Wave Radio

By J. H. Reyner, B.SC.HONS., A.C.G.I., etc. A reliable guide to modern developments in the use of the short, ultra-short and micro-waves. *Fourth Edition* 10/6 net.

"Reliable and readable."— ELECTRICAL REVIEW.

The Principles of Television Reception

By A. W. Keen, M.I.R.E., A.M.BRIT.I.R.E. A systematic treatment, including a stage-by-stage examination of the receiver, and a review of the problems of natural-colour television. *Illustrated* 30/- net.

"Can be thoroughly recommended to the student and service engineer."—
WIRELESS AND ELECTRICAL TRADER.

Antenna Theory and Design

2 VOLS.

By H. Paul Williams, PH.D., A.M.I.E.E., etc. *Illustrated.*
Vol. I (Foundations of Antenna Theory) **21/-** net.
Vol. II (The Electrical Design of Antennæ) **63/-** net.

"All radio engineers concerned in any way with aerials will want to find a place for this exhaustive work on their bookshelves."— JNL. OF THE BRIT. INST. OF RADIO ENGINEERS.

PITMAN, Parker Street, Kingsway, London, W.C.2

RADIO CLEARANCE, Ltd.

TELEVISION! Set of 3 components, comprising line output trans., with E.H.T. winding to give 7 kV, using EY51 (heater winding for EY51 also included), and fitted with width control scanning coils, low impedance line and frame, focus coil (res. 10,000Ω, current approx. 20 mA): the set of 3 for 42/- plus 1/6 post; scanning coils, as "Viewmaster," low imp. line and frame, 12/6 plus 9d.

MINIATURE iron cored coils, former size 1⅝"×⅝in. adjustable core, set of 4 coils, M.W., A.F. and OSC. S.W., A.F. and OSC. 5/11, post 6d; mains dropping resistors for .15a valves, 920Ω, tapped at 850 and 700Ω, small size (3in×⅝in), 2/3.

A.C./D.C. amplifiers, complete kit for construction of 20w. gram amplifier, by McMurdo, all first-class components, by Partridge, Gardner, etc., valves 4×CL33, 2×EF37, 2×UR3C, black crackle, chassis and case, isolated from mains, and drilled, circuit diagram supplied, everything complete, £10/19/6, carr. paid; television focus coils, for 9 or 12in mag. tubes, res. 10,000Ω, average current 20mA, 7/6, post paid.

PERSONAL receiver, 3 valve T.R.F. using 1T4's, contained in handsome bakelite case with lift-up lid, size 7×6½×5in with lid closed, plastic carrying handle, tram AE in lid, these receivers cover the medium waveband and operate from self-contained dry batts., standard types, W1435 and U2, output to a pair of lightweight 'phones (H.R.) controls, SM tuning and reaction, opening lid switches on, supplied brand new, with valves, batteries, 'phones, an ideal set for invalids, hosp. patients, etc., these receivers are not Govt. surplus and are offered ready to play, carr. paid, £3/19/6.

CHASSIS, Steel, 5½in×5½in×1¼in, drilled, 4-button base holes, 1/9. 5×9×1½in, drilled, 7-button base holes, 2/3; all., 17×9½×2½in, drilled, 7 int. octal and square, open ends, 4/-. E.H.T. trans., 4kv 250v C.T. 2a, sec., primary, 230v, 50c/s, gives approx. 5,500v with usual smoothing, 29/6; primary, 0-110-210/240v, 50c/s, sec., 300-0-300v, 80mA, 6v 2a, 6.3v 2.5a, 15/6; all trans. post paid; smoothing chokes, 20H 80mA, 350ohm, 6/11; 5H 200mA, 100Ω, 5/6; 6H 200mA 100Ω, 6/6; 8H 250mA 50Ω, size 4×5×5, shrouded, 10/6; all post pd.; electrolytics, 8mf 450v, 2/3; 16+8 350v C.T. 2a, sec., 2/-; 32 450v card, 2/6; 25 25v, 1/3, 25 50v, 1/3; 50 25v, 1/3; 100 12v, 1/-; 50 12v 9d; output trans., 2,000/2Ω, 2,500/2Ω, 2,750/2Ω, 3,000/2Ω, 5,000/2Ω, 7,000/4Ω, all 5/6 a ratio, 7,000-5,500-1,750/4Ω, 4/-; switches standard Yaxley, 2p 4w 2b, 2/-; 2p 4w 1b, plus additional wafer with shorting plate, 2/-; all have 3in spindles; superhet coils, 1¼in×1⅝in, 4 ranges, M wave, HF, Ae., Osc. L wave H.F.Ae., Osc., 1/6 per coil, midget I.F. trans., 465kc/s, iron cored, size 1⅜in dia., 1¼in height, 10/- pair.

METERS, metal cased, 2in circular, 0-15/600v req. ext. res. 6/6, 0-20A or 0-40A with shunts, 5/-; bakelite, cased 2in square 0/1mA 8/6, 0/5mA 6/-, 0/50mA 7/-, 0-300v series res. supplied 7/-, 0/20v 5/-; bakelite cased 2½in circular 0/30mA 7/-, 0/100mA, 0/200mA 8/6, all meters flush mounting, post extra; SM dial as on RF26, etc., less cursor, 3/11; rotary power units type 104, 12v D.C. input 250v 60mA, 6.5v, 2.5A, D.C. P.M. rotary mounted on chassis with supp., 6/-, post paid; Type 87, 24v input, output as 104, 5/6; plugs and sockets, bakelite with keyway, 5, 7 and 10 way, 1/6 pair; 8 way "Jones," plugs and sockets with cover, 1/6 pair; bakelite cases with lid, inside meas. 6×6¼×3¼in without lid, lid in deep with former for tram AE, lid required fixing, ideal for personal sets, meters, etc., 7/6, post paid; extension speaker contro's, 10Ω wire wound, ¼in spindle, 9d each.

RADIO CLEARANCE, Ltd., 27, Tottenham Court Rd., London, W.1. Tel. Museum 9188. [0015

OFFERS wanted for 200 5-gang variable condensers, 100 pf with 5 air speed trimmers and worm reduction drive.—26, Watford Rd., Kings Norton, Birmingham, 30. Tel.: Kings Norton 1946. [6441

AMATEURS, dealers servicemen, why pay fancy prices? "Be in the know." Send s.a.e. today for list that will save you pounds; goods c.w.o. only; mone back guarantee; don't delay! No c.o.d.
ANNAKIN, 25, Ashfield Place, Otley, Yorks.

NEW silver mica condensers, 30, 33, 47, 50, 58, 60, 70, 75, 120, 140, 150, 200, 500, 1,900, 3,000, 4,000 pf, 2/6 doz, 22/6 gross, £6/15 per 1,000, including postage; any values, mail orders only.—I. A. Duck, 97, Belgrave Rd., Ilford, Essex. [6443

50 kVA Hackbridge transformer, no-mal input 11,500 volts, 3-phase 50 cycles, with tappings plus or minus 2½% and 5%; output voltage 400 3-phase or 230 volts single phase; price £80.—The Brereton & Tubular Rivet Co., Ltd., Aylesbury, Bucks. [6446

OSCILLOSCOPE cabinets, 11×9×6¼, complete with chassis containing support and holder for VCR 139 tube, 2 potentiometers, various resistors, etc.; the cabinet has hinged viewing hood with plate glass window; supplied with full conversion data, 10/- each, plus 1/4 postage; 2in moving coil microphone inserts, 45 ohm, suitable for microphones or miniature extension speakers, 3/- each, plus 4d postage.

VALVE volt meter, pocket size, complete kit of parts for home construction which includes black crackle case size 4½in×3½in×1½in already drilled with hinged back, high-class moving coil mete miniature valve and base, switch, leads, battery, etc., with full instructions; this instrument, when constructed, will cover ac, audio and RF test work over the low voltage range of 0-5 volt, price 27/6 and postage 1/-.

NEW 0-5 ma moving coil meters, 7/6, post 6d. TELEKIT SUPPLY COMPANY, 51, Addington Rd., West Wickham, Kent. [6509

NORTH BRITISH TRANSFORMER CO.

TRANSFORMER HOUSE,
215, BARKEREND RD., BRADFORD,
YORKS.

All Transformers guaranteed against faulty workmanship

ALL PRIMARIES ARE TAPPED 200/250 v. INPUT

MAINS TRANSFORMERS

DT/150, 350-0-350 v. 150 m/a., 6.3 v. 4 a. C.T., 5 v. 3 a.	35/6
MF/150, 350-0-350 v. 150 m/a., 6.3 v. 4 a. C.T., 5 v. 3 a.	37/9
DT/100, 350-0-350 v. 100 m/a., 0-4-6.3 v. 3 a., 0-4-5 v. 3 a.	25/6
MF/100, 350-0-350 v. 100 m/a., 0-4-6.3 v. 3 a., 0-4-5 v. 3 a.	27/9
DT/80, 350-0-350 v. 80 m/a., 0-4-6.3 v. 3 a., 0-4-5 v. 3 a.	24/3
MF/80, 350-0-350 v. 80 m/a., 0-4-6.3 v. 3 a., 0-4-5 v. 3 a.	26/6
DT/M3, 350-0-350 v. 80 m/a., 6.3 v. 3 a., 5 v. 2 a.	22/6
MF/350, 350-0-350 v. 250 m/a., 6.3 v. 6 a., 4 v. 8 a., 0-2-6.3 v. 2 a., 4 v. 3 a.	68/6
MF/160, 350-0-350 v. 160 m/a., 6.3 v. 6 a., 6.3 v. 3 a., 5 v. 3 a.	44/6
MF/120, 350-0-350 v. 120 m/a., 6.3 v. 4 a., 5 v. 3 a.	34/6
DT/120, 350-0-350 v. 120 m/a., 6.3 v. 4 a., 5 v. 3 a.	33/9
DT/M2, 250-0-250 v. 80 m/a., 6.3 v. 3 a., 5 v. 2 a.	20/6
DT/80, 250-0-250 v. 80 m/a., 6.3 v. 3 a., 5 v. 2 a.	21/6
MF/M2, 250-0-250 v. 80 m/a., 6.3 v. 3 a., 5 v. 2 a.	22/9
Williamson O.P. Transformer	67/6
Williamson Mains Transformer, 425-0-425, 6.3 v. 4 a. C.T., 5 v. 3 a., 6.3 v. 4 a. C.T.	53/6
Williamson Choke, 30 H., 20 m/a., shrouded	22/3
Williamson Choke, 30 H. 50 m/a., shrouded	24/9
Williamson Choke, 10 H., 150 m/a., shrouded	33/6
Williamson Pre-Amplifier Transformer	23/9

WE HAVE A SPECIALS DEPARTMENT WHICH DEALS SOLELY WITH WINDINGS TO ANY SPECIFICATION.

DT = Drop Through type. **MF** = Fully shrouded type. **DT/M** = Smaller Drop-through type. **MF/M** = Smaller fully shrouded type.

WILCO ELECTRONICS

RECEIVER R.1155. One of the best communication receivers covering 7.5 Mc/s to 75 Kc/s in 5 wavebands, complete with 10 valves. Brand new in maker's transit case, **£12/10/-.** Cge. 7/6.

PORTABLE TEST METER, just the job for the home constructor, in neat case 6 x 5 x 4in., reading 1.5, 3, 150 volts, 6 and 60 m/a, 5K and 25K ohms. D.C., **50/-.** Post free.

PYE STRIP, 45 Mc/s complete with 6 EF50 and an EA50, **62/6,** or without valves, **37/6** each.

PHILIPS CAPACITY-RESISTANCE BRIDGE, 110 and 230 v. A.C. ex-Govt., new but need slight attention, **£6/10/-.** Post and pkg. 5/-.

AMPLIFIERS, 50 watt. Rack mounting by "Tannoy" including 10 valves: 4 **L63**; 4 **6L6**; in Push-Pull, 2 **FW4/500,** for 200/250 v. A.C. 50 cyc., complete with output transformer **£12/10/-.** Also some "Marconi" 15 watt, complete with valves, **£8/10/-.**

POWER PACK, Type 3, for R1132A receiver. Brand new, in perfect condition, input switched 200 to 250 volts, A.C. 50 cycle, with two smoothing chokes, fitted D.C. voltmeter 0-300, milliampere meter 0-150, fuses, etc. A superb job, **£4/19/6.** Pkg. and Cge. 10/-.

TEST SET, Type 205. 3.05 to 3.35 centimetres with 9 valves including Magic eye. Klystron. 100 Microamp. meter. Blower motor, etc., in good condition, **£20.**

TEST SET, Type 28. Incorporating a 50 Microamp. meter, in steel case 6in. x 3½in. x 3in. with carrying handle, **50/-.**

204, LOWER ADDISCOMBE RD., CROYDON

RELAYS, P.O. Type 3000, etc. Siemens' High Speed. Key Switches, Uniselectors, Jack Sockets, Plugs, Handsets.

RACKS. Standard P.O. Channel Type for 19in Panels. Bulbs, Switches, Rectifiers, Slydlok Fuses, Brieze Plugs and Sockets, American Test Equipment, etc.

WHOLESALE ONLY

L. WILKINSON
19, LANSDOWNE RD., CROYDON, SURREY

A WINDOW WORTH LOOKING INTO

Rotary Convertors. 12 volt D.C. input 230 volt A.C. mains output up to 200 watts, complete with meter and voltage regulator, £4/10 each, 24 volt ditto 65/-, both supplied with wooden carrying cases.

Mains Transformers. 230 volt input, output 1,800 volt 20 m/a, 21/- each.

Condensers. Mansbridge 6 mfd. 1,000 volt working, 2/6 each, 16 mfd. 700 volt Electrolytic Condensers, 5/6 each. 16 x 16 x 16 mfd. 450 volt Electrolytic Condensers, 3/6 each. .5 mfd. 3,500 volt Mansbridge, 3/6 each. .5 mfd. 6,000 volt Mansbridge, 4/6 each.

Condensers. "Trouble Free" Oil Filled High voltage .1 mfd. 3,000 volt, 4,000 volt and 5,000 volt, 2/9 each.

Modulators Type 67. Containing complete A.C. mains Pack giving 345-0-345 volt 200 m/a 6.3 volt 5 amp., 6.3 volt 1 amp., 5 volt 2/3 amp., complete with 5U4G rectifing valve plus 8 other valves, condensers and many other useful parts, brand new, 52/6 each, input voltage 230.

Pots., Heavy Duty Type. 3,000 ohms and 10,000 ohms 8 watt rating, 3/6 each. 5,000 ohms ditto 3in. dia., 4/6 each. All wire wound.

American Telephone Hand Sets. "Weston Electric" type, type I.F.I. AW3, complete with inserts, brand new, 15/6 each.

American Rotary Transformers. Ex-"Command Receivers" 27 volt input, output 280 volts 60 m/a, 7/6 each.

Chokes. 200 m/a 3 Henry, 3/6 each. 200 m/a 5 Henry resistance 100 ohm, 3/6 each. 20 Henry 80 m/a resistance 360 ohms, 4/6 each.

Television. 45 Mc/s I.F. Strips, brand new, complete with 6 EF 50s and 1 EA 50, 59/6. Less valves, 37/6.

Accumulators. Unspillable Lead Acid. 2 volt 7 amp. Brand new, 4¼ x 3¼ x 1¾in., 6/6 each.

Accumulators. Brand new. 6 volt 85 amp. Lead Acid. Teak boxes, 55/- each.

Television. 2 valve amplifiers. 45 M/cs, complete with 2 EF 50s, 13/6 each.

R1355 Receivers. Brand new. Complete with all valves, 49/6 each.

Rectifiers. Full wave L.T. 24 volt 5/8 amps., 32/6 each. 12 volt 5/8 amps., 17/6 each.

25/73 Receivers. Brand new. Complete with all valves, 22/6 each.

Open all day Saturday.

G. W. SMITH & CO.
(RADIO) LTD.
3, LISLE STREET, LONDON, W.C.2
Phone: GERrard 8204

SYNCHRONOUS clock units, self-starting, 200-250v a.c., 50 cycle, fitted Sangamo motors, consumption 3½ watts, size 2¾in diam., 2in deep, geared 1 rev 60 mins friction reset.
IDEAL movements for making electric clocks, time switches, etc., complete with 12 to 1 dial train and 5in hands, price 22/6, post paid.
SANGAMO as above, final speed one rev per min, less dial train, ideal for dark room process time, etc., price 20/- each, post paid.
CRYPTO rotary converters, input 24 volts d.c., output 230 volts a.c., 50 cycles, 100 watts, fitted carrying case, £4/15 each.
H.F., aerial change-over switches, type 78A manual or relay operation, 24 volts, size 5½in × 4in × 2in, £1/7/6 each.
COLVERN wire wound potentiometers with switches, sizes 10, 25, 500, 50 and 1,000 ohms, in lots of twelve or more, 32/- per doz.
PERFORMANCE meters type No. 2, fitted standard mains 230v a.c., 50 cycle, power pack, 2 V.R.91, 1 V.R.137, 1 SZ4G, 1 C.V.51, 1 V.R.92, and other useful components, £2/5 each, carriage 3/6.
L.T. transformers, input 200/250v, 50 cycles, output 12/25v, 250 v.a., in metal cases, £2/15 each; metal rectifiers, 180v, 3½amps, £3/5 each; rectifier units, a.c. to d.c., input 200/250v, 50 cycles, output 160/200 v.d.c., ¼ amp, £2/1 each; large quantity of new Uniselector spares, comprising of banks, wipers, coils, etc., to be sold in one lot, enquiries invited.
NEW ex-R.A.F. English Electric electronic ignition testers, type Ref. No. 5G/447, input 230 volts a.c. 50 cycles, 6/12/24 volts d.c.; £19 each.
STEP-DOWN transformers, input 250v a.c., 50 cys., output 6.3-0-6.3 volts 19 amps; £2/12/6 each.
ADMIRALTY pattern heavy duty L.t. transformers, primary 230 volts 9 amps, secondary 18 volts 108 amps, centre tapped; £12/10 each.
WESTINGHOUSE rectifier sets, style 28B, G.P.O., input 200-250 volts a.c., 50 cycles, output 50 volts d.c., 1½ amps; £3/10 each, carr. paid.
DITTO rectifier sets, output 50 volts d.c., 3 amps; £6 each.
JANETTE rotary converters, input 115 volts d.c., output 110 volts a.c., 50 cy., 150 watts; £4/15 each.
A LARGE assortment of various ex-W.D. radar and radio equipment, relays, power packs, oscillograph units, gears, photographic apparatus available; s.a.e. for lists.
H. FRANKS, 56, New Oxford St., London, W.C.1. Tel. Museum 9594. [0057

3cm radar equipment. Philco, ex-U.S. Navy, complete with plugs, junction box, scanner, separate repeater P.P.I., instruction manual, etc., etc., total weight 3 cwt; £250.—Box 8285. [6471

"YOU'LL probably get it at Smith's, Edgware Rd.!" Everything for the constructor, from a 1/10watt resistor to a radiogram cabinet, lowest prices, biggest variety.—Near Metropolitan Music Hall. Pad 5891. [0114

LAST chance to obtain receiver 25/73 in spot condition (less valves) at 6/6 post free; electrolytics: 32mf 350v, 4 for 10/9; U.S.A. 0-500 microamp meters, 6/6; speakers, 5in 11/6, 6in 12/6, 8in 14/6, 10in 16/6, 12in 45/-; mains trans., 350-0-350 6v, 4a, tapped at 4v 90ma, 16/6; new metal rect., 250v 80ma, 6/6; resistors, 10k, ¼w, 30ohm, ¼w, 1800ohm 1w, 2/-, 3/- and 4/- doz; V/controls, ¼ and ½meg, L/sw, 1/6 each; ½meg, W/sw, L/spindle, 3/3. Full range Amphlex controls in stock, 10k to 2meg, 4/-; SP/sw 5/9, DP/sw 6/6; new component list available; stamp please.
RADIO UNLIMITED, Elm Rd., London, E.17.

COOL that tube! 24-volt blower motors with 7" fan, 10/6; 12 volt with fan 4½in blades, 7/6; 24-volt, both ac/dc; valve holders, ceramic EF50, 1/6 dozen; Paxolin British 4-pin or U.S.A. 5-pin UX, 1/6 dozen; aerial metering units contain W.I. Westector, 1/3; bulbs MES 6 volt 0.3A, 6 volt 0.24 watt, 4/6 dozen, 12 volt 2.2 watt, 6/- dozen; also 6-12-24 volt telephone-type at 4/6 dozen, 22 volt 12 watt M.B.C., 5/- dozen, 24 volt B.B.C. pearl, 80 watt, 8/- dozen; projector bulbs 250 volt 250 watt E.S. class BI, 7/6; 4mfd condenser, 750 volt, 2/-; 0.5mfd 500 volt, 2/6 dozen. 50mfd 40 volt, 3/6 dozen; controls 10,000 ohms carbon preset, 3/- dozen, fixed resistances, 22,000 1 watt, 2/6 dozen, 33,000 2 watt, 3/6 dozen; Co-ax 2-yard lenghts with Pye socket, 1/3.
PASSINGHAM, 95, North St., Keighley. [0002

G. E. RYALL, Utopia, Mayfield Rd., Herne Bay, Kent, offers post-free bargains; meters, m/c boxed, new, 0-30ma 2½in (3¼in) overall, flush mtg., 5/9; also 2in square front flush, 0-300 volts, separate series resistance (5ma), 5/9; also 0-5ma 2in best make, 5/9; instrument boxes metal black finish, size 3½ × 7½ × 3¼ deep, with Paxolin ¼in panel, fixing lugs for flat or wall, corner sockets for panel fixing, 6/9 each; headphones, high res. 1,600 ohms pair, complete with good type carbon microphone, all wired into four cleft plug, with sponge rubbers and padded headbands, ex-R.A.F., used but in good condition, 5/9 set; Paxolin panels quarter inch, 12 × 12, 4/9, 12 × 8, 4/-, strips Govt. grade about ¾in, 12 × 5 approx, 2/-; all undrilled; special offer 12 × 12 ¼in slightly soiled, two for 5/-; and clearance resistor and condenser panels assemblies, over one hundred items, all new and clean; twenty assorted panels, 12/9; trimmers ceramic, 25mm., boxes ten new, 5/-; valve holders Paxolin Int. Octal chassis, 3/- dozen; British-pattern 5-pin, a moulded base type, 3/- dozen; special list available for trade, including twelve thousand Yaxley-type switches, 10,000 25mm ceramic trimmers, 100,000 yards high-voltage and plastic sleeving; 15,000 moulded mica 0.004mf, tags, 1,250v wkg insulation perfect, 1,000 small control boxes with switch, suitable television junction with co-axial input and output; 10,000 low-tension vitreous resistors, etc. [0005

EARLY BIRDS ARE WELL ADVISED

Since we wrote our resolution for 1951 prices of magnet castings have jumped up nearly 15 per cent. This is the most costly item in any good speaker, so such increases have a serious effect on total works production costs. We shall absorb the present rise ourselves, but there is a limit.

We have no doubt that the steep rises in metal prices must before long have an effect on amplifiers, turntables and other essential items for good quality sound reproduction. May we then advise you to consider what you wish to listen to, even as far ahead as next winter, and act soon to obtain your needs.

If you believe in having the best and

MOST NATURAL REPRODUCTION

of your favourite music and artists, we believe that you MUST sooner or later have one of our speakers. Basically, and irrespective of cost, our drive and cone give a closer approach to truth than any we have heard elsewhere—an opinion shared by many experienced and critical owners.

This is not just a matter of giving 50 to 15,000 c.p.s.: that is not really very difficult to do. BARKER SUPREMACY lies in absolute smoothness and control at every part of the scale; in definition and transients which delight the ear; in entire absence of boom, peaks, or sizzle.

If these ideas appeal to you, and you are really interested in getting the nearest approach to Natural Sound Reproduction in your own home, write to-day for details of our speakers and the new 501 cabinet.

BARKER NATURAL REPRODUCERS
BCM/AADU
LONDON, W.C.1.

DUKE & CO.

SUPERHET RECEIVER, 9/6 with 3 wave band mains conversion drawing FREE. I.F.465, also well worth as spares. It includes 4 tuning condensers, 24 fixed cond., 32 resist., transformers, switches, volume controls, valve holders and all the usual parts. This 25 (1196) set is a good buy. Post 1/6.

H.T. BATTERIES, 5/6, still our best seller, 150 volt guaranteed minimum, tapped 21-90-111, 1½ L.T. All-dry. All are tested before despatch. Allow 1/6 for post.

ELECTRIC MOTORS, 30/-, 1/3rd H.P. S/Phase A.C. 110 v. easily rewound to 230 v. Or will work from transformer or resistance, complete with Forge type blower 3¼in. dia., outlet. Motor is 2,850-3,450 r.p.m. ¼in. spindle. Carriage extra.

CAR HEAD LAMPS, 7/6 only, ex-L.P.T.B., standard single bolt fitting.

LAMPS, ex-L.P.T.B. standard B.C. fitting, 24 v., 12 watt, and 12 v., 12 watt. Ideal for boats, caravans, etc., 9/- doz.

GERMAN INVASION CRAFT, 30/-, 20 to 30ft. by 6 to 8ft., tough vulcanised rubber inflatable. Room required. Sizes as they come, carriage extra.

SEATS. Moquette, hide or leatherette covered, plywood base, ex-coach, approx. 3ft. long by 16 x 4in. thick. A few backs to match, both 15/- each, plus carriage.

DUMPY BUCKET SEATS. Single, ex-coach. Ideal for T.V. viewing, small cars, vans, garden, etc., 17/6, plus 4/- carriage.

HEAD SETS, 1/9, new with the flat type head bands, very comfortable, and extremely sensitive, single set. Post 6d.

TINY TIMS, £17 10/-. Four stroke design, press button starting. Has an output of 300 watts at 12 volts. New, carriage extra.

REMEMBER. We are the largest valve stockists in East London. Money back guarantee if not satisfied. Cash with order please, and allow sufficient for post or carriage. Stamps ONLY for lists.

REMEMBER, if interested in FISHING ask for our separate ANGLING CATALOGUE.

219, ILFORD LANE, ILFORD, ESSEX. ILFord 0295.

NEW ELECTRONIC SUPPLIES Co.

281 LEEDS ROAD, FAGLEY, BRADFORD, YORKS.

MAIL ORDER ONLY.

ALL PRIMARIES 200/250 INPUT. HARD VARNISH, BAKED AND IMPREGNATED **ALL NEW GOODS.** NO SURPLUS OR EX-GOVT. STOCK. F = FULLY SHROUDED TYPE. S = HALF SHROUDED OR SUNK TYPE. QUOTES FOR SPECIALS WITHIN 48 HOURS. PLEASE ORDER EARLY AS PRICES ARE GOING UP AND SUPPLIES GOING DOWN. TERMS—C.W.O. (CARRIAGE PAID).

S260 260/0/260 v. 60 mA, 6.3 v. 3 a., 5 v 2 a. ..... at **18/11**

S275 260/0/260 v. 75 mA 6.3 v. 3 a. 5 v. 2 a. ..... at **20/11**

*S350 350/0/350 v. 90 mA ..... at **21/3**

*S250 250/0/250 v. 110 mA ..... at **23/11**

*S300 300/0/300 v. 110 mA ..... at **25/3**

*S310 350/0/350 v. 110 mA ..... at **26/11**

Above 4 marked * have LT 0-4-6.3 v. 4 a. 0-4-5 v. 2 a.

S356 350/0/350 v. 160 mA 6.3 v. 3 a., CT 5 v. 3 a. ..... at **29/11**

F315 350/0/350 v. 160 mA, 6.3 v. 6 a., 6.3 v. 3 a., 5 v. 3 a. ..... at **43/9**

*F359 350/0/350 v. 90 mA ..... at **22/3**

*F250 250/0/250 v. 110 mA ..... at **22/6**

*F300 300/0/300 v. 110 mA ..... at **25/11**

*F350 350/0/350 v. 110 mA ..... at **27/11**

Above 4 marked * have LTs 0-4-6.3 v. 4 a. 0-4-5 v. 3 a.

Williamson O.P.T. to specification ..... at **78/6**

Williamson Mains to specification, Type F425 ..... at **82/11**

Williamson Choke 30H 20 mA, CK10 at **18/-**

Williamson Choke 10H 150 mA CK9 at **29/11**

Williamson Choke 50H 50 mA, 1500 Ω CK8 ..... at **21/11**

Above Chokes fully shrouded heavy jobs

CK11, 8H, 110 mA. Upright mount at **12/11**

CK15, 3H, 40mA. Clamped ..... at **5/11**

CK12, 5H, 90mA. Clamped ..... at **9/11**

CK14, 5H, 60 mA. Clamped ..... at **7/6**

TERMS: CASH WITH ORDER. CARR. PAID

OUR latest bargain list is now ready; send stamp or large stamped addressed envelope today.
WALTON'S WIRELESS STORES, 203, Staveley Rd., Wolverhampton. [0061

LITTLEWOODS, North London's best selection of radio and television components; pay us a visit or post or 'phone your enquiries; no lists. LITTLEWOOD & GRUNER, Ltd., 27, Ballards Lane, Finchley, N.3. Fin. 3060. [0055

RATHONIC DISTRIBUTORS offer amplifiers R. 6v, 30w, negative back feed remote control relay for distant operation. 200/250v 50 cycles input, suitable mic or gram. tapped outputs 3 to 60 ohms, tuner and pre-amp plugs incorporated, valve line 2 EF36, 1 ECC31, 2 EL35, 1 U52, practically new and tested, made by well-known manufacturer, suitable fro rack mounting if required; worth £35; our price, including packing and carriage, £10.
INDICATOR units, type 6, suitable inexpensive television, Wireless World oscillope, as new and unused, valves 4 VR91 (EF50), 3 VR92 (EA50), 1 VR54, C.R. tube VCR97; our price 60/-; carriage and packing 7/6, in maker's original box 10/- extra; special price for quantities.
TRANSMITTER receiver, type 3510. 13 valves covering 150 to 250mc/s range, complete with power pack for ground operation, complete with two meters, slow motion dials, and 13 valves in steel cabinet, size 17in×17in×13in. with folding doors, as new and unused; £3/19/6, a fraction of its original cost; carriage and packing 10/6.
RECEIVER unit, type AP57951. 11 EF50 valves, suitable for two meter fans, in original manufacturer's case; only 39/6; few only so get in first; carriage 10/-.
TYPE 26A tuning unit, silver wire wound coil for 2.5 to 15mc/s, R/F meter rev counter in metal box, ideal for determining antena length, 25/-, carriage 2/6; master oscillator units, type 123, silver wire coil in brass case, packed in instrument wooden original box, 10/6, post and packing 1/6; mains transformers, American (new), 110-250v. 350 o 350 150 mils, 6.3v 4amp, 5v 3amp. shrouded drop through, beautiful job, 25/-, post 2/-. also 500 o 500 250 mils and heater wind ng, 35/-, post 2/-; American crystals, 10 in box, new covering, 100 to 156 megs. 60/-, post 1/-; Selenium rectifiers, 37-plate (new), 4/9 each, post 6d. special price for quantities: Govt. converted motors to approx. ¼hp. 2,000 revs, suitable driving small lathes, etc., in your workshop, absolute bargain, 3/8; spindle only, 19/6, carriage 3/-; power units, type 33a and 35a, 35/-. carriage 5/-. special price for quantities; Pointalites, suitable for photograph enlarging, stills and projection, complete with lamp, 35/-, carriage 6/-, lamp alone cost 50/-; Nife accumulators, 2.5v 15amp hours, unused, will last a lifetime, 6/-, post 6d each. special price for quantities; Klystron magnets, suitable for "Wireless World" ribbon speaker, 15/-. carriage and packing 3/-; American blower motors, 28v with 8uf condenser, will work off 200-250v mains, ideal for hair driers, etc., only 6/-, post 1/-; 6-way coil packs with Yaxley-type switch and condensers, beautiful job, 5/-, post 1/-; 16uf 350v electrolitic condensers. 2/-, 32uf 2/-. 8uf 500v 2/6, 16uf ditto 2/6; ¼ meg volume control with switch (new), 2/9; post on last five items 3d each; number of type 106 signal generators, 2 to 55mc/s, square wave and various types of equipment and receivers too numerous to mention in this advert. for callers only; hours of business 9 to 6, except Sats., 1 p.m.; c.w.o. unless by other arrangement; all goods subject to being unsold.
RATHONIC DISTRIBUTORS, 63, Oldhill St., London, N.16. Sta. 2660. [6513

COMMUNICATION receivers in stock. Hammerling Super Pro. H.R.O. Seniors Hallicrafter S.52, C.R.100, R.88D., A.R.88L.P., etc., all in perfect order; R.1155 receivers in new condition; your enquiries are invited for rotary convertors and electric motors, most sizes and types available from stock; motor alternators, 110v d.c. input 230v a.c., 50 cycles, 250 watt output, £9; special clearance of F.H.P. electric motors, 55/-, 110v-250v a.c.
UNIVERSAL a.c./d.c. motors, suitable for sewing machines, 40/- each; 12v-15v a.c./d.c. motors with extended spindle, suitable for models, etc., 9/3; 20watt P.A. rack mounting amplifier, new and complete with heavy duty a.c. power pack, 200/250v, PX25 P.P. output, £4/10, less valves; new moving coil microphones, hand type, heavy duty and complete with 12yd screened cable, £3/15; 2 only as new B.T.H. Jenson cinema speakers, energised, and twin unit multi-cellular horn unit; 20ft telescopic tubular T/V mast, 15/6 each; large selection of test equipment; multi-range meters, valve testers, signal generators, oscilloscopes, bridge meggers, and meggers, etc., all at reasonable prices; hand bearing prismatic compasses with provision for battery in handle, perfect, 40/- each; very large stocks of transmitting valves, Klystron, of all types, send us your requirements; special offer of new, but ex-W.D., mains transformer, semi-shrouded, 200/250v tapped primary, 250-0-250, 100ma., 5v 3amp, 6v 4amp, 20/- each; large stocks of L.T. transformers, special sizes and ratings wound to specification; auto-record changers in stock from £10/15; switchboard mounting voltmeters, ampmeters, various ranges a.c. and d.c. available at cheap prices to clear; large stocks of enamelled wire, 28 s.w.g., 1lb and 2lb s.w.g., D.S.C., No. 15 U.X. base American valves available. Special offer: H.R.O. coils, .48-.98 m/c and 180-430 k/c, 45/- each; quantity of 1lit and nickel chrome wire available; 3in Panoramoscope model 5A-3, type T200, £25; 62A indicator units, less valves and tube, 22/6; 100 micro-mp meters, 2¼in scale, new, 70/- each; type 74 in.'cator units, complete with tube, as new, £5 each; Fluxmeters, model WY.0023, complete, new, £5/10; prices do not include postage.
SERVICE RADIO SPARES, 4 Lisle St., W.C.2. Gerrard 1734. [0188

FIDELIA *De luxe*

Luxury 9 valve Radiogram chassis with 7 watt triode push-pull output stage and wide range electronic tone control circuit. Designed to provide high fidelity reproduction from: microgroove recordings as well as the standard 78 r.p.m. recordings. Circuit includes variable selectivity, cathode follower detector, audio frequency response 30-20,000 cycles within one d.b. Price **£21/5/-**

Other models in our range are:

Fidelia Standard 7 valve model **£18/5/-**.
Fidelia Plus 8 valve model **£20 12/-**.
Preciton 5 valve model **£12 17 6**.
All Fidelia models have variable selectivity, wide range electronic tone control, Triode output stages, cathode follower detectors. Three wavebands 16-50, 185-550, 1,000-2,000 metres. All equipment guaranteed 12 months. Technical data sheets willingly sent on request.

ELECTRONIC Acoustic DEVELOPMENTS

18 Broad Road, Willingdon, Eastbourne

NEW S.T.C. SELENIUM RECTIFIERS. Largest L.T. range in Great Britain. Current products. NOT SURPLUS. E.H.T. H4/200 W.W. Televisor replaced by N2/100, 17/-; for VR97, N2/50 12/-. Post 6d.

Note Increased Prices from 1st Jan. 1951.

HALF WAVE RECTIFIERS.

16v. ¾a., 7/6; 1a., 9/2; 2a., 10/8; 3a., 17/6; all post 6d. 4a. 18/-; 6a., 23/9; post 10d. 30v. 1a., 13/6; 2a., 15/10; 4a., 28/-; 6a., 41/6; 48v. 1a., 17/10; 2a., 21/3; 4a., 40/6; 6a., 58/-; 100v. 2a., 39/6; 4a. 74/-; 6a., 108/-; all P. 1/-.

HALF WAVE HEAVY DUTY 7¼in. SQUARE COOLING FINS.

16v. 5a., 24/3; 10a., 26/-; 20a., 48/6; 30v. 5a., 39/6; 8a., 43/6; 40v. 2.5a., 29/6; 5a., 54/3; 8a., 61/-; all post 1/-.

BRIDGE CONNECTED FULL WAVE.

17v. 1.25a., 13/9; 1.7a., 17/7; 2.5 a., 22/9; 3a., 24/9; 4a., 28/-; 5a., 29/6; all post free. 33v. ¾a., 21/-; 1a., 24/3; 1.5a., 32/-; 2a., 35/-; 3a., 40/4; 4a., 46/-; 5a., 50/-; all post 10d. 54v., 1.5a., 44/-; 2a., 54/-; 3a., 61/-; 5a., 75/-; 72v., 1.5a., 57/-; 2a., 69/-; 5a., 98/-; 100v. 1.5a., 82/-; 2a., 100/-; 5a., 144/-; all P. 1/-.

BRIDGE CONNECTED HEAVY DUTY 7¼in. SQUARE COOLING FINS.

17v. 6a., 38/10; 10a., 47/6; 12a., 82/-; 20a., 90/-; 33v., 6a., 73/-; 10a., 81/-; 12a., 142/-; 20a., 160/-; 54v. 6a., 102/-; 10a., 114/-; 72v. 6a., 132/-; 10a., 146/-; 100v. 10a., 215/-; all P. 1/6.

BRIDGE INDUSTRIAL FUNNEL COOLED. 17v. 12a., 86/-; 20a., 99/-; 30a., 140/-; 50a., 212/6; 33v. 6a., 79/-; 10a., 90/-; 12a., 142/-; 20a., 164/-; 54v. 6a., 104/-; 10a., 122/-; 72v. 6a., 130/-; 10a., 154/-; 100v. 6a., 180/-; 10a., 217/6; all post 1/6.

VALVE CHARGER REPLACEMENTS. Send Circuits, max. A.C. voltages marked and max. No. 2v. cells chargeable, for reply.

Wholesale & Retail

T. W. PEARCE (Est. 19 yrs.)
66 GREAT PERCY STREET, LONDON, W.C.1
Off Pentonville Rd. Between King's Cross and Angel

POTENTIOMETERS

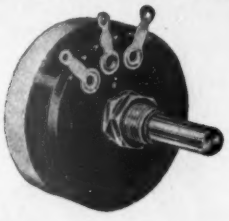

by RELIANCE

Wire wound and Composition types, Single, Ganged, Tandem Units.

Characteristics: linear, log, semi-log, non-inductive, etc.

Full details from

RELIANCE

Manufacturing Co. (Southwark) Ltd.

Sutherland Rd., Higham Hill, Walthamstow, E.17

Telephone: LARkswood 3245

MAGNETIC TAPE

Recording Equipments and Components

OSCILLATOR UNIT. Constructed on small chassis suitable for sub-assembly, provides r.f. for erase and bias at 45 kc/s. Requires 250 v. h.t. and 6.3 v. for operation. Complete with 6V6 valve, **£3.**

OSCILLATOR COIL ASSEMBLY. Comprises high "Q" coil and condenser tuned to 45 kc/s. Specially designed to provide highly symmetrical sine wave output for low tape noise. **10/6.**

RECORD/REPRODUCE HEAD. Impedance: 100 ohms at 1 kc/s. High quality response. Totally enclosed. Gap length 1 mil., **£2/2/-.**

REPRODUCE HEAD. As above, but gap length 0.5 mil. (suitable for 2-head systems), **£3/3/-.**

ERASE HEAD. Capable of erasing new high coercive force tape when used with oscillator unit above, **£2/2/-.**

TAPE. New high coercive force tape suitable for high fidelity recording at slow speeds. 7in. (1,200ft.) reels, **£1/10/-.** Spare reels, 7in., 4/6 each. 11in. (1,000 metre) reels also available.

INPUT TRANSFORMER. Ratio 1/40. Frequency response: ± 2 db. 50 c.p.s.—20 kc/s. Suitable for head to grid step up. Mumetal core, **17/6.**

TRANSFORMER. As above, but fitted in 16 S.W.G. mumetal screening can, **30/-.**

Send for further details including circuits. Trade and export enquiries invited.

CABOT RADIO COMPANY LIMITED

Electronic Equipment Manufacturers

28, BEDMINSTER PARADE, BRISTOL, 3.

Telephone 64314.

230/115v step-down transformers, 75-watt, 6/6; heavy duty output transformers, weight 3½lb, two primaries, one centre tapped and one secondary 4 taps, these can also be used as small mains transformers, delivering 150-0-150v at 100 ma and 10-20-30-40v all at 65 ma. 230v input, only 4/6; amplifier chassis with 2X6AC7, 1XGAG7, and chockful of useful parts, 12/6; wanted, tape or wire recorder.—Haynsons, 14, St. Mary's, Bedford. 'Phone 5566.

NOTICES

BRITISH SOUND RECORDING ASSOCIATION.

THE current lecture season is meeting with great success, membership of the Association has become essential to everyone actively engaged or keenly interested in high quality sound recording and reproduction; lectures and demonstrations on all aspects of electro-acoustics are given at the meetings; reports, papers and other valuable material appear in the journal; a few specimen copies of which are available to non-members, price 2/9 p.f.; the very successful 1950 Exhibition will again be held in 1951 and preparations have already commenced, this will be the outstanding event of the coming year and is free to members; full information is contained in the brochure and other material which, with a Membership Application Form, may be obtained from the Membership Secretary: Harrie J. King, 48, Mount View Rd., North Chingford, London, E.4. [0119

WANTED EXCHANGE, ETC.

WEARITE tape deck or recorder wanted, new or used.—Box 7995. [6402

BUSH 1939/40 SUG 65 or 55, PB65 or 55.—9 Dugdale's, Paignton. [6451

FEW Magnetron permanent magnets, state size and price.—Box 7994. [6397

WANTED, Magnetophon Tone B, with spares (amplifier not required).—Box 2665. [0198

WANTED, dynamometer a.c. test set, also oscilloscope type 339A, also L050A oscillator.

LESLIE DIXON & Co., 214, Queenstown Rd., Battersea, S.W.8. Macaulay 2159. [0176

E.M.I. type 12 hypersensitive pick-up.—Bradley, 20, Church Rd., Perry Barr, Birmingham, 22b. [6476

WANTED to buy or on loan, service sheet for push button K.B. Model 760.—Haworth, 58, Hozier Ct., Blackburn, Lancs. [6479

WANTED, HRO coils, Rx's, etc., AR88's, BC348's, 827's, etc.—Details to R.T. & I. Service, 254, Grove Green Rd., London, E.11. Ley. 4986. [0165

WANTED, laboratory test equipment including standard signal generator, watt meter, oscilloscope, bridges, recorders; send price and details to:

HATFIELD INSTRUMENTS, 175, Uxbridge Rd., Hanwell, W.7. Tel. Ealing 0779. [0037

WANTED, oscilloscopes, second-hand, in good condition.—Particulars to Lyddiard, 26, Northumberland Avenue, Gosforth, Newcastle-on-Tyne, 3. [6455

VOIGT corner horn with or without speaker unit, also Leak pick-up, condition of movement immaterial.—Details 24, Meadow Bank, Manchester, 21. [6442

WANTED, all types of radio equipment, test instruments, radio receivers, personal sets, television, components, etc., etc.; call, write, send or 'phone.

MILLER'S RADIO, 38a, Newport Court, Charing Cross Rd., London. [5211

WANTED, surplus relays, impulse switches, sparking plugs, 5-way, push-button units; any condition; large or small quantities; highest prices paid.—Box 4660. [5579

WANTED, Antenna tuning units type BC-939-A and T-50 microphones and junction boxes JB-70A.—PCA Radio, The Arches, Cambridge Grove, W.6. Tel. Riv. 3279. [0167

WANTED, RCA speech amplifiers type MI-11220 J or K and telephones type EE8, offers stating quantity and price to—PCA Radio, The Arches, Cambridge Grove, W.6. [0093

WANTED, BC-610 Hallicrafters transmitter, SX-26; AR-88's HRO receiver and spare parts for above; best price.—Write Box 864, c/o Spiers Service, 69, Fleet St., London, E.C.4. [0080

WANTED, AN/APR-4 receiver, any units; any other good quality U.S. surplus radio and radar, tubes, test sets; laboratory equipment, etc.; give condition and price in first letter.—Littell, Farhills Box 26, Dayton 9, Ohio, U.S.A. [6346

AERIAL single pole change-over knife switches urgently required for marine use, must be capable of handling 50W transmitters; these should be new or Govt. surplus; small or large quantities; state type, condition, quantity, price.—Woodson's, 76, Regent Quay, Aberdeen. [6456

REPAIRS AND SERVICE

MAINS transformers rewound, new transformers to any specification.

MOTOR rewinds and complete overhauls; first-class workmanship, fully guaranteed.

F.M. ELECTRIC Co., Ltd., Potters Bldgs., Warser Gate Nottingham. Tel. 1917. Tel. 5855

LOUDSPEAKERS repaired promptly, any make.—Model Loudspeaker Service, 34a, Bullingdon Rd., Oxford. [6519

REWINDS Philips neg. feedback output trans. motors, armatures, main trans., Solenoid and mag. coils., etc.

A. McLUCKIE, 259, Warwick Rd., Carlisle.

REPAIRS to moving coil speakers, cones; all coils fitted, field rewound or altered; speaker transformers, clock coils rewound; guaranteed satisfaction, prompt service.

L.S. REPAIR SERVICE, 49, Trinity Rd., Upper Tooting, London, S.W.17. Balham 2559. [0110

REPAIRS.—E.H.T., mains and O.P. transformers, field coils and chokes; also armatures and motors; new transformers designed to any specification; all work fully guaranteed.

WILLESDEN TRANSFORMER Co., Ltd., 791, Harrow Rd., N.W.10. Tel. No. Ladbroke 2846.

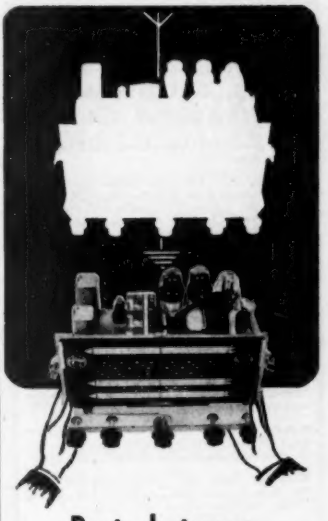

Best between Aerial and Earth

Armstrong chassis are designed and built for those who demand something more than ordinary commercial receivers can offer. Very—but very—brief details of the range are given below, but we'll gladly send you full specifications and data on any model(s) that interest you if you'll drop us a line.

Model EXP83/3. An 8-stage all-wave radio chassis. Fly-wheel drive and 8 watts output. A.C. 200-250 volts. **£15.8.8** Plus P.T.

Model RF103/3. A 10-valve all-wave radio chassis for A.C. operation, 200-250 volts. **£19.19.0** Plus P.T.

Model 125/2. A 14-valve five-band radiogram chassis with three S.W. bands down to 10.9 metres. A.C. 200-250 volts. **£33.12.0** Plus P.T.

ARMSTRONG T/V MODEL TV20. A wide range 20-valve instrument with 12" C.R. tube. Models for both London and Sutton Coldfield transmitters available. **£52.10.0** Plus P.T.

Armstrong

THE CHASSIS PEOPLE

Armstrong Wireless and Television Co. Ltd., Warlters Road, Holloway. London, N.7.

Telephone: NORth 3213.

5362

M. & J. PEARSON

263, GALLOWGATE, GLASGOW, C.4.

Offer the following clearance lines for one month only.

Test Set Type 74. Input 230 volts, 50 cys. Valves VR135, 5Z4, VU120, 6J5, 6Q7 and 5. VR65, in reasonable condition but less VCR 139A. Ideal for conversion to Scope. Special price £2/7/6, including carriage.

Receiver R28/ARC5. Coverage 100-150 M/cs. Valves 4 717A. Mushroom Type, 3 of 12SH7, 2 of 12SL7, 12A6M, would convert to 2 metres. Brand new. £1/12/6 each.

Command Receivers. 6 Valve Superhet Covering 1-5 to 3 M/cs. Valves, 3, 12SK7, 12KB, 12SR7, 12A6. Black Crackl Finish. Brand new in Cartons. £2 each.

Communication Receivers Type R.1155. Perfect condition in Transit Cases. Complete with valves, £8 each.

R.A.F. Aircraft Clocks 8-day Dashboard Type 2in. dial, with mounting flange, suitable for Workshop Bench, Car or Boat. 32/6 each.

Receiver Type 78, 5 Valve Superhet with 100 KC. Crystal ECH35, EF39, 6J5, VR91, VR92. Good condition, 35/- each.

Sperry Bombsight Computor. Contains a wealth of gears, spindles, wheels, rollers, etc., 2, 24 Volt Motors 1-5 Amp., with pulley shaft each end and reversing clutch mechanism, also 24 v. Selsyn repeater Motor and many other parts. Brand new in Transit Case, £2/10

All prices include carriage or post.

Cash with Order and please write name clearly.

SOLONS FOR YOUR SOLDERING JOBS!

Types available—65 watt oval tapered bit, 65 watt round pencil bit, 125 watt oval tapered bit, 125 watt round pencil bit, 240 watt oval tapered bit.

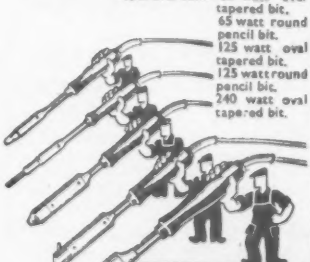

These five models will satisfy practically every soldering demand whether for the occasional household job or continuous soldering under workshop or factory conditions. With the Solon the heat is in the bit itself . . . continuously . . . hour after hour; all connections housed at end of handle away from heat. Each model complete with 6 feet Henley 3-core flexible. Now available from stock. Write for folder Y.10

W. T. HENLEY'S TELEGRAPH WORKS CO. LTD.
51-53 Hatton Garden, London, E.C.1

MAINS transformers rewound or constructed to any specification; prompt delivery.—Bede Transformer Co., Ltd., Bedesway, Bede Trading Estate, Jarrow. [3195

RADIO MAINTENANCE SERVICE for guaranteed rewinds and repairs; armatures, F.H.P. motors, vac. units, portable tools, etc.; good deliveries.—139, Goldhurst Terrace, N.W.6. Mai. 6133. [9925

"SERVICE with a smile."—Repairers of all types of British and American receivers; coil rewinds; American valves, spares, line cord. —F.R.I., Ltd., 23, Howland St., W.1. Museum 5675. [0112

ELECTRICAL measuring instruments of every make, multi or single range, repaired and standardised; prompt attention.—The Electrical Instrument Repair Service, 329 Ellburn Lane, London, W.9. Tel. Lad. 4168 [3715

TELEVISION, radio and amplifier repairs, conversions and modifications; home-built receivers aligned; commercial radios rebuilt, send equipment with full instructions for quotation by return post; 12 months' guarantee on all work done.
BERNARDS, Radio Engineers, 12, Chelverton Rd., Putney, London, S.W.15. [0099

24-HOUR service, 6 months' guarantee, any transformer rewind, mains outputs and L.f.s., etc.; all types of new transf., etc., supplied to specification; business heading or service card for trade prices.—Majestic Winding Co., 180, Windham Rd., Bournemouth. [6520

METROPOLITAN RADIO SERVICE for rewinds, mains and E.H.T. transformers, chokes and field coils; new transformers designed and manufactured singly or in quantities.—Metropolitan Radio Service Company, 1021, Finchley Rd., London, N.W.11. Tel. Speedwell 3000. [0130

WORK WANTED

RADIO, electronics, etc., skilled assembly, wiring, inspection, test, small capacity available for regular flow, S.E. London.—Box 7996. [6403

DRAUGHTING, tracing and photoprinting services; estimates free; contractors to the Ministry of Supply and the Admiralty for drawing and tracing work to their requirements and specifications; sub-contracting work of this nature undertaken.
DRAWING & TRACING, Ltd., 456a, Ewell Rd., Tolworth, Surbiton. Tel. Elmbridge 7406. [5975

J. MORT, B.Sc., M.I.E.E., offers to the trade and amateur a service of technical advice, design and construction of special test gear, receivers and other apparatus, including correction of faults in home-built apparatus.—J. Mort, BCM/HIFIDEL, W.C.1. [5752

MISCELLANEOUS

SURPLUS to requirements.

ONE Hilger HRX crystallographic X-ray unit, complete with tools and spares, output 50 kV peak, 25 mA at each of four windows.
FOCAL spot 0.6mm wide, target area opposite each window interchangeable during operations.
STANDARD TELECOMMUNICATION LABORATORIES, Ltd., Progress Way, Great Cambridge Rd., Enfield, Middlesex. [6418

WALNUT radiogram cabinets; stamp leaflets. —Cabinetware, Is., Heyes St., Blackburn.

WALNUT radiogram cabinets, stamp details. —E. Wisker, 501, Hale End Rd., Highams Park, E.4. [6436

PROC. I.R.E., July, 1945 onwards, J.I.E.E., all parts from 1943, offers; Hunt's Capacity Bridge, new, £11.—Box 7991. [6506

WALNUT radiogram and television cabinets, sample designs, few only; stamp details.—Shaw, 69, Fairlop Rd., Leytonstone, E.11. [6373

CABINETS.—Over 85 mixed T.V. and radio table models, £2 each, or reduced price for bulk purchase.—Tel. How. 1067, after 6 p.m. [6321

T.V. Console cabinets! (2-door type) for Viewmaster and other kits; send s.a.e. for illustrated leaflet to: D. Church, Esq., 14a, Harrow Rd., Wembley, Middx. [6444

METALWORK: all types cabinets, chassis, racks, etc., to your own specifications.
PHILPOTT'S METAL WORKS, Ltd. (G4BI), Chapman St., Loughborough. [6472

CABINET, 19in×10½in×10in., with handles and chassis, fitted HRO type dial, unused; £5; P.O. rack, 53in×19in., 30/-; small mains motor (converted), 7/6.—Box 8268. [6438

ENGRAVING, amateurs and trade could take the opportunity of engraving problems in the future by getting in touch with A. G. Engravings, 19a, Windmill Rd., London, S.W.18. Brass, bronze, erinoid, perspex dials; one knob or repetition equally entertained. [0034

ALLSCREWS, Ltd., for B.A. screws, nuts, washers, studding, grub-screws, bolts, soldering tags, woodscrews, etc., plain or nickel or cadmium plated, one-gross packets or large quantities; stamp for list.—270a, King St., Hammersmith, W.6. Riv. 7762. [5426

COPPER wires enamelled, tinned, Litz, cotton, silk covered, all gauges; B.A. screws, nuts, washers, soldering tags, eyelets; ebonite and laminated bakelite panels, tubes, coil formers; Tufnol rod; headphones, uexes, etc.; latest radio publications, full range available; list, s.a.e.; trade supplied.—Post Radio Supplies, 33, Bourne Gardens, London, E.4. [0138

FLUORESCENT chokes, 80w 18/6, tapped 22/6, kit of essential parts with circuit, but less 5ft 80w tube, 35/9; 80w Batten fitting less tube, £3/7/6; miniature battery chargers, these are a new idea for charging 1½v and 3v dry flashlamp cells, (will recharge a No. 800 cycle battery in 4 hours). O.K. for 2v accumulators, price 18/6; bench grinders, 2,000 rpm with 4in stone 37/6; all above items are for 200-250v a.c. mains use.—Post your order to Malden Transformer Supplies, 200-202, Cambridge Rd., Kingston-on-Thames, Surrey.

RELIABILITY & ACCURACY

PIONEERS OF LONG-SCALE ELECTRICAL MEASURING INSTRUMENTS

"RECORD" ELECTRICAL INSULATION and TESTING SETS are daily giving a wide range of service for TESTING. Their reliability and accuracy stems from the skill of the "RECORD" Technicians. Other Record Instruments are provided for a variety of purposes.

THE RECORD ELECTRICAL CO. LTD.
BROADHEATH · ALTRINCHAM · CHESHIRE
Phone : Altrincham 3221/2/3
Cables and Grams : "Circscale" Altrincham
London Office : 28 Victoria Street, London, S.W.1.
Phone : Abbey 5148
Grams : "Circscale," Sowest, London
Cables : "Circscale," London

SELENIUM, H.T. & L.T. RECTIFIERS, CHARGER KITS, CHARGERS

New Goods with Full Guarantee

S.T.C. SELENIUM RECTIFIERS, up to 300 watts. A few of our large stock, 2 v./6 v., ½ amp., **4/10**; 6 v./1 amp., **6/6**; 6 v./2 amp., **9/-**; 6 v./4 amp., **16/-**; 6 v./10 amp., **22/6**; 12/15 v./1 amp., **10/6**; 12/15 v./2 amp., **13/-**; 12/15 v./3 amp., **17/-**; 4 amp., **19/6**. Huge finned type 6 amp., **27/6**; 24 v./2 amp., **28/-**; 60 v./1.7 amp., **50/-**; Post 6d. up to 16/-, 1/2 above.

"AUTOMAT" FOOLPROOF HEAVY DUTY HOME CHARGER for car or radio cells, virtually unwreckable, 6 v./12 v./1 amp. as illus., 7lb. wt., **48/6**, post 1/6, ditto but larger model 8½lb., 2 amp., **59/6**, post 1/8; 6v./12v. 5 amp. truck or car charger 16lb. wt., **£5 19/6**, carr. 3/-. All with 12 months' guarantee. **CHARGER KITS:** foolproof and easy to make kits, 2 amp. kit for 2 v., 6 v., 12 v. transformer 45 watt, 2 amp. rect., ballast bulb, **38/6**, post 1/4. Ditto with handsome case, as illus., **52/-**. As above but 1 amp. kit, **32/-**, or with case, **44/-**, post 1/4. 6 v. 2 amp. kit, trans., rect., ballast bulb, **22/-**. Ditto 1 amp., **27/-**. Larger kit, 12 v. 4 amp. S.T.C. rect., 70 watts trans., ballast bulb, for 2 v., 6 v., 12 v. charger, **52/6**; or W'house 12 v. 3 amp. rect., 55 watt trans., ballast bulb for 2 v., 6 v., 12 v., **47/-**, post 1/6.

TRICKLE CHARGER KIT, 2 v. 0.5 amp., rect., 6 watt trans layer wound for 2 v. charger, **12/6**, post 8d.

HEAVY DUTY KITS, S.T.C. 12/15 v. 4 amp. rect., 100 watt trans, worm drive slider res., ammeter, for 6 v./12 v. charger, **75/-**, wt. 16lb. Post 2 p'cls., **3/-**. Ditto but with 6 amp. giant finned rect. and 120 watt trans., **87/-**. For radio cell charging, 18 v. 4 amp. rect., 120 watt trans., 8 ohm slider res., ammeter will charge up to 18 cells at 2 amps., **95/-** carr. 3/-.

ELIMINATOR KIT, for 120 v. 20/30 mA elim., with trickle charge, 22 watt trans. layer wnd., selenium h.t. and trickle rects., 2 × 8 mfd. condensers, handsome steel case, **43/-**, post 1/2.

SMALL SPACE H.T. RECTS., for A.C./D.C. sets 250 v. 60 mA. new, wrapped in maker's wrappings, **7/-**. 250 v. 100 mA bridge, **12/-**, 110 v. 60 mA for U.S. midgets, **6/6**, 350-0-350 v. 80 mA, **13/6**, post 6d. on all.

"RENEWBAT" battery desulphator and conditioner, **1/9**, post 4d.

CHAMPION PRODUCTS
43 Uplands Way, London, N.21. Phone LAB 4467

SUCCESSFUL SALES! SATISFIED CUSTOMERS!

PENNINE RADIO

THE ALL SEASON SENSATION. ACCLAIMED THE COUNTRY OVER. THE INTIMATE RECEIVER WHICH COMBINES APPEARANCE AND PERFORMANCE. HOUSED IN A BEAUTIFUL WALNUT CABINET. EACH SET FULLY GUARANTEED.

HEIGHT 18", WIDTH 12½", DEPTH 5½"
4 Valve SUPERHET

THE SET THAT SELLS ITSELF! UNBEATABLE VALUE £11 9 7 INC. TAX.

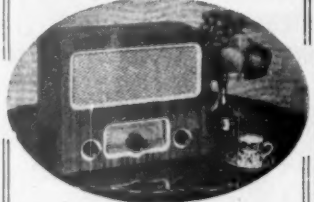

"THE ROVER"

SUPPLIED ONLY THROUGH SELECTED WHOLESALERS. ILLUSTRATED LEAFLETS AND ATTRACTIVE DISPLAY CARDS.

PENNINE AMPLIFIERS

ELLAND YORKS ENGLAND

TEL. ELLAND 2107

. . . Sincerely appreciated is your letter of 29th Nov. 1950, relative to the use of p.p. 6146's with a Savage 2B36B. It is indeed seldom that such thoughtful information is received from a manufacturing firm. . . . Again, in closing, may I express sincere thanks for your thoughtful attention.

H.D.T., U.S.A.

SAVAGE TRANSFORMERS LTD.
Nursteed Road · Devizes · Wilts
Tel: Devizes 536

15-INCH Emiscope cathode ray tube for sale. 12 hours' use: complete with deflector and focus coils, line output transformer, white mask; all as new; would separate; offers.—Beckett, 7, Whitehouse Rd., Ipswich. [6374

SITUATIONS VACANT

ASSISTANT Editor.

EXPERIENCE of radio journalism, preferably in professional capacity; active radio amateur, sound, not highly specialised, technical knowledge; commencing salary up to £450 according to age and experience.—Box 8286. [6474

E.M.I. INSTITUTES.

PRINCIPAL: Professor H. F. Trewman, M.A. (Cantab), M.I.E.E., M.I.Mech.E., M.Brit.I.R.E. THE introduction of our four-year course has created vacancies for lecturers in electronic and telecommunications engineering; applicants for these posts should be graduates in physics or electrical engineering and should possess industrial experience, with preferably some instructional experience; applicants should be between 23 and 30 years of age; the commencing salary depends on qualifications and experience and will be in the range of £510–£730 per annum.—Applications, stating age, qualifications and experience, with the names and addresses of two persons to whom reference may be made, should be sent to The Principal, E.M.I. Institutes, Ltd., 10, Pembridge Sq., London, W.2. [6391

CROWN Agents for the Colonies.

RADIO Officer required by the East Africa High Commission for the Directorate of Civil Aviation for one tour of 48 months in the first instance; commencing salary according to age and experience in scale £550 rising to £715 a year; gratuity of 13½ per cent of total salary received is payable on satisfactory termination of contract; outfit allowance £50; free passages; candidates, under 40, should hold a First Class Air Operator's Licence and have had not less than 1,000 hours flying experience on civil aircraft; they should have had considerable experience in the operation of medium and high frequency radio stations; experience in the operation of modern radio and/or radar navigational aids, and the day to day maintenance of modern radio equipment, and experience as a Signals Officer in Civil Aviation or the Services, would be an advantage.—Apply at once by letter, stating age, full names in block letters, and full particulars of qualifications and experience, and mentioning this paper to the Crown Agents for the Colonies, 4, Millbank, London, S.W.1, quoting M.25107/B. on both letter and envelope. The Crown Agents cannot undertake to acknowledge all applications and will communicate only with applicants selected for further consideration. [6502

DEPARTMENTAL Examiners (Electronics) MINISTRY OF SUPPLY.

VACANCIES exist in the Greater London Area for men with skilled experience in radio, radar, VF and carrier telecommunication, electronic test gear, etc., either in the services or in industry; applicants must be of British nationality and must be prepared to travel throughout the United Kingdom in the course of their duties, employment is conditional upon satisfactory references and the passing of a medical examination.

THE starting rate of pay for a 44-hour, five-day week will be 122/- with a further increase after satisfactory completion of a three months' probationary period; in addition an examination bonus of 25/6 is payable during employment in the grade; further particulars supplied on application.

ALL applications should be made in writing to, the Ministry of Supply, Chief Inspector, Electrical & Mechanical Equipment, c/o Registry, Ivy Bridge House, John Adam St., W.C.2. [6464

WOOLWICH POLYTECHNIC, London, S.E.18.

THE Governing Body invite applications for the appointment of Lecturer in the Department of Physics and Telecommunications to teach chiefly electrical subjects to the standard of the Intermediate B.Sc. examination and the Higher National Certificate in Telecommunications. Candidates will be preferred who have a degree in physics and a knowledge of some branch of Telecommunications, but a candidate with a suitable degree in electrical engineering will be considered.

BURNHAM Technical Scale salary: Lecturer: £500–£15–£555 plus London allowance of £56–£48, plus the following where applicable (i) graduate allowance £50 above minimum and maximum; (ii) First Class Honours Degree—£15 above minimum and £30 above maximum; (iii) training allowance £15 for each year, up to three, for full-time study or training beyond two years—above minimum and maximum; (iv) increments for industrial experience up to 12 years above minimum; (v) increments for full-time teaching experience. It is anticipated that these Scales will be revised as from 1st April, 1951. Full particulars of the post and application forms may be obtained from the Clerk to the Governors, to whom they should be returned within two weeks of the date of this advertisement. [6523

BRITISH TELECOMMUNICATIONS RESEARCH, Ltd., have vacancies for design draughtsmen with experience on radio or communication equipment; applicants must have a good production background and be conversant with all phases of design and manufacture; these posts offer excellent opportunities in an expanding branch of a well-established organisation; salary in accordance with qualifications and experience; write to—The Chief Draughtsman, Taplow Court, Taplow, Bucks. [6490

SURPLUS BARGAINS

MANUFACTURERS' & BANKRUPT STOCKS
LIMITED SUPPLIES ONLY

We can offer for immediate delivery

Resistors: ¼, ½, 1, 1, 2 and 3 watt. ALL VALUES

16 foot sectional aerial in Canvas carrying bag.

Brand New Accumulators 6 v. 85 a. Size: 12 x 9 x 7in. Weight 45 lb. British Made.

Receivers: R1155, 1355 and 184 Brand New in original cases. Dinghy Radio Transmitter SCR 578.

EX-W.D.

AERIAL CAN ALSO BE USED AS A FISHING ROD

12ft. Steel Aerials (3 sections of 4ft.) packed in solid 4ft. cylindrical container.

MAKES IDEAL FISHING RODS

Charging Control Boards with Auto. cut out, 3 amp. 230 v.

2 Volt Accumulators, suitable for Radio or Model Driving, House Lighting, etc. Heavy Mass Type Plates. Pre-charged. Only need filling. Size: 7in. x 2in. x 2in.

Storage Secondary Portable Canadian Hart Batteries, 6 v. 100/125 amp.

Magnifying Lens, Rubber Masks, Burgoyne Solder Guns, Bakelite Accumulators, Ex-Govt. S.W. Condensers, All types. Meters, Switches, Toggle and Yaxley, Headphones, L/R and H/R Vibrators, 6 and 12 v. Speakers all types. Volume Controls. Output Transformers. Chokes. Crystals—Valves Type CV.101

Your enquiries are invited

WHOLESALE AND EXPORT ONLY

For further bargains call at our Counter or write for 12-page Bulletin.

RADIO MERCHANDISE CO. LTD.

65, Farringdon Road, London, E.C.1.

Telephone: HOLborn 6377.

"You can rely on us"

FOR CLEAN COMPONENTS AT COMPETITIVE PRICES

IMMEDIATE DISPATCH

MIDGET COIL-PACKS

These are an ideal miniature Coil-Pack especially suited where space is limited. They consist of iron-cored miniature coils for both Aerial and Oscillator stages, built-in Wavechange switch and midget trimmers. They are intended for an I.F. of 465 Kc/s, and I.F. Transformers type RS/GB 465 (12/6d. per pair) are the ideal companions for a trouble-free superhet.

TYPE "R"
MW/LW/GRAM. Ranges: 200-550 metres, 800-2,000 metres.
SIZE: Length 2½in. Width 1¾in. Depth 1¾in.

TYPE "S"
MW/SW/GRAM. Ranges: 200-250 metres, 17-50 metres.
SIZE: As Type "R."

TYPE "C"
LW/MW/SW. Ranges: 800-2,000 metres, 200-250 metres, 17-50 metres.
SIZE: Length 3½in. Width 1¾in. Depth 1¾in.

TYPE "R" and "S" each 25/-. TYPE "C" each 28/6. Post 6d.

All coils enclosed—all iron-dust cores adjustable. Completely wired, only five connections needed to external circuit.

Catalogue with Data, 3d.

RADIO SERVICING Co.

444, Wandsworth Road, London, S.W.8

'Phone: MACaulay 4155.

77, 77A, Bus: 28, Tram. Wandsworth Rd. S.R. Station
Open till 6.30 p.m.

NO REGRETS

if you make

HOLLEY'S RADIO STORES,

285, CAMBERWELL ROAD, S.E.5.

Your first call when purchasing new High Fidelity Equipment.

Side by side Demonstrations of

NEW ACOUSTICAL Q.U.A.D. RADIO TUNER AND AMPLIFIER
CHARLES R.C. TUNING UNIT AND K5I HIGH FIDELITY AMPLIFIER
LEAK TI2 AMPLIFIER, R.C. PAU PRE-AMP and SUPERHET RADIO TUNER
WILLIAMSON AMPLIFIER AND TUNER BY GOODSELL
SOUND SALES A-Z AMPLIFIER AND DX PLUS RADIO TUNERS
ARMSTRONG ALL WAVE CHASSIS
FELICITY L.P. JUNIOR AMPLIFIER AND TUNER

Recommended SPEAKERS
TANNOY "DUAL CONCENTRIC"
WHARFEDALE CORNER DUAL
BARKER 148a and 150 UNITS
GOODMANS AXIOM 150 AND AUDIOM 60
DECCA CORNER SPEAKER AND LONG PLAYING RECORD EQUIPMENT
TWO-SPEED MOTORS AND L.P PICK-UPS
RADIOGRAM AND CORNER SPEAKER CABINETS

Open all day Saturday.
'Phone: RODney 4988

INTERNATIONAL AERADIO, Ltd.

INTERNATIONAL AERADIO, Ltd., require radio mechanic, ground duties overseas; single candidates preferred; experience installation, maintenance airfield equipment; minimum inclusive emoluments approximately £500; free quarters, passages; low tax; pensions fund.—Write Personnel Officer, 40, Park St., W.1. [6428

ELECTRONIC Development Engineers. Vacancies exist for:
(1) SENIOR DEVELOPMENT ENGINEER to be responsible, under Technical Director, for the development and design of a wide range of C.R.O. and associated electronic equipment. Applicants must have an Hons. Degree in Physics or Electrical Engineering (Telecommunications) and some industrial experience, first-class opportunity for a man with original ideas and a keen interest in the subject.
(2) DEVELOPMENT ENGINEER for work on interesting development projects; a degree in Physics or Electrical Engineering is essential and some industrial or research experience desirable; salaries according to age and qualifications.—Apply with full details to Southern Instruments, Ltd., Fernhill, Hawley, Camberley, Surrey. [6478

SKILLED tradesmen are wanted as armament artificer staff sergeants in R.E.M.E.
QUALIFICATIONS: (i) Full apprenticeship as electrical fitter, radio technician, instrument maker or motor fitter; or (ii) full apprenticeship with a knowledge of motor vehicles, as fitter, toolmaker or machinist; (iii) between 20 and 35 years of age. With these qualifications you can be appointed acting sergeant in R.E.M.E. after a short period of military training (6 weeks or less if you have previous military service). Promotion to staff sergeant automatically follows a technical course on the latest types of Army equipments of approximately eighteen months' duration. Pay after 26 weeks initial military training, 18s a day, after 18 months' technical training, 21s 6d a day. Staff Sergeants, R.E.M.E., are eligible for promotion to warrant officer Class 1 and commissioned rank as electrical and mechanical assistant engineers. Marriage allowance of 49s to 52s 6d a week. Rations and clothing are free. Men engaged for 12 years which may be extended. After 22 years an armament artificer is eligible for pension. Full particulars from any Army Recruiting Office or write to War Office (AG21), London, S.W.1. [6504

DESIGN project engineer, for electronic development, salary £400—£500 p.a.
CHARGE-HAND, to control section engaged on light engineering assembly and wiring, salary £7/10—£8 p.w
ALL-POWER TRANSFORMERS, Ltd., Chertsey Rd., Byfleet, Surrey. [6493

RADIO testers and fault finders required.—Write or apply Dulci Co., Ltd., 97-99, Villiers Rd., N.W.2. [6510

WANTED, radio television engineer; state qualifications, experience, and wage required; for Preston, Lancashire.—Box 8271.

VACANCIES exist for production inspectors at various Admiralty Establishments and in shipbuilding and industrial centres in various parts of the country.
THE duties involve work in connection with the manufacture, inspection, test and installation of a wide variety of mechanical and electrical equipment for H.M. Ships; for certain of the posts experience of electronics, including radar, apparatus will be advantageous.
CANDIDATES, who must be at least 25, should have served a recognized engineering apprenticeship or have had equivalent training, followed by at least three years' relevant experience in industry or Government Service; they should preferably be in possession of Higher National Certificate or equivalent, a lower qualification such as Ordinary National Certificate might, however, be considered.
APPOINTMENTS will be unestablished, but there may be opportunities at a later date of competing for permanent posts; the salary scale is £500 by £20 to £625 per annum and entry will be at the minimum, subject to a deduction of £20 for each year by which the age of entry falls short of 30; rates outside London are a little lower.
WRITE quoting D33/51-A to the Ministry of Labour and National Service, Technical and Scientific Register, (E) York House, Kingsway, London, W.C.2, for application form which must be returned completed by 15th March, 1951. [6496

A RADIO and television engineer required for Lancaster and Morecambe area, able to drive.—Reply, giving full details of previous experience, to Box 8266. [6426

RADIO Mechanic wanted for development of industrial electronic equipment; Teddington area; write, stating experience and salary required to—Box 7992. [6387

EXPERIENCED (radio and television) manager, engineers, storekeeper, and despatch clerk wanted.—The Radio Centre, 33, Tottenham Crt. Rd., London, W.1. [6447

TELEVISION engineer, competent, part- or full-time, highest rates, excellent prospects, congenial.—Hendon.—Harris, 40, Cresp'gny Rd., N.W.4. [6466

EXPERIENCED Radio Storekeeper required for employment in Acton; write or call.—V.E.S. Wholesale Services, Ltd., 11, Gunnersbury Lane, Acton, W.3. [6487

RADIO Service Engineer required in West London district; sound theory, 7 years' commercial experience; write, stating age with full details of experience to—Box 8272. [6449

TELEVISION Service Representative required for London area, preferably with own car; must be experienced in television service technique; good salary and car allowance.—Box 8290. [6483

A REMARKABLE ACHIEVEMENT IN FILTER DESIGN

Pat. Applied For

E.M.G. STEEP-CUTTING INFINITELY VARIABLE FILTER

- Cuts at any selected frequency between 4,000 and 8,000 c.p.s.
- Average steepness of cut 30 db. per octave.
- Connects between secondary of output transformer and speaker (15 ohms. rated impedance).
- Specially valuable for use with new microgroove records.
- Greatly reduces needle-hiss on ordinary records with minimum high note loss, and suppresses high pitched interferences on radio.
- No distortion, and no appreciable loss of volume.
- Leaflet available from the manufacturers.
- *Novel circuit, patents pending.*

£4 - 10 - 0

Trade Enquiries invited

E.M.G. HANDMADE GRAMOPHONES, LTD.
6 Newman St., Oxford St., W.1.
Telephone: Museum 9971-2-3.

SQUARE-WAVE GENERATORS

Driven by any A.F. Oscillator. Rise time less than one micro-second. Extremely wide frequency range. A high grade instrument for laboratory use.

Full details on request.

DUN ELECTRONICS,
Riley Works, Riley Street, Chelsea, S.W.10.
Telephone: FLA 3217.

SPENCER WEST

Descriptive leaflets are available on request for Television Pre-Amplifiers, Electronic LOFT aerials, etc. The Type AC/3 Pre-Amplifier employing two triode valves is guaranteed to improve Long Distance Television reception. Price **10 gns.** complete.

The new type AC7 Converter unit (illustrated here) permits a London type receiver to receive Sutton Coldfield. No alterations of any sort are required. Price **£9/18/6** complete.

SPENCER WEST
QUAY WORKS, Gt. YARMOUTH

OPPORTUNITIES IN RADIO

Get this FREE Book!
'ENGINEERING OPPORTUNITIES'
reveals how you can become technically-qualified at home for a highly-paid key-appointment in the vast Radio and Television Industry. In 176 pages of intensely interesting matter, it includes full details of our up-to-the-minute home study courses in all branches of **TELEVISION and RADIO, A.M. Brit. I.R.E., City & Guilds, Special Television, Servicing, Sound Film Projection, Short Wave, High Frequency, and General Wireless Courses.**
We definitely **Guarantee**
"NO PASS—NO FEE"
If you're earning less than £10 a week, this enlightening book is for you. Write for your copy today. It will be sent **FREE** and without obligation.

BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY
388b SHAKESPEARE HOUSE
17/19 STRATFORD PLACE, LONDON, W1
BIET

THIS IS
REOSOUND
REG. TRADE MARK

AMPLIFIER CHASSIS AND COVERS

SIZE A.
Chassis in 18 Gauge Steel 17 x 12 x 2½in. fitted with base plate having rubber feet and cover in 20 Gauge Steel with radiused top corners giving 7in. clearance above chassis : louvred back and front, complete with two Handles..... £3 5 0

SIZE B.
Chassis 17 x 10 x 2½in. as above, with one Handle £2 17 6

SIZE C.
Chassis 14 x 9 x 2½in. as above, with one Handle £2 12 6

STANDARD FINISHES : Black, Grey or Brown Wrinkle Enamel.

CARRIAGE : Paid on Orders Over £5.

ILLUSTRATED LISTS AND TRADE TERMS ON APPLICATION

REOSOUND ENGINEERING & ELECTRICAL COMPANY, "Reosound Works," Coleshill Road, Sutton Coldfield.
Tel. : SUT. 4053. Grams : Reosound, Sutton Coldfield

RADIO and Television Engineer required to take charge Service Dept., able to drive; retail, N.E. London area; excellent salary and prospects, carte blanche.—Write Box 8293. [6489

TELEVISION and radio engineer required for service dept., able to drive van; perm. position with good working conditions; salary £500 per annum.—Apply Harris's, Owen St., Tipton.

ELECTRICAL engineer/physicist with practical experience in electronic circuits required for laboratory in Oxford; initial salary £450 to £525 p.a. according to qualifications.—Box 8280. [6461

RADIO and television engineers required by well-known Sutton, Surrey, dealers; competent and experienced men essential.—Write stating previous experience and salary required to Box 8261. [6462

SALES technician required, must have good knowledge of radio components and valves; permanent job with good prospects. Write in first instance stating experience and salary required to:—
ELECTRONIC PRECISION EQUIPMENT, 46, Windmill Hill, Ruislip, Middx. [6507

RADIO service engineer required for public address equipment, knowledge of signal clocks and time recorders desirable.—Apply in writing to Genaigh, Ltd., 73, Great Peter St., London, S.W.1. [6495

SOBELL INDUSTRIES, Ltd., require experienced television engineers in and around London, North of Thames; pay and prospects extremely good.—Tel. Supervisor, Valentine 8766 (evenings) for particulars. [6409

RADAR engineers required by London firm specializing in marine radar; applicants should be ex-Army staff sergeants or Navy P.O. grades with experience Service radar and passed long radar course.—Apply Box 7999. [6424

ELECTRONIC engineer with physics or engineering degree capable of lecturing semi-technical and technical students on theory and practice of radar required by large light engineering company, East London district.
APPLICATIONS in writing giving details of age and qualifications to Box 7997. [6406

BOYD, Ltd., require radio/television engineers for their London and Provincial branches; excellent prospects and salary.—Apply in first instance to Service Supervisor, 101, King St., Hammersmith, W.6. Tel. Riverside 4491. [6401

RADIO and television engineer required immediately, must be fully experienced (R.T.R.A. standard); highest wages paid but efficiency is essential.—Matt Radio Service, 29, Castle St., Kingston-on-Thames, Surrey. Tel. Kingston 8353. [6512

RADIO service engineer reqd. by old-estab. dealer, seaside town; varied work, opportunity for initiative and experiment; test gear of lab. standard; perm. job, good salary, with tuition to high standard if desired.—Gerry 56, Bank St., Newquay. [6396

ELECTRICAL and mechanical engineers, preferably graduates, urgently required on electronics development for factory near Manchester, 5-day week, good conditions, attractive salaries to suitably qualified persons; full particulars to—Box 8341. [6516

SUPERINTENDENT Television Engineer required to take charge of a department responsible for the installation and maintenance of television receivers in Nottingham; some experimental work also required; progressive post with scope for advancement.—Box 8289. [6482

SENIOR draughtsmen required in radio and television drawing office of large company; applicants should have practical experience and several years in radio or some allied drawing office.—Kindly state full details of experience, with age and salary required, to Box 8312. [6505

RADIO mechanic required, West London, for assembly, fitting, and wiring variety of high-grade electronic equipment, small batch production; progressive opening for reliable, adaptable type with some technical knowledge; state age, details experience, and salary required.—Box 8269. [6439

CINE-SALES assistant, 20-25, must have knowledge of sub-standard, sound and silent projectors, cameras, amplifiers, etc., able to drive; good prospects for keen, conscientious applicant.—Write, stating full particulars, to John King, 7-9, Glentworth St., Baker St., N.W.1. [6427

MARCONI'S WIRELESS TELEGRAPH Co., Ltd., invite applications from persons interested in joining teams which will spend a considerable time in various parts of the world carrying out wave propagation experiments leading to the selection of sites for the erection of wireless stations.
PREFERABLY applicants should possess a university degree, but consideration will be given to those possessing other qualifications. Selected applicants will be trained under expert guidance in this country before taking up duties, and will be employed in the laboratory during intervals of home service. In addition to normal home pay, successful applicants will receive an overseas allowance and liberal expenses whilst abroad. The company operates a staff pension scheme.—Apply, quoting ref. 833, to Central Personnel Services, English Electric Co., Ltd., 24-30, Gillingham St., London, S.W.1. [6357

DRAUGHTSMEN required to assist designers; capable of producing detail drawings from layouts and sketches to standards suitable for quantity production of radio and radar equipment.—Apply, giving full details, to Personnel Department, Murphy Radio, Ltd., Welwyn Garden City. [6521

A NUMBER of senior and junior vacancies for radio, radar, electronic, television, etc., development, service engineers, draughtsmen, wiremen, testers, inspectors, etc., urgently required 30 television service engineers.—Write in confidence, Technical Employment Agency, 179, Clapham Rd., S.W.9. (Brixton 3487.) [0105

SUPACOILS

OFFER

THE LATEST EDITION OF THE

HOME CONSTRUCTOR'S HANDBOOK

No keen radio enthusiast should be without this invaluable booklet which is of equal use to beginner, amateur or professional radio engineer. It contains, among other things :
- Circuits of Feeder units, Superhet receivers, Test equipment, Amplifiers and power packs, etc.
- Pages of servicing and constructional information which will assist you in YOUR radio problem.
- Complete resistance colour code.
- A considerable amount of invaluable general Radio information.
- A comprehensive catalogue.
- Above all it is profusely illustrated with half tone blocks and costs 1/6 only or a copy will be given **FREE** with every order for £1 or more.

We also offer the following selection from our stocks of quality components :
- **COILS.** A complete series of High Q variable iron dust cored coils (as recommended for the P.W. 9 valver) in wavelengths 10-30, 16-50, 30-75, 75-200, 190-550 and 800-2000 metres ; Aerial, H.F. or Oscillator at the remarkable price of 3/- each.
- **MODEL 30** famous 3 waveband superhet Coil Packs, aligned, 40/11 inc. full connection details and instructions given with every pack.
- **MODEL 40** Coil Packs—similar, with R.F. stage, aligned, 70/3 inc.
- **MODEL 30 TUNING UNIT** consisting of 30 Coil Pack, pair of I.F. Transformers, matched 2-gang and attractive Dial. Components aligned together as a unit and sealed. 49/9 inc.
- **MODEL 40 TUNING UNIT,** similar with R.F. stage ..... 99/6 inc.
- **CHASSIS.** Good quality aluminium chassis in stock for 5 v. Rec. 11/- ; 6 v. Rec. 12/-. Amplifiers and Feeder Units, etc., from 7/-
- **J.B. SLS SPIN WHEEL** Tuning Assembly to suit Coil Packs and Chassis above ..... 25/- each
- **COIL GROUPS.** The very popular Coil Group A 26/9
  Coil Group B..... 40/9
- **MM I.F. TRANSFORMERS.** These renowned permeability tuned, high stability, high gain I.F. Transformers (already aligned to 465 Kc/s). available at..... 15/- pair

SUPACOILS MAIL ORDER OFFICE
98, Greenway Ave., London, E.17

AMPLIFIERS *Quality* **KIT** *for* **HOME CONSTRUCTORS**

A complete set of components to construct a 10 watt amplifier including Woden potted mains transformer. 5 valves. 10 in. speaker with transformer. Components of the highest quality. No Govt. surplus. Three switched inputs, negative feed back, push-pull output, tone control, steel chassis. Suitable home or small hall. *CASH WITH ORDER.*

Price Complete to the last screw
£8 0 0
(Subject)

BEETHOVEN LTD
ELECTRIC EQUIPMENT
Chapel Lane, Sands, High Wycombe Tel: 1152/3

THE "FLUXITE QUINS" AT WORK

"Our T.V. is now good as new,
Every wire in its place, good and true.
All fixed with FLUXITE
Now an aerial this height
will stop chimneys blocking the view!"

See that **FLUXITE** is always by you—in the house — garage — workshop — wherever speedy soldering is needed. Used for over 40 years in Government works and by leading engineers and manufacturers. Of all ironmongers—in tins, from 1/- upwards.

TO CYCLISTS! For stronger wheels that will remain round and true, here's a time tested tip. Tie the spokes where they cross with fine wire AND SOLDER. It's simple — with FLUXITE — but IMPORTANT.

The **FLUXITE GUN** puts **FLUXITE** where you want it by a simple pressure. Price 2/6, or filled, 3/6.

FLUXITE

SIMPLIFIES *ALL* SOLDERING

Write for Book on the Art of "SOFT" Soldering and for Leaflet on CASE-HARDENING STEEL and TEMPERING TOOLS with FLUXITE. Price 1d each

FLUXITE LTD. (Dept. WW), BERMONDSEY STREET, LONDON, S.E.1.

TELEVISION COMPONENTS

FOR THE

VIEWMASTER, "P.W." & "E.E." TELEVISORS IN STOCK

Price Lists of specified and alternative components for "P.W." and "E.E." TV. available.

J. T. FILMER MAYPOLE ESTATE, BEXLEY, KENT. Tel.: Bexleyheath 7267

SAMSONS SURPLUS STORES

R.1132 RECEIVERS. 100-126 Mc/s., complete with 11 valves, aluminium grey cabinet 19in. x 11in. x 10in. As new. £4/10/-, carriage 4/-.

FILAMENT TRANSFORMERS. Pri. 220-240 v. 50 cy. Secondary, 6.3 v. 15 amps. Brand new. 17/6, post 1/6.

MASTER VOLTMETERS. 0-20 volts, made by Metrovick, 6in. mirrored scale, moving iron 50 cy. Brand new. 22/6, post 1/-.

RECORD BOND TESTERS. 0-1 ohms, operates on a Nife cell. Brand new. 17/6, post 1/-.

V.C.R. 97 CATHODE TUBES. Brand new in maker's cases. 35/-, carriage 3/6.

NIFE BATTERIES. 1.4 v. Dim 6in. x 3in. x 1in. 10 A.H. 7/6, post 9d.

36FT. AERIAL MASTS. Ex-R.A.F. "Type 50." Complete kit consists of 9 tubular length 4ft., dia. 2in., set of pickets, top plate guys and complete fittings. Brand new in canvas hold-all carrying case. £6/10/-, carriage 7/6.

BRAND NEW WALKIE TALKIES. 5-valve Trans-receivers No. 38, freq. range 7.4, 9 Mc/s. Complete with phones, throat mike, set of aerial rods and comprehensive instructions. Guaranteed in working order. £4/19/6, carriage 7/6. Set less accessories, £4, carr. 1/-.

169/171 Edgware Road, London, W.2. Pad. 7851
125 Tottenham Court Rd., W.1. Eus. 4982

All orders and enquiries to our Edgware Road branch, please.

BOYD, Limited, require radio/television salesmen to train as prospective managers for their expanding organization; applicants must be of smart appearance, possess drive and initiative; excellent prospects.—Apply Mr. D. C. Samphier, Boyd, Limited, 33, New Bond St., London, W.1. 'Phone for appointment: Mayfair 7831. [6511

RADIO and television development engineers required by large company in East London area; applicants should have technical qualifications and several years' laboratory experience or radio development work; permanent positions with good prospects.—Kindly state full details of qualifications and experience with age and salary required to Box 8000. [6425

EX-R.E.M.E. officer or mechanical engineer with organizing ability required to assist in the organizing of light engineering constructional work, and supervise field trials of a novel device.—Apply, giving full details, and mentioning Ref. 467, to Central Personnel Services, English Electric Co., Ltd., 24-30, Gillingham St., London, S.W.1. [6416

RADIO engineer required for test instrument laboratory, with experience of design and manufacture of test apparatus; one without experience but having good qualifications and an interest in the subject would be considered.—Write giving full particulars, age and salary required, to Personnel Dept., Murphy Radio, Ltd., Welwyn Garden City. [6499

RADIO mechanics; British European Airways require skilled men, preferably with aircraft experience, for existing and possible future vacancies. Radar knowledge an advantage. Basic pay 2/7 per hour. Bonus schemes in operation, sick pay and pension schemes.—Write to Personnel Officer, Northolt Base, B.E.A., Ruislip, Middlesex. [6326

MATHEMATICIANS experienced in electromagnetic theory and statistics are required by Marconi's Wireless Telegraph Co., Ltd., Chelmsford, for radio research in propagation and communication theory.—Please apply giving full details and quoting Ref. 849 to Central Personnel Services, English Electric Co., Ltd., 24-30, Gillingham St., London, S.W.1. [6453

TELEVISION. Applications are invited for position as works manager of new factory opening shortly in Scotland for production of television receivers. Only those who have held similar positions, or positions as assistant works manager with established manufacturers need apply. Must be able to organise production and be fully aware of the latest technical developments.
COMMENCING salary £1,500 p.a. with house provided.—Apply in confidence, stating age and full details of past experience and present position, to Box 8279. [6460

RADIO engineer required for factory laboratory with experience of technical problems associated with the manufacture of radio and television receivers; an engineer with some design experience wishing to apply his knowledge in the factory would be considered.—Write giving full particulars, age and salary required, to Personnel Department, Murphy Radio, Ltd., Welwyn Garden City. [6498

E.M.I. ENGINEERING DEVELOPMENT, Ltd., have a number of vacancies for engineers and senior engineers on interesting development work in various electronic engineering projects; the posts are for permanent pensionable staff and offer good prospects; qualifications: a degree in physics or engineering or equivalent, together with several years' experience or specialised experience in the following fields:—
(a) L.F. equipment.
(b) TELEVISION equipment.
(c) MICROWAVE techniques.
(d) PULSE techniques.
(e) SERVO mechanisms.
(f) TEST gear design.
(g) INSPECTION.
APPLICANTS should write, giving full details of experience and type of work required, and quote ED/55, to Personnel Department, E.M.I. Engineering Development, Ltd., Blyth Rd., Hayes, Middlesex. [6394

TECHNICAL writers (female) required to prepare and edit reports and handbooks for publication; qualifications: a good general training in electronics with practical experience of electronic equipment desirable; marked critical faculty and ability to write clear English.—Applicants should write, giving full details and quoting ED/19, to Personnel Department, E.M.I. Ltd., Blyth Rd., Hayes, Middx. [6390

REQUIRED by the British Telecommunications Research, Ltd., at their research and development laboratories in Bucks, several senior radio communication engineers for project work in the V.H.F. and U.H.F. fields; salary range £400 to £800 p.a.; application forms available from the Senior Radio Engineer, B.T.R., Ltd., Taplow Court, Taplow, Bucks. Suitable applicants will be invited for interview. [6386

A works manager is required by a Midland firm producing electrical resistors, switches and other small parts for the communications industry; experience of light assembly work, machine shop practice and plastic moulding is essential, together with ability in production planning and stock control; salary according to qualifications.—Painton & Co., Ltd., Kingsthorpe, Northampton. [6468

WANTED, an engineer to take charge of the design and production of sound reproduction equipment, microphones, audi-frequency amplifying equipment and complete public address systems in an Australian factory; applicants should possess the usual engineering qualifications, and previous experience in both design and production of sound equipment is essential; commercial experience also an advantage; salary A£1,250.—Reply to Box 7998. [6407

THE HOUSE FOR QUICK DELIVERY

The following Goods Ex Stock.

Cash with Order, or C.O.D.

ADVANCE Signal Generator ...	£23 10 0
AVO Meter Model 7	£19 10 0
WHARFEDALE—	
W.15/CS 15in.....	£12 0 0
W.12/CS 12in.....	£7 10 0
Golden 10in.	£4 0 0
Super 8	£3 10 0
COLLARO Single Record Player complete with Pick-up.....	£5 18 2
PLESSEY Single Record Player...	£6 16 2
CHARLES Concert Master.....	£29 10 0
LEAK TL/12 Watt Triple Loop Feedback Amplifier	£25 15 0
LEAK RC/PA/U Pre-Amplifier.....	£8 15 0
GARRARD "S" Unit in Metal Carrier Container Complete with Plugs, Connection, etc.	£9 15 0
MARCONIPHONE Model 14 Light Light Weight Pick-Up Incl. P. Tax	£2 11 8

Please Note : *These prices are subject to any increases by the makers due to rise in costs*

A. ERNEST BUCHAN, (M.O. Dept.), 28, BELMONT STREET, ABERDEEN

Phone 23570

RADIO G220 OFFERS

MAGNETOSTRICTION Echometers type 446A by Marconi. 24 v. D.C. Maximum sounding depth 180' Very suitable for yachts, survey vessels, coastal vessels, etc. The complete equipment, **£75.** *RT-3A/ARN-1. Complete with all valves 50/-

Trade and overseas enquiries invited.

ARTHUR HOILE *'Phone : 2812*
55, UNION ST., MAIDSTONE, KENT

B. & H. RADIO

EAST STREET, DARLINGTON

BASS & TREBLE SEPARATOR
Divides output to Bass and Treble speakers. Permits adjustment of treble relative to bass and allows speakers of different impedances to be matched together. Kit of Parts £1 9 6

SCRATCH FILTER
Gives marked reduction of scratch level and cleans treble without serious attenuation 15 0

VARIABLE SELECTIVITY I.F. TRANSFORMERS. 465 K/cs. Give 3 degrees of selectivity. Per pair £1 0 0

WHISTLE FILTER
Is very simply inserted in the speaker wiring and gives a very sharp narrow cut which completely eliminates 9 K/cs whistle £1 13 6

SIGNAL GENERATOR
A complete portable signal source operating from a 4.5 volt battery £2 10 0

COILS : I.F. Transformers, Oscillator Coils etc. Rewound and returned C.O.D. Also Coils made to specification for Radio or Audio Frequencies. All Goods Guaranteed satisfactory or money refunded.

THE
BRITISH NATIONAL
RADIO SCHOOL
ESTD. 1940

NOW IN OUR ELEVENTH YEAR AND STILL

NO B.N.R.S. STUDENT HAS EVER FAILED

to pass his examination(s) after completing our appropriate study course!

NOTHING SUCCEEDS LIKE SUCCESS

and what we have done a thousand times already, for others, we can do again, for YOU!

A.M.Brit.I.R.E. and CITY and GUILDS Radio and Telecommunications Exams., etc., etc.

Six months' trial period without obligation to continue.

Please mention this advt. and send for free booklet and sample lesson to:—

STUDIES DIRECTOR
BRITISH NATIONAL RADIO SCHOOL
66, ADDISCOMBE ROAD, CROYDON
Phone: Addiscombe 3341

Some Bargains for YOU

METERS. Portable Test Set fitted 2½in. flush meter D.C. moving coil reading Volts: 1.5, 3, 150. Milli-amps: 6 and 60, Ohms 25,000; knife edge needle zero adjuster and rotary switch. The whole in black bakelite case with working instructions **29/6.** Post 2/-.

FREQUENCY TUNING FORKS for operating L.F. Phonic Motors, fork tines of Mild Steel, constancy of frequency 1 in 2,000 with ordinary room temperature changes. Price **£7/10/-.** Low Frequency Phonic Motor designed for use with the above Fork, laminated 4-pole stator, 6-pole rotor running on B. Bearings, stator poles wound and designed for supply from intermittent D.C. Mercury filled flywheel on rotor spindle for smooth running **£12/10/-.** Write for full descriptive leaflet.

SIGNAL GENERATORS Type 101 frequency range 370/640 Mc/s. Piston attenuator, max. output 100 m/V Prov. for internal sine mod. and exter. pulse mod. mains operated. Several other models in stock; write for leaflet.

TELEPHONE EXCHANGE manual 5-line with drop indicators, speaking and Ringing Keys, Operators call bell and terminals for operators headset **75/-** carr. 5/-. Limited stock. 25-200 line G.E.C. automatic Telephone Exchanges prices on application.

HOUSE OR OFFICE TELEPHONES. Ex-G.P.O. wall type telephone constructors parts comprising Magneto Bell in pol. wood box fitted Transformer condenser, Microphone, connection strip, switch-hook and contacts, G.P.O. Receiver separate hand magneto Generator and wiring instructions **35/-** per pair, carriage 5/- extra.

TRANSFORMERS. Auto Transformers 230/110 volts 75 watts **25/-**; 100 watts **30/-**; 150 watts, **35/-**; 200 watts **40/-**; 300 watts **65/-**; 1 K.W. **£7/10/-.** Booster Transformer, 230 volts 50 cy. input 53 volts 15 amps. output **£4/10/**: carriage **7/6.**

NIFE CELLS. New, type F.4, 12 volts, 45 a.h., 9 cells in wood crate, **£8/10/-.** Carriage 10/-.

ELECTRADIX RADIOS
214 Queenstown Road, London, S.W.8
Telephone: MACaulay 2159

A VARIED and interesting opportunity occurs for versatile Physicists or Electronic Engineers who wish to apply scientific principles to a wide range of problems in the Engineering Industry.—Applications are invited for posts in the West London area, and should give full details of education, qualifications, experience, and salary required to Box A.E.220, c/o Central News, 17, Mourgate, London, E.C.4.

AN opportunity exists for a young man to join leading radio and television manufacturer for training as sales/technical assistant and correspondent; a basic knowledge of radio and television theory desirable; successful applicant must have personality and drive, and be prepared to work for the future.—Applications by letter to The Sales Manager, Ultra Electric, Limited, Western Ave., Acton, W.3. [6494

HOUSE (married accommodation) available for senior engineer for experimental work on radar, radio and/or electronics for important defence project in English Electric Company laboratory; honours degree preferable; commencing salary £700-£900 p.a.—Apply, giving full details and quoting Ref. 456C, to Central Personnel Services, English Electric Company, Ltd., 24-30, Gillingham St., London, S.W.1. [6413

THE Home Office invites applications from men with a good knowledge of V.H.F. radio for temporary posts of wireless technician in London; salary within the range £300-£400, according to age and experience; 44-hour, 5½-day week.—Applications, giving full details of qualifications and experience, to the Establishment Officer, Home Office (Room 224), Whitehall, S.W.1, not later than March 8th, 1951.

WANTED, experienced electronics engineer to take charge of investigations with effects of vibration or electronic gear and development of anti-vibration measures, in special English Electric Company laboratory; starting salary £600-£800 p.a., according to qualifications.—Apply, giving full details and quoting Ref. 850, to Central Personnel Services, English Electric Co., Ltd., 24-30, Gillingham St., London, S.W.1.

THE RESEARCH DIVISION of THE FAIREY AVIATION Co., Ltd., offer the following excellent opportunities to young men who are studying or intending to study for their Higher National Certificate (electrical or mechanical):
(a) Junior Test Engineers required for development work on servo mechanism installation and associated equipment; experience of wiring automatic and remote control circuits essential.
(b) Assistants required for installation or testing of pneumatic and electrical servo controls; experience of instrument assembly desirable.
Training will be given in this type of work and promotion would follow the award of the Higher National Certificate.
Junior Staff Vacancies exist for men with experience of assembly and testing of electrical and gyroscopic instruments in automatic control systems; previous experience of similar work essential.
Graduate Engineers with experience in design of servo mechanisms and control systems required for research and development work in connection with automatic control of experimental aircraft; some electronics experience is desirable.
Development and Test Engineers required for work on servo mechanism installations and associated control equipment. Minimum qualifications Higher National Certificate (electrical or mechanical); design experience on the above an advantage and some knowledge of electronics desirable.
All the foregoing vacancies are at Heston, Nr. Hounslow, Middx. Pension Scheme. Apply in writing, giving full details of experience and qualifications to—Personnel Manager, The Fairey Aviation Co., Ltd., Hayes, Middx, quoting reference RD/BE. [6448

HOUSE (married accommodation) available for senior engineer for experimental work on servo-mechanisms required for important defence project in special English Electric Company laboratory; permanent post; good experience in servo loop design essential; commencing salary £700-£900 per annum.—Apply, giving full details and quoting Ref. 844A, to Central Personnel Services, English Electric Co., Ltd., 24-30, Gillingham St., London, S.W.1. [6414

STRUCTURAL designer required by Marconi's Wireless Telegraph Co., Ltd., Chelmsford. Must have experience of guyed radio masts and towers or similar structures, together with some general mechanical engineering experience. A senior designer-draughtsman with suitable qualifications and proven ability would be considered.—Please apply, giving full details and quoting Ref. 854, to Central Personnel Services, English Electric Co., Ltd., 24-30, Gillingham St., London, S.W.1. [6506

A TECHNICAL assistant is required with considerable experience of the wire and cable industry for light current and electronic engineering; the position involves a wide knowledge of specifications, the ability to prepare and maintain a classified index of cables, and the experience to assist designers in choosing cables; laboratory experience in testing cables would be advantageous.—Apply, giving age, fullest details of experience, etc., to Personnel Department, E.M.I. Engineering Development, Ltd., ED/B, Blyth Rd., Hayes, Middx. [6450

PROTOTYPE engineer required for producing highest grade television transmission and other equipment; applicants should possess sound fundamental knowledge of both radio and television, together with some experience of layout and wiring of video equipment; wiring to be of instrument standard and applicants must be capable of producing own component layouts; City & Guilds, Higher Nat. or similar qualifications desirable but comprehensive practical experience acceptable in lieu.—Write, stating age, experience, and salary required to CINEMA-TELEVISION, Ltd., Worsley Bridge Rd., Lower Sydenham, S.E.26. [6417

NEW PRODUCTS

CHANCERY ADAPTOR. Place it on any 78 r.p.m. turntable (single record or autochange, rim or centre drive) and it gives you 33 r.p.m.—no fuss, no alterations **£3/12/6**; Decca lightweight pickup fitted Acos GP20 permanent sapphire for L.P. to match above, height and tone compensated **£2/13/-.** Both fittable by layman. **£6/3/-** the two, ins. post 2/6. Ex stock.

DECCA dual-speed motor and substantial turntable for 78 and 33 r.p.m. **£5/19/10,** ins. post 2/6. Lightweight Pickup fitted Acos GP reversible head presenting two permanent sapphires for Standard and L.P. to match: **£3/19/6,** post 1/6. Pickup fitted GP20 sapphire for L.P. only **47/6.** All ex-stock.

COLLARO STANDARD MICROGRAM CASES. Take above or any gram unit, brown rexine covered, carrying handle, uncut motorboard, measure 16½in. x 13in. x 7in. Price **50/-** carr. pd.

DECCA LONG-PLAYING RECORDS by Post. Send 2½d. for list of titles.

SYMPHONY NO. 1 (AMPLIFIER) by N.R.S. The most versatile domestic Audio Amplifier on the market today! Independent control of Bass, Middle and Top, separate Scratch Cut, negative feedback. For A.C. 200-250 v., input for magnetic, crystal and hi-fi pickups also Tuner. 5-watt output. Price 3 ohm model **£9/9/-**; 15 ohm model **£9/17/-.** Money refunded if not delighted!

SYMPHONY NO. 2. Same theme as No. 1 but having 10 watts Push-Pull output: 3, 7.5 and 15 ohms. Inputs as No. 1—full provision for Tuner. Woden Mains Transformer, Output trans. and Choke. Price **£13/19/6.**

NO. 1 TUNER. Specially recommended for above amplifiers and Leak, Williamson and other Quality Amplifiers. L. & M. wave T.R.F., neg. feedback detector—virtually distortionless. Price of Complete Kit and Constructional Manual **£4/15/-** or Ready-built **£5/15/-.**

NO. 2 QUALITY SUPERHET TUNER. L.M. & S. waves, special bandwidth, large full-vision Dial Assembly, spin-wheel tuning. As kit **£8**; Ready-built **£9.**

BASS-REFLEX CABINET KITS give superb bass response and top. (¾in. patent timber) full instructions supplied. 8in. speaker model 2ft. 6in. high x 1ft. 3in. x 1ft. deep. Price **80/-**; 10in. speaker model **90/-**; 12in. speaker model **100/-.** Any of above ready built for **7/6** extra. Carriage in any case 5/-.

RECOMMENDED HI-FI SPEAKERS. Full Wharfedale range in stock.

Send 2½d. now for new CATALOGUE AND BARGAIN SUPPLEMENT, indispensable to all Quality Enthusiasts. TERMS c.w.o. or c.o.d. Callers welcome. Demonstrations Monday to Saturday 9 a.m. to 6 p.m.

NORTHERN RADIO SERVICES,
16 Kings College Road, London, N.W.3
Phone: PRimrose 8314.

CRYSTALS

of OUTSTANDING QUALITY

TYPE "S"

Frequency range: 100 Kc/s to 15 Mc/s. Black bakelite case, 1⅛" high, 1⅛" wide, ⅜" thick, with two ¼" diameter pins spaced ¼" apart.

BROOKES CRYSTALS
10, Stockwell St., Greenwich, London, S.E.10
Phone: GREenwich 1828. Cables: Xtals London Grams: Xtals Green, London

Cabinets of Distinction . . .

RADIOGRAM CABINETS
RECEIVER CABINETS
RECORD CABINETS
DRAWER UNITS

Catalogue available on request.

Chassis

A.C., 5-valve 3 w/b Superhet Radiogram chassis. Absolutely complete kit of parts including wiring diagram . . . . **£10 . 0 . 0**

Or fully wired and tested . . . . . **£11 . 15 . 0**

Amplifiers

Four to fifteen watts output. Wired, or in kit form from . . . . . **£3 . 15 . 0**

Full details of above available on request.

LEWIS RADIO CO.
(DEPT. 351), 322, HIGH ROAD, WOOD GREEN, LONDON, N.22
Telephone - - - BOWes Park 5997

BRASS, COPPER, DURAL, ALUMINIUM, BRONZE
ROD BAR, SHEET, TUBE, STRIP, WIRE.
3,000 STANDARD STOCK SIZES
No Quantity too Small. List on application.
London: H. ROLLET & Co. Ltd. Liverp'l: **6, Chesham Place, S.W.1. Kirkby Estate.**
SLOane 3463. SIMONSWOOD 3271/3

QUARTZ CRYSTAL UNITS

QCC

For—

AIRCRAFT, MARINE AND COMMERCIAL USE are available in the complete range from 35 kilocycles to 15 megacycles.

Alternative mountings in standard two-pin A.M. pattern 10X, International octal, and miniature type FT243, can be supplied for most frequencies.

Prices are fully competitive, and we specialise in prompt deliveries for urgent requirements.

WE WELCOME YOUR ENQUIRIES.

THE QUARTZ CRYSTAL Co., Ltd
63-71 Kingston Road, NEW MALDEN, SURREY
Telephone: MALden 0334

AN experienced valve engineer is required for employment at Chelmsford; applicants should be 25-35 years of age, qualified engineers, and preference will be given to those with previous design or production experience of small transmitting valves.—Write, giving full details of experience, mentioning ref. 4976, to Central Personnel Services, English Electric Co., Ltd., 24-30, Gillingham St., London, S.W.1. [6262

DRAUGHTSMEN and designers are required by the research laboratories of The General Electric Co., Ltd., Wembley, Middx., for work of great national importance in the field of electronics; preference will be given to candidates aged 21-30, who have had practical workshop or laboratory experience; attractive starting salaries will be paid.—Applications should be sent in writing to the Personnel Officer (Ref. GBLC/412) and should give details of age, qualifications and experience. [6411

JUNIOR engineers interested in radio/radar and servo-mechanisms are required in special Enfield Electric Company laboratories, working on new defence project; preference given to applicants with Ordinary or Higher National Certificate in electrical engineering; progressive post; commencing salary £400-£600 p.a., according to qualifications.—Write, giving details and mentioning Ref. 815, to Central Personnel Services, English Electric Co., Ltd., 24-30, Gillingham St., London, S.W.1.

A VACANCY exists for a Deputy Chief of Test in Messrs. E. K. Cole, Ltd., Electronics Division; applicants must have sound technical background to standard of A.M.I.E.E. or equivalent; experience of production test methods and design of test apparatus in connection with Nucleonic, Radar, V.H.F. and frequency modulated equipments essential; knowledge of Ministry inspection and test procedure an advantage; details in first instance to—Personnel Manager, Electronics Division, Ekco Works, Malmesbury, Wilts. [6485

A RADAR Engineering post offering great scope for advancement in well-paid and interesting work is available immediately; applicant must be a competent and well-qualified engineer, with sound and broad experience in modern design techniques, who can quickly prepare himself for a senior position, involving responsible development work in the field of high voltage pulse techniques; applications, giving age, qualifications and experience to—The Radar Laboratory, Decca Radar Ltd., Shannon Corner, New Malden, Surrey. [6383

APPOINTMENTS in Civil Aviation.—Radio Mechanics are required at Ministry of Civil Aviation aerodromes and radio stations in various parts of the United Kingdom; if you have had practical experience in the maintenance of radio or radar equipment, call, write or telephone to Ministry of Civil Aviation, Room 310A 19/29, Woburn Place, London, W.C.1 (tel. Terminus 3366, extension 4153), or call at any Ministry of Civil Aviation aerodrome for particulars, or any local office of the Ministry of Labour and National Service. [6481

INTERNATIONAL AERADIO, Ltd., has vacancies at Bovingdon Airport, near Watford, for radio mechanics, experienced installation and maintenance ground equipment, for radio work of national importance; possibility overseas appointment later if desired; minimum commencing salary £336 p.a. (2/7 per hour plus 4½d lieu bonus); pension scheme; two weeks paid annual leave; single accommodation may be available; canteen facilities.—Write quoting reference RMH and this newspaper, Personnel Officer, 40, Park St., London, W.1. [6497

INSTRUCTOR in radio and television servicing required for the Manchester area; in addition to taking charge of short practical courses in television servicing, this instructor should be able to lecture to the level of the City and Guilds Radio II and Radio III examinations; the commencing salary depends on experience and qualifications and will be in the range of £450 to £650 per annum.—Applications, with the names and addresses of two persons to whom reference may be made, should be sent to The Principal, E.M.I. Institutes, Ltd., 10, Pembridge Sq., London, W.2.

MARCONI'S WIRELESS TELEGRAPH Co., Ltd., Chelmsford, require engineers for their Marine Development Group; applicants should have good knowledge and practical experience in the design of low power M.F. and H.F. transmitters; a knowledge of other marine communication and navigational aid equipment would be an advantage; salaries in the range £400 to £600 p.a. will be paid according to qualifications and experience.—Please apply giving full details and quoting Ref. 848, to Central Personnel Services, English Electric Co., Ltd., 24/30, Gillingham St., London, S.W.1. [6431

ATTRACTIVE staff vacancies for draughtsmen exist at Chelmsford and in London with Marconi's Wireless Telegraph Co., Ltd. Continued expansion of the company's work calls for increased D.O. output, and electrical or mechanical draughtsmen are invited to apply for these permanent staff positions on the design and development of radio and radar equipment. Vacancies also exist for young men of at least O.N.C. standard as trainee draughtsmen.—Write, giving full details, quoting Ref. 142B, to Central Personnel Services, English Electric Co., Ltd., 24-30, Gillingham St., London, S.W.1. [6291

IF you are between 21 and 25 years of age, and have at least 3 years' electrical or mechanical engineering workshop experience, the English Electric Group are willing to consider you for training as a draughtsman. This paid training will be up to six months' duration to fit suitable applicants for employment as either electrical or mechanical draughtsmen at Acton, Bradford, Chelmsford, Liverpool, Preston, Rugby or Stafford. Preference will be given to men who have reached O.N.C. standard of technical study.—Apply, quoting ref. 842, to Central Personnel Services, English Electric Co., Ltd., 24-30, Gillingham St., London, S.W.1.

PRESS BUTTON OHMMETER
FOR THE
SPEEDY
MEASUREMENT OF RESISTANCE

An instrument for high speed modern production, enabling continuity and resistance checks to be made on all types of electrical equipment.

Features

- Six ranges selected by press buttons
  0-100 ohms.
  0-1,000 ohms.
  0-10,000 ohms.
  0-100,000 ohms.
  0-1 Megohm.
  0-10 Megohms.
  Accuracy ± 1%
- Large eight inch diameter easily read meter
- Accuracy unaffected by variation of mains volts
- Mains operated 200-250v. 40-100~
- Low price—**£25**

For further particulars of this and other high-grade electronic instruments, write to :

HATFIELD INSTRUMENTS
175 Uxbridge Road, Hanwell, London, W.7
Telephone : EALing 0779

" GLOBE-KING "

Short Wave Kits and Components. Production fully booked up until new series commence Autumn, 1951.

Watch this Magazine for later announcements.

JOHNSONS (Radio)
MACCLESFIELD

AUTOMATIC SWITCHES
(RECORD TIMED)

ELECTRIC 1 to 100 AMPS. **CLOCKWORK** 7 to 35 DAYS

From **35/-** EACH

All guaranteed for a year.

Write for illustrated lists : **DONOHOE,**
2, UPPER NORFOLK ST., NORTH SHIELDS, NORTHUMBERLAND.

WANTED

BC312 Receivers for 12 volt operation and **BC348 Receivers** preferably not converted.

BC221 Frequency Meters in good condition.

State price and condition to

Box No. 8287,
c/o Wireless World.

AN IMPORTANT ANNOUNCEMENT!

to all interested in passing their G.P.O. MORSE CODE TEST for an Amateur Transmitting Licence.

We have been pleased to arrange a Special Candler course (at a fee within the reach of all) which includes all the training essential to enable you to be successful.
Full details will be sent to all who apply for the CANDLER "BOOK OF FACTS".

Read the following extracts from unsolicited testimonials sent us by Candler students.

Ref. 7376 : "I am very pleased with this method of training and I passed the G.P.O. Morse test after third lesson. Since getting my call sign I have been complimented very often on my "good fist." W.E.

Ref. 5173 : "So far, after only completing half the course, I am pleased to say that my speed in both sending and receiving has risen from a mere 5 w.p.m. to a steady and 100 per cent correct 15 w.p.m. This has enabled me to obtain my Amateur's Licence here within a very short time of commencing my study of the code." L.R.

Ref. 7161 : "I may add that I passed my G.P.O. Morse test for the Amateur Transmitting Licence a week or so ago and am very pleased that the first five lessons enabled me to do so. It was not as difficult as I had imagined." J.R.D.

Ref. 3301 : "I have successfully passed the P.M.G. Amateur's Licence test and have been allotted my call sign. I took it with ease, after completing lesson three." V.H.T.

IMPORTANT. Mention "Special Course" when you apply for a copy of the "BOOK OF FACTS".

THE CANDLER SYSTEM CO.,
(55W) 121 KINGSWAY, LONDON, W.C.2
Candler System Company, Denver, Colorado, U.S.A.

If you care to call at

MODERN ELECTRICS LTD.,
164, CHARING CROSS ROAD, W.C.2
TEMple Bar 7587

we should be pleased to demonstrate and give immediate delivery of the

"SOUND MIRROR"
TAPE RECORDER

as described and illustrated on Page 45

" NOT the cheapest but certainly the BEST "

S.A.E. please for catalogue

Export enquiries welcome!

UNIVERSITY students in physics, electrical and mechanical engineering, who are taking their Finals this year, are invited to send details of their records to the Personnel Officer (Ref. GBLC/672) Research Laboratories of The General Electric Co., Ltd., North Wembley, Middx; a number of interesting vacancies on experimental work will occur during the summer and selected candidates will be invited for interview during the Easter vacation; certain openings will be reserved for men with post-graduate research experience, particularly in the fields of vacuum physics and electronics.

LABORATORY assistants and radio mechanics with ordinary or Higher National Certificate or City and Guilds Full Technological Certificate are required at Stanmore, Middx., for work with research engineers engaged on new developments; experience in a radio or television laboratory and ability to construct, wire and test communications equipment and to use machine tools are essential.—Replies will be sent to all applications sent to the Personnel Officer, Research Laboratories of The General Electric Co., Ltd., East Lane, North Wembley, Middx. (Ref. GBLC/446), which give details of age, qualifications and experience. [6432

MARCONI'S WIRELESS TELEGRAPH Co., Ltd. have vacancies for technical assistants for contract work in their broadcasting division; applicants should have had works experience, preferably in the planning and progressing of production; some experience of broadcasting or television equipment would be an advantage; successful candidates will be paid a salary in a grade which rises to a maximum of £515 p.a.; a staff pension scheme is in operation.—Please write, giving full details and quoting Reference 847, to Central Personnel Services, English Electric Co., Ltd., 24-30, Gillingham St., London, S.W.1. [6406

BRITISH EUROPEAN AIRWAYS invite applications for the post of development engineer (radio) at Northolt, for development of current aircraft radio equipment, inspection of technical defects and preparation of radio modifications; considerable experience of modern civil aircraft radio systems and technical qualifications not less than City and Guilds Radio Communication II or equivalent standard are essential; salary scale £620–£790 per annum.—Write giving details of age, experience and qualifications, and quoting reference 10/51, to Personnel Manager, B.E.A., Keyline House, Ruislip, Middlesex. [6475

NELSON Research Laboratories, English Electric Co., Ltd., Stafford, have a vacancy for a senior electronic engineer for work on high-speed automatic electronic digital computers. Applicants should have honours degree in physics or engineering, with a sound knowledge of the principles of circuit design and have had three or four years' experience in radar or electronic development. The appointment will be in the London area for an initial period of at least one year and then at Stafford.—Apply giving full details and quoting Ref. 305, to Central Personnel Services, English Electric Co., Ltd., 24-30, Gillingham St., London, S.W.1. [6458

SENIOR engineer required to take charge of tendering section in sales office of a large South-East London firm of telecommunications engineers; applicants, who should have trained on telecommunications engineering and have had at least three years' experience as a design or equipment engineer on switching systems, must possess an Engineering Degree (Grad. I.E.E. or comparable qualifications; practical knowledge of telephone instruments and switchboard design essential and a broad knowledge of automatic switching methods an advantage; the post is an interesting one which offers good scope for a man with drive and initiative; salary according to qualifications.—Write giving fullest possible details to Box D 9999, A.K.Advtg., 212a, Shaftesbury Ave., London, W.C.2. [6465

APPLICATIONS are invited by the Ministry of Supply from physicists and electronics engineers for unestablished appointments in the experimental officer class in research and development establishments located mainly in the South of England; candidates should preferably possess one of the following qualifications or its equivalent: Inter. B.Sc. in Science or Engineering; Higher National Certificate with reference to light electrical engineering, radio, etc., preferably following on a full engineering apprenticeship; the final City & Guilds certificate of a 5-year grouped course in a relevant subject such as telecommunications; graduate or corporate membership of the Institute of Physics or Electrical Engineers or equivalent professional body; a University degree in physics or in electrical engineering; applications from candidates not so qualified who can show evidence of considerable experience in scientific research and development in the field of electronics may be accepted; some experience in electronics, in industry or a technical branch of the Forces, would be an advantage.

STARTING salary will be determined on an assessment of the successful candidate's qualifications and experience within the following ranges: Male: senior experimental officer (minimum age 35), £735–£935 London, £705–£895 Provincial; experimental officer (minimum age normally 28), £525–£675 London, £495–£645 Provincial; assistant experimental officer (minimum age 18), £230–£490 London, £220–£460 Provincial; rates for women somewhat lower.

APPLICATION forms obtainable from Ministry of Labour and National Service, Technical and Scientific Register (K), York House, Kingsway, W.C.2, quoting A.360/50A. [6517

NUSOUND PRODUCTS
136 WARDOUR STREET, LONDON, W.1
(Oxford Street end)
Tel : GERrard 8845

NUSOUND QUALITY AMPLIFIERS.
3) WATT OUTPUT. PP 6V6—Independent bass and treble boost and cut—switch for L.P. records—neg. feedback—provision for radio feeder unit—freq. response 25 to 20,000 c.p.s. ± ½ d.b.—hum 80 d.b. down at 6.5 watts—feedback 14 d.b.—sensitivity .06 volt. Price only **£14/14/-**.

4) WATT OUTPUT—Independent bass and treble boost—preamp.—provision radio feeder unit, **£10/10/-**. Constructional booklet, **1/6**, post free. Complete kit, **£8**.

NUSOUND QUALITY FEEDERS.
Pre-set TRF—Home, Light and Third with gram. position—air spaced trimmers for stability of tuning. Size 6in.–7in., height 6in., **£6/10/6**, inc. Constructional booklet, **1/6** post free. Can be built for **£3/10/-**.
Pre-set S/Het.—Home, Light, and Third—choice of MW and LW Light—Gram. position. Size 6in.–7in., height 4½in., **£6/10/6** inc. (Please send S.A.E. for descriptive leaflet on all our products.)

VARIABLE RADIO TUNER UNIT—MW and LW Bands—S/Het. of small dimensions—R/Gram. switch, etc. Our latest model. Price **£9/9/-** inc.

NUSOUND REMOTE CONTROL & PRE-AMP. UNIT. Base boost—Treble boost and cut—V/C and switch—L.P. correction switch—Gives a gain of 10 : 1 in voltage—Ideal for Williamson and W.W. Amplifiers. Price **£4/10/-**.

REFLEX CABINET.
At last, a reflex cabinet for the famous Wharfedale 10in. Speakers. Sizes 30½in., 15in., 12in. Complete with reflector—Bass port—Polished finish. A handsome piece of furniture. Price **£9/9/-**.
A 12in. Model is also available at **£10/-/-**.

GRAMOPHONE EQUIPMENT. Connoisseur P/up. Standard L/weight, **£3/19/-**; Trans. **13/-**; Super L/weight, one head, **£5/14/6**; Micro-groove head, **£3/11/8**; Trans. **15/-**; Fibre P/up, **£4/3/-**; Special Trans. **25/-**; Garrard plug-in heads, standard **29/6**; Miniature, **42/-**; H/ Fi, **64/3**; Adaptor **6/-**; Collaro AC47 78 r.p.m. centre drive, **£5/18/2**; Decca Dual-speed Motor, **£5/19/10**; Decca Turnover Xtal P/up L.P. or 78 **79/4**.

WHARFEDALE L/SPEAKER SEPARATOR, £3/5/-.
Collaro A.C./D.C. motors, 12in. turntable, **£9/3/6**. Chancery L.P. Attachment G.32, **£3/12/6**, with Decca L.P. Xtal P/up, **£6/2/3**.
Full range Wharfedale Speakers.

TELEVISION.
We stock all the parts for the Viewmaster and Electronic televisors inc. Black Filters, 9in. **15/6**; 12in. **22/6**. All Haynes components—9in. lens. **50/-**; 9in. with filter, **55/-**; 12in. lens, **70/-**; 12in. with filter, **75/-**.

NUSOUND TRANSFORMERS AND CHOKES.
A selection from our range and we can wind to your spec., delivery approx. 7 days. Estimates free.
350-0-350 v. 150 mA, 6.3 v. 4 a., 5 v. 3 a., **40/-**.
350-0-350 v. 100 mA, 6.3 v. 2 a., 5 v. 2 a., **31/-**.
300-0-300 v. 100 mA, 6.3 v. 3 a., 5 v. 2 a., **28/6**.
6.3 v. 1½ a. Heater trans. 230 pri. only, **7/-**.
4 v. 2 a. Heater trans. 230 pri. only, **7/-**.
6 v. 6 a. C.T. Heater trans. 230 pri. only, **17/3**.
6.3 v. 3 a. C.T. Heater trans. 230 pri. only, **12/6**.
12 v. 1 a. C.T. Heater trans. 230 pri. only, **8/6**.
CH4, 10 H, 150 ohms, 75 mA, **4/9**.
CH5, 10 H, 300 ohms, 60 mA, **4/9**.
Please add Postage.

Our comprehensive list of TV—Radio and Gramophone equipment, etc., is now available. Price **4d.** post free.

YOUR METER DAMAGED?

Leading Electrical Instrument Repairers to the Industry.

Repairs by skilled craftsmen to all makes and types of Voltmeters, Ammeters, Microammeters, Multirange Test meters, Electrical Thermometers, Recording Instruments, Synchronous Clocks, etc. Quick deliveries—for speedy estimate send defective instrument by registered post to

L. GLASER
Electrical Instrument Repairers
341 CITY ROAD, E.C.1
Tel. Terminus 2489

NOW AVAILABLE

GERMANIUM CRYSTAL DIODES

LATEST, SMALLEST, SUPREME CRYSTAL DETECTOR.
Midget Size, 5/16in. x 3/16in.
Wire Ends for Easy Fixing.
4/6 each, postage 2½d.
Technical Details and Selected Types available.

COPPER INSTRUMENT WIRE
ENAMELLED, TINNED, LITZ, COTTON AND SILK COVERED.
Most gauges available.
B.A. SCREWS, NUTS, WASHERS, soldering tags, eyelets and rivets.
EBONITE AND BAKELITE PANELS, TUFNOL ROD, PAXOLIN TYPE COIL FORMERS AND TUBES, ALL DIAMETERS.
Latest Radio Publications.
SEND STAMP FOR LISTS.
TRADE SUPPLIED.

POST RADIO SUPPLIES
33 Bourne Gardens, London, E.4

ELECTRONICS
DUPLEY
LTD.
CRANMER AV. EALING.W 13.
Transformer and Coil Manufacturers to the Trade
Telephone: EALing 5688

LOCKWOOD
makers of
Fine Cabinets
and woodwork of every description for the Radio and allied trades
LOCKWOOD & COMPANY
Lowlands Rd., Harrow Middlesex. Byron 3704

MAGNETIC TAPE RECORDERS and COMPONENTS
from
WILL DAY, LIMITED
19 Lisle Street, London, W.C.2.
GERrard 7105 and 4476
LIST SENT BY RETURN

THIS — *Does these*

ACCURATELY and QUICKLY Chassis, Brackets, Shrouds, Condensers and Transformer Clips, in Steel or Aluminium (Five sizes—12" to 36") Trepanner available "SNAP" Cutter, Notcher and Shearer.
Details with pleasure.

A. A. BENDERS are proving invaluable to Electronics, Electro-Medical, Radio and other Research Workers.

Please ask for copy of our NEW 6-page FOLDER which contains much new and useful information about their many applications.

A. A. TOOLS (W), 197a, Whitecroc Road ASHTON-U-LYNE

EXPERIENCED Designer required for Audio and small Power Transformers; write, giving full details to:—
WODEN TRANSFORMER Co., Ltd., Moxley Rd., Bilston, Staffs. [6389

TV and radio engineer, experienced, required by N. London dealer; competence and ability to drive essential.—Box 8278. [6457

RADIO/RADAR development engineers urgently required, accommodation available. Applications are invited from senior and junior development engineers, preferably with experience of radar or microwave technique, who are capable of developing equipment or components to service specifications. Successful candidates will be employed on work of great national importance.—Write quoting reference CHC(5) to Personnel Officer, General Electric Co., Ltd., Radio and Television Works, Spon St., Coventry.

MARCONI'S WIRELESS TELEGRAPH Co., Ltd., require an additional lecturer in electronic engineering at Marconi College, Chelmsford. The applicant must be a graduate in physics or engineering, with preferably some experience in one or more branches of electronics. Duties will include lecturing, supervision of experimental work, and development of equipment for the present and future college courses. Salary according to qualifications and experience. Good staff pension scheme.—Write giving full details and quoting Ref. 260A, to Central Personnel Services, English Electric Co., Ltd., 24-30, Gillingham St., London, S.W.1. [6459

DRAUGHTSMEN are invited to make an appointment with E.M.I. Engineering Development, Ltd., to discuss the several vacancies available at their Hayes and Feltham branches; all grades of designers and draughtsmen are required for a wide range of engineering products for which your experience may be suited; details will be sent by post on request and/or strictly confidential interview arranged without obligation; posts available offer a maximum of interest, technical information and experimental facilities, and long term employment prospects with good salary to suitable applicants.—Apply, giving fullest details of experience, qualifications, etc., to Personnel Department ED/G, E.M.I. Engineering Development, Ltd., Blyth Rd., Hayes, Middx. [6400

GRADUATE physicists and engineers are required by the Research Laboratories of The General Electric Co., Ltd., North Wembley, Middx., for (a) a research group concerned with microwave valves; applications are invited from those interested in both the theoretical and experimental aspects of the fundamental problems concerned with the interaction of electrons with electromagnetic fields. (b) Work concerning problems of experimental valve constructional techniques; a man with experience in this field would be preferred. (c) Problems of waveguide transmission; a sound theoretical knowledge of this field of work is required together with an interest in the engineering applications.—Candidates should write to the Personnel Officer (Ref. GBLC/448), giving age, qualifications and experience. [6423

MINISTRY OF SUPPLY invite applications for Technical Class Grade III officers for an establishment in Western England. Qualifications: British of British parentage; regular engineering apprenticeship, good general experience in drawing office and workshop practice in radio or electrical engineering and able to interpret engineering drawings and specifications. Ordinary National Certificate or an equivalent standard of technical education. Duties: preparation of schedules (including classification and indentifications for radio installations and equipment; also preparation of technical information for modifications. Salary range: £360 (at age 26)—£495 per annum (slightly less below age 26). The appointment will be unestablished but opportunities to compete for establishment occur periodically. Applications, by letter only, stating age, the name and address of present employer and full particulars of experience in chronological order, should be forwarded within 10 days of the appearance of this advertisement to Ministry of Labour and National Service, Appointments Department, 1-6, Tavistock Square, London, W.C.1, quoting reference (DT/1633). In no circumstances should original testimonials be forwarded. Only candidates selected for interview will be advised. [6522

B.B.C. invites applications for post of engineer in planning and installation department, London; applicant have a good basic knowledge of electrical engineering and television; a University degree in electrical engineering is a desirable, but not essential, qualification; preference will be given to applicants who have had practical experience of cinematographic equipment used for sound and picture recording and who have a wide knowledge of photography and the control of film processing; a knowledge of the mechanical design of film cameras would be an advantage; the work is in connection with the development of television recording processes and the duties of the post will include the preparation of appropriate specifications for the manufacture of such television equipment, the supervision of its installation, subsequent acceptance trials and the conduct of relevant correspondence; starting salary £745 p.a. (may be higher if qualifications and experience are exceptional) rising by annual increments on a five-year progression to £965 p.a.; the successful applicant will become eligible for consideration for appointment to established staff (contributory pension scheme) after two years' qualifying period.—Applications, stating age, qualifications and experience, to reach Engineering Establishment Officer, Broadcasting House, London, W.1, within 7 days.

CHASSIS

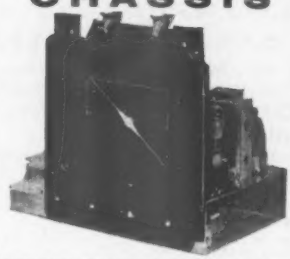

HAYES RG 120 RADIOGRAM CHASSIS. The demand for this attractive and popular chassis increases month by month. The total price of £13/7/6 includes an 8in. loudspeaker, and all packing and carriage charges, representing real value-for-money in these days of rising prices. A 10in. L.S. can be supplied at a slight extra cost. Fully guaranteed for one year. Full details will gladly be sent you by return of post.

ARMSTRONG CHASSIS. We hold the largest stocks of Armstrong chassis in the Midlands, and are the sole Birmingham agents. The full range as shown on page 91 can be seen and heard in our showroom. Open all day Sats.

THE HAYES COMPANY
1 ALCESTER RD., MOSELEY, BIRMINGHAM, 13
Phone: SOUTH 0202

mathematics
Maths become really easy and interesting when you enrol for a Home-Study Course with the
T. & C. RADIO COLLEGE
Write to the Principal for free booklet 'W':
R. Heath Bradley,
58 Harland Rd., Southbourne, Bournemouth.

BULLANCO 66 QUEENS R^D S E.15 NEW CROSS 1092
ALUMINIUM
SHEET EXPANDED TUBES, ANGLES, BARS, RODS, MOULDINGS RIVETS
ANY SIZES CUT OR FOLDED

Television Demonstration
of Sets and components every Friday 8-10 p.m.
TELEVISION CIRCUITS FOR THE CONSTRUCTOR
New Second Edition 1/6 post free.
HAYNES RADIO Ltd.
Manufacturers of the complete range of Television Receiving Equipment.
Queensway . Enfield . Middlesex

ENGINEERS!
Whatever your age or experience, you must read "ENGINEERING OPPORTUNITIES". Full detail of the easiest way to pass A.M.I.Mech.E., A.M.I.C.E., CITY & GUILDS (Electrical, etc.), MATRIC., etc., on "NO PASS—NO FEE" terms and details of Courses in all the branches of Engineering—Mechanical, Electrical, Civil, Auto., Aero., Radio, etc., Building, etc. If you're earning less than £12 a week, tell us what interests you and write for your copy of "ENGINEERING OPPORTUNITIES" today—FREE!
176 PAGES
Free!

B.I.E.T.
357 Shakespeare Hse., 17-19 Stratford Place, London, W.1.

E.M.I. ENGINEERING DEVELOPMENT, Ltd., require experienced electronic engineers, including team leaders, for the development and design of radar equipment; applicants should have a sound technical training with a degree, or equivalent qualification, and several years experience in this field, a thorough knowledge of microwave technique and ability to originate circuitry is essential; the appointments are for permanent pensionable staff and carry a good salary and excellent prospects.—Applicants should write, quoting ED/34, and give full details to Personnel Department, E.M.I. Engineering Development, Ltd., Blyth Rd., Hayes, Middx. [6410

SITUATIONS WANTED

WIRELESS engineer, qualified, widely experienced V.H.F. communication system, engineering, seeks position in industry offering incentive, encouragement and scope for ability.—Box 7988. [6382

TECH. administration, engineer, aged 30, capable technical writer and correspondent, seeks post with scope for initiative, experienced in administration of service department of large company.—Box 7990. [6385

AMBITIOUS, energetic electrical engineer (Nat. Dip., H.N.C., Grad.I.E.E.), desires interesting post in/near Leeds, Yorks, experience incs. elec. instruments, light elec. machines, radar (4 yrs. R.A.F.), electronic development work.—Box 6367. [6435

SERVICE manager, qualified radio and T/V engineer, in complete charge service depot, requires change, preferably coastal district, experienced most makes and types receivers, full member G.R.S.E., on T/V section Trade Register, clean driving licence; age 30, married, accommodation desirable.—Box 8284. [6470

MANUFACTURERS—We hold large stocks of components and can offer Immediate Delivery of many components that are in short supply. Send us your enquiries or 'Phone Luton 2677.

Express Delivery from

COVENTRY RADIO

189, Dunstable Road, Luton

★

'Radiospares' Quality Parts

The Service Engineer's First Choice

★

FIZZ CRACKLE POP!

No, this is not a new brand of mineral water! We would just like to remind you that if you want to avoid hearing similar noises from that new set you are building, you should play safe, and fit AMPLION "moulded track" volume and tone controls. The result of extensive research these controls are individually numbered, and covered by a unique guarantee. Small in size, they can be fitted to existing sets with ease, and once fitted, can be forgotten. Values: 50K, 100K, ¼, ½, 1 or 2 Meg. Less switch 4/-, single pole switch 5/9 d.p.s., 6/6. Ex-Govt. types, less switch 2/9, with switch 4/6.

CHOKES: Ex-Govt. 20 hy. 80 mA., unused, 6/6, 9d. post.

CONDENSERS: New ex-Govt; tubular 0.1, 0.05, 0.01, 0.005, 3d., mica 0.0005, 0.0002, 4d., others available.

SILVERED MICA CONDENSERS, 25, 50, 75 pf., 3d. 120, 200, 3,000, 4,700 pf., 4d.

HIGH VOLTAGE CONDENSERS: 0.002 mfd. 5,000v. mica, 1/6. 6 mfd. 2,000v. test, in cartons, 3/6.

The above are just a few items from our list of ex-Govt. and other bargains. Please send for a copy, it will save you £££s! Post paid on orders over 15/-. (Mail order only please).

REED & FORD

448 Grosvenor Road, SOUTHPORT

BUSINESSES FOR SALE AND WANTED

RADIO and television business in North Herts town, excellent position, living accommodation, double fronted shop ,lease at low rent, present gross £80 per week, growing, good agencies; £3,250 including equipment (s.a.v.).—Apply Box 8277. [6458

VERY modern and well-established radio and electrical business occupying a multiple position in busy West Country market town, turnover £21,000, long lease at moderate rent, main agencies both radio and electrical, good experienced staff, owner retiring, will give every assistance after purchase, genuine offer; price £6,500, s.a.v. about £4,500.—Box 6292. [6488

FINANCIAL PARTNERSHIPS

PARTNERSHIP offered for young radio and TV engineer, small capital needed, North London.—Box 6293. [6467

TECHNICAL TRAINING

CITY & Guilds (Electrical, etc.), on "No Pass—No Fees" terms. Over 95% successes. For full details of modern courses in all branches of Electrical Technology send for our 176-page handbook, free and post free.—B.I.E.T. (Dept. 388A), 17, Stratford Place, London, W.1.

PAINTS, CELLULOSE, ETC.

PAINT spraying handbook, 5/6, post free; cellulose and synthetic paints and all spraying requisites supplied; catalogue free.—Leonard Brooks, 53, Harold Wood, Romford. [0207

TUITION

TELEVISION.

THE GOTHIC TELEVISION SCHOOL is the only school in Great Britain devoted solely to training in television; the school specialises in providing guaranteed home-study training for the R.T.E.B. Television Servicing Certificate and the Brit.I.R.E. Television examination; full details from—The Principal, Gothic Television School, 13, North Ave., London, W.13. [0051

UNIVERSITY COLLEGE, Southampton. Department of Electronics.

THE Department of Electronics (Professor E. E. Zepler) gives an advanced course at Honours Degree standard in electronics. The course is full-time for one academic year and the College grants a diploma by examination to students who successfully complete the course. Entry qualification is a University degree in Physics or Electrical Engineering, or its equivalent. The fifth of these courses will commence in October, 1951, and application for admission should be made now to the Academic Registrar, from whom further details may be obtained.

RADIO training.—P.M.G. exams. and I.E.E. Diploma; prospectus free.—Technical College, Hull. [0111

WIRELESS operating; attendance and postal courses; stamp for reply to Manager, The Wireless School, Manor Gdns., London, N.7.

A.M.I.Mech.E., A.M.Brit.I.R.E., City and Guilds, etc., on "no pass—no fee" terms; over 95% successes. For details of exams. and courses in all branches of engineering, building, etc., write for 176-page handbook—free.—B.I.E.T. (Dept. 387B), 17, Stratford Place, London, W.1. [0118

HALLICRAFTER BC 610E

Complete station including speech amplifier, special aerial coupler, 30 mcs. tuning unit, LF conversion kit, junction box, multi tapped auto transformer, dynamic and carbon mike and £50 worth of brand new spares, service manual, aerial mast, guys, spare valves to keep transmitter serviced for years £175. Carriage free U.K. or U.K. port. Shipped anywhere quickly at cost in original shipping crate. Demonstration by appointment.

Box 8189 c/o "Wireless World."

TELECRAFT

AERIALS ENSURE THE

BEST TELEVISION

TRY ONE AND SEE FOR YOURSELF

"Quixo" RADIO Cell Tester

Accurate tests High, Low and Grid Bias Batteries. Write for leaflet 30M.

RUNBAKEN MANCHESTER 1

Favourably reviewed in "Wireless World," Nov., 1948

The "j" Operator Simply Explained
by W. H. Miller 3/-

A.C. Network Analysis
by W. H. Miller 4/-

CLASSIFAX PUBLICATIONS
9 White Moss Avenue, Manchester, 21

NOTHING succeeds like success! What we have done a thousand times we can do again for you.—See the B.N.R.S. Advt. on page 97. [0172

SEE the world, 600 Radio Officers required; send 2d stamp for prospectus to Britain's leading college; we train most, in shortest period, at lowest cost.—Wireless College, Colwyn Bay.

TELEVISION postal course for radio trades Examination Board's diploma; also postal courses for P.M.G. 2nd and 1st class Certificates and Amateur Radio Transmitting licence. —Apply British School of Telegraphy, Ltd., 179, Clapham Rd., London, S.W.9. (40 years' experience in coaching students in wireless telegraphy and allied subjects.) [0124

THE Institute of Practical Radio Engineers have available home study courses in every phase of radio and television engineering, specialising in the practical training of apprentices in the retail trade; enrolments limited, fees moderate.—The Syllabus of Instructional Text may be obtained post free from the Secretary, I.P.R.E., Fairfield House, 20, Fairfield Rd., Crouch End, London, N.8. [0088

BOOKS, INSTRUCTIONS, ETC.

FIRST book about transmitters, "Radio Communication Transmitters," by J. J. Huperti, Prof. de Paul University, Chicago, U.S.A.: published by ATA SCIENTIFIC PROGRESS, Ltd., 63, Kensal Rd., London, W.10. Price 24/-. [6379

I.P.R.E. Technical Publications; 5,000 alignment peaks for superheterodynes, 4/9 post free; The Practical Radio Engineer, quarterly publication of the Institute, sample copy 2/- post free; membership and examination data 1/- post free.—Secretary, I.P.R.E., 20, Fairfield Rd., London, N.8. [0089

THE POLYTECHNIC
309 REGENT STREET, W.1

Electrical Engineering Department

Head of Department:
W. H. DATE, B.Sc. (Eng.), M.I.E.E.

A Special course of four lectures on ULTRASONICS and its Applications in Industry will be given by L. F. FARREN, M.B.E., Whit. Schol., M.I.E.E., D.I.C., Member of the Staff of the Research Laboratories of the General Electric Company Ltd., on Fridays at 6.30 p.m., commencing March 2nd, 1951.

Fee for the Course - - - 10s.

A syllabus may be obtained on application to the undersigned.

J. C. JONES,
Director of Education.

TAMSA

spells Quality in Tape & Wire Recording

Heads, Amplifiers, Tape, etc.

ORDER YOUR HIGH QUALITY TAPE MECHANISM NOW!

Constructor's Envelope: Amplifier Equipment. 4/3 Post Free (G.B.)

"Magnetic Tape Recording", 4th Edition revised & enlarged. 7/- Post Free (G.B.)

Write for Latest Price List

AUDIGRAPH LTD.

Dept. MR3, 74, Great Hampton Street, HOCKLEY, BIRMINGHAM 18

5460A

RADIO UNLIMITED

ELM ROAD, LONDON, E. 17 Tel.: Key 4813

AMPLIFIER. A.C. mains, 3-valve, 5 watt chassis. Ideal for Mic. & Gram. reproduction. Fitted with Vol. and Tone controls, and complete with valves, KT61, 6J7 and 5Z4. **Price £6/7/6 Carr. Paid.**

MOBILE AMPLIFIER. (6-volt). Housed in metal carrying case, complete with plug-in vibrator power supply. (Full details on request.) S.A.E. **Price 9 gns. Carr Paid.**

AMPLION. Guaranteed Volume Controls. Semi-midget 10K to 2 Meg. 4/-; SP/sw 5/9; DP/sw 6/9.

AMPLION. Guaranteed Coil Pack. 3 waveband with Gram. switch. 40/4 inc. tax.

AMPLION 10-Range AC/DC Test Meter, 77/6.

EGEN Volume controls 10K to 2 Meg. L/spindle. Less switch 2/9, W/sw 4/-.

SPEAKERS. P.M. lightweight. Leading makes. 5in. 11/6; 6in. 12/6; 8in. 14/6; 10in. 16/6; 12in. 45/-.

INDEX TO ADVERTISERS

	PAGE
A.A. Tools	100
Acoustical Mfg. Co., Ltd.	17
Acru Electric Tool Mfg. Co., Ltd., The	102
Adcola Products, Ltd.	84
Aerialite, Ltd.	12
Allan, Richard, Radio, Ltd	44
Ambassador Radio	39
Anders Radio, Ltd.	82
Antiference, Ltd.	8
Armstrong Wireless & Television Co., Ltd.	91
Ashworth, H.	8
Audigraph, Ltd.	101
Audix, B. B., Ltd.	75
Automatic Coil Winder & Electrical Equipt. Co., Ltd., The	1
A.W.P. Radio Products	82
B. & H. Radio	96
Bakers "Selhurst" Radio	37
Barker, A. C.	89
Beethoven, Ltd.	95
Belling & Lee, Ltd.	73
Berry's (Short Wave), Ltd.	83
Birmingham Sound Reproducers, Ltd...	32, 48
Bradmatic, Ltd.	14
Brierley, J. H. (Gramophones & Recordings), Ltd.	84
Britain, Chas. (Radio), Ltd.	80
British Communications Corpn., Ltd.	28
British Institute of Engineering Technology	95, 100
British Insulated Callender's Cables, Ltd.	Cover ii
British National Radio School	97
British N.S.F. Co., Ltd.	13
British Physical Laboratories	14, 42
British Rola	54
Brookes Crystals, Ltd.	97
Brown, S. G., Ltd.	36
Buchan, A. E.	96
Bulgin, A. F., & Co., Ltd.	Edit., 123, 80
Bull, J., & Sons	87
Bullanco	100
Bullers, Ltd.	2
Cabot Radio Co., Ltd.	91
Candler System Co.	99
Champion Products	92
Chapman, C. T. (Reproducers), Ltd.	84
Charles Amplifiers, Ltd.	10
Cinema-Television, Ltd.	5
Classifax Publications	101
Clydesdale Supply Co., Ltd.	67
Cohen, D.	70
Cosmocord, Ltd.	52
Cossor, A. C., Ltd.	21
Coventry Radio	101
Davis, Alec, Supplies, Ltd.	77
Davis, Jack (Relays), Ltd.	84
Day Will, Ltd.	100
Denco (Clacton), Ltd.	24
Donohoe, J.	98
Drayton Regulator & Instrument Co., Ltd.	90
Dubilier Condenser Co. (1925), Ltd.	25
Duke & Co.	90
Dun Electronics	94
Dupley Electronics, Ltd.	100
Edison Swan Electric Co., Ltd.	15
Egen Electric, Ltd.	22
Electradix Radios	97
Electro Acoustic Developments	90
Electro Technical Assemblies	46
Electronic Instruments, Ltd.	18
Electronic Precision Equipment	64, 65
E.M.G. Handmade Gramophones, Ltd.	94
E.M.I. Institutes	36, 46
Erskine Laboratories, Ltd.	35
Eta Tool Co. (Leicester), Ltd.	32
Felicity Amplifiers	79
Filmer, J. T.	96
Fluxite, Ltd.	96
Frith Radiocraft Ltd.	38
Furzehill Laboratories, Ltd.	75
Galpins	73
Gardners Radio, Ltd.	44
Garland Bros.	68
General Electric Co., Ltd.	3, 6
Glaser, L.	99
Goodmans Industries, Ltd.	39
Goodsell, Ltd.	56
Grampian Reproducers, Ltd.	18
Gray, Arthur, Ltd.	76
Hallam, Sleigh & Cheston, Ltd.	20
Hartley, H. A., Co., Ltd.	86
Hatfield Instruments	98
Hayes Co., The	100
Haynes Radio, Ltd	100
Hazlehurst Designs, Ltd.	38
Henley's, W. T., Telegraph Works Co., Ltd.	30, 92
Henry's	78
Hivac, Ltd.	37
Holle, Arthur	96
Hopley's Radio Stores	94
Home-lab Instruments	47
H.P. Radio Services, Ltd.	77
Hunt, A. H., Ltd.	58
Imhof, Alfred, Ltd.	81
Industrial Electronics	40
International Correspondence School, Ltd.	40
Jackson Bros. (London), Ltd	4
Johnsons (Radio)	98
Lasky's Radio	72, 73
Lawrence, G., & Co.	74
Leak, H. J., & Co., Ltd.	59
Lewis Radio Co.	98
Lockwood & Co.	100
London Central Radio Stores	53
London Radio Supply Co.	41
Lowther Mfg. Co.	30
Lyons, C.aude, Ltd.	26
Lyons Radio	82
Mail Order Supply Co.	71
Major Distributors	4
Marconi Instruments, Ltd.	9
Marconi's Wireless Telegraph Co., Ltd.	30, 56
McElroy-Adams Mfg. Group, Ltd.	76
McMurdo Instrument Co. Ltd.	35, 79
Measuring Instruments (Pullin), Ltd.	16
Metro Pex, Ltd.	41
Modern Book Co.	86
Modern Electrics, Ltd.	99
M.R. Supplies, Ltd.	16
Mullard Electronic Products, Ltd.	31, 50
Multicore Solders, Ltd.	Cover iv
Mycalex, Ltd.	81
New Electronic Supplies Co.	90
New London Electron Works, Ltd., The	94
North British Transformer Co.	88
Northern Radio Services	97
Nusound Products	99
Oliver Pell Control, Ltd.	14
Olympic Radio Components	78
Osmor Radio Products, Ltd.	26
Painton & Co., Ltd.	26
Park Radio, Ltd.	42
Parmeko, Ltd.	16
Partridge Transformers, Ltd.	85
P.C.A. Radio	80
Pearce, T. W.	90
Pearson M. & J.	92
Pennine Amplifiers	95
Philips Electrical, Ltd.	2
Pitman, Sir Isaac, & Sons, Ltd.	88
Polytechnic, The	101
Post Radio Supplies	100
Pratts Radio	82
Premier Radio Co.	60, 61, 62, 63
Quartz Crystal Co., Ltd.	98
Radar, Radio & Television	78
Radio Exchange Co.	87
Radio Merchandise Co., Ltd.	93
Radio Servicing Co.	94
Radio Supply Co.	76
Radio Unlimited	101
Radiomenders, Ltd.	80
Radiosphere, Ltd.	101
Rainbow Radio Mfg. Co., Ltd.	82
Record Electrical Co., Ltd., The	92
Redifon, Ltd.	24
Reed & Ford	101
Reosound Engineering & Electrical Co.	95
Reproducers & Amplifiers, Ltd.	34
Reliance Mfg. Co. (Southwark) Ltd.	91
Robinson, F. C., & Partners, Ltd.	12
Roding Laboratories	22
Rogers Development Co.	42
Rollet, H., & Co., Ltd.	98
Royal Air Force, The	11
Rubber Bonders, Ltd.	29
Runbaken Electrical Products	101
Salford Electrical Instruments, Ltd.	27
Samsons Surplus Stores	96
Sangamo Weston, Ltd.	57
Savage Transformers, Ltd.	93
Scharf, Erwin	44
Sifam Electrical Instrument Co., Ltd.	24
Simon Sound Service	18
Smith, G. W. (Radio), Ltd.	89
Sound Sales, Ltd.	54
Southern Radio Supply, Ltd.	88
Sphere Radio Ltd.	28
Stability Radio Components, Ltd.	22
Standard Telephones & Cables, Ltd.	51
Steatite & Porcelain Products, Ltd.	7
Stern Radio, Ltd.	69
Sugden, A. R., & Co. (Engineers), Ltd.	47
Supacoils	95
Szymanski, S.	84
T. & C. Radio College	100
Taylor, Tunnicliff (Refractories), Ltd.	19
Telecraft, Ltd.	45, 101
Telegraph Condenser Co., Ltd.	Cover iii
Telegraph Construction & Maintenance Co., Ltd., The	46
Tele-Radio (1943), Ltd.	40
Thermionic Products, Ltd.	45
Transradio Ltd.	28
Trix Electrical Co., Ltd.	Edit 121
Ultra Electric, Ltd.	36
United Insulator Co., Ltd.	43
Universal Electrical Instruments Corpn.	66
University Radio, Ltd.	83
Valradio, Ltd.	34
V.E.S. Wholesale Services, Ltd.	84
Vitavox, Ltd.	23
Vortexion, Ltd.	55
Walton's Wireless Stores	78
Wayne Kerr Laboratories, Ltd., The	10
West Spencer	94
Westinghouse Brake & Signal Co., Ltd.	32
Weymouth Radio Mfg. Co., Ltd., The	34
Wharfedale Wireless Works	45
Whiteley Electrical Radio Co., Ltd.	58
Wilco Electronics	88
Woden Transformer Co., Ltd.	6
Wolf Electric Tools, Ltd.	20
Wright & Weaire, Ltd.	58
Young C. H.	82

The

PYROBIT

Neon Mains Tester, with Screwdriver detects voltages from **60-750**

Incorporating the most sensitive neon bulb ever made. Indicating—Polarity. Potential, High Frequency, Aerial Radiation, etc. etc.

THE ACRU ELECTRIC TOOL MFG. CO. LTD.
123 Hyde Road, Ardwick, Manchester, 12

Printed in Great Britain for the Publishers, ILIFFE & SONS LTD., Dorset House, Stamford St., London, S.E.1, by CORNWALL PRESS LTD., Park Garden, London, S.E.1. *Wireless World* can be obtained abroad from the following: AUSTRALIA AND NEW ZEALAND: Gordon & Gotch, Ltd. INDIA: A. H. Wheeler & Co. CANADA: The Wm. Dawson Subscription Service Ltd.; Gordon & Gotch, Ltd. SOUTH AFRICA: Central News Agency, Ltd., William Dawson & Sons (S.A.), Ltd. UNITED STATES: The International News Co.

Condenser leadership -from the inside!

I am Mr. Quest — *my task is to ensure that the materials stand up to their jobs, and — by constant experiment — to improve both materials and methods.*

Solid foil and paper : non-inductive assembly
Non-hygroscopic processing for high performance
Hermetic sealing by rubber bung : max. creepage path
Rigid outer aluminium casing
Vice-like grip of bung on wire prevents disconnections

The 'Metalmite' construction shown here is a typical example of T.C.C. design : it has set a new standard both for compactness and ability to withstand extreme tropical conditions. Details of any T.C.C. range are available on request.

TCC

I am Mr. Test — *my eagle eye makes certain that every condenser maintains the T.C.C. reputation for high quality, faultless performance and long life.*

"METALMITE" TUBULAR PAPER CONDENSERS

THE TELEGRAPH CONDENSER CO. LTD · *RADIO DIVISION* · LONDON · W.3 · Tel : ACORN 0061 (9 lines)

WHY IT PAYS TO USE
Ersin Multicore Solder

Radio Manufacturers and Service Engineers all over the world prefer to use *Ersin Multicore Solder* in their factories and workshops. Even in the U.S.A. where more cored solder is produced than anywhere else in the world, many leading firms insist on British made *Ersin Multicore*, despite the freight charges and import duties which raise its cost above that of the locally made single-cored product. Below are some of the reasons why *Ersin Multicore* has attained such world-wide popularity.

FOR MANUFACTURERS

Ersin Multicore Solder is the only solder containing 3 cores of non-corrosive Ersin Flux. Ersin is a high grade rosin which has been subjected to a complex chemical process to increase its fluxing action, whilst still retaining the non-corrosive properties. Ersin Flux makes precision soldering quicker and more economical —it not only prevents oxidation during soldering, but actually cleans the surface to be soldered, removing any oxide from the metal.

Three cores of flux ensure flux continuity throughout the length of the solder wire. There are no lengths without flux—that means no wasted solder, no wasted time, and freedom from 'dry' or H.R. joints.

The correct proportions of flux to solder are always assured—no extra flux is required. Three cores of flux provide thinner solder walls, giving instantaneous melting —an important factor in speeding up repeat soldering operations.

Soldered joints made with Ersin Flux do not corrode even after prolonged exposure to any degree of humidity. This has been tested under climatic conditions ranging from the Arctic to the Tropics.

Only the finest virgin tin and lead are used in the manufacture of *Ersin Multicore*, giving complete freedom from impurities.

CUTS PRODUCTION COSTS

The economies effected by using *Ersin Multicore Solder* play an important part in cutting production costs and keeping down the price of radio equipment. You get more joints per lb. of *Ersin Multicore*—there is no waste. Soldering with *Ersin Multicore* is quicker, too, and every joint is a perfect electrical connection. This saves time in your inspection department—fewer sets are rejected on test.

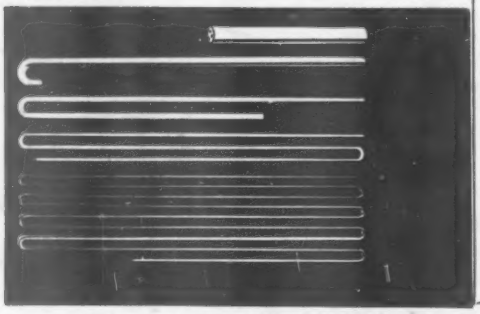

FOR FACTORY USE

Ersin Multicore Solder is made as standard for factory use in 5 alloys and 9 gauges, and is supplied on nominal 7 lb. reels. Other Alloys and Gauges can be supplied to special order. Bulk prices on application.

ALLOYS. This table shows the Melting Points of the three principal Alloys used in Electronic and Telecommunication industries

Alloy	Colour Code	Sol.	Liq.	Bit. Temp.	USES
60/40	Red	183 °C	190 °C	230 °C	High quality work
45/55	Crimson Buff	183 °C	227 °C	267 °C	Hand soldering radio and electrical
40/60	Green	183 °C	238 °C	278 °C	

GAUGES. Approximate number of feet per lb.

Standard Wire Gauge	Diam. in inches	Diam. in M/ms.	ALLOY		
			60/40	45/55	40/60
10	0.128	3.251	25.2	23.5	23.0
12	0.104	2.642	38.1	35.2	34.9
13	0.092	2.337	48.7	45.3	44.5
14	0.080	2.032	64.4	59.2	58.6
16	0.064	1.626	100.5	94.3	92.1
18	0.048	1.219	178.5	167.8	163.5
19	0.040	1.016	257.5	240.4	235.5
20	0.036	0.914	318.0	302.5	291.0
22	0.028	0.711	526.0	492.0	481.0

FOR SERVICE ENGINEERS

Most service engineers safeguard their reputation for quality by using only *Ersin Multicore Solder*, which gives them a guaranteed standard of sound, precision soldered joints.

The repair of old receivers may involve making connections to highly oxidised tags. The extra speed of the non-corrosive Ersin Flux—contained in the 3 cores of *Ersin Multicore Solder* —will enable satisfactory joints to be made quickly. There is no waste with *Ersin Multicore*, the correct proportions of flux and solder are always present, and as the flux does not tend to run out of the cores, there is always a supply available for the next joint.

Ersin Multicore Solder is made in 4 specifications for Service Engineers, packed in the well-known Size One Carton, which provides the most convenient method of carrying solder in the Service Engineer's Kit. The wire is drawn out through a hole in the top, and cannot become tangled.

SIZE ONE CARTONS. Contain 60/40 High Tin Television and Radio Quality or 40/60 Radio and Electrical Alloy.

Catalogue Ref. No.	Alloy Tin/Lead	S.W.G.	Approx. length per carton	Retail Price Subject
				s. d.
C 16014	60/40	14	16 feet	5 0
C 16018	60/40	18	41 feet	5 0
C 14013	40/60	13	15 feet	5 0
C 14016	40/60	16	29 feet	5 0

Specification C16018 is particularly recommended for soldering television equipment.

MULTICORE SOLDERS LTD.

MELLIER HOUSE, ALBEMARLE STREET, LONDON, W.1 • Telephone: REGent 1411